

デザイン・ガイド: TIDA-01292

低周波数のオフラインUPSおよびインバータ用の、ヒートシンク不要の650W電力段のリファレンス・デザイン



概要

このリファレンス・デザインは、12Vバッテリーで動作する低周波数(変圧器ベース)の単相UPS用に設計された、650Wのインバータ電力段です。

このデザインにより、SON5x6パッケージで $R_{DS(ON)}$ が非常に低く、ゲート電荷(Q_g)も低いTI SMD MOSFETの利点を活用し、外形が小さく効率が非常に高い実装が可能になります。フルブリッジ電力段の各legに2つのデバイスを並列に使用することで、この電力段はヒートシンクが不要となり、システム全体のコストを低減できます。

このデザインでは MOSFET を駆動するために LM5101B を使用しています。これはスルー・レートが高い 2A のゲート・ドライバで、さらにスイッチング損失を抑えることができます。双方向電流センス・アンプINA181が、高精度の電流センシング、過電流、および短絡保護に使用されます。TIの Piccolo™ マイクロコントローラTMS320F28027 LaunchPad™ を使用して、高周波数の正弦PWM動作用のファームウェアと堅牢な保護が実装されています。

この基板は、抵抗性負荷と誘導性負荷の両方の条件で、低周波数変圧器(12V AC:220V AC)を使用して動作がテストされています。また、この基板は低電圧、過電圧、過負荷、および短絡の状況について、動作の堅牢性と組み込みの保護機能を検証済みです。

リソース



TIDA-01292	デザイン・フォルダ
CSD17573Q5B	プロダクト・フォルダ
LM5101B	プロダクト・フォルダ
INA181	プロダクト・フォルダ
TLV704	プロダクト・フォルダ
LMV431B	プロダクト・フォルダ
LMT88	プロダクト・フォルダ

特長

- 100~850VAのスタンバイまたはオフラインUPS用に設計、追加のFETを並列接続することで1.5kVAまで拡張可能
- SMD MOSFETを使用するソリューションにより、UPSの製造と組み立てを容易化
- 電力放散用のヒートシンクが必要ないため、システム・コストと製造時間を削減
- バルブ負荷で100~650Wの動作をテストし検証済み
- 標準効率 ≈ 95%、最大効率 > 98.5%
- 過電流、短絡、過電圧、低電圧の保護

アプリケーション

 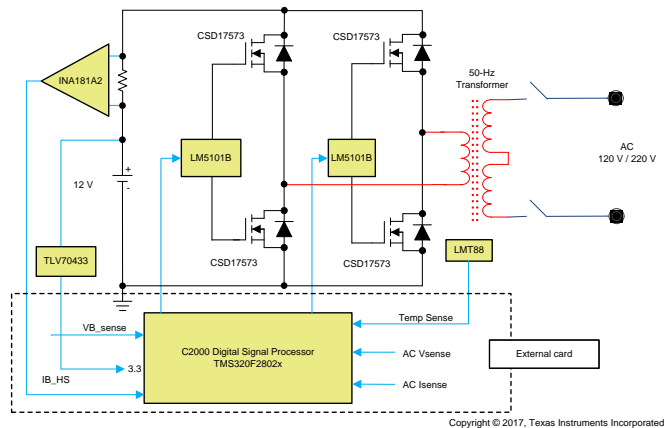- オフラインおよびスタンバイUPS
- DC/ACインバータ
- エネルギー・ストレージ・システム
- 家庭および住居用インバータ




E2Eエキスパートに質問



使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE (重要な注意事項)をご参照くださいますようお願いいたします。

1 System Description

A power inverter is a device that converts electrical power from a DC form to an AC form using electronic circuits. Its typical application is to convert battery voltage into conventional household AC voltage, allowing one to use household electronic equipment when AC power is not available. There are three kinds of inverters. The first set of inverters made produced a square wave signal at the output as shown in  1; however, these are now obsolete.

The modified-square wave, also known as the modified-sine wave inverter, produces square waves with some dead spots between positive and negative half-cycles at the output. The cleanest utility supply-like power source is provided by a pure sine wave inverter. The present inverter market is going through a shift from traditional modified-sine wave inverters to pure sine wave inverters because of the benefits that these inverters offer.

These inverters are also part of energy storage systems where the charging of the battery is done through renewable energy means such as solar and wind, and DC-to-AC conversion is done through inverters.


 


図 1. Types of Inverter Outputs

1.1 Design of Pure Sine Wave Inverter

Figure 2 shows the system block diagram of a single-phase UPS.

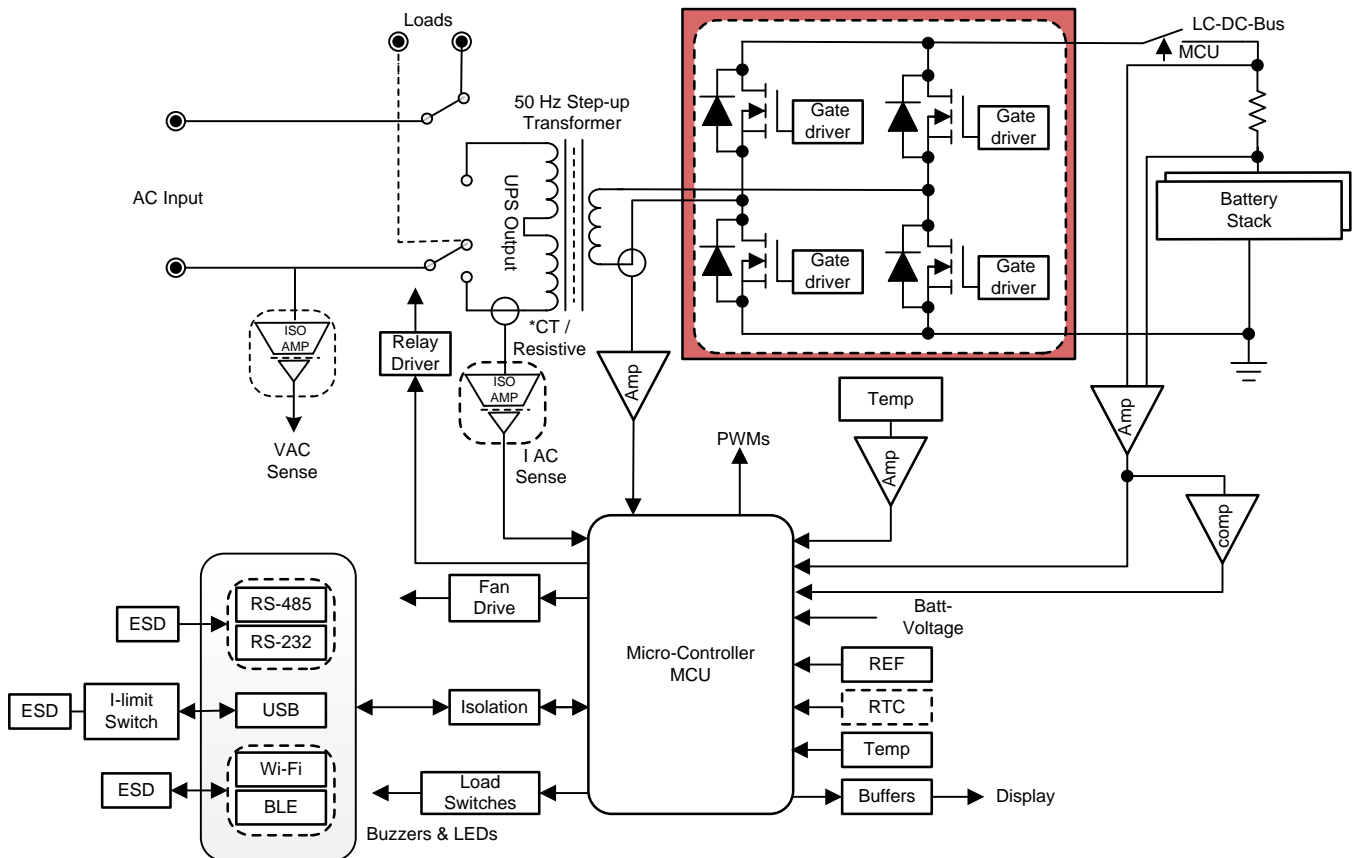

Copyright © 2017, Texas Instruments Incorporated

Figure 2. System Block Diagram of Single-Phase UPS

There are two modes of operation in a residential inverter: mains mode and inverter mode. An inverter not only converts the battery voltage to 220/120-V AC but also charges the battery when the AC mains is present.

The method in which the low-voltage DC power is converted to AC is generally done in two steps:

1. Convert low-voltage DC power to a high-voltage DC source.
2. Convert high-voltage DC to AC waveform using pulse width modulation (PWM). This step is also called a transformer-less approach.

Another method to achieve the desired outcome would be to first convert the low-voltage DC power to AC, then use a transformer to boost the voltage to 120 or 220 V (thus called the transformer-based inverter). This method is widely used in residential inverters, on which this reference design is based.


1.2 Key System Specifications

表 1. Key System Specifications

PARAMETER	MIN	TYP	MAX	UNIT
Input voltage	10	12	14	VDC
Rated output power	550	650	750	W
Switching frequency	—	12	—	kHz
Cooling	400	600	800	LFM
Operating ambient	-20	25	55	°C
Efficiency	—	95	98.6	%
Protections	Overcurrent			
	Overvoltage			
	Undervoltage			
	Overtemperature			
Board specification	90 mm x 155 mm, two-layer, 2-oz copper			

2 System Overview

2.1 Block Diagram

 

2.2 Highlighted Products

2.2.1 CSD17573Q5B

This design uses eight CSD17573Q5B MOSFETs to form the inverter stage. This FET was chosen due to its low $R_{DS(on)}$ of 0.84m Ω and a low-gate charge, designed to minimize the losses in power conversion and switching applications. The device comes in a compact, 8-pin SON 5-mm \times 6-mm package.

Key features of the CSD17573Q5B include:

- Low Q_g and Q_{gd}
- Ultra-low $R_{DS(on)}$
- Low-thermal resistance
- Avalanche rated
- Lead-free terminal plating
- RoHS compliant
- Halogen free
- SON 5-mm \times 6-mm plastic package

2.2.2 LM5101B

This design uses two LM5101B devices. The LM5101B high-voltage gate driver is designed to drive both the high- and the low-side N-channel MOSFETs in a synchronous buck or a half-bridge configuration. The floating high-side driver is capable of operating with supply voltages up to 100 V. The LM5101B provides 2 A of gate drive. The outputs are independently controlled with CMOS input thresholds.

An integrated high-voltage diode is provided to charge the high-side gate drive bootstrap capacitor. A robust level shifter operated at high speed while consuming low power and providing clean level transitions form the control logic to the high-side gate driver. Undervoltage lockout is provided on both the low-side and the high-side power rails.

Key features of the LM5101B include:

- Drives both a high- and low-side N-channel MOSFETs
- Independent high-and low-driver logic inputs
- Bootstrap supply voltage up to 118-V DC
- Fast propagation times: 25 ns typical
- Drives 1000-pF load with 8-ns rise and fall time
- Excellent propagation delay matching: 3 ns typical
- Supply rail undervoltage lockout
- Low power consumption

2.2.3 INA181

This design uses the INA181 to sense the current through MOSFETs and to protect the system for overcurrent. The INA181 device is a bidirectional current sense amplifier that senses voltage drop across current sense resistors at common-mode voltages from -0.2 to 26V, independent of the supply voltage. This design uses the A2 version with fixed gain of 50, which is achieved by integrated matched resistor gain network to minimize the gain error and reduce the temperature drift.

Key features of the INA181 include:

- Common-mode range (V_{CM}): -0.2 to 26 V
- High bandwidth: 350 kHz
- Offset voltage:
 - ± 150 μ V (max) at $V_{CM} = 0$ V
 - ± 500 μ V (max) at $V_{CM} = 12$ V
- Output slew rate: 2 V/ μ s
- Bidirectional current-sensing capability
- Accuracy:
 - $\pm 1\%$ gain error (max)
 - 1- μ V/ $^{\circ}$ C offset drift (max)
- Gain Options:
 - 20 V/V (A1 devices)
 - 50 V/V (A2 devices)
 - 100 V/V (A3 devices)

- 200 V/V (A4 devices)
- Quiescent current: 260 μ A (max per channel)

2.2.3.1 INA185

For higher-performance current sensing and overcurrent protection, the INA185 current sense amplifier can be considered.

Benefits of the INA185 over the INA181 include:

- Offset voltage:
 - $\pm 55 \mu\text{V}$ (max) at $V_{\text{CM}} = 0 \text{ V}$ (A2 device)
 - $\pm 130 \mu\text{V}$ (max) at $V_{\text{CM}} = 12 \text{ V}$ (A2 device)
- Accuracy:
 - $\pm 0.2\%$ gain error (max, A2 device)
 - $0.5\text{-} \mu\text{V}/^\circ\text{C}$ offset drift (max)
- Small package:
 - SOT-563 (6): $1.6\text{mm} \times 1.6\text{mm}$ (including pins)

2.3 System Design Theory

2.3.1 Inverter Operation and PWM Explanation


The DC-to-AC inversion can be achieved using two methods:

1. The first is the conversion of low-voltage DC to a high-voltage DC followed by the conversion of this high-voltage DC to AC using PWM.
2. Another method is to first convert the low-voltage DC to AC and then use a transformer to boost the voltage to 120 or 220 V.

This design uses the second method of inverting DC to AC using an H-bridge circuit where the MOSFETs are switched with high frequency SPWM signals. The switching waveforms used for this design is explained in the following subsections.

2.3.1.1 Switching Waveforms

Figure 3 shows the sine PWM used for each switch:

 

Copyright © 2017, Texas Instruments Incorporated

Figure 3. SPWM Sequence Used for TIDA-01292


The switching algorithm as shown in Figure 3 can be broken in following sequence:

1. The 50-Hz sine output can be divided into two time intervals of 10 ms each.
2. During the first 10 ms:
 - The left leg is switched at 50 Hz (that is, the top-left FET) is continuously on for 10 ms and the bottom-left FET is continuously off for that time.
 - The top- and bottom-right FETs are switched at a high frequency (12 kHz in this case) such that the duty cycle for the bottom FET goes from 0 to maximum and back to 0 while the duty cycle of the top FET varies from maximum to 0 and back to maximum in sinusoidal modulation.
3. During the next 10 ms:
 - The right leg is switched at 50 Hz (that is, the top-right FET) is continuously on for 10 ms and bottom-right FET is continuously off for the same 10ms period.
 - The top- and bottom-left FETs are switched at a high frequency (12 kHz in this case) such that the duty cycle for the bottom FET goes from 0 to maximum and back to 0 while the duty cycle of the top FET varies from maximum to 0 and back to maximum in sinusoidal modulation.

2.3.1.2 Power Flow


Figure 4 to Figure 7 show the power flow for the entire 50-Hz cycle.

Figure 4 shows the power transfer from input to output during the positive half cycle where, as mentioned earlier, the top-left FET remains on and the bottom-left FET remains off continuously for 10 ms while the right-side FETs are switched at a high-frequency SPWM. As seen in Figure 5, during the positive half cycle, the current freewheels through the body diode of the top-right FET until the FET is switched on. This makes sure the design has ZVS switching across the top FET.

 

Copyright © 2017, Texas Instruments Incorporated


Figure 4. Increasing Positive Output

 

Copyright © 2017, Texas Instruments Incorporated


Figure 5. Decreasing Positive Output

 A similar power flow sequence takes place in the negative half cycle where the top-right FET is continuously on and the bottom-right FET is continuously off while the left leg is switched. As a result, the power flow takes place when the left bottom FET is on and freewheeling happens when the left top FET is on, as shown in 図 6 and 図 7.



Copyright © 2017, Texas Instruments Incorporated

図 6. Increasing Negative Output

 

Copyright © 2017, Texas Instruments Incorporated

図 7. Decreasing Negative Output

The positive peak of the sine wave is achieved during maximum duty cycle switching of the bottom-right FET, and the negative peak is observed when the bottom-left FET is switched at the highest duty cycle. Also, the top FETs are always synchronous switching, which reduces the switching loss across them, while the bottom FETs are kept off for half the cycle and only switched during the other half, which reduces the conduction losses across them.

2.3.2 Gate Driver Design

2.3.2.1 Bootstrap and VDD Capacitor

The bootstrap capacitor must maintain the HB pin voltage above the UVLO voltage for the HB circuit in any circumstances during normal operation. Thus, the maximum allowable drop across the bootstrap capacitor is calculated with lowest battery voltage, as shown in 式 1:

$$\Delta V_{HB} = V_{DD} - V_{DH} - V_{HBL} = 10 - 0.7 - 6.7 = 2.6 \text{ V} \quad (1)$$

where:

- V_{DD} = Supply voltage of the gate drive IC
- V_{DH} = Bootstrap diode forward voltage drop
- $V_{HBL} = V_{HBR} - V_{HBH} = 6.7 \text{ V}$, HB falling threshold based on the [LM5101B datasheet](#) (SNOSAW2)

The maximum quiescent current required by the driver and the bootstrap circuit is 0.2 mA as per the LM5101B datasheet. Also, due to the kind of switching scheme implemented for the inverter, the top FET remains on for 10 ms continuously; thus, the bootstrap capacitor must be able to supply the charge required during this entire time. The total charge required by the bootstrap capacitor can be calculated using 式 2:

$$Q_{\text{Total}} = Q_{g\text{max}} + I_{HB\text{max}} \times T_{\text{on}} \quad (2)$$

where:

- $Q_{g\text{max}}$ is the total gate charge of the FET
- $I_{HB\text{max}}$ is the maximum quiescent current requirement of the driver and the bootstrap circuit
- T_{on} is the maximum on time of the FET (10 ms)

The total charge required by the bootstrap capacitor is: $Q_{\text{Total}} = 64 \text{ nC} + 0.2 \text{ mA} \times 10 \text{ ms} = 2.064 \text{ } \mu\text{C}$

The value of the bootstrap capacitor is calculated using 式 3:

$$C_{\text{BOOT}} = \frac{Q_{\text{Total}}}{\Delta V_{HB}} = \frac{2.064 \text{ } \mu\text{C}}{2.6 \text{ V}} = 0.8 \text{ } \mu\text{F} \quad (3)$$

In practice, the value for the C_{BOOT} capacitor must be greater than the calculated value to allow for situations where the power stage may skip a pulse due to load transients. It is recommended to use 10 times the calculated value and place the bootstrap capacitor as close to the HB and HS pin as possible. A 10- μF capacitor is used for C_{BOOT} in this design.

As a general rule, the local V_{DD} bypass capacitor must be 10 times greater than the value of C_{BOOT} . For this design, a 100- μF electrolytic capacitor and a 10- μF ceramic capacitor is used for the V_{DD} supply.


2.3.2.2 External Bootstrap Diode and Resistor

The bootstrap capacitor is charged by the V_{DD} through the internal bootstrap diode every cycle when the low-side MOSFET turns on. The charging of the capacitor involves high-peak currents; therefore, transient power dissipation in the internal bootstrap diode may be significant and dependent on its forward voltage drop. Both the diode conduction losses and reverse recovery losses contribute to the total losses in the gate driver and need to be considered in the power dissipation of the gate driver.

For high-frequency and high-capacitive loads, consider using an external bootstrap diode placed in parallel with the internal bootstrap diode to reduce power dissipation of the driver. For this design, a 20-V Schottky diode with a typical forward voltage drop of 0.38V at 1A is used in parallel to the internal bootstrap diode.

Bootstrap resistor R_{BOOT} is selected to reduce the inrush current in D_{BOOT} and limit the ramp-up slew rate of the voltage of HB-HS. This resistor serves two purposes: one is limiting the inrush current through D_{BOOT} ; the other is protecting the driver from the negative voltage spikes at the common-mode point. The value of this resistor must be just large enough to protect the diode. A very large value resistor cannot be used because this creates a potential difference between the source of the high-side MOSFET and the HS pin of the driver at the beginning of the PWM cycles until the C_{BOOT} is not charged to full voltage. Due to this potential difference, the gate of the FET is only pulled low to the HS pin voltage level and not to the actual source level, which might create issues. For this design, a 1- Ω R_{BOOT} resistor is used in the path of C_{BOOT} and common-mode point, as shown on 8.

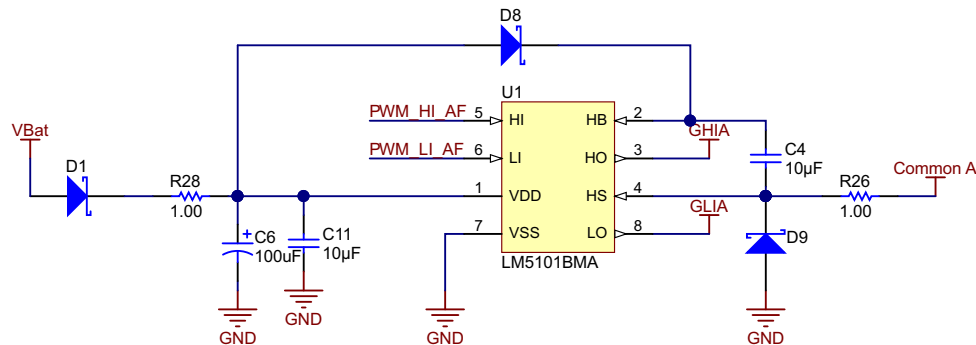It is also recommended to place a Schottky diode at the HS pin to further protect the driver from negative spikes.



Copyright © 2017, Texas Instruments Incorporated

8. Gate Driver Schematic

2.3.2.3 Gate Drive Resistor

Resistor R_{Gate} is sized to reduce ringing caused by parasitic inductances and capacitances and to limit the current coming out of the gate driver. For this design, a 6- Ω resistor is used for turnon and a 3- Ω resistor for turnoff. Maximum high-side and low-side turnon and turnoff currents are calculated using 式 4 to 式 7.

$$I_{HOH} = \frac{V_{DD} - V_{DH} - V_{OH}}{R_{Gate}} = \frac{10 \text{ V} - 0.7 \text{ V} - 0.45 \text{ V}}{6 \Omega} = 1.475 \text{ A} \quad (4)$$


$$I_{LOH} = \frac{V_{DD} - V_{OH}}{R_{Gate}} = \frac{10 \text{ V} - 0.45 \text{ V}}{6 \Omega} = 1.592 \text{ A} \quad (5)$$

$$I_{HOL} = \frac{V_{DD} - V_{DH} - V_{OL}}{R_{Gate}} = \frac{10 \text{ V} - 0.7 \text{ V} - 0.25 \text{ V}}{3 \Omega} = 3.02 \text{ A} \quad (6)$$

$$I_{LOL} = \frac{V_{DD} - V_{OL}}{R_{Gate}} = \frac{10 \text{ V} - 0.25 \text{ V}}{3 \Omega} = 3.25 \text{ A} \quad (7)$$

 2.3.3 Current Sensing

To protect the FETs from overcurrent failure, a current sensing circuitry is implemented in this design. Usually, an inverter requires to sense both the battery charging and discharging current. Thus, it is necessary to sense current in both directions. This design uses the low-cost bidirectional current sense amplifier INA181 with low-offset voltage, high-gain bandwidth product, and high accuracy, which can be used for high-side and low-side sensing. The current sensing schematic is shown in [Figure 9](#).



Copyright © 2017, Texas Instruments Incorporated

Figure 9. Current Sensing Schematic

The LMV431B is used for shunt reference, which provides a reference voltage of 1.24 V. [Equation 8](#) shows the transfer function of current sensing circuitry.

$$\frac{V_{OUT}}{V_{IN}} = (I_{LOAD} \times R_{SENSE} \times Gain) + V_{REF} \tag{8}$$

To provide flexibility for overall gain, two sense resistors are used in parallel. The TIDA-01292 design uses two 0.5-mΩ resistors in parallel for R_{SENSE} and the INA181 with a fixed gain of 50. This design also uses a low-pass filter with a cutoff frequency of around 13 kHz at the input of the INA181.

A provision to use an op amp and external resistors for adjustment of gain is also provided in this design.

2.3.4 Loss Calculation

Loss calculation is important to theoretically estimate the temperature of various components on the board to estimate the total power handling capability of the design.

The majority of losses that take place in the inverter are the conduction loss, switching loss, body diode conduction loss, loss in the current sense resistor, and loss in the bulk of the PCB.

2.3.4.1 Conduction Loss in MOSFETs

To calculate conduction loss, have the equivalent RMS current through each MOSFET. Due to the nature of the switching technique used, calculating RMS current is not as straight forward as for a normal sine wave.

To calculate the RMS current, the 50-Hz sine wave is divided is two time intervals of 10 ms each. For 10 ms, the top FET is conducting continuously while the bottom FET is off. During this time, conduction loss happens only in the top FET. For the other 10 ms, the top and bottom FETs are switching with sinusoidally varying duty cycle. Note that at any instant, the peak current through the FETs is also varying sinusoidally. Based on [Fig 4](#) to [Fig 7](#), the current through top and bottom FETs would look something like [Fig 10](#) and [Fig 11](#), respectively.

 


図 10. Current Waveform Through Top FET

 


図 11. Current Waveform Through Bottom FET

During the switching period, the total current through the bottom FET is $D_n \times I_{Pn}$ while the current through top FET is $(1 - D_n) \times I_{Pn}$, where D_n is the duty cycle and I_{Pn} is the peak current at that particular switching instant n .

To calculate the total RMS current, the current waveform is divided into two parts of 10 ms each. The RMS current through each FET then would be calculated using 式 9:

$$I_{RMS} = \sqrt{\frac{(I_{RMS1})^2 + (I_{RMS2})^2}{2}} \quad (9)$$

where:

- I_{RMS1} is the RMS current in the first 10 ms
- I_{RMS2} is the RMS current in the next 10 ms

For the bottom FETs, current flows through them only for 10 ms. To calculate the overall RMS current for the waveform as shown in 図 11, first find out the RMS current for each switching instant given that the duty cycle and peak current for each instant is different and varies sinusoidally. For doing so, all the pulses can be assumed as square pulses because the time period is very small when compared to the 50-Hz sine. For a square pulse of magnitude A , the RMS value is $\sqrt{D} \times A$, where D is the duty cycle of the given pulse. Similarly, the RMS values for the individual pulses shown in 図 11 is $\sqrt{D_n} \times I_{Pn}$, where n is the instant of switching. Total switching instants are calculated using 式 10:

$$n = \frac{f_{sw}}{50 \text{ Hz}} = \frac{12 \text{ kHz}}{50 \text{ Hz}} = 240 \quad (10)$$

The RMS current through the bottom FET at any instant n is calculated as 式 11:

$$I_{RMSn_B} = \sqrt{D_n} \times I_P \times \sin\left(\frac{2n\pi}{240}\right) \quad (11)$$

To get sinusoidal output, the duty cycle is also varied in the same fashion. Assuming a modulation index of 1, the duty cycle for n^{th} instant can be calculated using 式 12. Because the current through the bottom FET flows only for half the time (10 ms), for these calculations, n varies from 0 to 120.

$$D_n = \sin\left(\frac{2n\pi}{240}\right) \quad (12)$$

The total RMS current for this 10 ms is calculated using 式 13:

$$I_{RMS1_B} = \sqrt{\frac{\sum_{n=1}^{120} I_{RMSn_B}^2}{120}} \quad (13)$$

Therefore, the RMS current for bottom FET I_{RMS_B} is calculated using 式 14:

$$I_{RMS_B} = \sqrt{\frac{(I_{RMS1_B})^2 + (I_{RMS2_B})^2}{2}} = \sqrt{\frac{\left(\sqrt{\frac{\sum_{n=1}^{120} I_{RMSn_B}^2}{120}}\right)^2 + (0)^2}{2}} = \sqrt{\frac{\sum_{n=1}^{120} I_{RMSn_B}^2}{120 \times 2}} \quad (14)$$

I_{RMS2} for the bottom FET is zero because one of the bottom FETs is continuously off for 10 ms.

Calculating the RMS current for the top FET is similar to the bottom FET. The only difference is that the conduction time for the top FET is $(1 - D_n)$ for I_{RMS1} , ignoring the dead time, and I_{RMS2} is not zero but a sine output. Again approximating the pulses to be square, the I_{RMSn} for n^{th} switching instant for the top FET can be calculated using 式 15:

$$I_{RMSn_T} = \sqrt{(1 - D_n)} \times I_p \times \sin\left(\frac{2n\pi}{240}\right) \quad (15)$$

Calculating D_n remains same as given by 式 12. The RMS current for the switching time, I_{RMS1} , for the top FET is calculated using 式 16:

$$I_{RMS1_T} = \sqrt{\frac{\sum_{n=1}^{120} I_{RMSn_T}^2}{120}} \quad (16)$$

The total RMS current for top FET is thus calculated using 式 17:

$$I_{RMS_T} = \sqrt{\frac{(I_{RMS1_T})^2 + (I_{RMS2_T})^2}{2}} = \sqrt{\frac{\left(\sqrt{\frac{\sum_{n=1}^{120} I_{RMSn_T}^2}{120}}\right)^2 + \left(\frac{I_p}{\sqrt{2}}\right)^2}{2}} = \sqrt{\frac{\frac{\sum_{n=1}^{120} I_{RMSn_T}^2}{120} + \left(\frac{I_p}{\sqrt{2}}\right)^2}{2}} \quad (17)$$

2.3.4.2 Switching Loss

One calculates the total switching loss usually by multiplying the energy lost and frequency to get the power loss. But in this case, because the peak current at every switching instant is different, the energy transferred at each instant is also different. Thus, to find out the total switching power loss, add up the energy transferred at each instant and find its average over the 50-Hz cycle.

The average of 式 4 and 式 5 gives the average turnon current (I_{Turnon}), and the average of 式 6 and 式 7 gives the average turnoff current ($I_{Turnoff}$). Because a 2-A driver is used for this design, the upper limit on the source and sink current is 2 A.

The energy transferred during the n^{th} turnon and turnoff instant is calculated using 式 18 and 式 19, respectively:

$$E_{Turnon_n} = \frac{1}{2} \times V_{DS} \times I_n \times \frac{(Q_{gs} - Q_{gs(th)} + Q_{gd})}{I_{Turnon}} \quad (18)$$

$$E_{Turnoff_n} = \frac{1}{2} \times V_{DS} \times I_n \times \frac{(Q_{gs} - Q_{gs(th)} + Q_{gd})}{I_{Turnoff}} \quad (19)$$

where:

- V_{DS} is the drain-source voltage across FET
- I_n is the current at n^{th} switching instant and is given by 式 20
- Q_{gs} is the total gate-source charge of the MOSFET, 17.1 nC for the CSD17573Q5B FET
- $Q_{gs(th)}$ is the gate-source charge at the threshold voltage, 8.6 nC for the CSD17573Q5B
- Q_{gd} is the gate-drain charge of the MOSFET, 11.9 nC for the CSD17573Q5B

$$I_n = I_p \times \sin\left(\frac{2n\pi}{240}\right) \quad (20)$$

The total power loss at turnon and turnoff is calculated using 式 21 and 式 22:

$$P_{\text{loss_on}} = \frac{\sum_{n=1}^{120} E_{\text{Tturnon}_n}}{20 \text{ ms}} \quad (21)$$

$$P_{\text{loss_off}} = \frac{\sum_{n=1}^{120} E_{\text{Tturnoff}_n}}{20 \text{ ms}} \quad (22)$$

Note that any of the four MOSFETs switches, only for half the cycle (10 ms)—thus only 120 energy instants—are added up to calculate power loss. Due to the switching scheme used, the top FET is always soft switching. As a result, the majority of switching losses are in the bottom FETs only. To calculate the switching loss across top FET accurately, replace V_{DS} with the forward drop of the body diode of the FET.

2.3.4.3 Body Diode Loss

To ensure there is not any shoot-through condition, a dead time of 500 ns is provided in the firmware. During this dead time, the entire load current flows through the body diode, causing power loss across it. Because the dead time appears twice during one switching cycle, that is at turnon and turnoff, consider it twice at all switching instants. Again, because the peak current flowing through it varies sinusoidally, calculate the energy at all these instants, add them up, and find the average over one entire cycle of 50 Hz. The energy at any instant n is calculated using 式 23:

$$E_{n_body_diode} = 2 \times V_f \times I_n \times t_d \quad (23)$$

where:

- V_f is the forward voltage drop of the body diode
- I_n is the current at n^{th} instant given by 式 20
- t_d is the dead time (500 ns for this design)

The total power loss in one leg is thus calculated using 式 24:

$$P_{\text{body_diode}} = \frac{\sum_{n=1}^{120} E_{n_body_diode}}{20 \text{ ms}} \quad (24)$$

Body diode loss occurs only in the top MOSFETs for the PWMs used for this design because bottom switches are hard switched every time.

2.3.4.4 Miscellaneous Losses

In addition to the major losses mentioned previously:


- Board copper: This loss depends on board dimension, Cu thickness, and FET placement. There is also a considerable amount of conduction losses in the board copper as well.
- Input bulk capacitors: The electrolytic capacitors present at the input also result in conduction loss depending on the ripple current and the ESR of the capacitor.
- Sense resistor: Because the load current for this design is large, there is conduction loss in sense resistor as well, which cannot be ignored.
- Other than these components, there is also power loss in the gate drivers and LDOs, but this is usually

very small compared to other losses and thus can be ignored.

3 Hardware, Testing Requirements, and Test Results

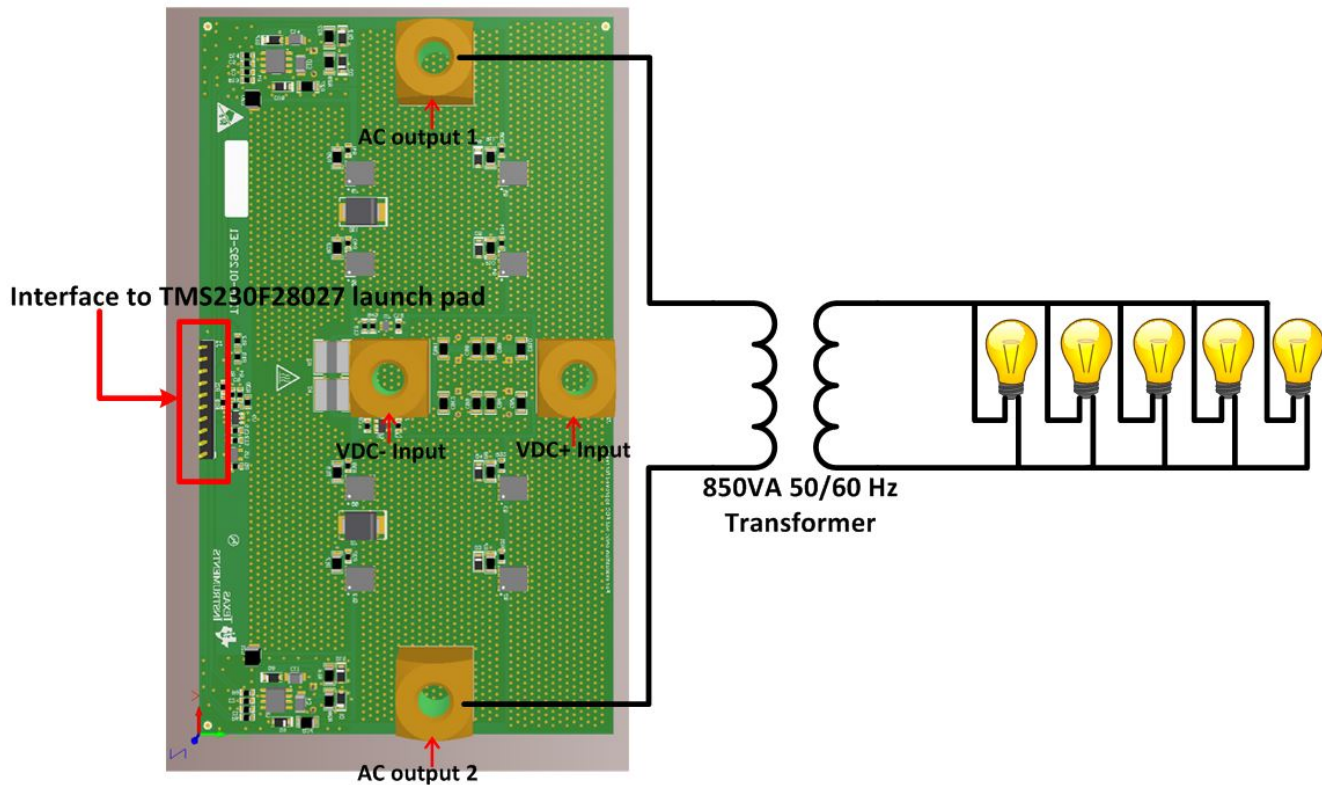3.1 Hardware

☒ 12 shows the test setup of the board with the transformer, bulb loads, and interface to the TMS320F28027 LaunchPad for firmware.



☒ 12. TIDA-01292 Test Setup

The details of the interface to the LaunchPad, connector J1 are as follows:

- Pin 1: Gate input for the high-side FET of left leg
- Pin 2: Gate input for the low-side FET of left leg
- Pin 3, 6, 7: Ground reference
- Pin 4: Analog output of current sense amplifier
- Pin 5: VDC sense output
- Pin 8: Temperature sense output
- Pin 9: Gate input for the high-side FET of right leg
- Pin 10: Gate input for the low-side FET of the right leg

3.2 Testing and Results

The TIDA-01292 design is tested with bulb loads and a 850-VA, 50-Hz transformer at the output.

3.2.1 Efficiency

The efficiency of the design is tested at various FAN speeds. 表 2, 表 3, and 表 4 show the efficiency of the design at 800-LFM, 600-LFM, and 400-LFM fan speeds with a 12-V battery input. The efficiency figures are for the TIDA-01292 board only and do not include the losses in the transformer.

表 2. Efficiency With 12-V Battery Input and 800-LFM Fan Speed

V_{IN_RMS} (V)	I_{IN_RMS} (A)	P_{IN} (W)	V_{OUT_RMS} (V)	I_{OUT_RMS} (A)	P_{OUT} (W)	EFFICIENCY
11.88	14.58	139.54	9.03	21.04	138.66	99.37%
11.83	26.43	250.07	8.88	33.30	246.88	98.72%
11.78	38.30	357.56	8.73	46.93	350.11	97.92%
11.73	49.50	456.03	8.59	60.18	442.76	97.09%
11.71	55.02	504.55	8.51	66.90	487.51	96.62%
11.68	60.42	550.85	8.44	73.45	529.71	96.16%
11.66	65.52	594.07	8.37	79.73	568.84	95.75%
11.64	70.44	635.16	8.30	85.89	606.28	95.45%
11.63	72.85	655.61	8.27	88.85	623.86	95.16%
11.62	75.13	674.30	8.24	91.70	640.38	94.97%

表 3. Efficiency With 12-V Battery Input and 600-LFM Fan Speed

V_{IN_RMS} (V)	I_{IN_RMS} (A)	P_{IN} (W)	V_{OUT_RMS} (V)	I_{OUT_RMS} (A)	P_{OUT} (W)	EFFICIENCY
11.94	4.14	21.37	9.22	15.14	21.31	99.72%
11.88	14.57	139.30	9.03	21.07	138.54	99.45%
11.83	26.42	249.88	8.88	33.29	246.56	98.67%
11.77	38.24	356.95	8.73	46.85	349.35	97.87%
11.73	49.42	455.98	8.59	60.12	442.26	96.99%
11.71	54.97	504.10	8.51	66.81	486.86	96.58%
11.68	60.33	550.21	8.44	73.36	529.13	96.17%
11.66	65.45	593.32	8.37	79.72	568.74	95.86%
11.64	70.38	634.89	8.30	85.77	605.15	95.32%
11.63	72.67	653.64	8.26	88.68	621.73	95.12%
11.62	74.91	671.90	8.23	91.47	638.22	94.99%

表 4. Efficiency With 12-V Battery Input and 400-LFM Fan Speed

V_{IN_RMS} (V)	I_{IN_RMS} (A)	P_{IN} (W)	V_{OUT_RMS} (V)	I_{OUT_RMS} (A)	P_{OUT} (W)	EFFICIENCY
11.88	14.56	139.07	9.03	21.10	138.43	99.54%
11.83	26.39	249.67	8.88	33.27	246.21	98.61%
11.78	38.21	356.72	8.73	46.82	349.14	97.88%
11.73	49.36	455.35	8.59	60.02	441.45	96.95%
11.70	54.93	503.56	8.51	66.79	486.64	96.64%
11.68	60.23	549.20	8.44	73.26	528.42	96.22%
11.66	65.28	591.93	8.37	79.49	567.01	95.79%
11.64	70.30	634.54	8.30	85.61	604.31	95.24%
11.63	72.60	653.54	8.27	88.50	621.06	95.03%
11.62	74.87	672.21	8.23	91.33	637.45	94.83%

The design was also tested for efficiency at 10-V and 14-V battery inputs at a 600-LFM fan speed. 表 5 and 表 6 show the data for the 10-V and 14-V battery inputs, respectively.

表 5. Efficiency With 10-V Battery Input and 600-LFM Fan Speed

V _{IN_RMS} (V)	I _{IN_RMS} (A)	P _{IN} (W)	V _{OUT_RMS} (V)	I _{OUT_RMS} (A)	P _{OUT} (W)	EFFICIENCY
10.06	2.03	13.74	7.78	6.77	14.30	104.05%
10.01	12.94	105.20	7.61	16.31	104.79	99.61%
9.96	23.84	190.11	7.47	28.90	187.55	98.65%
9.91	34.60	271.78	7.33	41.78	265.68	97.76%
9.87	44.65	346.19	7.20	54.05	335.75	96.98%
9.83	54.28	415.84	7.08	65.86	399.48	96.07%
9.81	58.54	445.90	7.02	71.18	426.65	95.68%
9.79	62.81	476.23	6.96	76.40	452.83	95.09%
9.78	66.72	503.00	6.90	81.36	476.59	94.75%
9.76	70.59	529.58	6.85	86.25	499.96	94.40%
9.74	75.15	560.71	6.79	91.95	525.88	93.79%
9.73	78.63	584.16	6.74	96.38	545.06	93.31%

表 6. Efficiency With 14-V Battery Input and 600-LFM Fan Speed

V _{IN_RMS} (V)	I _{IN_RMS} (A)	P _{IN} (W)	V _{OUT_RMS} (V)	I _{OUT_RMS} (A)	P _{OUT} (W)	EFFICIENCY
13.91	10.06	43.62	10.92	41.55	37.66	86.34%
13.83	17.07	182.85	10.48	34.48	179.27	98.04%
13.76	29.37	320.80	10.33	42.63	315.12	98.23%
13.72	42.07	456.39	10.18	54.67	445.75	97.67%
13.69	48.94	527.83	10.09	61.99	513.55	97.29%
13.65	55.50	595.23	10.00	69.28	576.93	96.93%
13.63	61.78	658.97	9.92	76.51	636.25	96.55%
13.60	67.94	720.42	9.83	83.69	692.64	96.14%
13.58	73.77	778.77	9.75	90.58	744.19	95.56%

3.2.2 Functional Waveforms

図 13 and 図 14 show the gate-to-source waveform of high- and low-side FET and drain-to-source waveform for the turnon and turnoff of the bottom FETs.

注: Channel 1 (Yellow): VDS_LS—Drain-source waveform of low-side FETs, 10 V/div
 Channel 2 (Green): VGS_LS—Gate-source waveform of low-side FETs, 10 V/div
 Channel 3 (Purple): VGS_HS—Gate-source waveform of high-side FETs, 10 V/div
 Time scale: 200 ns/div

 


図 13. Switching Waveform for Turnon of Bottom FETs

 


図 14. Switching Waveform for Turnoff of Bottom FETs

The TIDA-01292 design has a dead time of about 350 ns existing between the top and bottom FETs.

This design was also tested for inductive load where the primary winding of an auto-transformer was used as the inductive load. [Figure 15](#) shows the filtered voltage and current output for the inductive load.

 


Figure 15. Output Waveform for Inductive Load

To further protect the FETs, this design has an overload and overcurrent protection algorithm where if the current hits the assigned peak, the PWMs shut off for 2 ms before starting again. [Fig 16](#) and [Fig 17](#) show the response during the overcurrent situation.

注: Channel 2 (Purple): 220-V AC output voltage, 500 V/div
 Channel 3 (Green) : Output of INA181, 2 V/div
 Channel 4 (Teal): Output current, 100 A/div

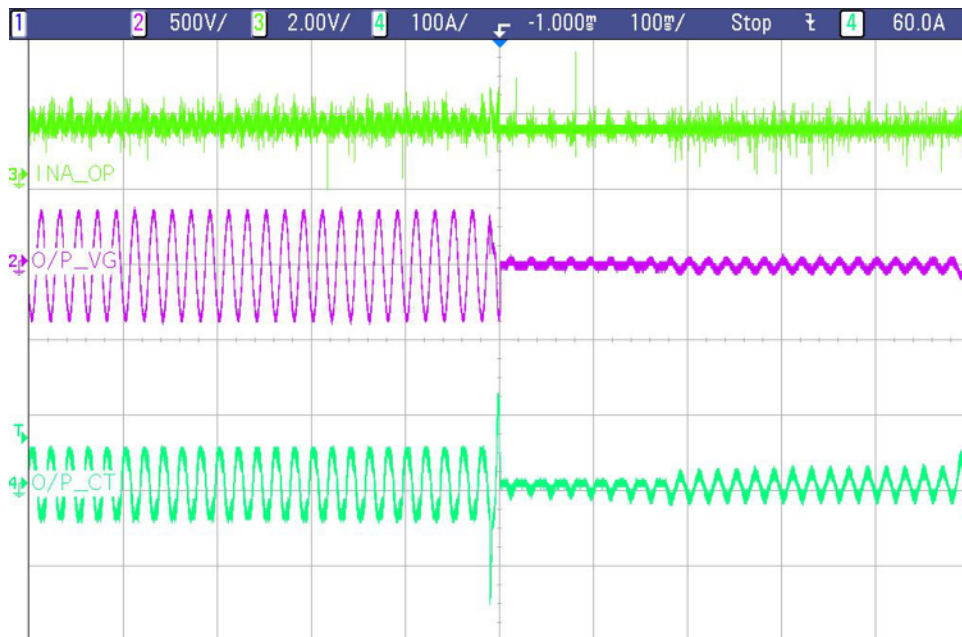


図 16. Overcurrent Protection

 


図 17. Overcurrent Protection (Zoomed)

3.2.3 Thermal Performance

Figure 18 shows the thermal performance of the design at full load, 12-V battery input, and 400-LFM fan speed.

 


Figure 18. Thermal Image at Full Load, 12-V Battery Input, and 400-LFM Fan Speed

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01292](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01292](#).

4.3 PCB Layout Recommendations

The optimum performance of high- and low-side gate drivers cannot be achieved without taking due considerations during the circuit board layout. Consider the following during the board layout:

- Connect low-ESR or ESL capacitors close to the device, between VDD and VSS pins to support the high-peak currents being drawn from VDD during turnon of the external MOSFET.
- Connect a low-ESR electrolytic capacitor between MOSFET drain and ground (VSS) to prevent large voltage transients at the drain of the top MOSFET.
- Minimize the parasitic inductances in the source of top MOSFET and in the drain of the bottom MOSFET to avoid large negative transients on the switch node (HS pin).
- Grounding considerations:
 1. The first priority in designing grounding connections is to confine the high-peak currents that charge and discharge the MOSFET gate into a minimal physical area. This current decreases the loop inductance and minimizes noise issues on the gate terminal of the MOSFET. Place the MOSFETs as close as possible to the gate driver.
 2. The second high-current path includes the bootstrap capacitor, the bootstrap diode, the local ground referenced bypass capacitor, and low-side MOSFET body diode. The bootstrap capacitor is recharged on a cycle-by-cycle basis through the bootstrap diode from the ground referenced VDD bypass capacitor. The recharging occurs in a short time interval and involves high peak current. Minimize this loop length and area on the circuit board to ensure reliable operation.

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01292](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01292](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01292](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01292](#).

5 Software Files

To download the software files, see the design files at [TIDA-01292](#).

6 Related Documentation

1. Texas Instruments, [AN-2296 SM72295: Highly Integrated Gate Driver for 800VA to 3KVA Inverter](#), Application Report (SNVA678)
2. Texas Instruments, [800VA Pure Sine Wave Inverter's Reference Design](#), Application Report (SLAA602)

6.1 商標

Piccolo, LaunchPad are trademarks of Texas Instruments.
すべての商標および登録商標はそれぞれの所有者に帰属します。

7 About the Authors

NEHA NAIN is a systems engineer at Texas Instruments, where she is responsible for developing reference design solutions for the power delivery, industrial segment. Neha earned her bachelor in electrical and electronics engineering from the PES Institute of Technology (now PES University), Bangalore.

SHREENIDHI PATIL is an analog application engineer at Texas Instruments, where he is responsible for supporting various customers in North India. Shreenidhi earned his bachelor in electrical and electronics engineering from the RV College of Engineering, Bangalore.

7.1 Acknowledgments

Special thanks to **VIKAS CHOLA**, Field Applications Engineer, for his invaluable assistance in helping with the firmware and implementing various protections while testing this design.

改訂履歴

資料番号末尾の英字は改訂を表しています。その改訂履歴は英語版に準じています。

Revision A (February 2018) から Revision B に変更 Page

- INA185 追加..... 8
-

2017年9月発行のものから更新 Page

- Omitted note for 式 14 16
-

重要なお知らせと免責事項

TI は、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Web ツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の黙示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または黙示的にかかわらず拒否します。

これらのリソースは、TI 製品を使用する設計の経験を積んだ開発者への提供を意図したものです。(1) お客様のアプリケーションに適した TI 製品の選定、(2) お客様のアプリケーションの設計、検証、試験、(3) お客様のアプリケーションに該当する各種規格や、その他のあらゆる安全性、セキュリティ、規制、または他の要件への確実な適合に関する責任を、お客様のみが単独で負うものとし、

上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されている TI 製品を使用するアプリケーションの開発の目的でのみ、TI はその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TI や第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TI およびその代理人を完全に補償するものとし、TI は一切の責任を拒否します。

TI の製品は、[TI の販売条件](#)、または [ti.com](https://www.ti.com) やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TI がこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

お客様がいかなる追加条項または代替条項を提案した場合でも、TI はそれらに異議を唱え、拒否します。

郵送先住所：Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2022, Texas Instruments Incorporated