

TI Designs: TIDA-01581

車載、昼間点灯ライト用、電流バランス機能付き2ストリングLEDドライバのリファレンス・デザイン



概要



この2ストリング発光ダイオード(LED)ドライバのリファレンス・デザインは、オペアンプを使用した回路を実装しており、2つのLEDストリングの電流バランスを確保できます。オペアンプ回路が基準ストリングの電流を検知し、ミラーリングしたストリングからのフィードバックを使用してMOSFETをバイアスするため、両ストリング間の電流をレギュレートできます。このリファレンス・デザインは、TPS92692-Q1マルチトポロジLEDドライバを昇圧構成で使用して、LEDを駆動します。TPS92692-Q1は、スペクトラム拡散周波数変調による低EMI (電磁干渉)、アナログ電流調整、内部PWM (パルス幅変調)調光を特長としています。このリファレンス・デザインは、LMT87-Q1アナログ温度センサを使用した可変線形熱フォールドバックや、ミラーリングしたストリングによる開路障害時の電流制限といった機能も備えています。また、最高輝度モード(昼間点灯ライト)と、輝度を下げるPWM調光モード(車幅灯)という2つの輝度モードをサポートしています。

リソース

TIDA-01581	デザイン・フォルダ
TPS92692-Q1	プロダクト・フォルダ
TLV2316-Q1	プロダクト・フォルダ
LMT87-Q1	プロダクト・フォルダ
LM2901-Q1	プロダクト・フォルダ



E2E™ エキスパートに質問

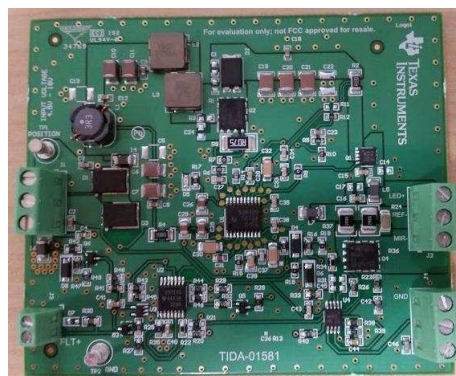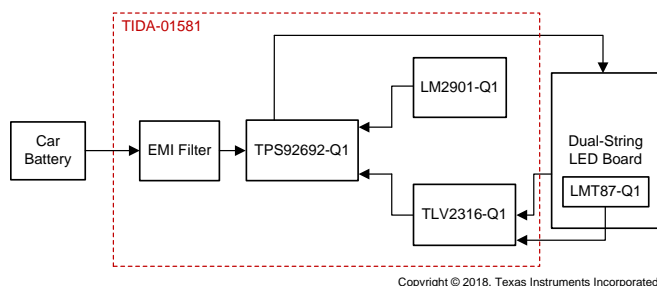

特長

- 1つのLEDドライバで2ストリング電流バランスを実現
- CISPR25 Class-5伝導および放射エミッションのテスト済み
- PWM調光により2つの輝度モードに対応
- 電流制限機能
- コールド・クランク時も動作
- マイクロコントローラ・ユニット(MCU)不要

アプリケーション

- 車載昼間点灯ライト
- 車載ヘッドライト
- 車載テールランプ/ブレーキランプ



使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE(重要な注意事項)をご参照くださいますようお願いいたします。英語版のTI製品についての情報を翻訳したこの資料は、製品の概要を確認する目的で便宜的に提供しているものです。該当する正式な英語版の最新情報は、www.ti.comで閲覧でき、その内容が常に優先されます。TIでは翻訳の正確性および妥当性につきましては一切保証いたしません。実際の設計などの前には、必ず最新版の英語版をご参照くださいますようお願いいたします。

1 System Description

This reference design details a solution for driving two parallel LED strings in applications for automotive daytime-running lights or position lamps using only a single LED driver, while keeping the current in the two LED strings equal. Implementation of this dual-string current mirror design can reduce the voltage required to drive the LEDs by half as compared to driving the same number of LEDs in series. The system also includes EMI filtering, thermal foldback, and current limiting. EMI filtering reduces conducted and radiated emissions. Thermal foldback can reduce the LED current as temperature increases, which protects the LEDs from thermal failure. Current limiting protects the reference string if the mirrored string fails to open. This feature is important because it prevents the intended current from doubling and flowing through the reference string in this condition.


1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Input voltage	6 V to 18 V, 14 V (typ)
Input current	980 mA at 14 V
Output current (per string)	200 mA
Output power (both strings)	12 W
Output voltage	30 V (typ)
Number of series LEDs	10
LED forward voltage	3 V (typ)
Current balance accuracy	±2%
Boost converter switching frequency	390 kHz
Spread-spectrum frequency modulation dither frequency	600 Hz
PWM dimming frequency	240 Hz
Form factor	77 mm × 66 mm, two-layer

2 System Overview

2.1 Block Diagram

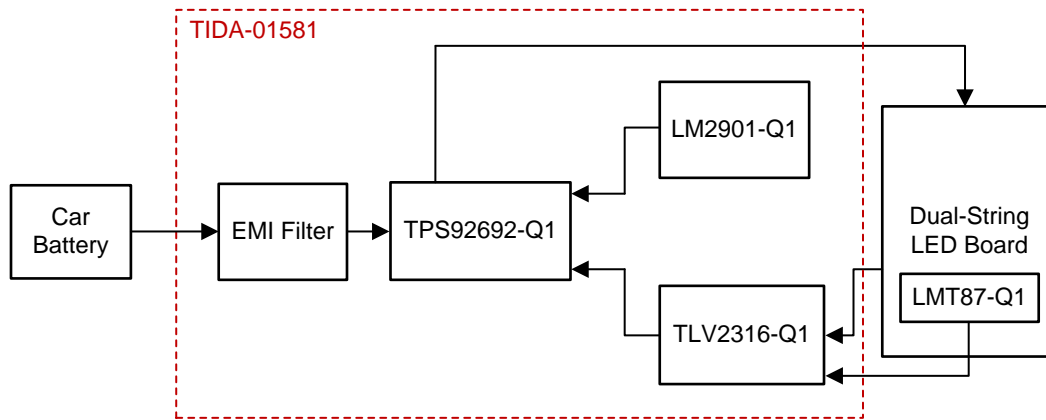

Copyright © 2018, Texas Instruments Incorporated

図 1. TIDA-01581 Block Diagram


2.2 Highlighted Products

2.2.1 TPS92692-Q1

The TPS92692-Q1 is a high-accuracy, multi-topology peak current mode controller designed for driving LEDs. The driver incorporates a rail-to-rail current amplifier to directly measure LED current. The driver can accept a wide input voltage from 4.5 V to 65 V and step-up or step-down the voltage based on the desired LED current. The user can enable spread-spectrum frequency modulation, which adds dither to the switching frequency, improving EMI performance. Additional features include analog dimming, integrated PWM generation, fault protection, current monitoring, and thermal protection. This device also has an accessible internal 5-V reference voltage which is used to power the other devices, and can source up to 30 mA.

Control the LED current with analog or PWM dimming. A linear analog dimming response can be achieved by varying the voltage of the high-impedance IADJ pin between 140 mV to 2.25 V. In this design, analog dimming is coupled with the LMT87-Q1 and an amplifier to achieve linear thermal foldback. Alternately, the average LED current can be controlled with the internal PWM generator. Accomplish this task by varying the voltage on the DIM/PWM pin between 1 V and 3 V, which sets the duty cycle of the PWM waveform.

図 2 shows the TPS92692-Q1 functional block diagram.

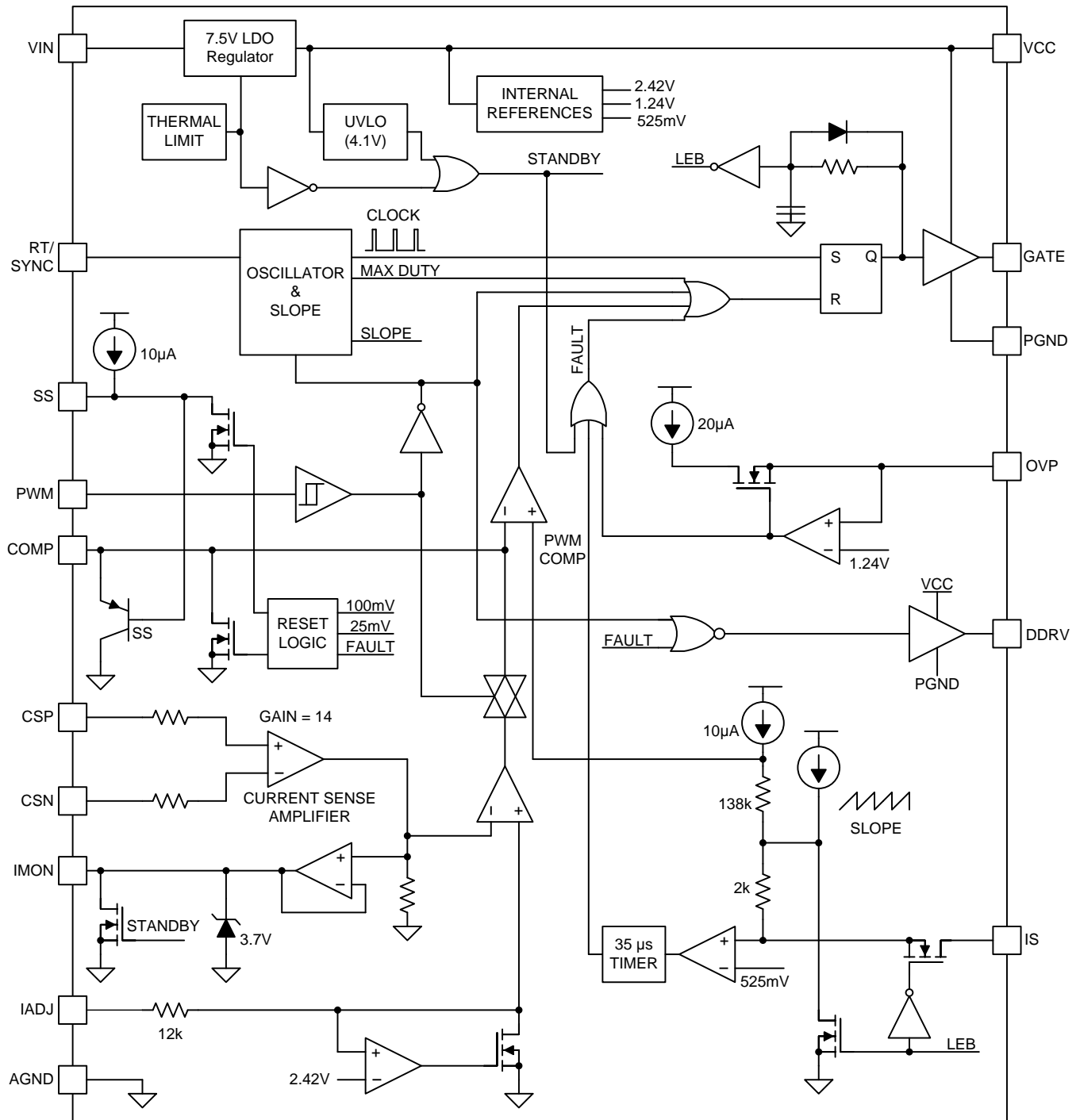

Copyright © 2017, Texas Instruments Incorporated

図 2. TPS92692-Q1 Block Diagram

2.2.2 LMT87-Q1

The LMT87-Q1 is a low-power, precision CMOS temperature sensor with a linear voltage output. The device emulates a negative temperature coefficient (NTC) thermistor by having an output voltage that is inversely proportional to temperature. Unlike a thermistor, the device has an exceptional linear response, which allows for linear thermal foldback in this design. The LMT87-Q1 resides on the printed-circuit board (PCB) containing the LED strings to sense the heat being generated by the LEDs, and reduce the current if necessary.

図 3 shows the LMT87-Q1 functional block diagram.


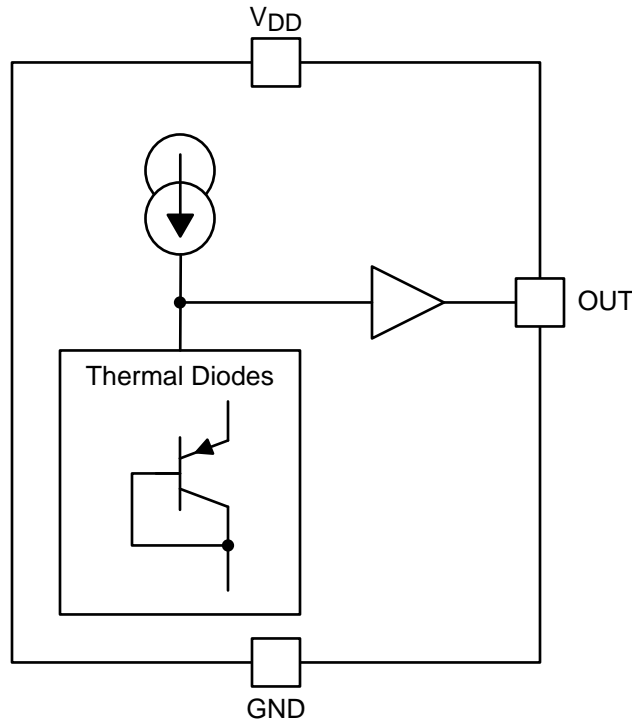


図 3. LMT87-Q1 Block Diagram

2.2.3 TLV2316-Q1

TLV2316-Q1 is a dual-channel, low-power, general-purpose op amp for cost-sensitive systems. The device features rail-to-rail input and output swings, low quiescent current, and a wide bandwidth of 10 MHz. In this design, the TLV2316-Q1 is coupled with a MOSFET to accurately balance the current between the two strings of LEDs. In addition, one channel is used for signal conditioning the temperature sensor and allows the designer to adjust the thermal foldback start point.

Figure 4 shows the TLV2316-Q1 functional block diagram.

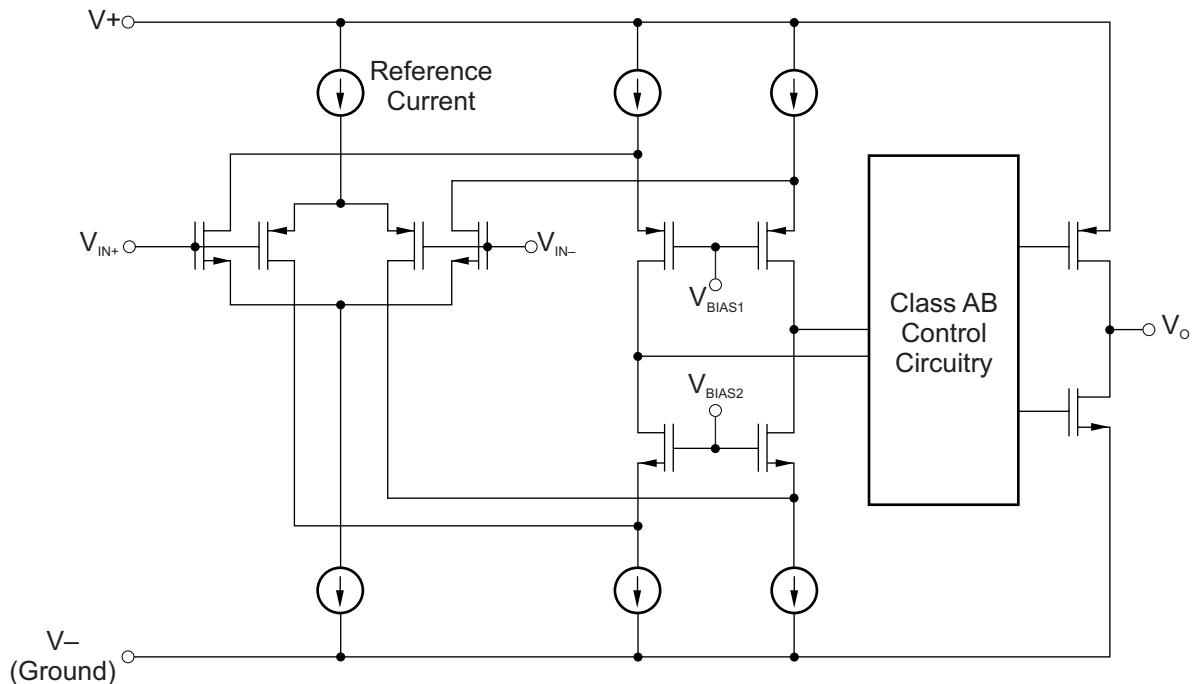


Copyright © 2016, Texas Instruments Incorporated

Figure 4. TLV2316-Q1 Block Diagram

2.2.4 LM2901-Q1

LM2901-Q1 is a quad-channel, high voltage comparator. In this reference design, one channel is used to current limit the reference string in the event of an open-circuit failure of the secondary string. The other channels can be used for fault detection or other functions.

Figure 5 shows the LM2901-Q1 functional block diagram.

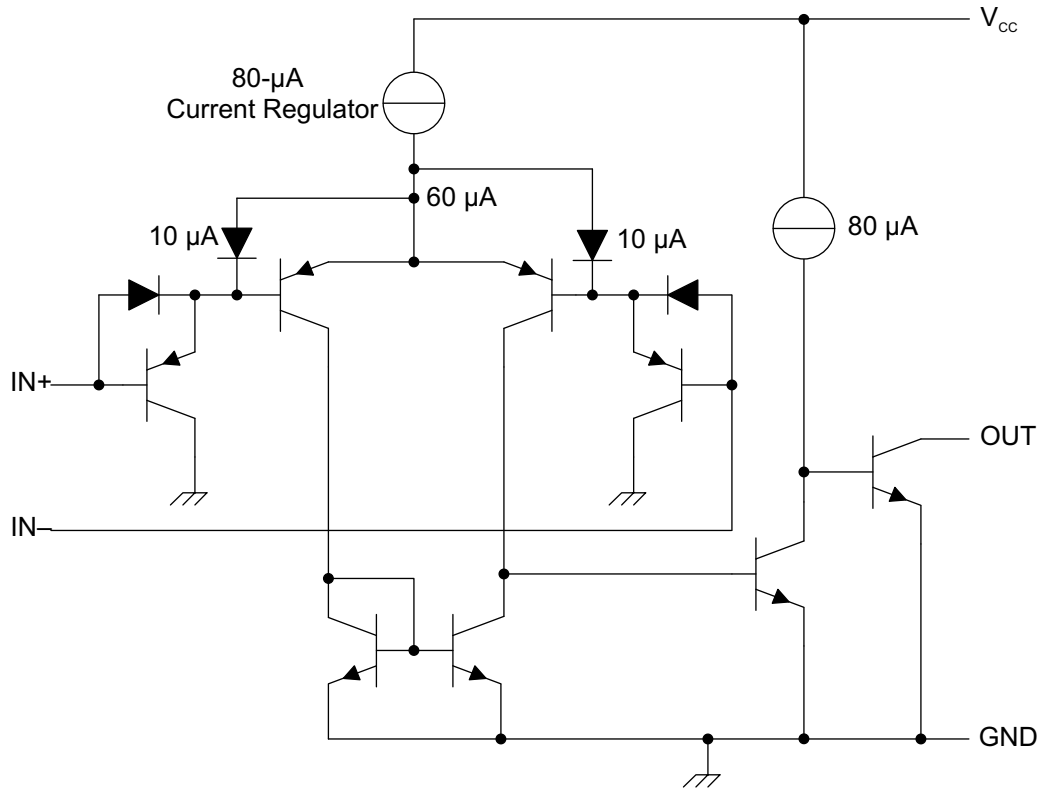

Copyright © 2016, Texas Instruments Incorporated

Figure 5. LM2901-Q1 Block Diagram

2.3 System Design Theory

2.3.1 Current Balancing

A requirement of this design is to use a single LED driver to drive two parallel strings of LEDs. If the LED strings are connected in parallel without a balancing circuit, the current in each string fluctuates due to variation in the LED forward voltage. The LED forward voltage can change with both temperature and manufacturing process variation. Use of an op-amp-based mirror accomplishes the current balancing in this design, as [Figure 6](#) shows. The low-side resistors measure the current in each string. The reference string is a string of LEDs with a low-side sense resistor that sets the current through the mirrored string. The mirrored string is in series with a low-side MOSFET that can control the amount of current flowing in the string. The op amp biases the MOSFET to force the voltage at the source to be equal to the voltage at the non-inverting terminal of the op amp. This biasing ensures that the current in each string is equal. A restriction on this circuit is that the forward voltage drop of the reference string must be greater than the mirrored string, which ensures that the MOSFET has sufficient headroom for correct biasing. The designer can accomplish this extra voltage drop in the reference string by implementing at least one more LED or a series resistor. This additional voltage drop is observable across the MOSFET in the mirrored string. Therefore, the MOSFET must dissipate the same amount of power dissipated by the additional LED or series resistor to ensure equal current in both strings. Although this requirement is restrictive, it allows for convenient fault detection that can detect a single LED that has been shorted or opened in either string.

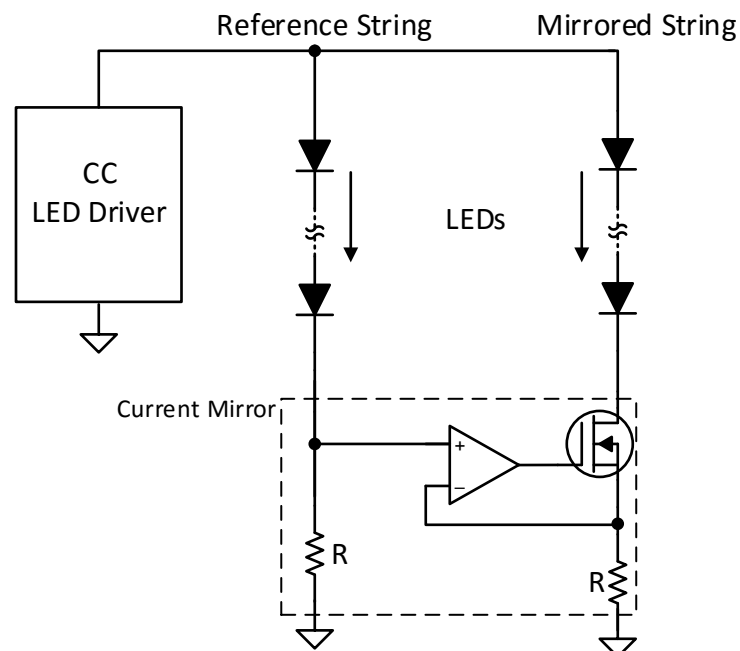


Figure 6. Block Diagram for Op-Amp-Based Current Mirror

2.3.2 Stability Analysis

Analyze the stability of this op-amp-based circuit and then provide any necessary compensation to achieve a stable design. Unstable designs may have unbalanced currents and undesired transient behavior. An effective way to perform this analysis is by using the TINA-TI™ SPICE simulation tool for AC loop-gain analysis.

To perform an AC loop-gain analysis, the user must first break the feedback loop and inject a small signal AC source. However, simply breaking the feedback path does not provide the correct DC operating point and causes the op amp to saturate to one rail. Instead, this reference design implements a circuit as shown in 図 7. The large capacitance of C1 allows AC to pass, while the large inductance of L1 blocks AC and allows DC to pass. This provides a correct DC bias point to the op amp circuit while still allowing the designer to inject a small signal source. In this circuit, VF1 represents the loop gain and indicates stability. For more information on op-amp AC analysis in TINA-TI, see the section regarding Stability in the *TI Precision Labs - Op Amps* training resource.

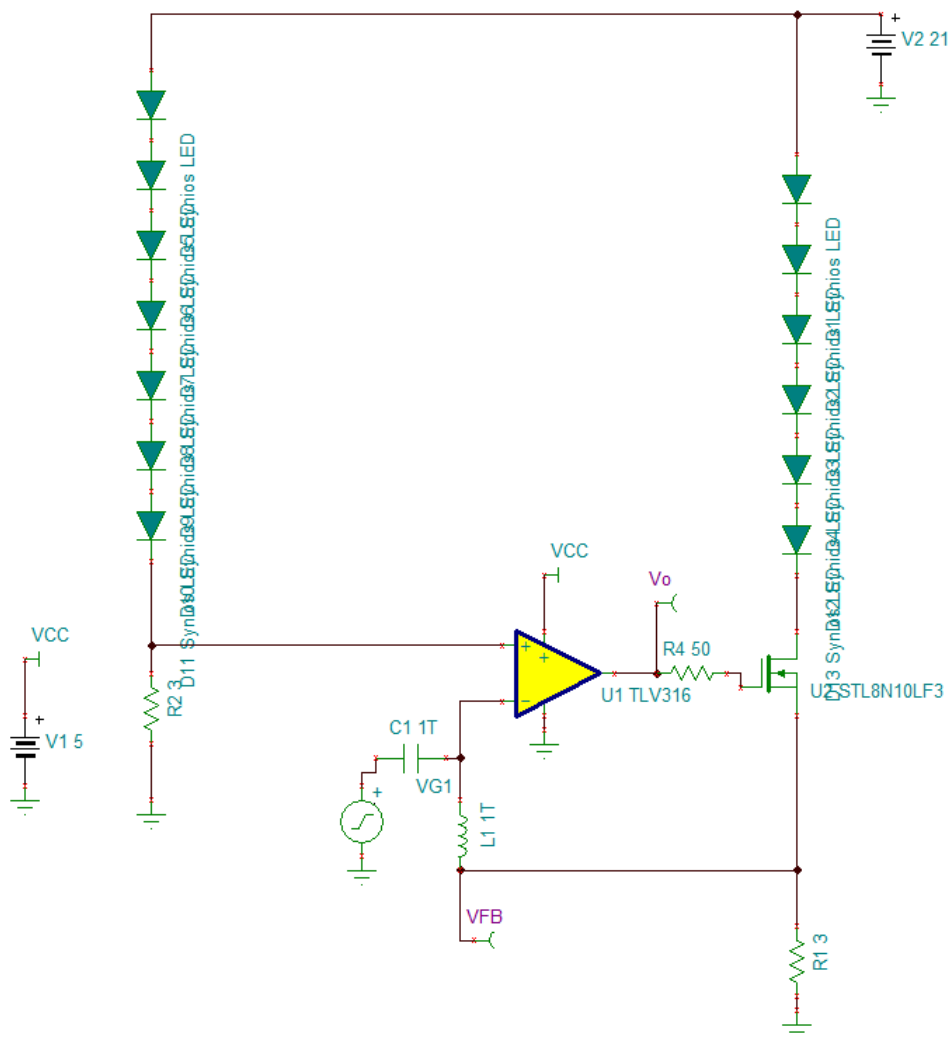


図 7. TINA-TI™ Circuit for AC Analysis

Figure 8 shows the results of an AC sweep. The phase margin is approximately 8° and the rate of closure is greater than 20 dB, so the system is unstable. Additional compensation is necessary to achieve a stable design.

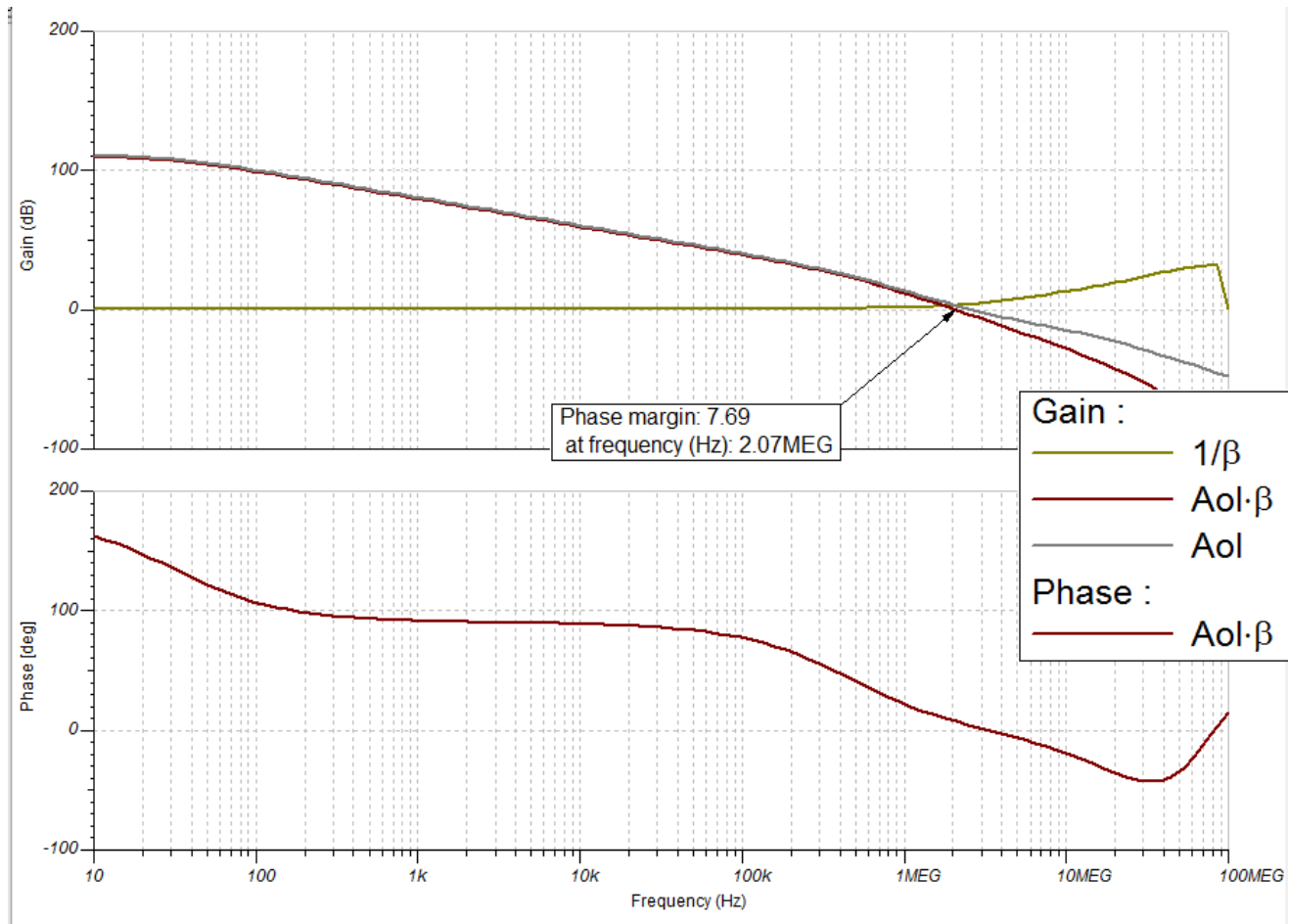


Figure 8. TINA-TI™ AC Sweep Showing Circuit Instability

Figure 9 shows the circuit with compensation. R3, R5, and C2 form a noise-gain compensation network that pushes up the loop-gain phase at the crossover frequency. Figure 10 shows the AC sweep after the compensation components have been added. The phase margin is approximately 49°. Noise-gain compensation adds a zero-pole pair to the 1/beta curve and increases the gain at high frequency. This compensation results in a lower frequency intersection of the Aol and 1/beta curves with a stable 20-dB per decade rate of closure between them.

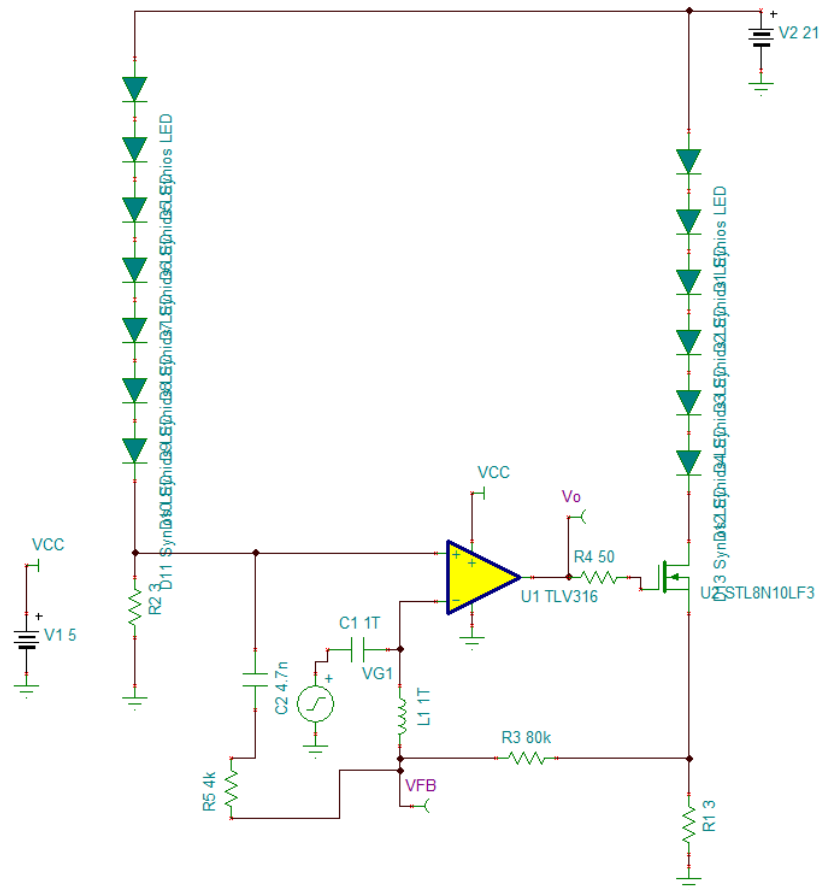


Figure 9. TINA-TI™ Compensated Current Mirror Circuit

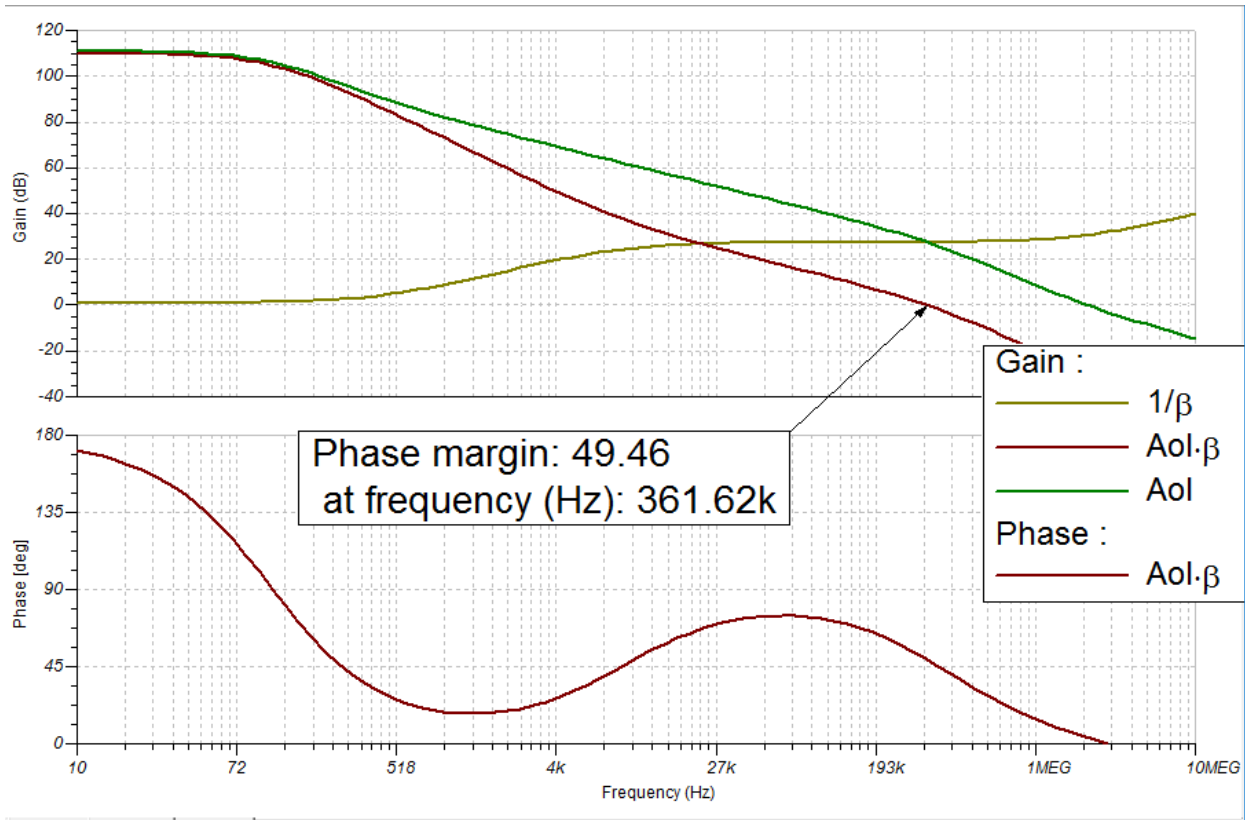


図 10. TINA-TI™ AC Sweep of Compensated Circuit

2.3.3 Position and DRL Modes

This design features two operating modes for setting the brightness of the LEDs: Position and DRL. In DRL mode, the LEDs operate at full brightness and the current is limited by the internal current sense amplifier connected to the current sense resistor R_{CS} . 式 1 sets the LED current. A value of 0.43Ω has been chosen to set the total current to approximately 400 mA, or 200 mA per string.

$$I_{LED} = 170.7 \frac{mV}{R_{CS}} \tag{1}$$

In Position mode, the LEDs are dimmed using the TPS92692 internal PWM generator. A voltage between 1 V and 3 V sets the PWM duty cycle between 0% and 100%, respectively. In this design, the duty cycle is set to 8% after enabling the Position mode. 図 11 shows the components used to set up the two modes. In Position mode, the resistor divider formed by R16 and R19 sets the voltage at the DIM/PWM pin. If connecting the DRL pin instead, the VBAT2 connection that sets the duty cycle to 100% overrides the voltage at this pin. R18 and R19 set the voltage.


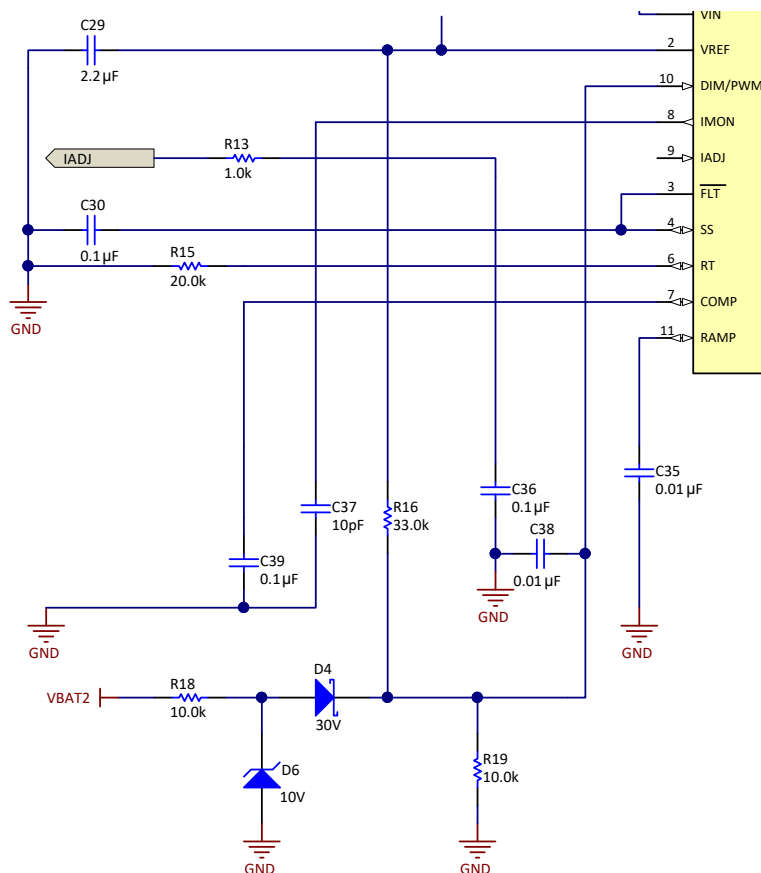
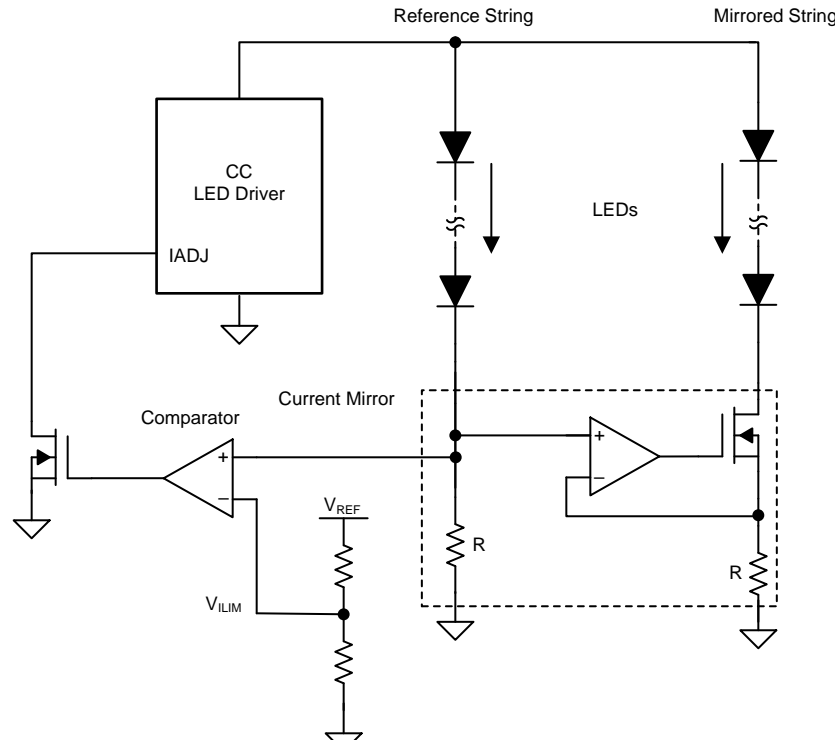


図 11. 'DRL' and 'Position' Schematic

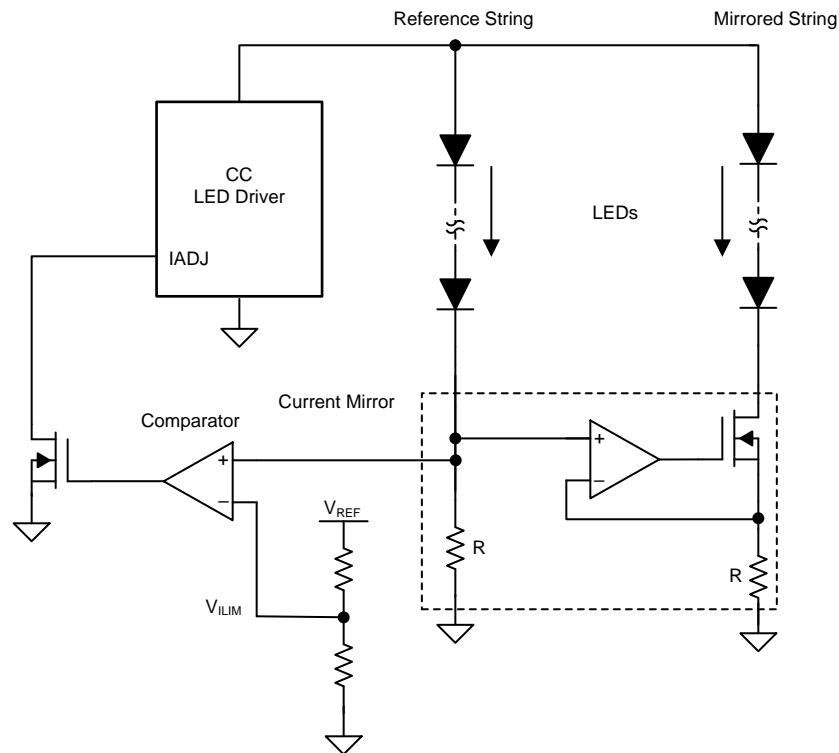2.3.4 Reference String Current Limit

Because the current-balancing circuit relies on the reference string, if the mirrored string fails to open, then all of the current is free to flow through the reference string. The driver monitors the current it delivers and increases the voltage to push the full current through one string, which doubles the intended current through the LEDs. This high current can generate heat and pose a hazard if the LEDs are not rated for the current.

To account for this hazard, use a simple comparator circuit to monitor the current in the reference string. If the current rises above a threshold, the comparator turns on a field-effect transistor (FET) and pulls down the IADJ pin. This process repeats when the current falls back below the threshold, which causes a flickering. The purpose is not to maintain operation of the LEDs, but to prevent an overheating condition. The fault detection circuit will indicate if the mirrored string has failed.  12 shows the current-limiting circuit. V_{ILM} is the voltage at which the current must be limited. Determine this voltage by using $V_{ILM} = I_{LM} \times R$ where I_{LM} is set at or below the maximum continuous LED current. In this case, the limit is set to 300 mA, which is the maximum current for these LEDs. If the LEDs used can handle double the intended current, implementing this circuit may not be necessary.



 12. Reference String Current Limit

2.3.5 Thermal Foldback

This design includes an adjustable thermal foldback that reduces the LED current as the LED board temperature increases. This foldback prevents the LEDs from overheating. Achieve this thermal foldback by using the LMT87-Q1 temperature sensor to adjust the voltage on the analog dimming pin (IADJ). Use a non-inverting amplifier to interface the temperature sensor with the LED driver. 図 13 shows the amplifier schematic. J4 connects directly to the temperature sensor on the LED PCB.

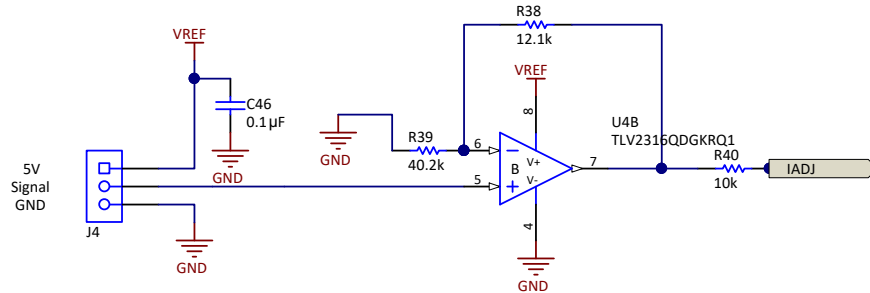


図 13. Thermal Foldback Amplifier Schematic

To set the led current between 0% and 100%, modulate the analog dimming pin (IADJ) between 140 mV to 2.25 V. The LMT87-Q1 varies the output voltage from 3.25 V to 0.5 V over a temperature range of -50°C to 150°C . Use the non-inverting amplifier to adjust the temperature at which the foldback begins, which is based on the gain value. 式 2 shows the output voltage of the LMT87-Q1 as a function of temperature.

$$V_{\text{TEMP}} (\text{mV}) = 2230.8 \text{ mV} - \left(13.582 \frac{\text{mV}}{^{\circ}\text{C}} (T - 30^{\circ}\text{C}) \right) - \left(0.00433 \frac{\text{mV}}{^{\circ}\text{C}^2} (T - 30^{\circ}\text{C})^2 \right) \quad (2)$$

図 14 shows the voltage at the output of the LMT87-Q1 device as well as the output amplified by a gain of 1.3, which is the voltage at the IADJ pin. The black horizontal line shows where the thermal foldback begins for each voltage curve. Higher gains cause the thermal foldback to begin at a higher temperature.

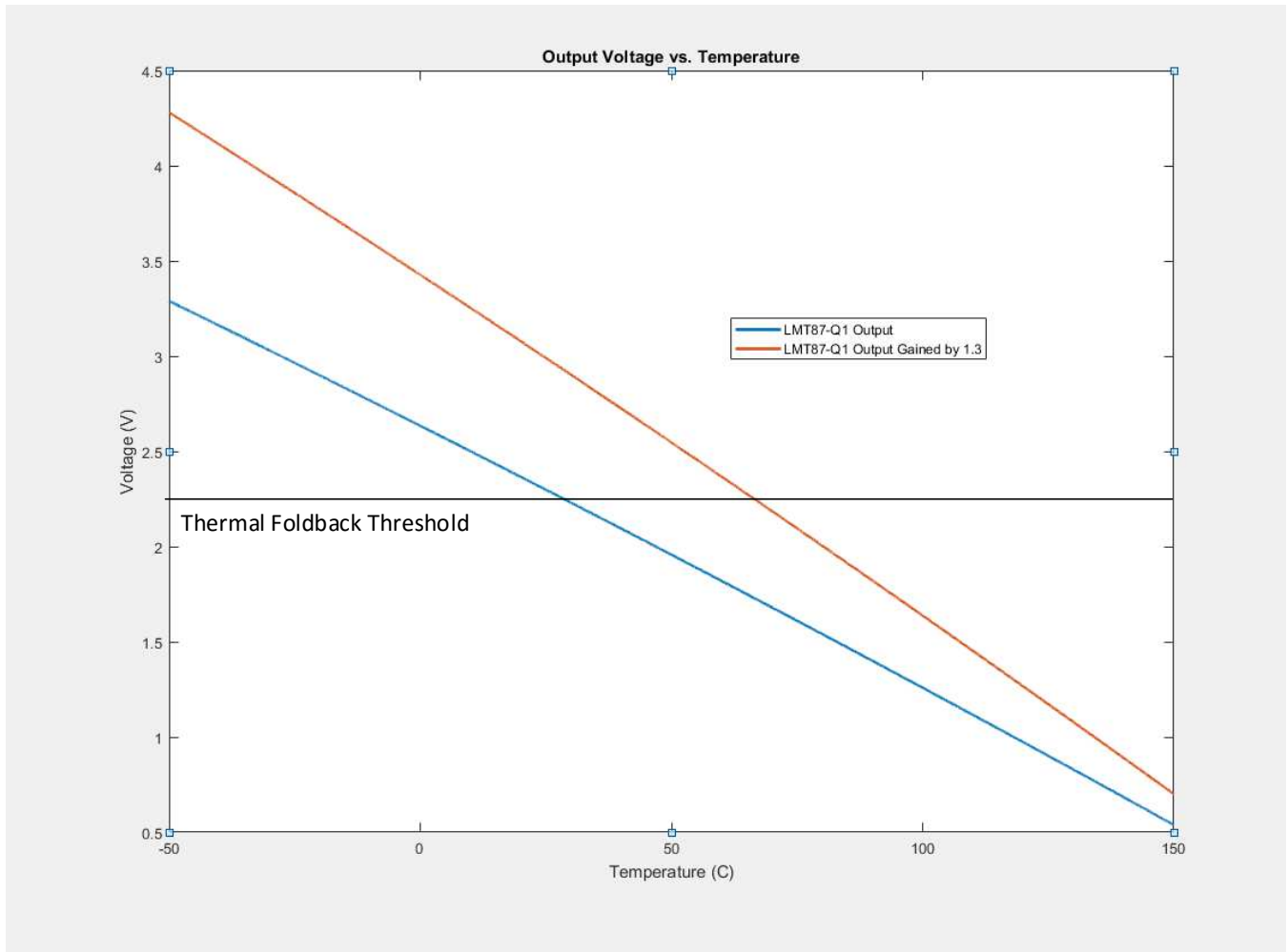


図 14. LMT87-Q1 Output Voltage and Amplified Output Voltage

The result as given by [Figure 15](#) is produced by multiplying the LMT87 output voltage by the chosen amplifier gain and calculating the LED current output. The gain in this design is set to 1.3.

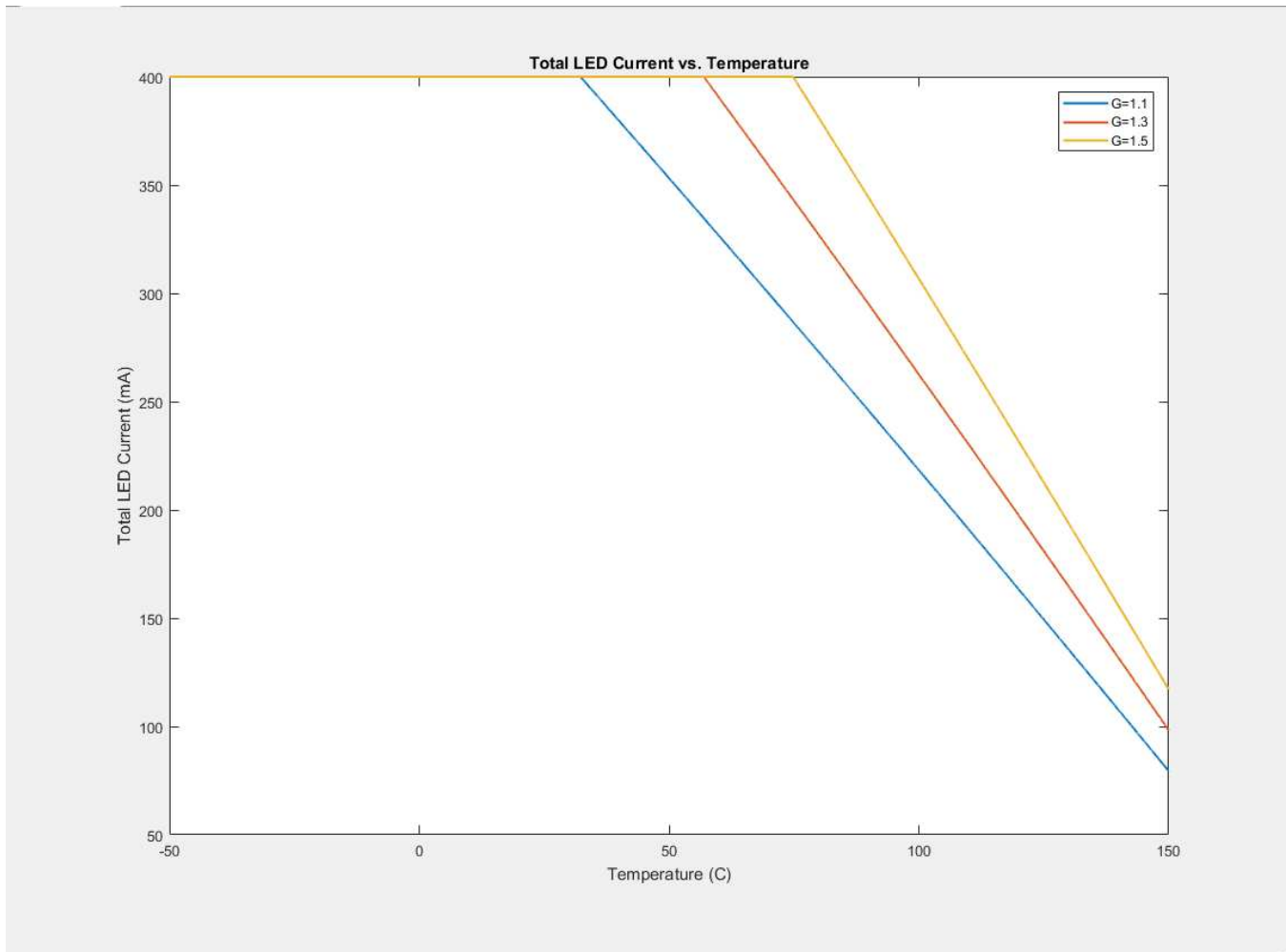


Figure 15. Thermal Foldback Response for Different Amplifier Gains

3 Hardware, Software, Testing Requirements, and Test Results

3.1 Required Hardware and Software

3.1.1 Hardware

The required hardware consists of the LED driver board and an LED daughterboard which contains the LEDs and temperature sensor. The LEDs used on the LED board for testing are Osram Synios P2720. The LED+ connection on the driver board must be connected to the positive of both LED strings. The negative of the strings must be connected REF– and MIR– connections on the driver board. The temperature sensor must be properly connected to the 5V, GND, and Signal connections of the driver board. [Figure 16](#) shows the proper way to connect the LED board and LED driver board.

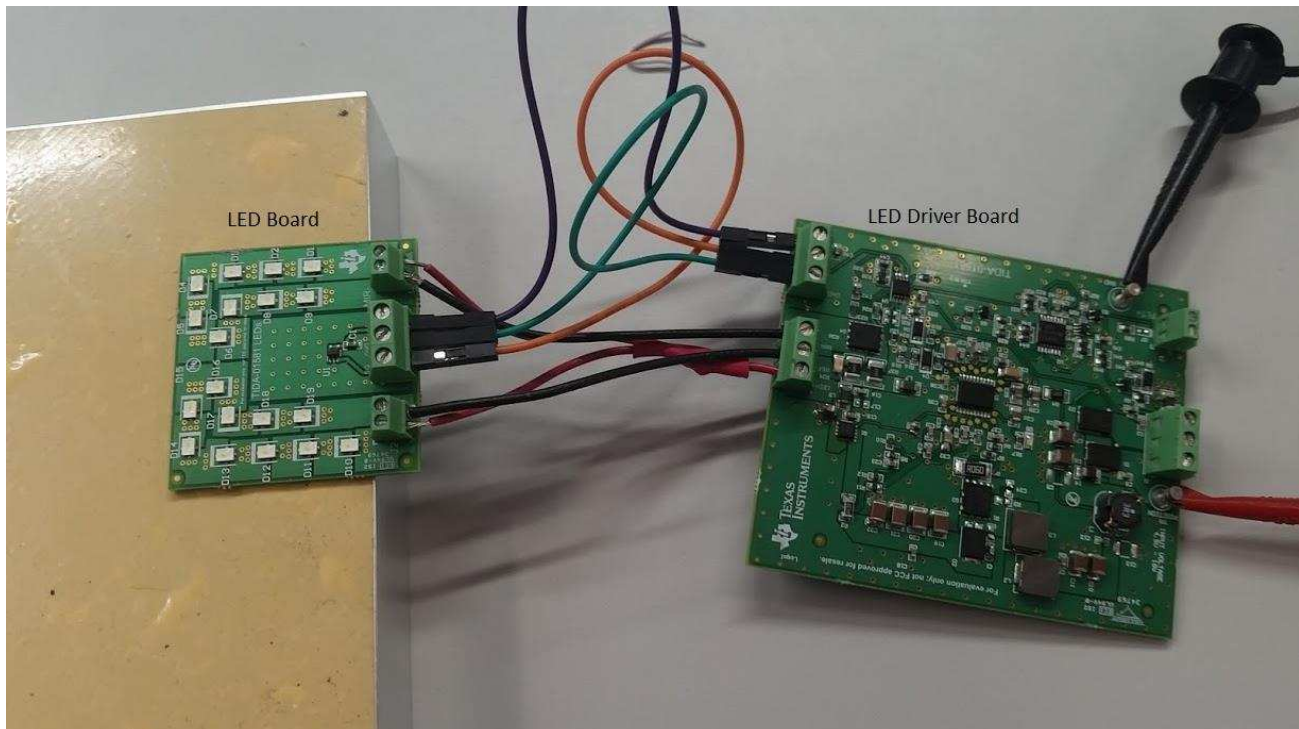


図 16. Driver Board and LED Board Connection

3.2 Testing and Results

3.2.1 Current Balance Accuracy

After connecting the LED driver board to the LED board, as specified in *Hardware*, a 14-V DC was applied to the DRL connection. Current probes were used to measure the current in each string during start-up. [Figure 17](#) shows the current in each string during start-up. This result shows that the current-balancing circuit accurately controls the current through both strings. The current in each string settles smoothly to 200 mA.

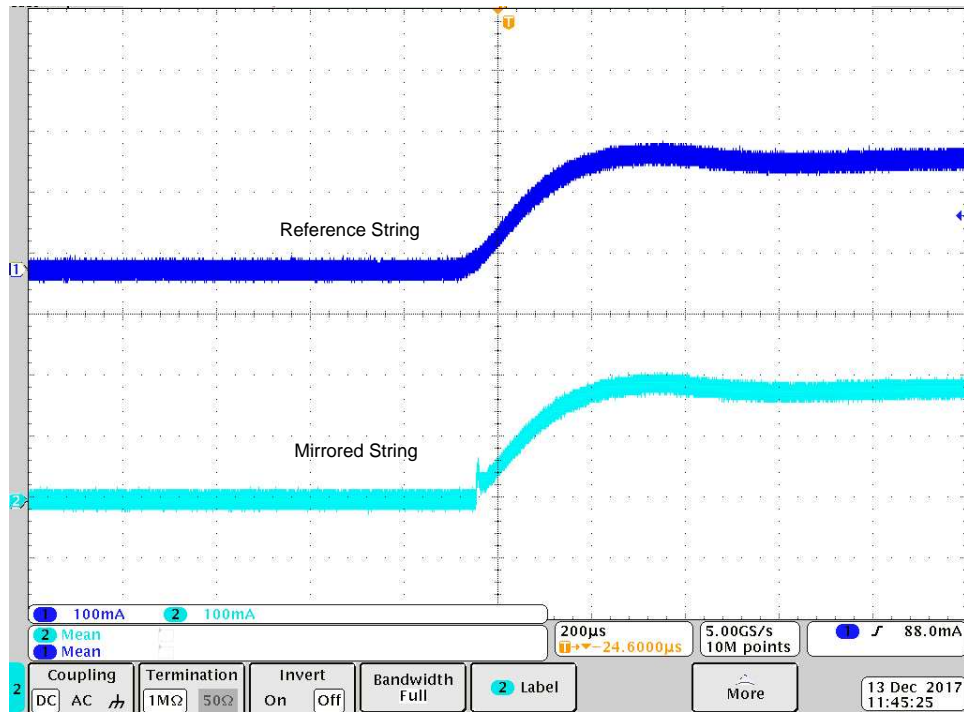


Figure 17. Turnon Current in Each String in 'DRL' Mode

The steady-state current in DRL mode was also measured in both strings to indicate the accuracy balance, which [Figure 18](#) shows. This result also shows a difference of 2 mA between the strings.

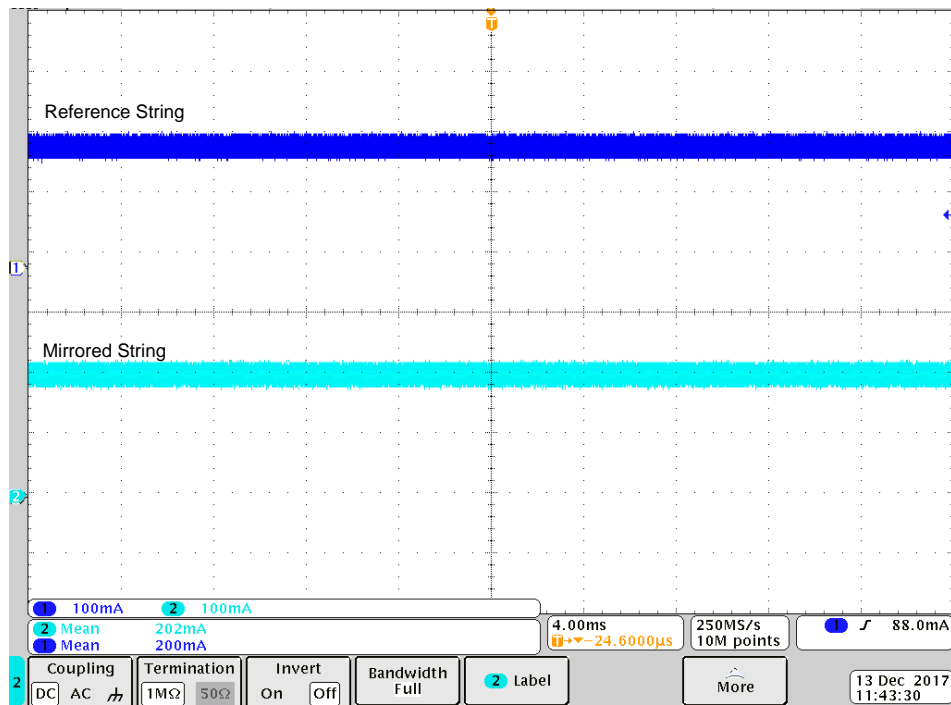
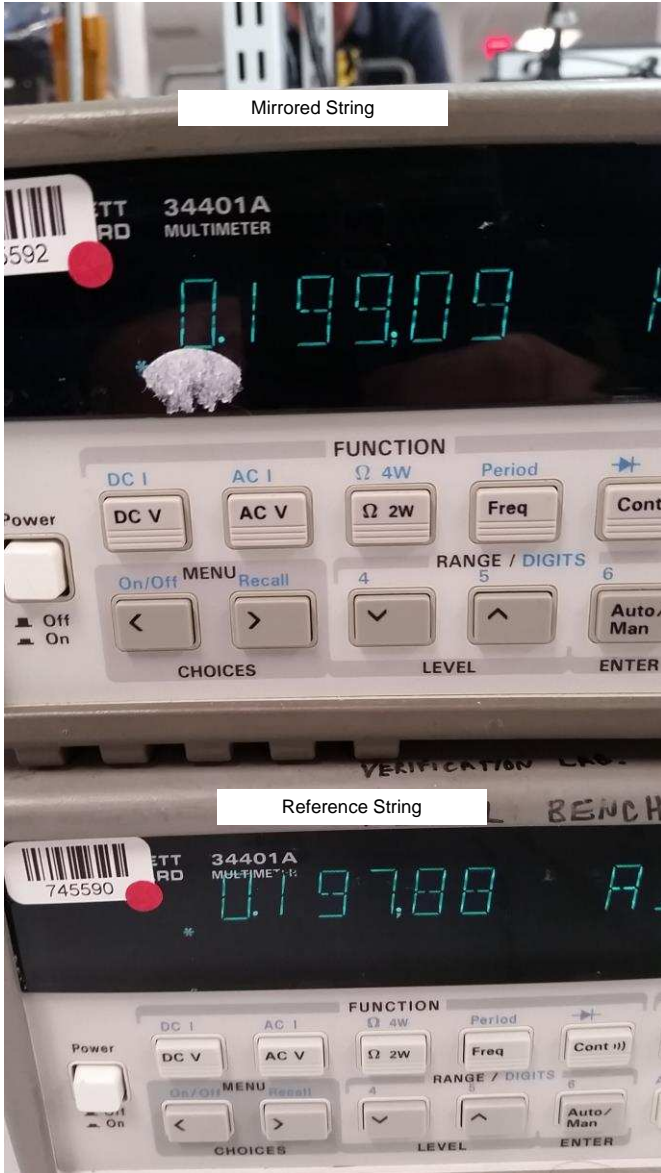


図 18. Steady-State Current Oscilloscope Capture in 'DRL' Mode

The average current in each string was also measured with two ammeters in DRL mode. This result is more accurate than the oscilloscope capture.  19 shows a photo of the results. The current difference between the strings is less than 1%.

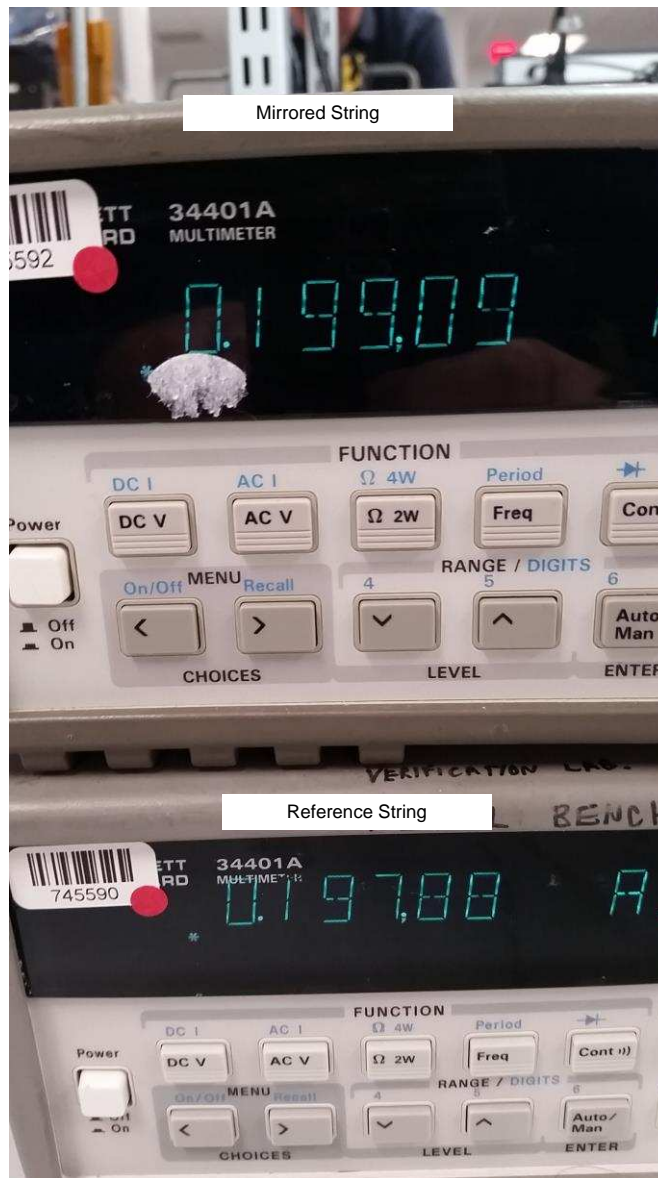

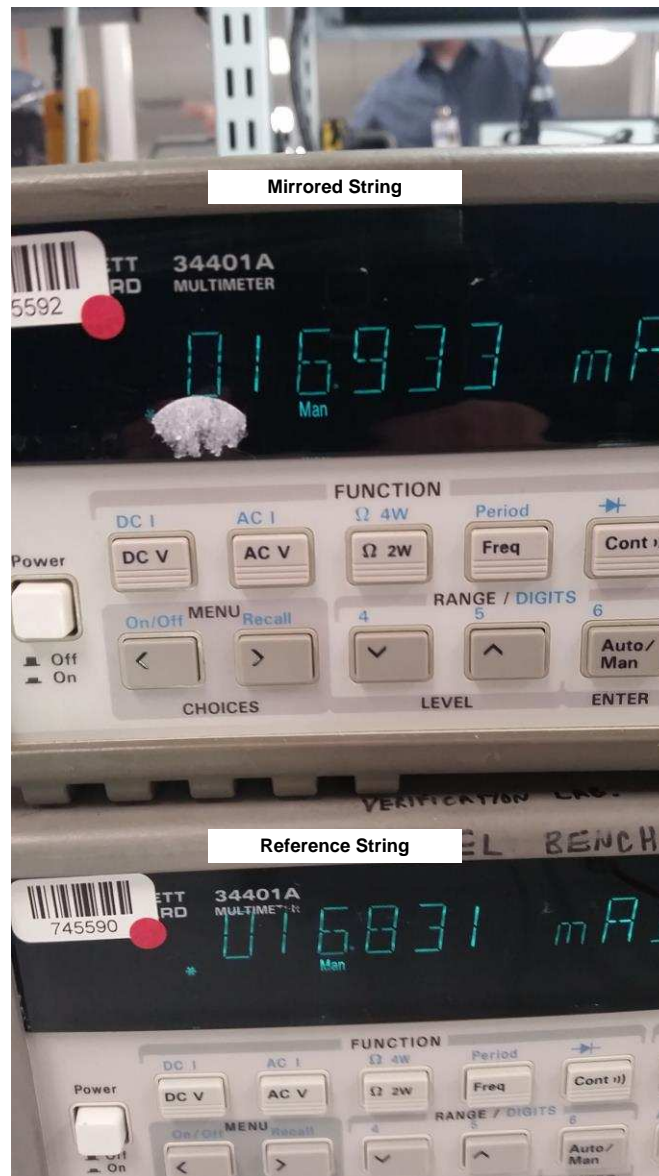


図 19. Ammeter Measurement of Average String Current in 'DRL' Mode

The ammeter measurement was repeated for the Position mode to compare the average currents between the two strings during PWM.  20 shows an image of this result. The current difference between the two strings is less than 1%.



 20. Ammeter Measurement of Average String Current in 'Position' Mode

Figure 21 shows the PWM transient. Channel 1 is the reference current and channel 2 is the mirrored current. This result shows that the circuit accurately balances the current during PWM dimming. This result confirms an equal brightness of the strings when using the Position mode.


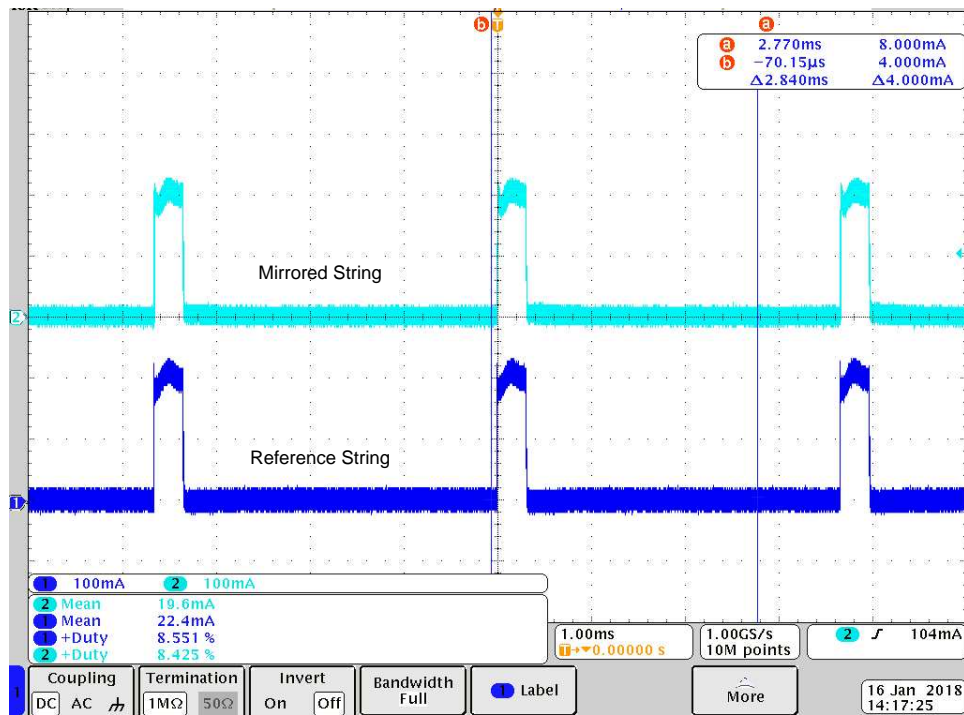
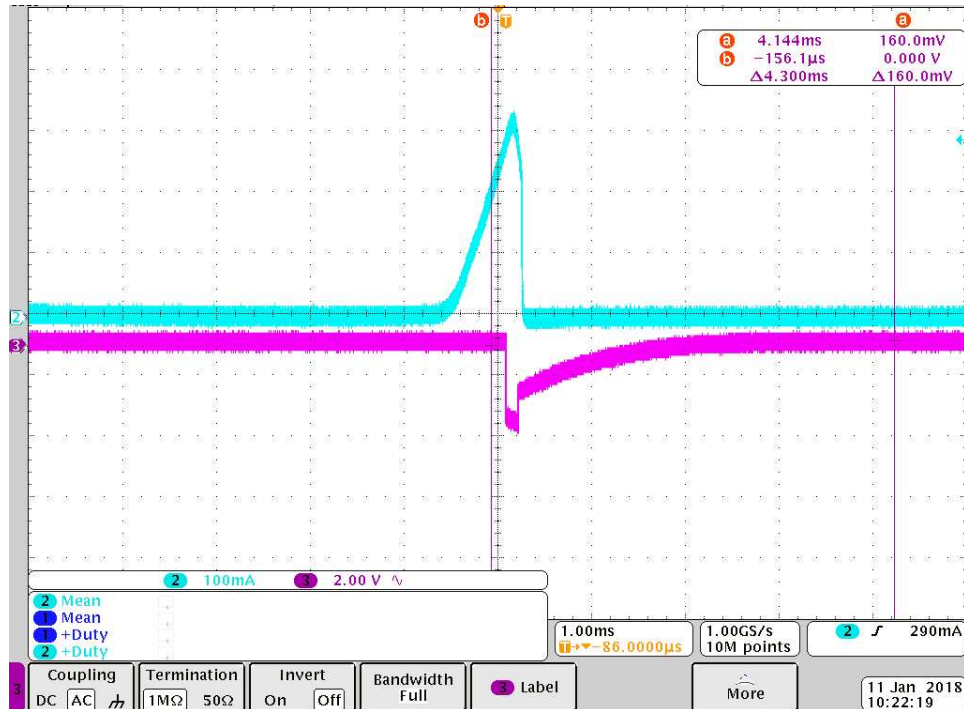


Figure 21. Reference and Mirrored-Current PWM Transient

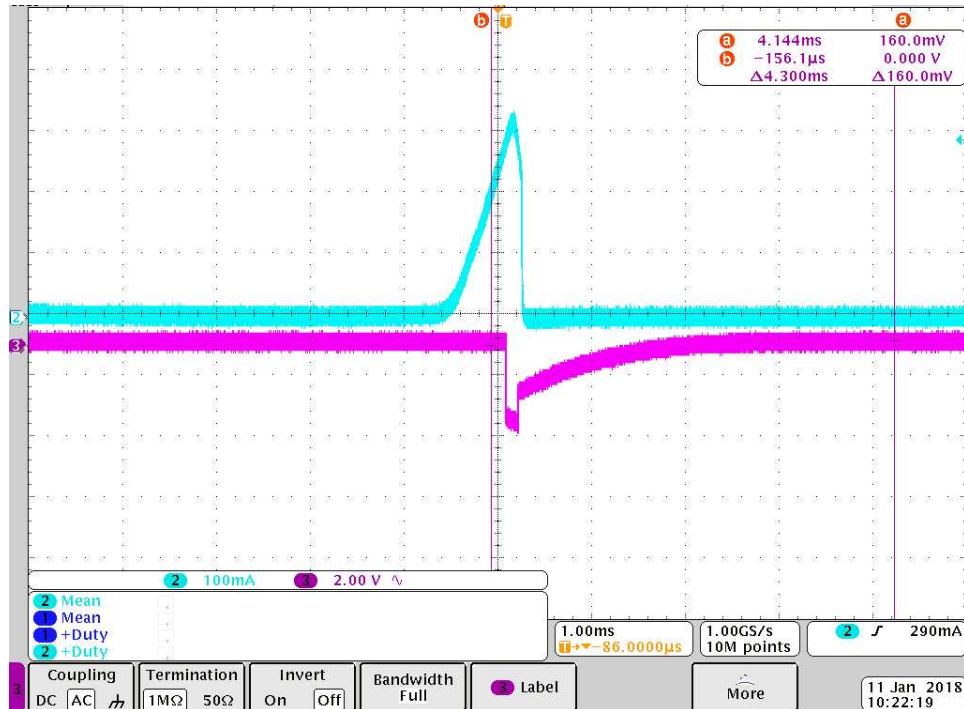3.2.2 Reference String Current Limit

The reference string current limit was tested by disconnecting the mirrored string of LEDs while the power is connected to the DRL input.  22 shows the current limit waveform. Channel 2 is the current flowing through the reference string of LEDs and channel 3 is the voltage of IADJ. When the current reaches 300 mA, the current limit circuit pulls IADJ to ground. This cycle repeats every 36 ms based on the LED driver fault timer because the device is in hiccup mode. The LEDs flicker in this condition.



 22. Waveform of Reference String Current Limit

3.2.3 Thermal Foldback Response

The LED board was heated from 20°C to 125°C and the current was measured. [図 23](#) shows both the calculated response and measured response. The measured response accurately corresponds with the calculated response described in [2.3.5](#).

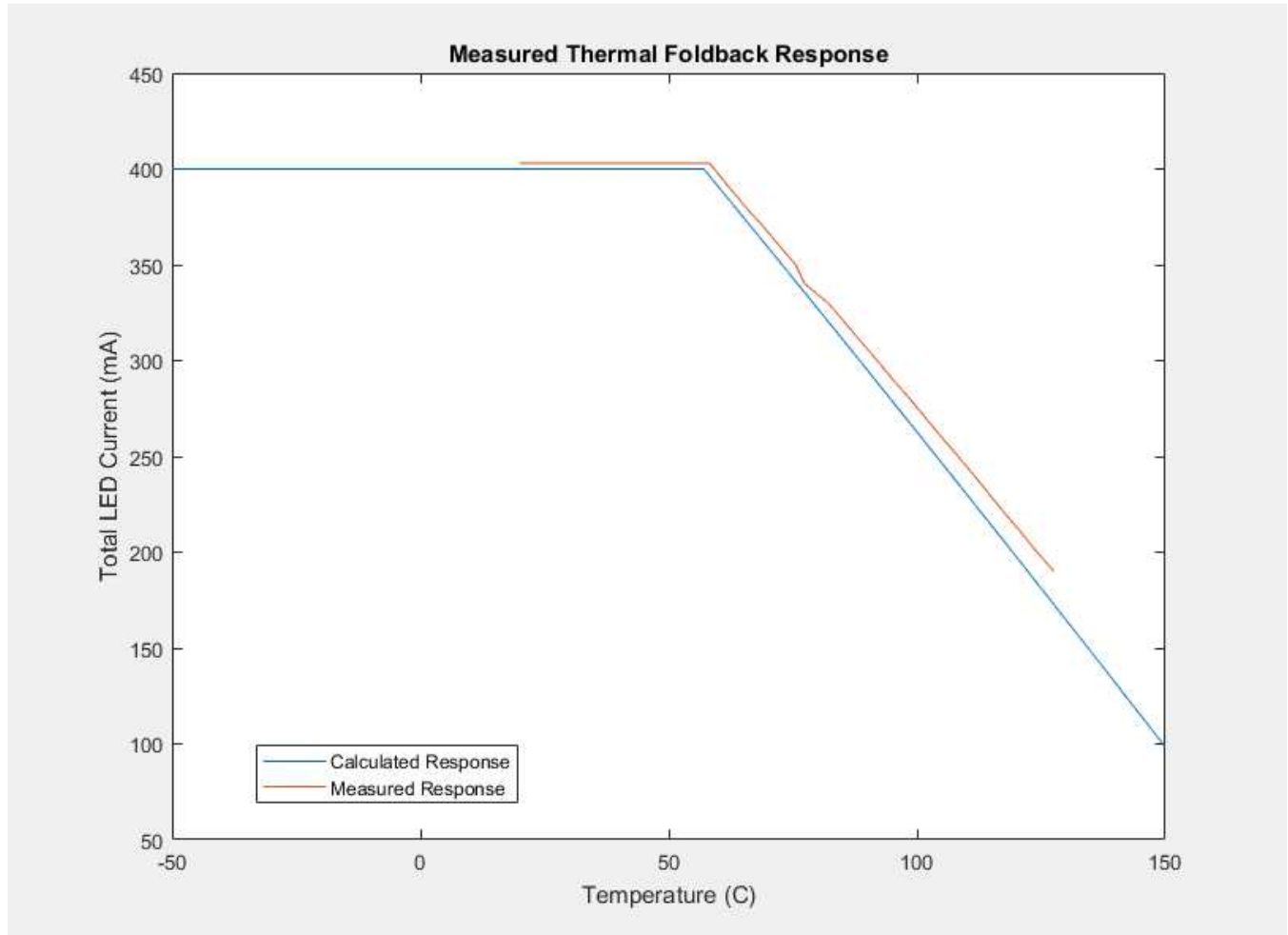


図 23. Calculated and Measured Thermal Foldback Response

3.2.4 Thermal Image

図 24 shows a thermal image of the reference design in DRL mode operation at room temperature with the board driving the LEDs at 12 W. The recorded maximum temperature is 50°C. The reverse polarity protection diode, the switched-mode power-supply (SMPS) switching MOSFET, and the current balancing MOSFET have the highest temperature regions.

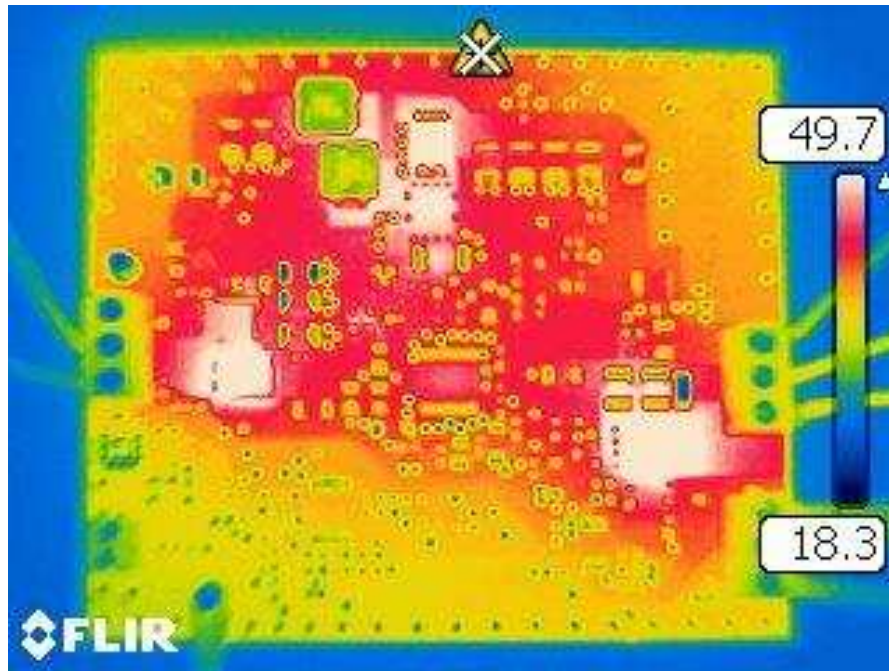


図 24. Thermal Image of TIDA-01581

3.2.5 EMI Testing Unshielded Inductors

The reference design was tested against CISPR25 Class-5 limits for both conducted and radiated emissions. The board was tested in DRL mode in which it drove 19 LEDs at a current of 200 mA and power of 12 W.

Before EMI testing, the switch node was examined for ringing. In 図 25, the switch node is the node connected to the output of the inductor (L3), the anode of the rectification diode (D2), and the switching MOSFET Q2. Switch node ringing has a significant negative impact on EMI results and must be addressed before running EMI tests. 図 26 shows the switch node waveform measured directly from the inductor output to ground using the tip and barrel method. Note the significant ringing on the rising edge of the waveform.

A snubber circuit across the rectifying diode was used to eliminate this ringing before EMI testing. 図 25 (R1,C1) shows this snubber circuit. The actual values used were $R1 = 15 \Omega$ and $C1 = 470 \text{ pF}$. The snubber effectively dissipates high-frequency AC signals such as the ringing waveform. For additional details on using an RC snubber to minimize ringing in a boost converter design, see [Minimizing Ringing at the Switch Node of a Boost Converter](#). A gate resistor was also added to the switching FET to slow the rise time, which results in a small decrease in efficiency but improves EMI performance.

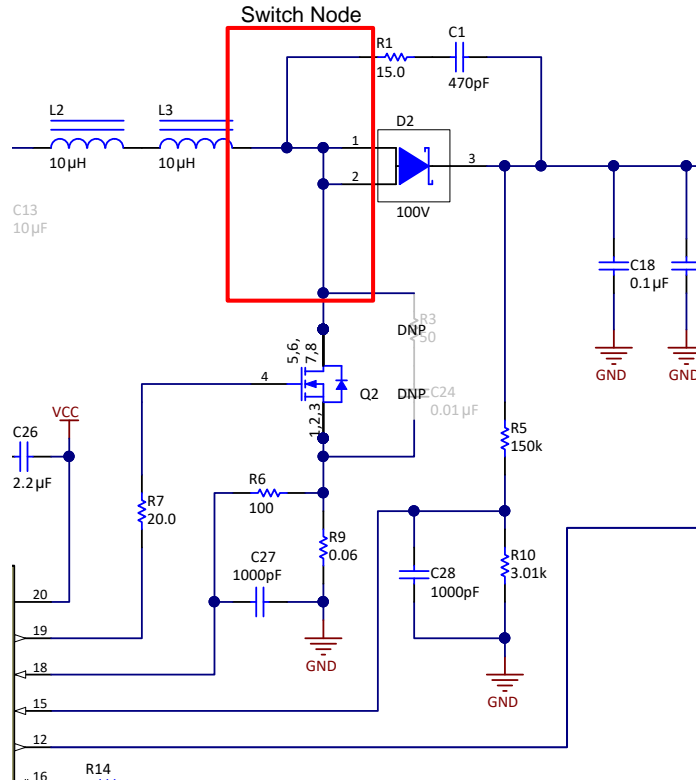


図 25. Snubber Circuit (R1,C1)

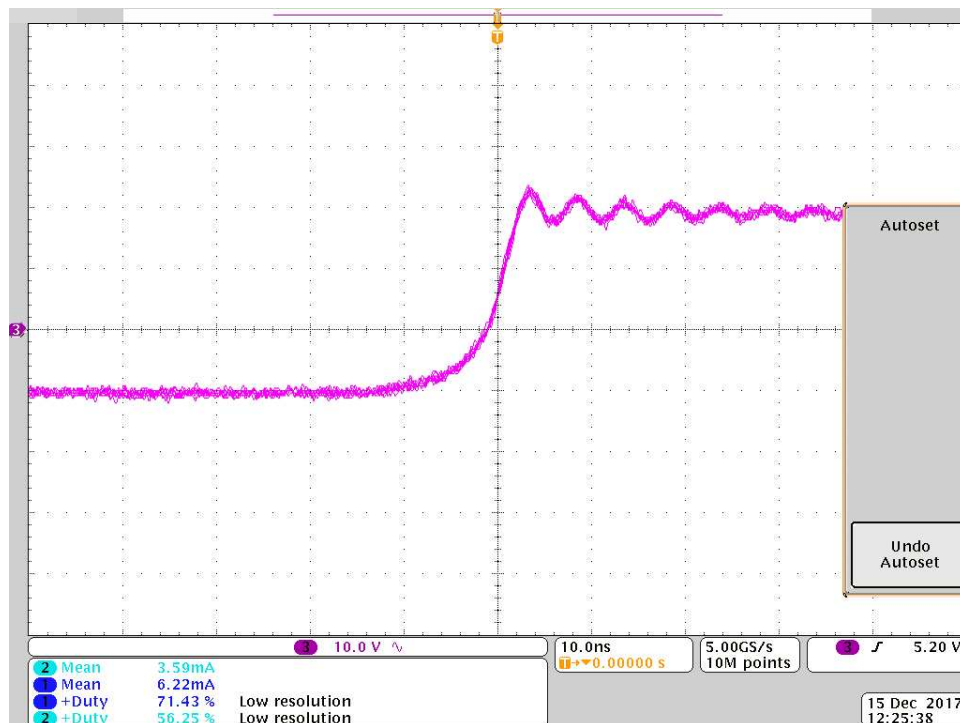


図 26. Switch Node Waveform

EMI tests were performed on the board with both unshielded and shielded inductors. [Fig 27](#) shows an image of the board with unshielded inductors (Vishay IHLP-2525BD-A1). In this design, two smaller inductors in series were used instead of one large inductor. In this case, two 10- μ H were placed in series instead of a single 22 μ H. The reason for doing this is because smaller components perform better in vibration and physical stress testing. The smaller inductors are less likely to have an issue, such as breaking off the board or breaking a solder joint during stress tests.



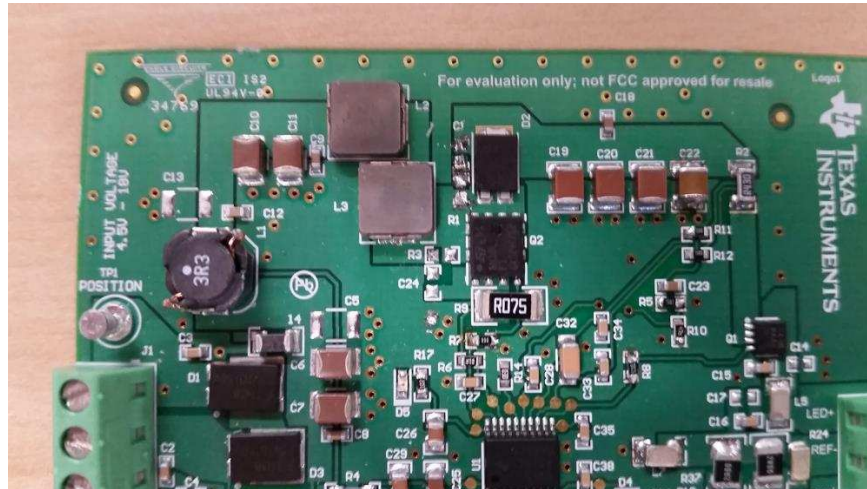
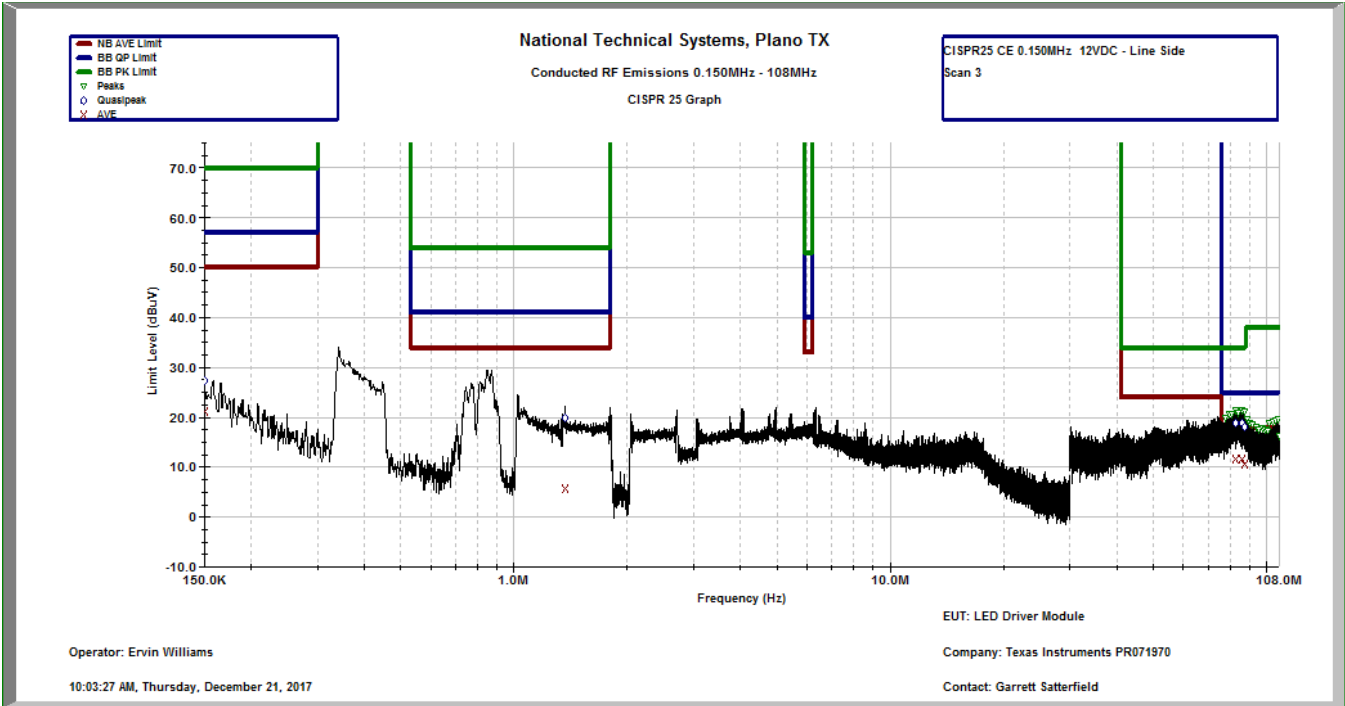
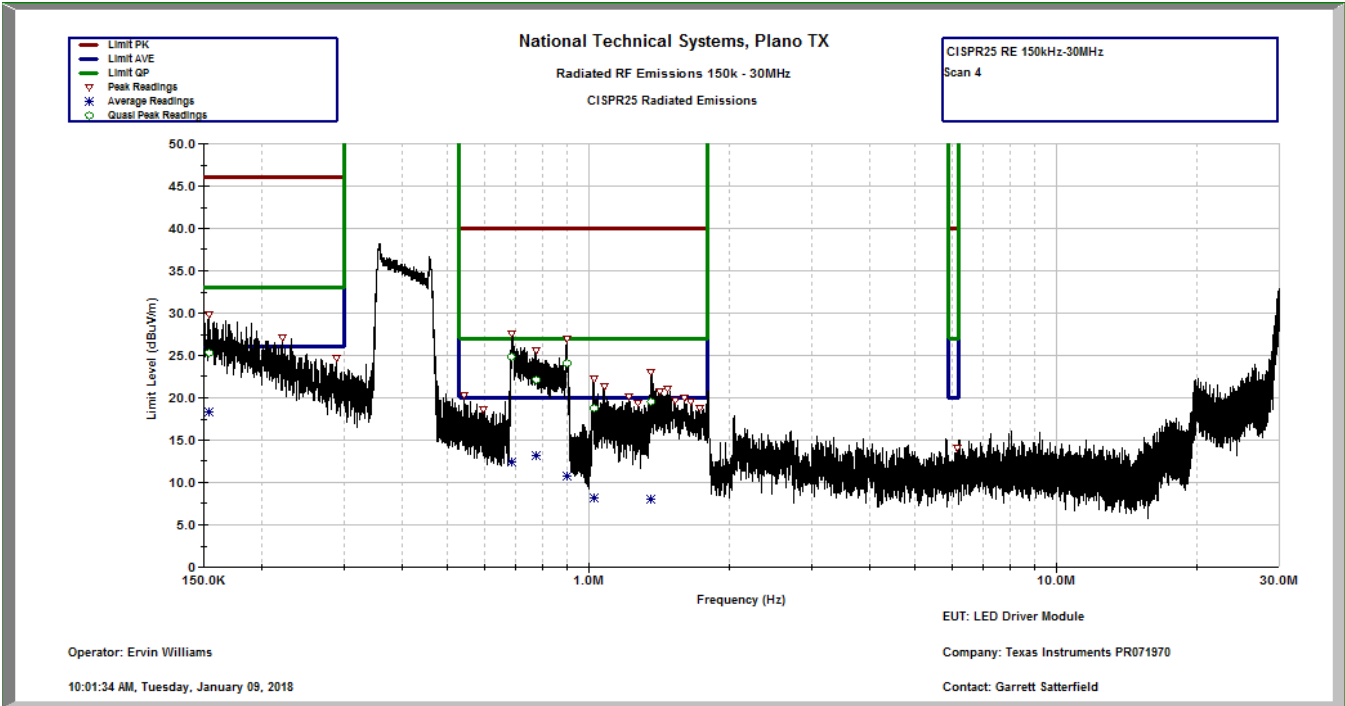


Fig 27. TIDA-01581 With Unshielded Inductors (Vishay IHLP-2525BD-A1)

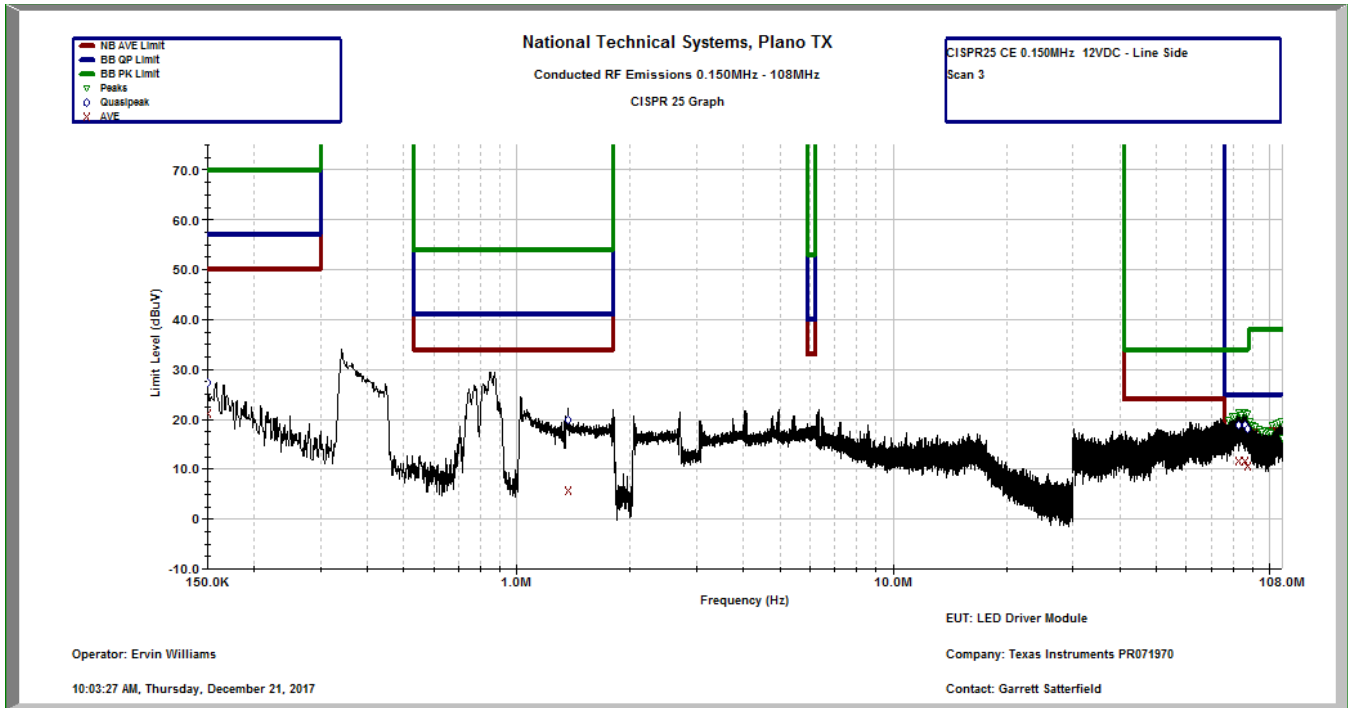The EMI test was set up according to the CISPR25 standard with Class 5 limits.  28 through  33 show the results of the EMI testing.



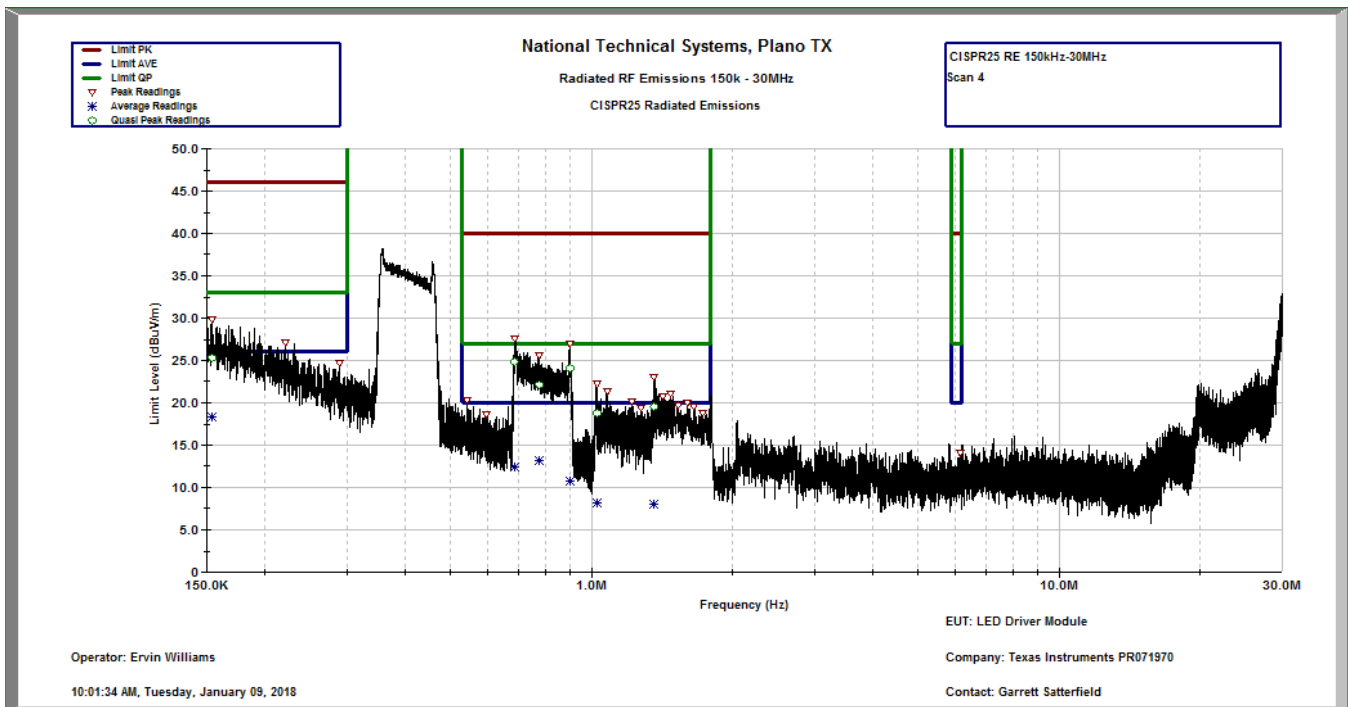 28. CISPR25 Class-5 Conducted Emissions (Line)



 29. CISPR25 Class-5 Radiated Emissions: 150 KHz to 30 MHz

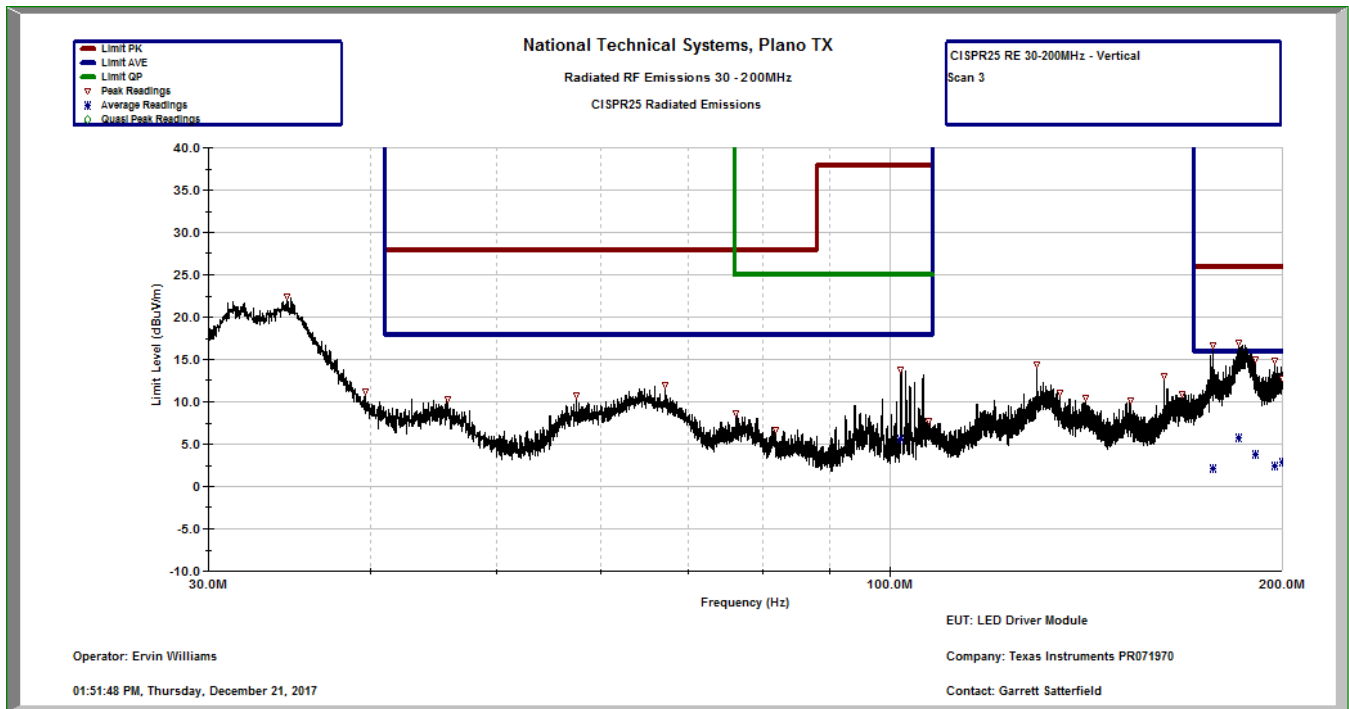


図 30. CISPR25 Class-5 Radiated Emissions: 30 MHz to 200 MHz (Vertical)

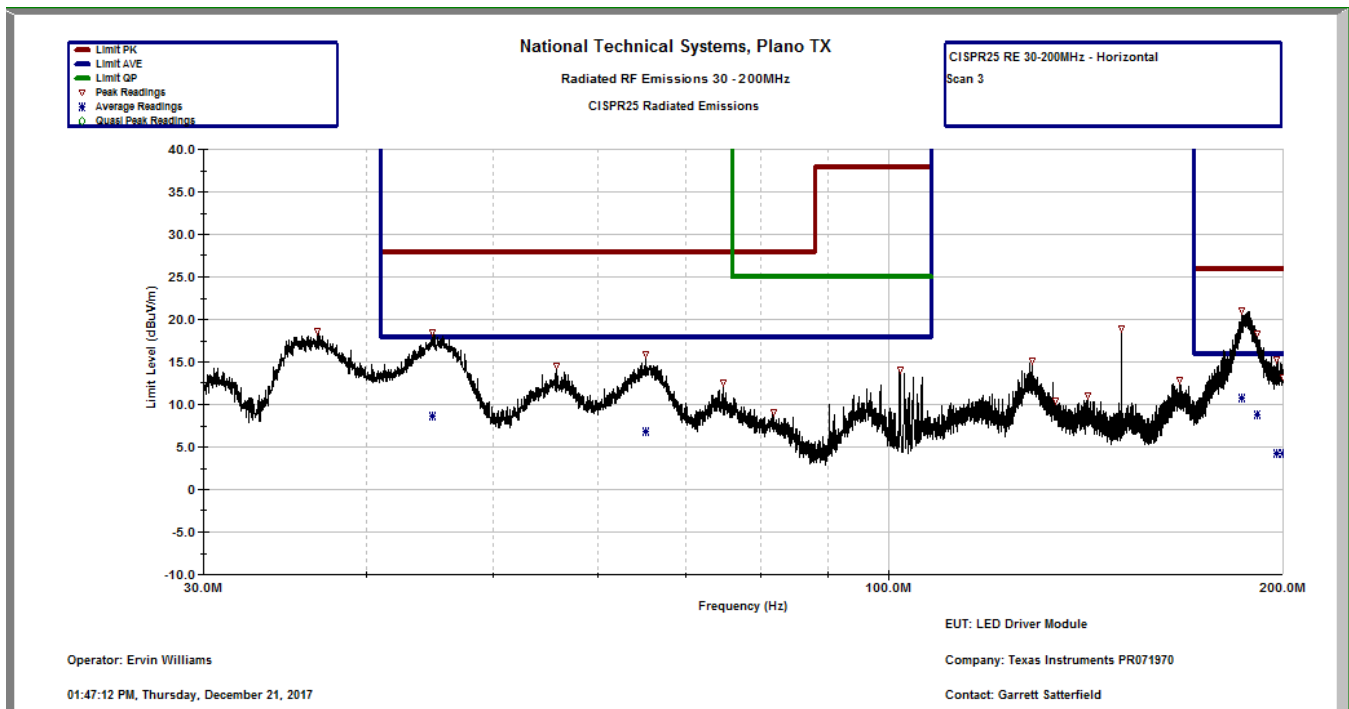


図 31. CISPR25 Class-5 Radiated Emissions: 30 MHz to 200 MHz (Horizontal)

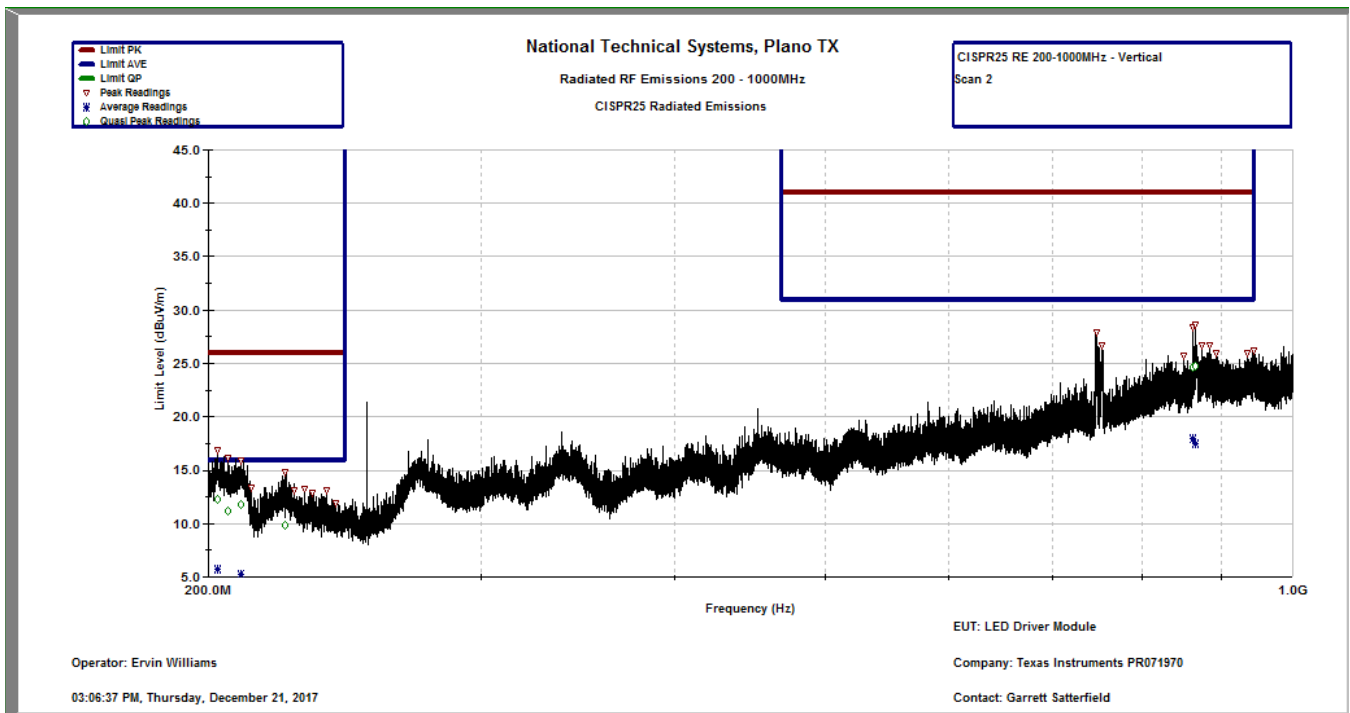


図 32. CISPR25 Class-5 Radiated Emissions: 200 MHz to 1 GHz (Vertical)


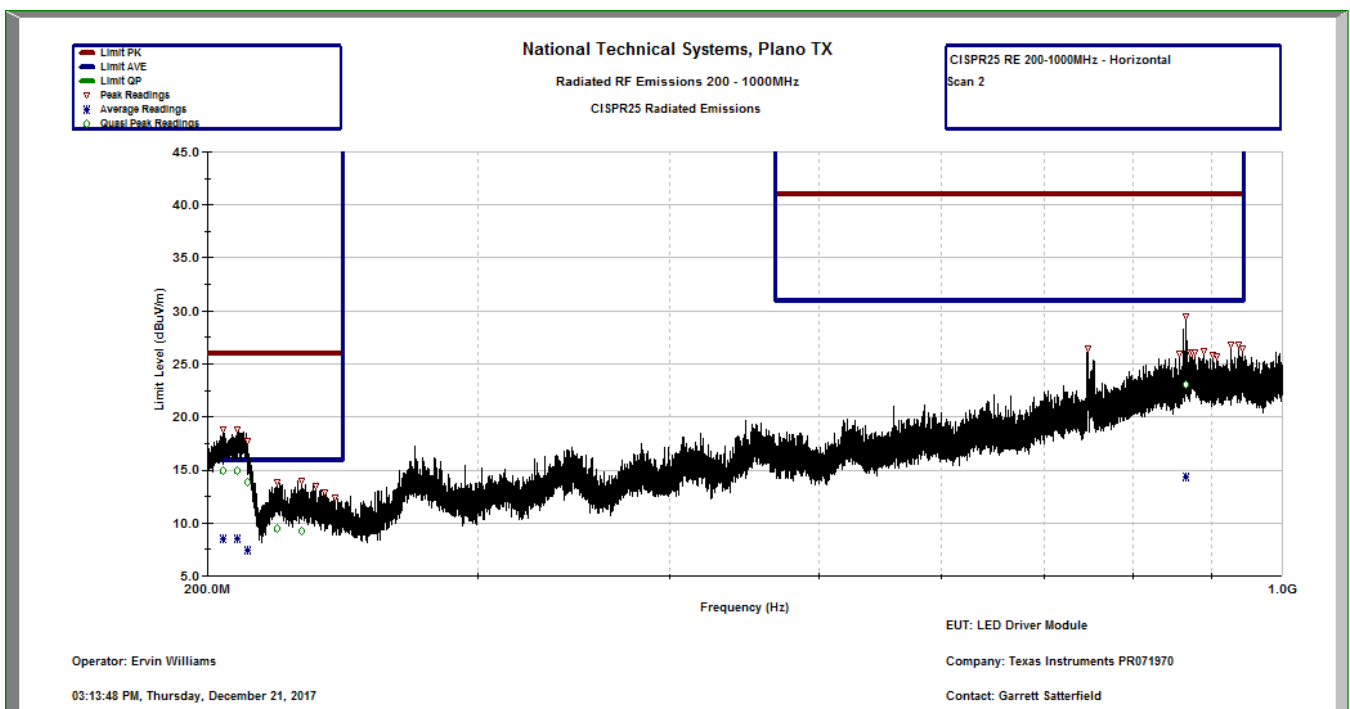
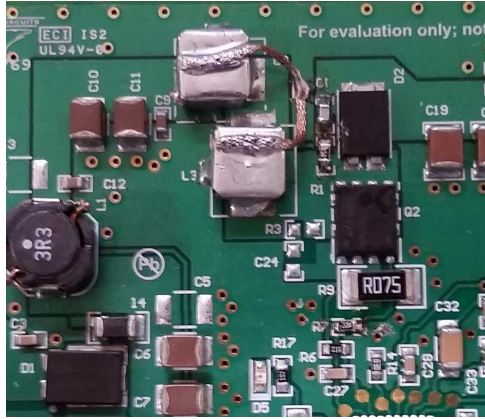



図 33. CISPR25 Class-5 Radiated Emissions: 200 MHz to 1 GHz (Horizontal)

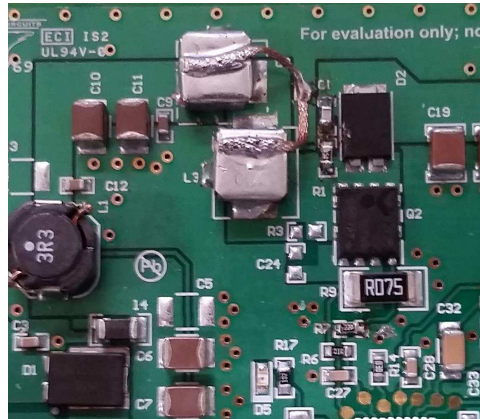
3.2.6 EMI Testing Shielded Inductors


Additional tests were completed using shielded inductors instead of the standard inductors.  34 shows how the shielded inductors were mounted to the board. The inductors used were Cyntec VCMT053-T-100MN5 (shielded). These inductors included two extra PCB connections that attach to ground and connect to the metal shield that covers the inductor.



 34. TIDA-01581 With Shielded Inductors Mounted (Cyntec VCMT053T-100MN5 Shielded)

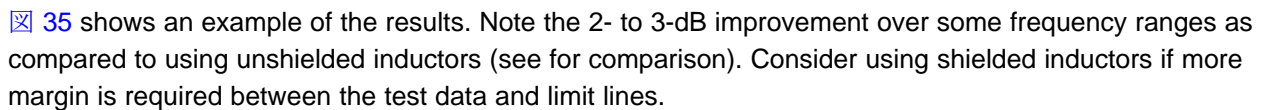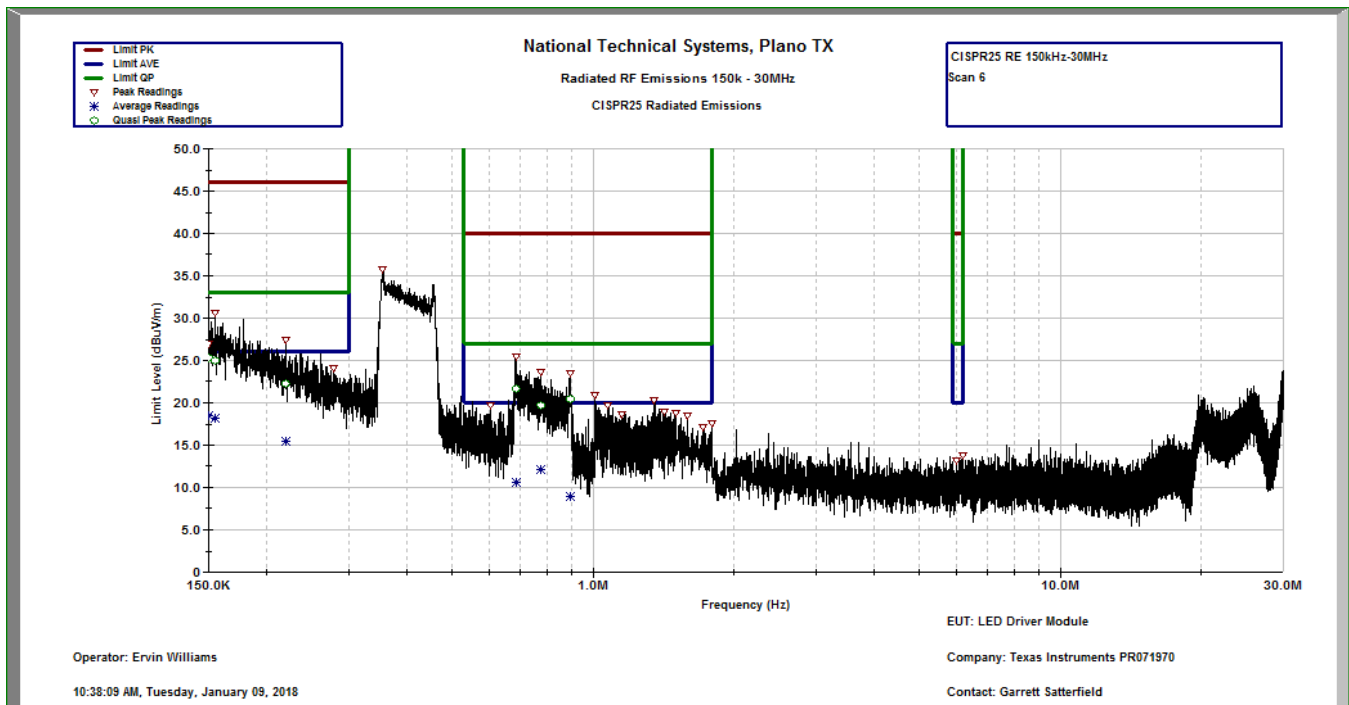 35 shows an example of the results. Note the 2- to 3-dB improvement over some frequency ranges as compared to using unshielded inductors (see for comparison). Consider using shielded inductors if more margin is required between the test data and limit lines.



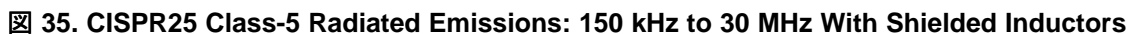 35. CISPR25 Class-5 Radiated Emissions: 150 kHz to 30 MHz With Shielded Inductors

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01581](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01581](#).

4.3 PCB Layout Recommendations

Use the following layout recommendations for optimal circuit and EMI performance:

- Use low equivalent series resistance (ESR) decoupling capacitors and place them as close to the IC pin as possible.
- Use copper pours in the boost converter component section instead of traces.
- Keep the output loop formed by the rectification diode, output capacitors, and low-side sense resistor as small as possible, as this is a discontinuous current path with high di/dt.
- Ensure that the traces cut as little as possible from the second-layer ground plane and that they do not cut in the path of the return current.
- Place the analog circuitry away from the switching power supply components.
- Keep the feedback traces that connect to CSP and CSN as short as possible.

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01581](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01581](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01581](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01581](#).

5 Software Files

To download the software files, see the design files at [TIDA-01581](#).

6 Related Documentation

1. Texas Instruments, [Minimizing Ringing at the Switch Node of a Boost Converter Application Report](#)
2. Texas Instruments, [Driving Daytime Running Lights LEDs With Thermal Foldback Reference Design](#)
3. Texas Instruments, [0-W, Dual-Stage LED Driver Reference Design With Pre-Boost Control for Automotive Headlights](#)

6.1 商標

E2E, TINA-TI are trademarks of Texas Instruments.

すべての商標および登録商標はそれぞれの所有者に帰属します。

7 Terminology

CMOS— Complementary metal–oxide–semiconductor

'DRL'— Full brightness mode

EMI— Electromagnetic interference

ESR— Equivalent series resistance

FET— Field-effect transistor

LED— Light-emitting diode

MCU— Microcontroller unit

MOSFET— Metal-oxide-semiconductor field-effect transistor

NTC— Negative temperature coefficient

Op Amp—Operational amplifier

PCB— Printed-circuit board

'Position'— PWM dimming mode

PWM— Pulse-width modulation

SMPS— Switched-mode power supply

8 About the Author

GARRETT SATTERFIELD is an applications engineer at Texas Instruments where he is responsible for developing reference designs for automotive systems. Garrett received his BSEE from The Georgia Institute of Technology in 2016.

TIの設計情報およびリソースに関する重要な注意事項

Texas Instruments Incorporated ("TI")の技術、アプリケーションその他設計に関する助言、サービスまたは情報は、TI製品を組み込んだアプリケーションを開発する設計者に役立つことを目的として提供するものです。これにはリファレンス設計や、評価モジュールに関係する資料が含まれますが、これらに限られません。以下、これらを総称して「TIリソース」と呼びます。いかなる方法であっても、TIリソースのいずれかをダウンロード、アクセス、または使用した場合、お客様(個人、または会社を代表している場合にはお客様の会社)は、これらのリソースをここに記載された目的にのみ使用し、この注意事項の条項に従うことに合意したものとします。

TIによるTIリソースの提供は、TI製品に対する該当の発行済み保証事項または免責事項を拡張またはいかなる形でも変更するものではなく、これらのTIリソースを提供することによって、TIにはいかなる追加義務も責任も発生しないものとします。TIは、自社のTIリソースに訂正、拡張、改良、およびその他の変更を加える権利を留保します。

お客様は、自らのアプリケーションの設計において、ご自身が独自に分析、評価、判断を行う責任がお客様にあり、お客様のアプリケーション(および、お客様のアプリケーションに使用されるすべてのTI製品)の安全性、および該当するすべての規制、法、その他適用される要件への遵守を保証するすべての責任をお客様のみが負うことを理解し、合意するものとします。お客様は、自身のアプリケーションに関して、(1) 故障による危険な結果を予測し、(2) 障害とその結果を監視し、および、(3) 損害を引き起こす障害の可能性を減らし、適切な対策を行う目的での、安全策を開発し実装するために必要な、すべての技術を保持していることを表明するものとします。お客様は、TI製品を含むアプリケーションを使用または配布する前に、それらのアプリケーション、およびアプリケーションに使用されているTI製品の機能性を完全にテストすることに合意するものとします。TIは、特定のTIリソース用に発行されたドキュメントで明示的に記載されているもの以外のテストを実行していません。

お客様は、個別のTIリソースにつき、当該TIリソースに記載されているTI製品を含むアプリケーションの開発に関連する目的でのみ、使用、コピー、変更することが許可されています。明示的または黙示的を問わず、禁反言の法理その他どのような理由でも、他のTIの知的所有権に対するその他のライセンスは付与されません。また、TIまたは他のいかなる第三者のテクノロジーまたは知的所有権についても、いかなるライセンスも付与されるものではありません。付与されないものには、TI製品またはサービスが使用される組み合わせ、機械、プロセスに関連する特許権、著作権、回路配置利用権、その他の知的所有権が含まれますが、これらに限られません。第三者の製品やサービスに関する、またはそれらを参照する情報は、そのような製品またはサービスを利用するライセンスを構成するものではなく、それらに対する保証または推奨を意味するものでもありません。TIリソースを使用するため、第三者の特許または他の知的所有権に基づく第三者からのライセンス、もしくは、TIの特許または他の知的所有権に基づくTIからのライセンスが必要な場合があります。

TIのリソースは、それに含まれるあらゆる欠陥も含めて、「現状のまま」提供されます。TIは、TIリソースまたはその仕様に関して、明示的か暗黙的にかかわらず、他のいかなる保証または表明も行いません。これには、正確性または完全性、権原、続発性の障害に関する保証、および商品性、特定目的への適合性、第三者の知的所有権の非侵害に対する黙示の保証が含まれますが、これらに限られません。

TIは、いかなる苦情に対しても、お客様への弁済または補償を行う義務はなく、行わないものとします。これには、任意の製品の組み合わせに関連する、またはそれらに基づく侵害の請求も含まれますが、これらに限られず、またその事実についてTIリソースまたは他の場所に記載されているか否かを問わないものとします。いかなる場合も、TIリソースまたはその使用に関連して、またはそれらにより発生した、実際の、直接的、特別、付随的、間接的、懲罰的、偶発的、または、結果的な損害について、そのような損害の可能性についてTIが知らされていたかどうかにかかわらず、TIは責任を負わないものとします。

お客様は、この注意事項の条件および条項に従わなかったために発生した、いかなる損害、コスト、損失、責任からも、TIおよびその代表者を完全に免責するものとします。

この注意事項はTIリソースに適用されます。特定の種類の資料、TI製品、およびサービスの使用および購入については、追加条項が適用されます。これには、半導体製品(<http://www.ti.com/sc/docs/stdterms.htm>)、評価モジュール、およびサンプル(<http://www.ti.com/sc/docs/sampterms.htm>)についてのTIの標準条項が含まれますが、これらに限られません。