

Designing a Thermal Monitor and Temperature Controller with TI's Programmable Logic Devices (TPLD)



Hannah Bludau and Ian Graham

Application Description

Data centers and other enterprise applications consume a significant amount of power due to the complex infrastructure of the system. In order to minimize the potential of overheating and impacting system performance, data centers implement techniques to ensure reliable performance. One such technique is to measure the temperature of the system and respond accordingly to high temperatures. The temperature can be determined by using a system that converts temperature to voltage by using a temperature resistor or thermistor. After being converted, several signal handling measures can be implemented. This application brief shows how TI's programmable logic devices (TPLD) can be configured to control a cooling unit using the voltage from the temperature sensor, as shown in Figure 1. Compared to a discrete design, this solution integrates a pair of analog comparators and a PWM generator into a single chip. This specific design was created using TPLD1201, but any TPLD with a pair of analog comparators can be used. For more on temperature sensing, see [Engineer's Guide to Temperature Sensing](#).

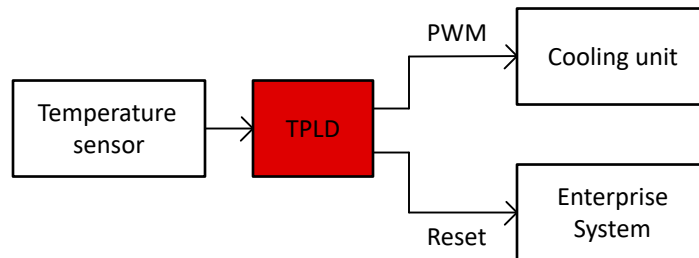


Figure 1. Simplified Block Diagram for Thermal Controller

Solution Description

For this programmable logic design, the thermal voltage generated from the temperature sensor is compared to a programmable reference voltage utilizing an analog comparator in order to turn on a fan at 50% duty cycle once the temperature is above 85°C. Another comparator in conjunction with a programmable reference voltage is used to reset the system and turn on the fan completely when the temperature exceeds 100°C.

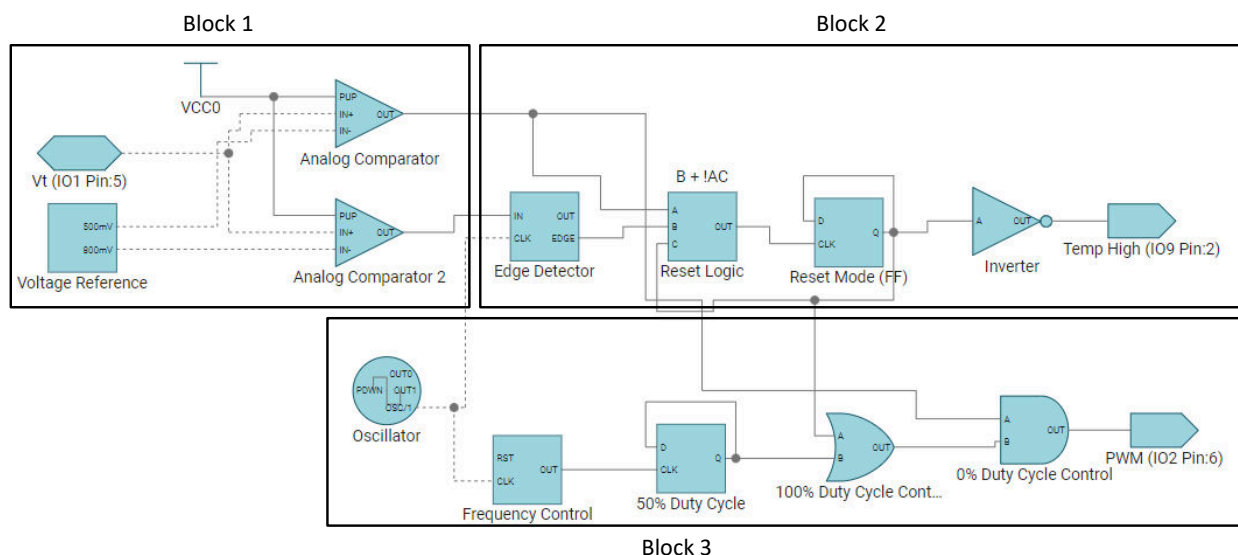


Figure 2. InterConnect Studio (ICS) Configuration

Figure 2 shows the entire solution using TI's Interconnect Studio. Block 1 is comprised of the analog comparators used to monitor the voltage outputs of the temperature sensors. The analog comparators compare the Vt input to the configurable voltage reference. In this example, we used 500mV to correspond to 85°C and 800mV to 100°C. These values are configurable and can be changed to match your system's needs. See below in the section "Design Calculations" for how we calculated our values in the system.

Block 2 detects when the temperature has exceeded a safe level and generates a signal that can be used to turn off an external system until the temperature falls. The delay block is used as a rising edge detector, which then sends the signal through a 3-input look up table denoted as reset logic, here is a screen grab of that table. The logic controls the clock of a flip-flop with an inverter output which drives the temp high output. Figure 3 shows the appropriate look-up table.

C B A Custom 3 Input Boolean Function Table

0 0 0	<input type="checkbox"/>
0 0 1	<input type="checkbox"/>
0 1 0	<input checked="" type="checkbox"/>
0 1 1	<input checked="" type="checkbox"/>
1 0 0	<input checked="" type="checkbox"/>
1 0 1	<input type="checkbox"/>
1 1 0	<input checked="" type="checkbox"/>
1 1 1	<input checked="" type="checkbox"/>

Figure 3. Reset Logic Lookup Table Logic

Block 3 controls a PWM signal for a cooling element such as a fan. The frequency control counter combined with the flip-flop divides the oscillator to produce a 1kHz signal to interface with common cooling elements. By setting the counters control data to 12, the counter pulses once every 12 oscillator cycles, which effectively divides the clock frequency by 12. The flip-flop further divides it by 2 giving a final frequency of 1.04kHz. The flip-flop is also used to create a 50% duty cycle and a series of logic element are used to control when the PWM is held high or low. The settings of the oscillator and counter from InterConnect Studio are shown in Figure 4 and can be configured to generate a signal with a different frequency.

OSCILLATOR ©		COUNTER ©	
Name	Oscillator	Name	Frequency Control
Label		Label	
Power Mode	Auto Power On	Clock Source	OSC/1
Clock Source	Internal RC Oscillator	Control Data	12
Frequency	25 kHz	Reset Mode	Both falling and rising edges
Clock Pre Divider	/1	Device MacroCell Allocated	Any(CNTDLY0)
OUT0 Second Stage Divider	/1		
OUT1 Second Stage Divider	/1		
Power Control Source Select	From register		
PDWN Control	Power down		
Device MacroCell Allocated	Any(OSC0)		

Figure 4. Oscillator and Counter Settings

Design Calculations

In our design, we used a thermistor resistor divider as shown in Figure 5.

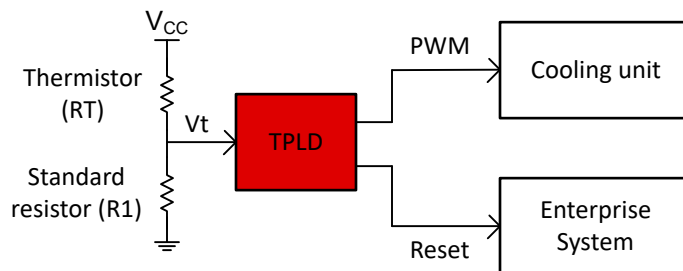


Figure 5. Thermistor Input Block Diagram

We calculated the value of the standard resistor using the following formula.

$$V_t = V_{cc} * (R_1 / (R_1 + R_T))$$

At 80°C, the value of the thermistor is 1.6 k-ohms, which gives us the equation:

$$0.5 = 3.3 * (R_1) / (R_1 + 1.6 \text{ k-ohms})$$

$$R_1 = 286 \text{ ohms}$$

We can then calculate the voltage reference corresponding to 100°C using the formula below:

$$V_t = V_{cc} * (R_1 / (R_1 + R_T))$$

$$V_t = 3.3 * (286 \text{ ohms}) / (286 \text{ ohms} + 900 \text{ ohms}) = 0.8V$$

Of course, other methods of temperature sensing can be used, such as an analog temperature sensor.

Simulation

When the input voltage rises to 0.5V, which corresponds to 85°C Celsius in this design, the PWM turns on with a 50% duty cycle. Once the voltage exceeds 0.8V, which corresponds to 100°C, the PWM then generates a 100% duty cycle and the system is held in reset until the input voltage falls below 0.5V. This behavior is shown in the ICS simulation shown in Figure 6.

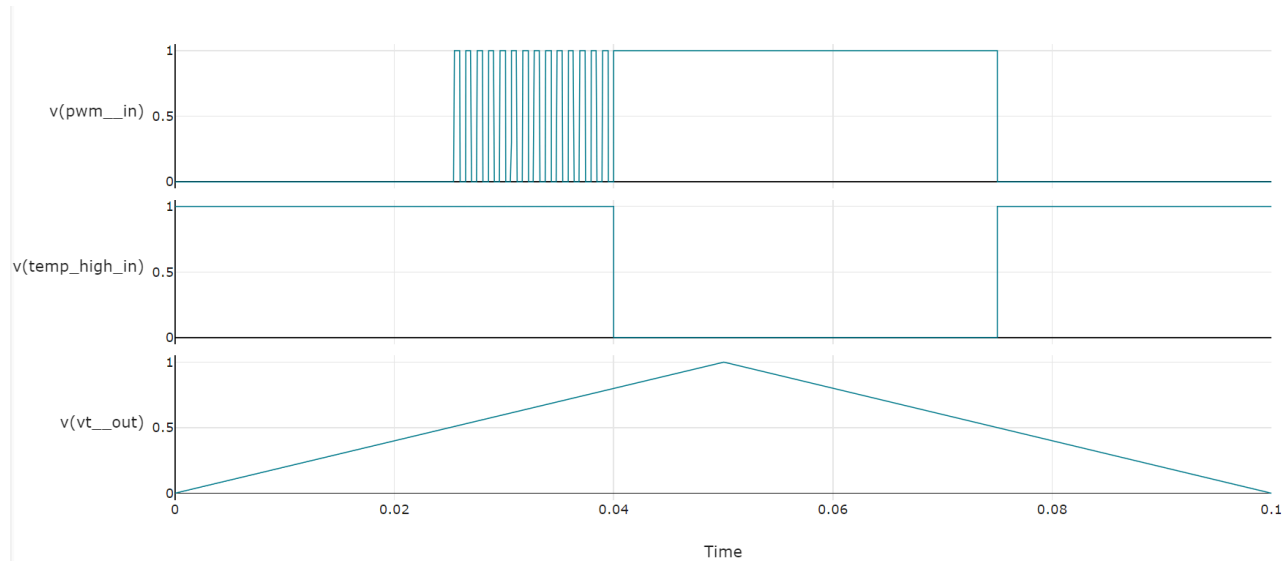


Figure 6. ICS Simulation

Design Considerations

- TPLD1201 can typically drive up to 50mA. Depending on the cooling system, this may not be sufficient. A load switch may be used if the cooling element requires more power.
- If the cooling element operates at a frequency different than 1kHz, Block 3 can be configured to produce other PWM frequencies up to the maximum frequency of the oscillator.
- The TPLD maximum operating temperature is 150°C, so it cannot be operated in an environment with a higher ambient temperature.
- The thermistor used in this design was the NTCG103JF103FT1. Different thermistors have different response curves that must be taken into account in a design.
- This configuration was designed to be operated at 3.3V. Operating at other voltages may require recalculating the resistance values used.

For more information on TPLD, visit the [TPLD1201 product page](#).

Need additional assistance? Ask our engineers a question on the [TI E2E™ Logic Support Forum](#).

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated