

# Laser Biasing and Optical Communication Applications With the AFE11612-SEP



Erin Guthrie

## ABSTRACT

This application note details how the AFE11612-SEP can be used in a multitude of optical communication applications, such as laser biasing, EML negative bias, and photodiode detection and measurement.

## Table of Contents

<b>1 Introduction</b> .....	2
<b>2 Laser and Semiconductor Optical Amplifier Biasing</b> .....	3
<b>3 EML Negative Bias Voltage</b> .....	4
<b>4 Photodiode Detection Measurement</b> .....	5
<b>5 Variable Optical Attenuator Control</b> .....	5
<b>6 Summary</b> .....	6
<b>7 References</b> .....	6
<b>8 Revision History</b> .....	7

## List of Figures

Figure 1-1. AFE11612-SEP Optical Networking Application.....	2
Figure 2-1. Laser Diode Bias Circuit.....	3
Figure 3-1. Inverting Op Amp Circuit.....	4
Figure 3-2. Inverting Op Amp Output.....	4
Figure 4-1. Photodiode Monitor Circuit.....	5
Figure 5-1. VOA Control Circuit.....	5

## Trademarks


All trademarks are the property of their respective owners.

# 1 Introduction

Optical and optical networking (ONET) applications require a variety of subsystems. These systems include:

- [Communications Payload](#)
- [Optical Imaging Payload](#)
- [Optical Module](#)


For optical and ONET applications in space, device selection can be limited and expensive. The AFE11612-SEP is a versatile, space-rated, integrated device that can consolidate the circuitry needed for optical and ONET subsystems. The AFE11612-SEP features twelve 12-bit digital-to-analog converters (DAC), a sixteen channel 12-bit analog-to-digital converter (ADC), and two remote temperature sensors.

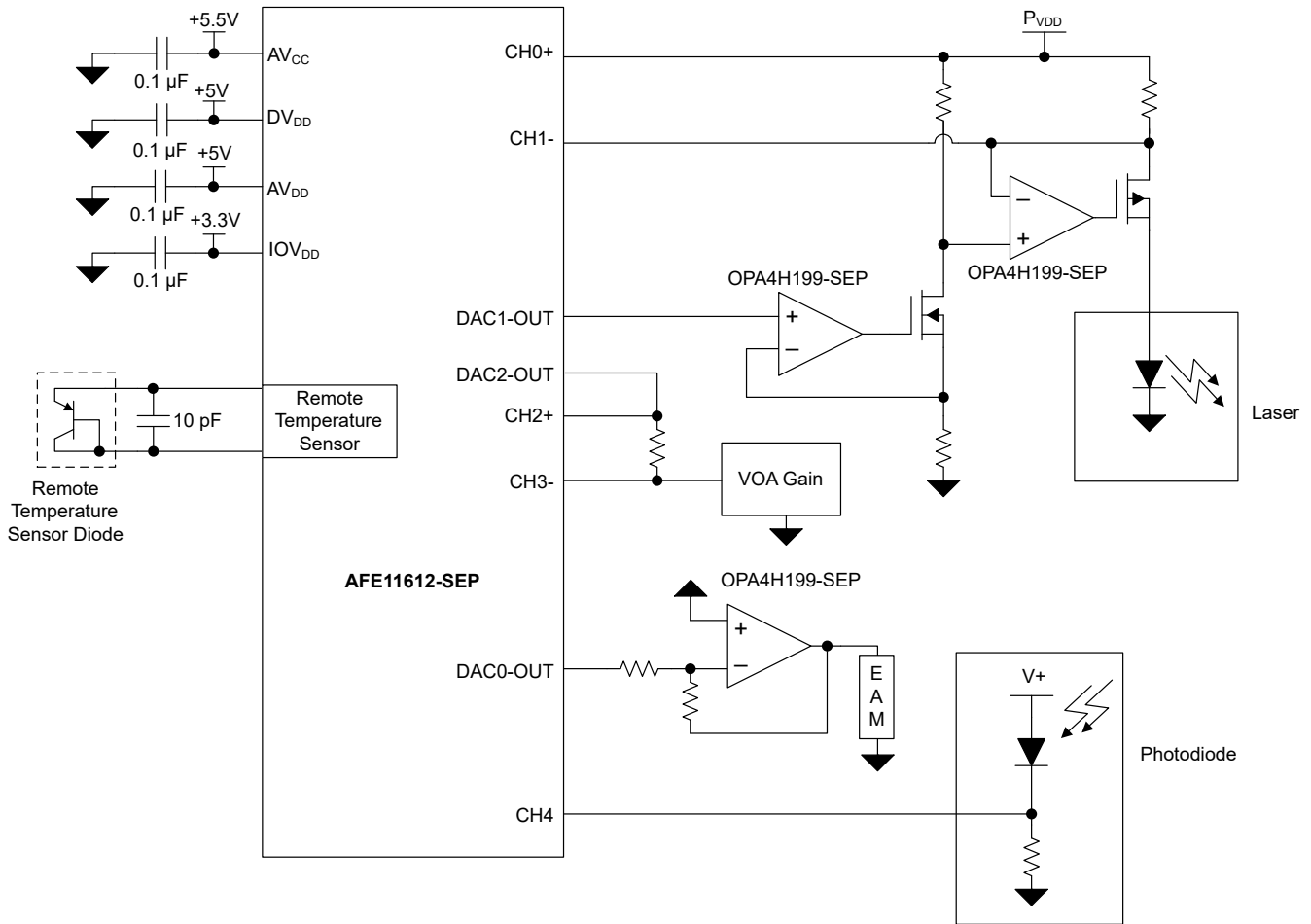

**Figure 1-1. AFE11612-SEP Optical Networking Application**

## 2 Laser and Semiconductor Optical Amplifier Biasing

Laser diodes and semiconductor optical amplifiers (SOAs) require a precision current source and current monitoring to be accurately biased. The AFE11612-SEP has twelve 12-bit DACs that can be configured to be a precision current source with external circuitry. The circuit in [Figure 2-1](#) uses the AFE11612-SEP DAC outputs, external operational amplifiers (op amps), and external MOSFETs to supply a programmable current to a ground-referenced load.

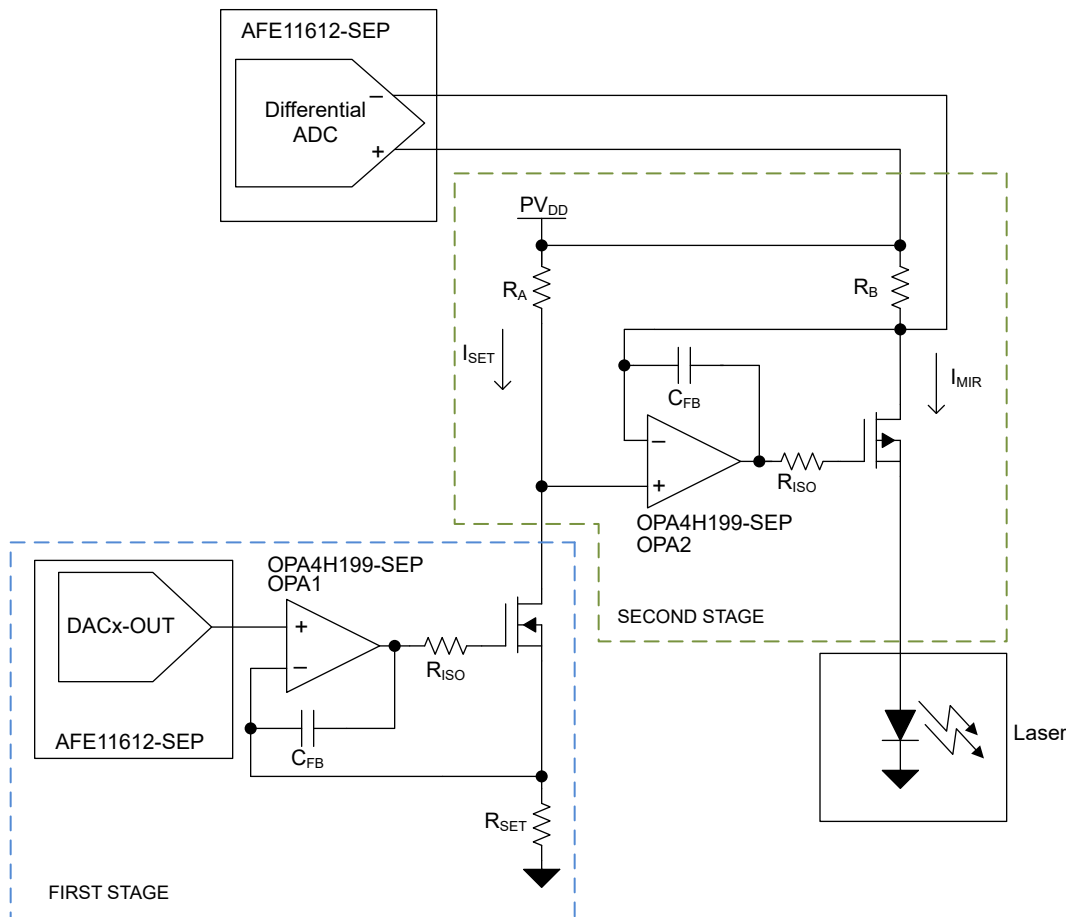

**Figure 2-1. Laser Diode Bias Circuit**

The first op amp stage uses  $R_{SET}$  and the DAC output voltage ( $V_{DAC}$ ) to set the reference current.  $V_{DAC}$  is applied to the noninverting input of OPA1, which sets the high-side of  $R_{SET}$  to the same voltage. This reference current ( $I_{SET}$ ) is calculated with [Equation 1](#).

$$I_{SET} = \frac{V_{DAC}}{R_{SET}} \quad (1)$$

The second op amp stage is a current-mirror with a gain set by  $R_A$  and  $R_B$ . The current flowing through  $R_A$  is equal to  $I_{SET}$ . This creates a voltage drop across  $R_A$ .  $R_B$  has the same voltage drop due to the op amp OPA2 feedback forcing the voltage at the low-side of  $R_B$ . Thus, with  $R_A$  and  $R_B$  having the same voltage drop, the current flowing through  $R_B$  can be tuned by picking specific resistor values. This current ( $I_{MIR}$ ) is the current that is used by the load. Use [Equation 2](#) and [Equation 3](#) to calculate the current gain.

$$I_{SET} \times R_A = I_{MIR} \times R_B \quad (2)$$

$$\text{Current Gain} = \frac{I_{SET}}{I_{MIR}} = \frac{R_A}{R_B} \quad (3)$$

The total gain of the system can be calculated by [Equation 4](#).

$$I_{MIR} = \frac{V_{DAC} \times R_A}{R_{SET} \times R_B} \quad (4)$$


For additional information on using voltage DACs to create programmable current sources, see [8-Channel, 16-Bit, 200-mA Current Output, Digital-to-Analog Converter Reference Design](#) and [Programmable, Two-Stage, High-Side Current Source Current](#).

Additionally, the AFE11612-SEP features an ADC with differential inputs which can assist in measuring the voltage differential across  $R_B$  to monitor current. The AFE11612-SEP ADC has a range of 5 V, so the  $P_{VDD}$  voltage must be taken into account when using the ADC for measurements. For use in higher voltage applications, an INA or a voltage divider circuit can be used to measure the voltage across  $R_B$ .


The AFE11612-SEP also has two remote temperature monitors that trigger an alarm when they detect temperature that exceeds a user-determined value. These can be placed near temperature sensitive components to make sure that the host is informed when the devices are overheating.

### 3 EML Negative Bias Voltage

Optical networking applications that use an electro-absorption modulated laser (EML) require a negative voltage to bias the integrated electro-absorption modulator (EAM). The AFE11612-SEP has an internal 2.5V reference that scales the DAC output range from 0V to 5V. The DAC output can be converted to a negative voltage through the use of an inverting op amp circuit that is powered by a negative power supply. The circuit in [Figure 3-1](#) uses the op amp OPA4H199-SEP to offset and scale the 5V output range to 0V to -5V. The feedback resistor ratio can be selected for an increased or decreased output range. The plot in [Figure 3-2](#) shows the OPA output voltage vs the input DAC voltage.

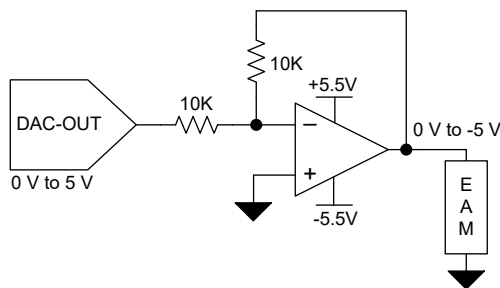

**Figure 3-1. Inverting Op Amp Circuit**

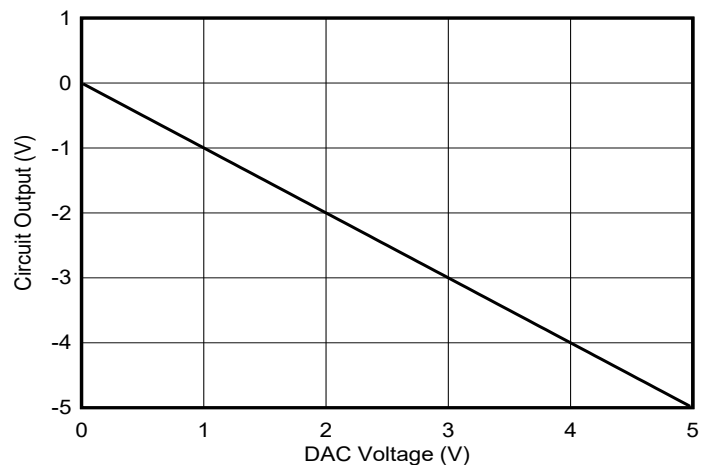

**Figure 3-2. Inverting Op Amp Output**

## 4 Photodiode Detection Measurement

The AFE11612-SEP has 16 ADC inputs that can be used for monitoring many functions, including measuring photodiode current. The device ADC is a successive-approximation register (SAR) ADC. SAR ADCs have an internal sampling capacitor which must be charged every time there is an ADC conversion. This capacitor must be charged within the sample acquisition time to ensure the ADC measures the voltage correctly. This is done using a charge-bucket filter with an external capacitor ( $C_{FILT}$ ). The filter resistor ( $R_{FILT}$ ) can be a low value so  $C_{FILT}$  can receive enough current to be charged for each sample. A sense resistor ( $R_{SENSE}$ ) turns the photodiode current into a voltage, and the resistor should be selected such that the resulting voltage is within the ADC 5-V input range. Figure 4-1 shows the charge bucket circuit.

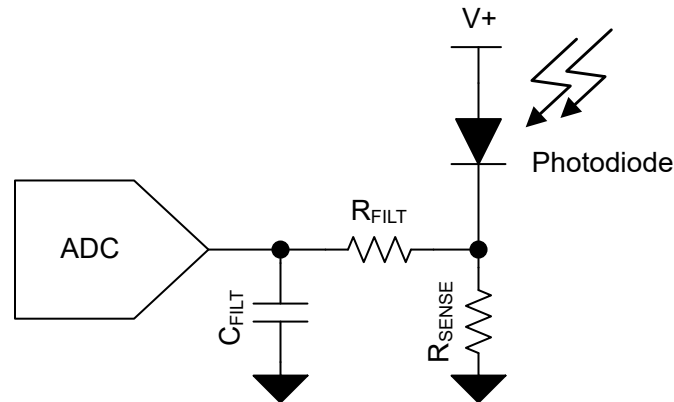


Figure 4-1. Photodiode Monitor Circuit

## 5 Variable Optical Attenuator Control

Variable optical attenuators (VOA) are commonly used in ONET applications to help control the light and power output of laser applications. The AFE11612-SEP DACs and differential ADCs can be used to control VOAs and also monitor the current and power of the attenuators. Similar to the laser current monitoring, an INA can be used instead of the AFE11612-SEP differential ADC inputs for higher voltage applications. Figure 5-1 shows a circuit that measures the current going into the VOA.

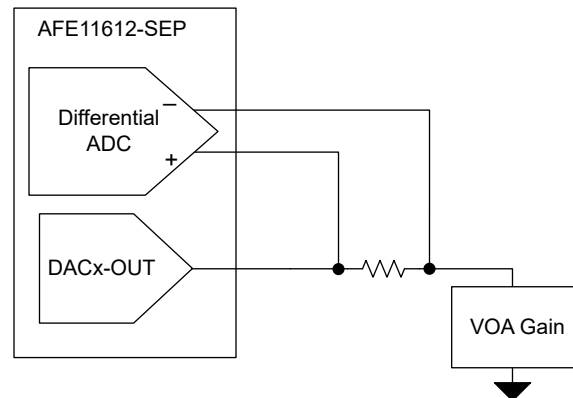


Figure 5-1. VOA Control Circuit

## 6 Summary

Space projects that require DACs and ADCs can be very costly and board insufficient, with limited amount of device options available. The multiple DACs and ADC inputs of the AFE11612-SEP make it an incredibly flexible tool that can support and consolidate the building blocks for optical and ONET applications.

## 7 References

1. Texas Instruments, [AFE11612-SEP Radiation-Tolerant, Analog Monitor and Controller with Multichannel ADC, DACs, and Temperature Sensors](#), data sheet.
2. Texas Instruments, [OPA4H199-SEP 40-V, Radiation Hardened, Rail-to-Rail Input/Output, Low Offset Voltage, Low Noise Op Amp in Space Enhanced Plastic](#), data sheet.
3. Texas Instruments, [8-Channel, 16-Bit, 200-mA Current Output, Digital-to-Analog Converter Reference Design](#).
4. Texas Instruments, [Programmable, Two-Stage, High-Side Current Source Current](#), analog engineer's circuit.

## 8 Revision History

<b>Changes from Revision * (August 2023) to Revision A (July 2024)</b>	<b>Page</b>
• Updated the numbering format for tables, figures, and cross-references throughout the document.....	1
• Deleted <i>INA240</i> throughout document.....	1

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated