

Buck Boost Charger with Power Path for Super Cap

Eric, Xiong; Wang, Li; Michael, Emanuel; Kelly, Bai
Field Applications

ABSTRACT

Super Cap is becoming very popular in many applications since its unique feature like more recharge cycle, better transient capacity, simpler charger management and less environment pollution. Typical multi-cell Cap in series requires buck boost topology to charge from empty to full when V_{IN} is below 5 V. BQ25703A is good device which can perform quick charging, power path and protection function in single chip. This paper discusses how to use it and some considerations in real application.

Contents

1	Typical Application Requirements	2
2	Super Cap Charger Based on BQ25703A	3
3	Summary	8
4	References	8

List of Figures

1	Buck Boost Charger With BQ25703A.....	3
2	Adapter Charging Profile with Pre-Charge and Fast-Charge	4
3	$R_{sr} = 2\text{ m}\Omega$	5
4	LDO Mode	5
5	Bypass Mode.....	5
6	Disable LDO Mode	5
7	1 A Fast Charge	6
8	0.4 A Fast Charge	6
9	USB Charging with Lower Current	6
10	Without DPM	6
11	With DPM	6
12	Charger with V_{IN} DPM Function.....	6
13	Passive Balance circuit example	7
14	Additional OVP circuit with HIZ	7
15	Passive Cell Balance Function.....	7
16	Charging with Cell Balance.....	8
17	Charging OVP Test.....	8
18	HIZ Mode OVP Protection	8

List of Tables

1	BQ2570x Series Buck Boost Charger	3
---	---	---

Trademarks

All trademarks are the property of their respective owners.

1 Typical Application Requirements

1.1 Application Example

- V_{IN} : 4.5~5.5 V.// Power source current limit is 0.5 A for USB and 2 A for Adaptor.
- CAP : Two cell in series.//25F/2.7 V for single cell.
- V_{BAT} : 0 V —4.8 V.// CAP from empty(0V) to full ($V_{CHG} = 4.8$ V).
- V_{SYS} range: 2.8 V~4.8 V.// $V_{sysmin} = 2.8$ V, $V_{CHG} = 4.8$ V.
- Cell balancer function.// 10 k Resistor in parallel with each Cap cell for passive balance.
- Power path function.// When ultra-low V_{BAT} and connect to AC, system start up instant.
- V_{IN} DPM function.// Protect V_{IN} from big drop when reach current limit.
- Cap OVP threshold: 5.2 V (MAX to 5.4 V).//Hardware OVP protection.
- Charge time: USB V_{IN} 120 s / Adaptor V_{IN} 30 s.// From V_{sysmin} to V_{CHG} .
- Working temp: -40~65 °C (up to 85 °C)

1.2 Test Equipment

- Agilent E3644 A 5 V / 3 A Power supply
- Tektronix MSO4054 Oscilloscope
- Agilent 34401 A Multi-meter
- TI BQ25703A EVM Board
- EV2400 USB to any board
- TI Battery Management Studio software
- Nesscap Two cell 25 F Super Cap

2 Super Cap Charger Based on BQ25703A

2.1 BQ25703A Key Features

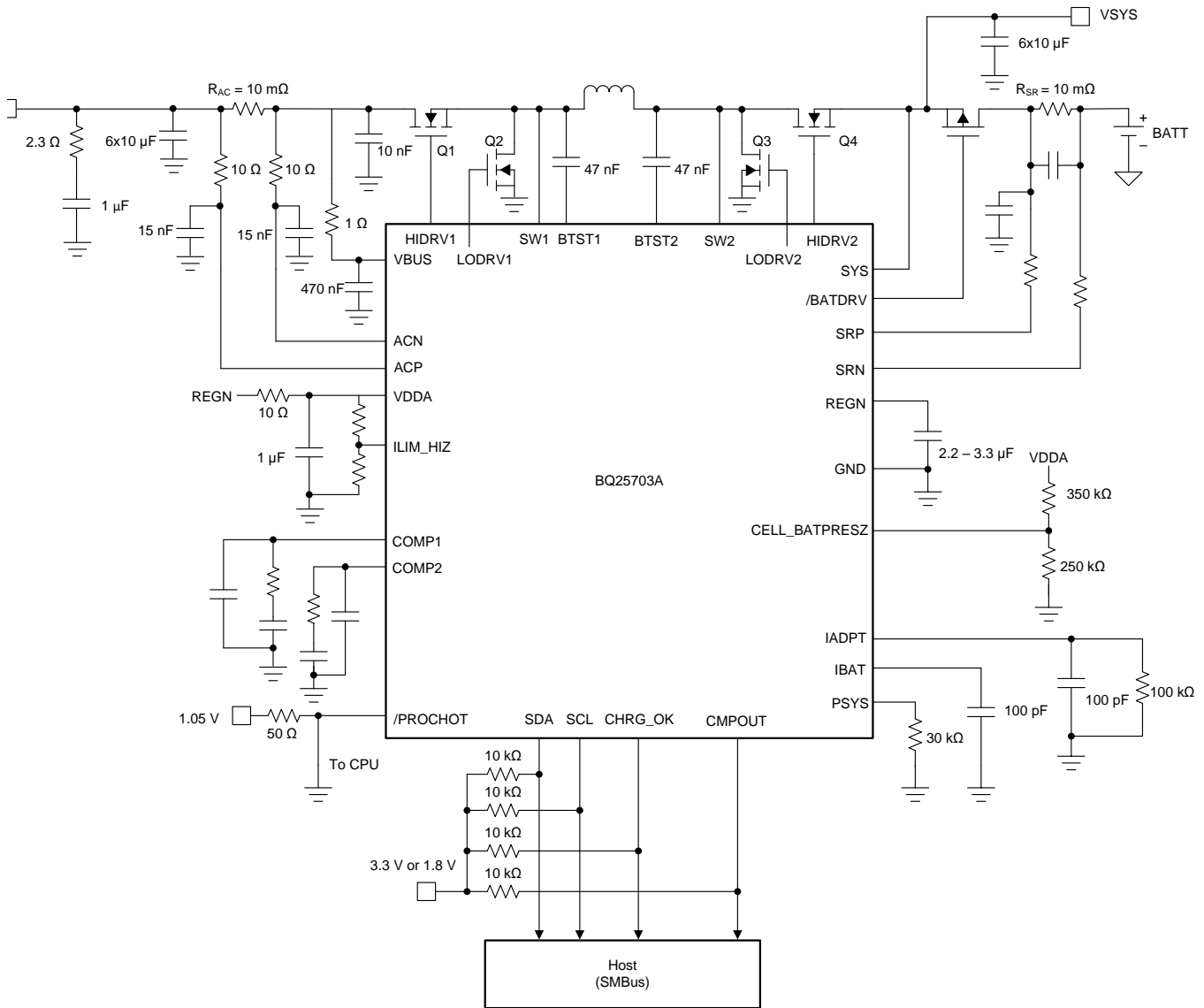


Figure 1. Buck Boost Charger With BQ25703A

BQ2570x series provide the flexibility for different application option, which shows as [Table 1](#).

Table 1. BQ2570x Series Buck Boost Charger

	BQ25700A	BQ25703A	BQ25708	BQ25710	BQ25713	BQ25713B
Interface	SMBus	I2C	SMBus	SMBus	I2C	I2C
Device Address	09h	6Bh	09h	09h	6Bh	6Ah
VAP for IMVP9	No	No	No	Yes	Yes	Yes
Pass Through Mode	No	No	No	Yes	Yes	Yes
OTG Mode	Yes	Yes	No	Yes	Yes	Yes
OTG Voltage Range	4.48 V — 20.8 V	4.48 V — 20.8 V	N/A	3 V — 20.8 V	3 V — 20.8 V	3 V — 20.8 V

Table 1. BQ2570x Series Buck Boost Charger (continued)

	BQ25700A	BQ25703A	BQ25708	BQ25710	BQ25713	BQ25713B
OTG Voltage Resolution	64 mV	64 mV	N/A	8 mV	8 mV	8 mV
Charging Voltage Resolution	16 mV	16 mV <td 16 mV	8 mV	8 mV	8 mV	

BQ25703A key features list below make it good single chip solutions for two cell super cap buck boost charger with full addition function.

- Large V_{IN} range: 3.5 V ~ 24 V.
- Buck-boost controller flexible for Multi-cell charging (Li-ion or CAP).
- NVDC power path – Instant-On with deeply discharged CAP.
- High charge current up to 6 A.
- DPM function against power source overload.
- High efficiency and Low Battery Quiescent Current
- IC Safety OVP/OCP/OT protection and integrated comp for flexible protection.
- High accuracy voltage (0.5%) and current regulation (2%).
- Integrated AMP/ADC to monitor charge status easily.

2.2 Typical Charging Profile

 


Figure 2. Adapter Charging Profile with Pre-Charge and Fast-Charge

Setup and Software Configure:

- * Chose Power supply is adapter 4.5 V ~ 5.5 V / 3 A.
- * Using $R_{sr} = 5\text{ m}\Omega$ for this example.
- * Set CELL_BATPRESZ for 1 Cell start up.
- * Power up. This would automatically enable 256 mA wake up charging current for 30 min. (128 mA for 10 m Ω); V_{SYS} would keep 3.58 V default value.
- * Set $I_{CHG} = 0\text{ A}$ (REG0x03/02) would stop wake up charging. And wait software configure.
- * Set $V_{SYSMIN} = 2.8\text{ V}$ (REG0x0D/0C), V_{SYS} would change from to 2.8 V immediately.
- * Set $V_{BAT} = 4.8\text{ V}$ (REG0x05/04). Full voltage of two cell cap. One cell can set up to 5 V.
- * Check the I_{LIM_HIZ} when higher $I_{CHG} > 2\text{ A}$. Or disable I_{LIM_HIZ} pin to set input current limit. (REG0x33/32)

bit 7=0)

- * Set $I_{CHG} = 2.048 \text{ A}$ ($REG0x03/02 = 1.024 \text{ A}$ for $10 \text{ m}\Omega$) would start charging.

2.3 Speed Up Pre-Charge Stage

With the default setting, the pre-charge current is about 384 mA for $10 \text{ m}\Omega$, the charge time from empty to full would reach up to above 100 s. This pre-charge current is fixed in device, two methods we can take to increase it and speed up charge process.

1) Use smaller $R_{sr} = 2 \text{ m}\Omega$.

Compared with $10 \text{ m}\Omega$, the pre-charge current would increase by 5 times which up to 1.9 A. When fast stage set to 2 A ($REG: 0.4 \text{ A}$ for 10 ohm), the charging time from empty to full would about 20 s.

 


Figure 3. $R_{sr} = 2 \text{ m}\Omega$

2) Disable LDO Mode

The main reason why pre-charge current small is IC working in LDO mode to key V_{sysmin} when ultra low battery voltage. Disable LDO mode can increase the pre-charge current but this would lose regulate high V_{sysmin} , and the current is controlled by V_{sr} , V_{BAT} and Cap internal resistance. The charge time would reduce to 40 s.

Figure 6. Disable LDO Mode

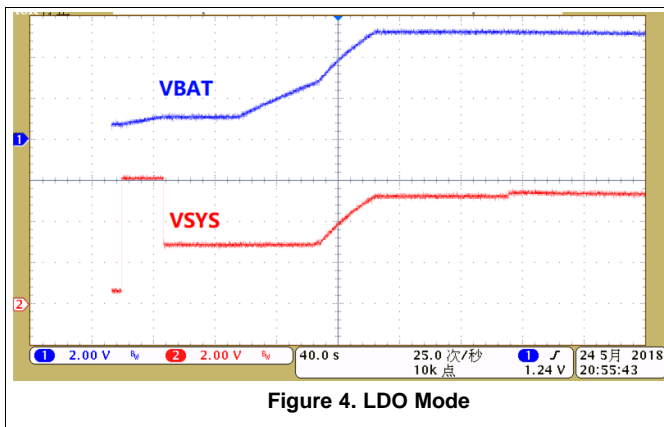


Figure 4. LDO Mode

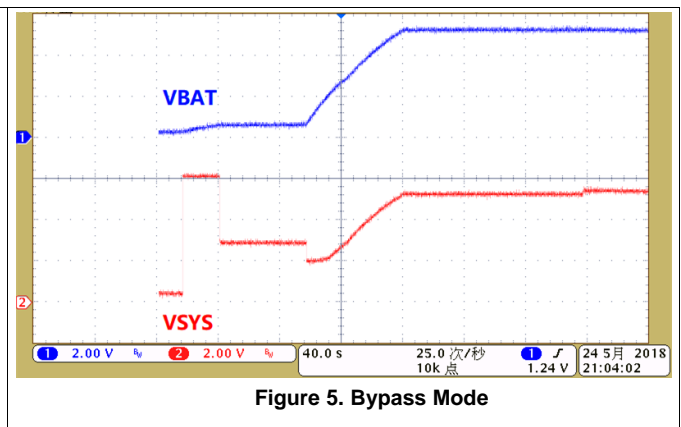


Figure 5. Bypass Mode

2.4 USB 0.5 A Charge

Some power supply current capacity is low, like USB 2.0 of computer which only have 0.5 A current limit. In these case, when high current charge process would make the V_{IN} drop out and system crashed. Two method can be taken to avoid V_{IN} big drop.

1) Reduce Precharge Current and Fast Charge Current


Suggest using large $R_{sr} > 5\text{ m}\Omega$ to limit the pre-charge current below 0.5 A.

$$\text{Min}(R_{sr}) = 10\text{ m}\Omega \times \frac{2.8\text{ V} \times 384\text{ mA}}{5\text{ V} \times 0.5\text{ A} \times 0.9} = 4.7\text{ m}\Omega \tag{1}$$

Set $I_{CHG} < 0.4\text{ A}$ to limit fast charge current below 0.5 A

Below is $R_s r = 5\text{ m}\Omega$ and $I_{CHG} = 0.4\text{ A}$, which could maintain V_{IN} keep 5 V not drop.


Figure 9. USB Charging with Lower Current

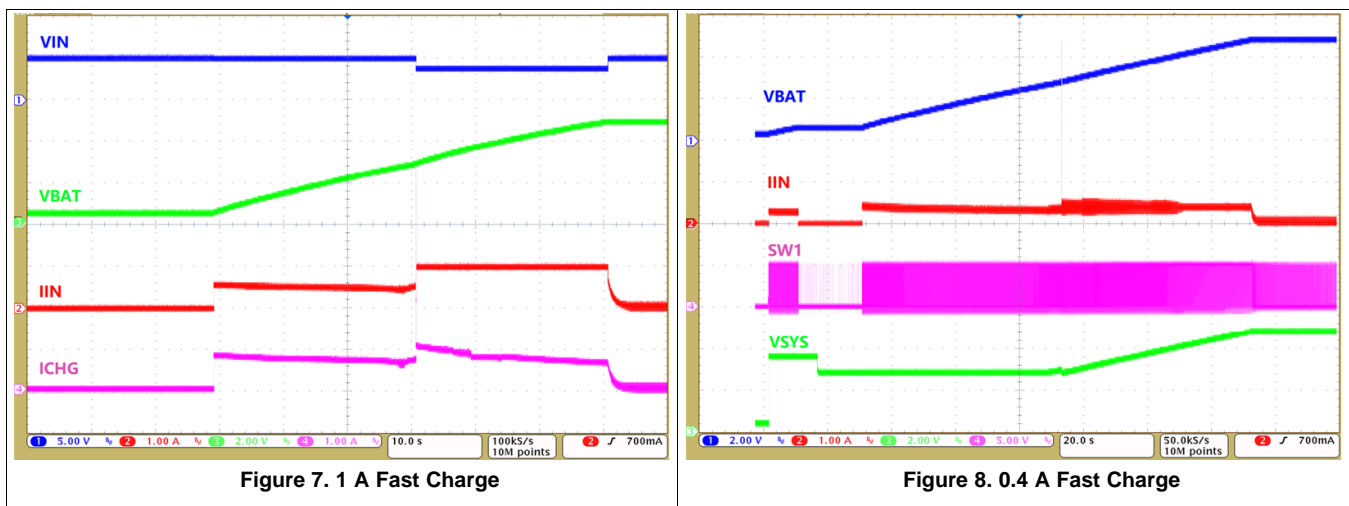

2) Use Integrated DPM Function

Figure 12 shows when DPM enabled and I_{IN} is reach up to 0.5 A , the charge current would reduce quick to maintain V_{IN} not drop. DPM function can make full use of any power source supply and avoid system crashed when input power is limited.

Figure 12. Charger with V_{IN} DPM Function

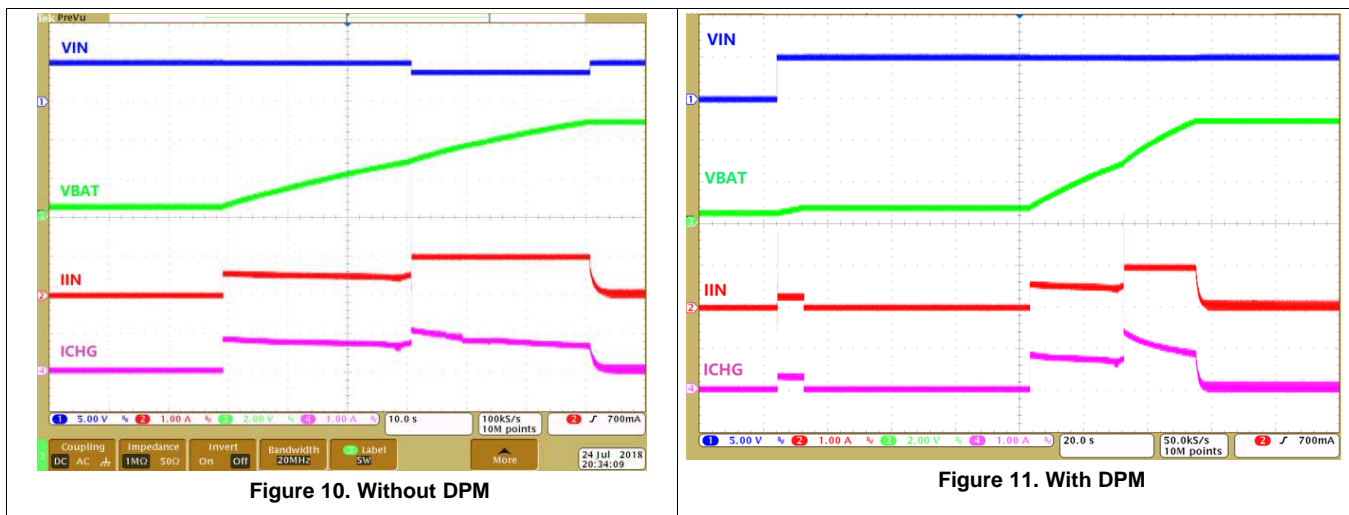


2.5 Cell Passive Balance

Cell balance function is important when mismatch between cells since manufacture and long term running. This could prevent one cell over charge while the other under charge to improve the life cycle of the super cap. Active balancer performance and efficiency are good while the control is complicated and cost is high. Passive balancer is simple and lower cost with tradeoff efficiency.

For 10 K ohm parallel resistance, there would be about 250 uA sell loss current. But compared with a typical 0.5 A current system, this small trickle can be ignored. For longer standby time or lower system current, suggest higher parallel resistance. The test waveform is as Figure 4 which shows cell voltage match well each other when charging.

Figure 15. Passive Cell Balance Function

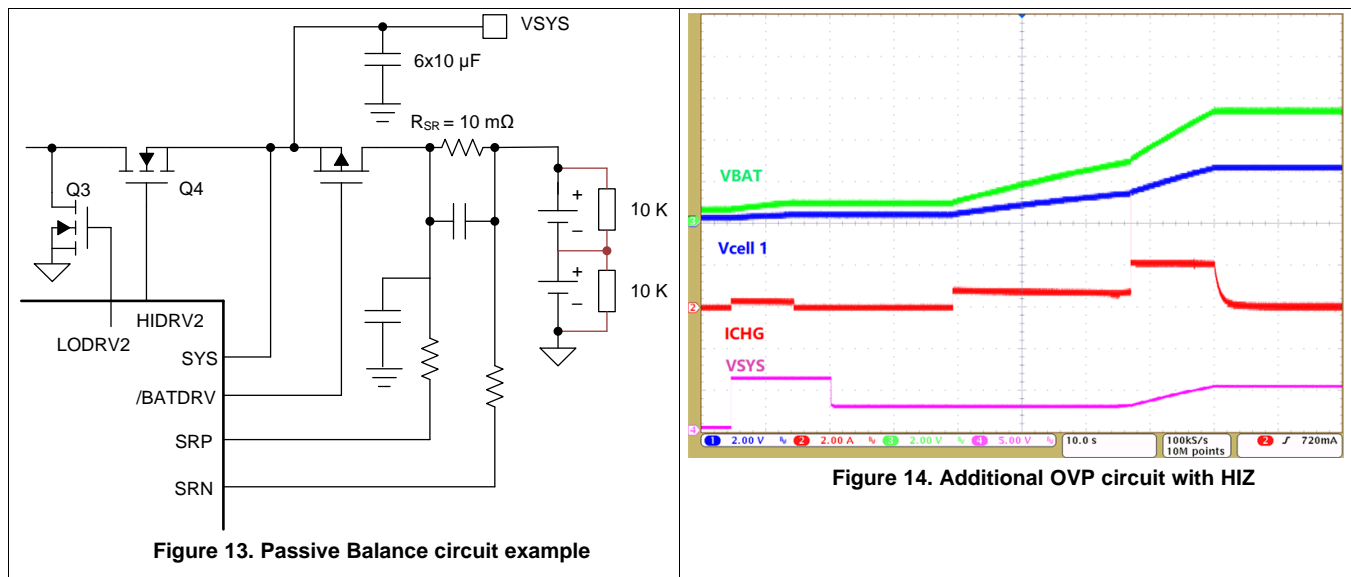

2.6 Hardware OVP Protection

BQ25703A have integrated Battery Overvoltage Protection (BATOVP). The BATOVP threshold is 104% (1 s) or 102% (2 s to 4 s) of regulation voltage set in REG0x05/04().

But in some case, when wrong high V_{CHG} setting or software control crashed, you need a additional way to protect OVP protection. BQ25703A have one internal comparator which is very suitable for addition protection like OVP, OCP and thermal protection. One method is using HIZ mode to disconnect V_{IN} when OVP. External control to cut off BATFET is another method to consider.

Figure 18. HIZ Mode OVP Protection

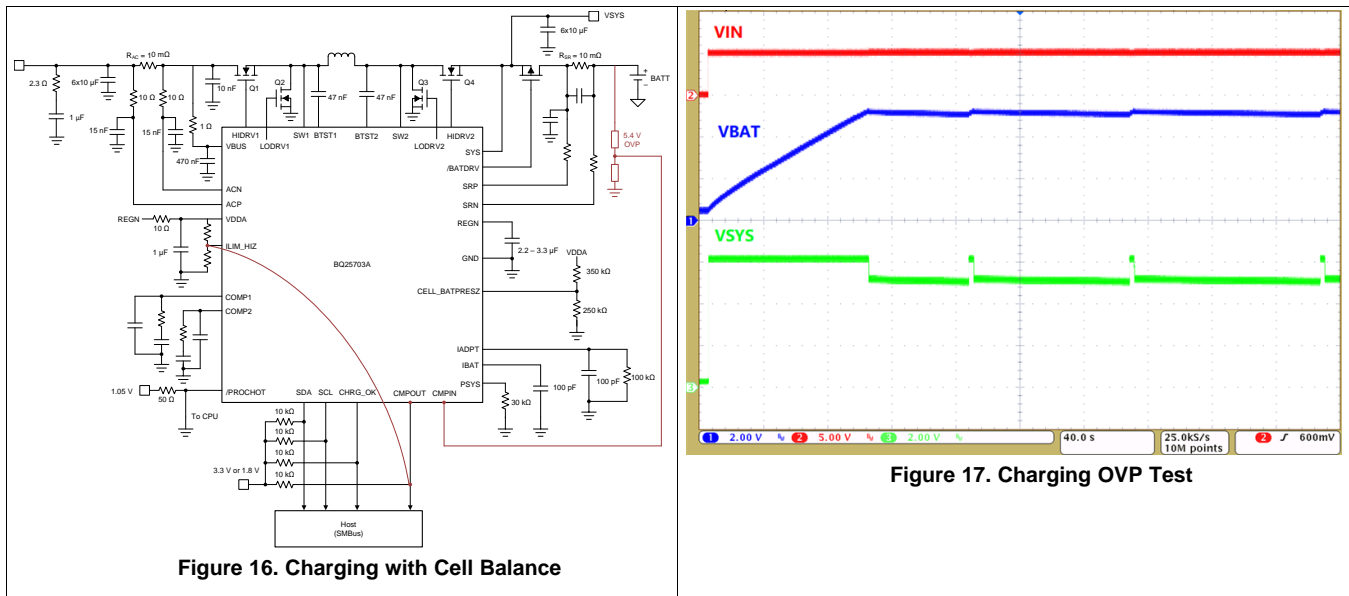


Figure 16. Charging with Cell Balance

Figure 17. Charging OVP Test

3 Summary

BQ25703A is a good device as buck boost charger for super cap application. Its NVDC power path, DPM function can make system works smarter and not add any cost. Additional feature like hardware OVP and passive balancer make solutions safer in real system.

4 References

- 1. Texas Instruments, [SLUSCU1A, BQ25703A product datasheet](#).
- 2. Texas Instruments, [SLUUBG6, "BQ2570x Evaluation Module" User's Guide](#).

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated