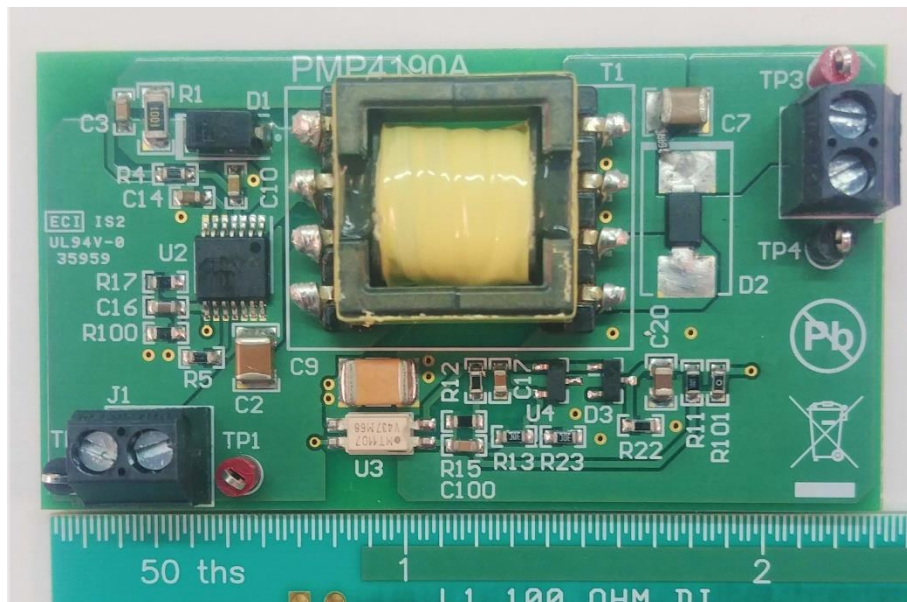


# Test Report: PMP4190 3-V to 6-V DC Input, 5-V/0.5-A, 1-MHz Isolated Flyback Reference Design



## Description

This simple and compact design demonstrates how integrated boost converters, usually relegated to portable applications, can be leveraged in isolated auxiliary supplies. This example showed how to use the TPS61175 with a low input voltage. This simple design can be placed in a small amount of board space. The design consumes a total of 1.8 in<sup>2</sup> on one side of the board.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage Range	3VDC – 6VDC
Output Voltage/Current	5V/0.5A


### 1.2 Required Equipment

- DC voltage source
- Electronic load
- Multi-meters
- Oscilloscope

## 2 Testing and Results


### 2.1 Efficiency

#### 2.1.1 5V Output

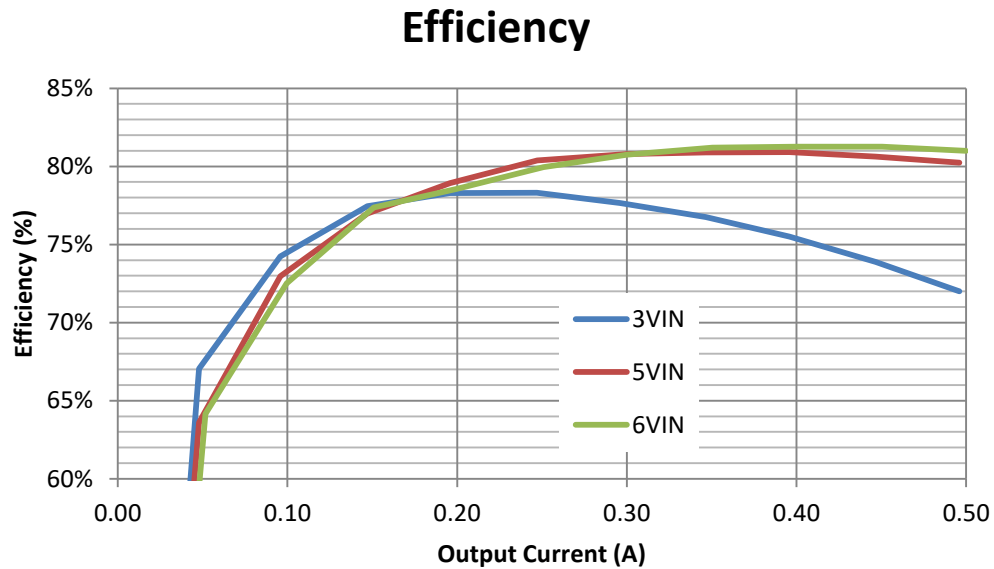

### 2.2 Losses

#### 2.2.1 5V Output

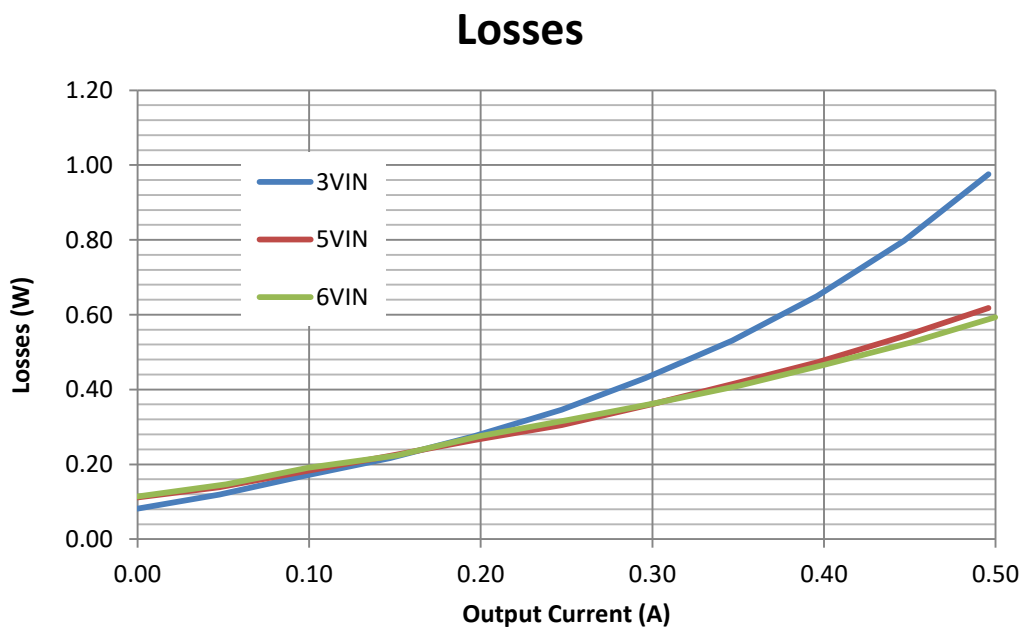


## 2.3 Thermal Images

Measured after 30 minutes at full load and 25° C ambient temperature with no external airflow.

### 2.3.1 3VDC Input, Top, 5V/0.5A Output

Sp1 – U2

Sp2 – D2

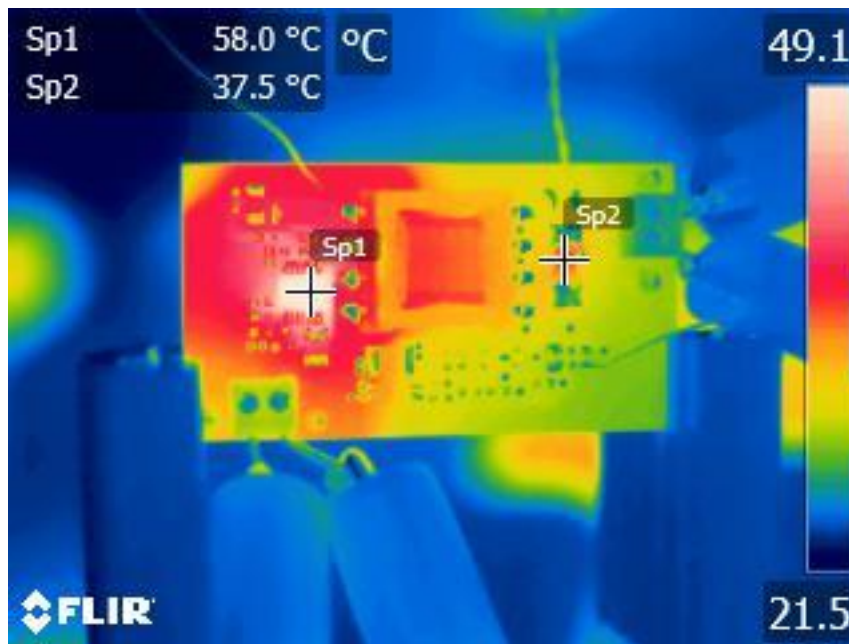


### 2.3.2 3VDC Input, Bottom, 5V/0.5A Output




### 2.3.3 5VDC Input, Top, 5V/0.5A Output

Sp1 – U2

Sp2 – D2

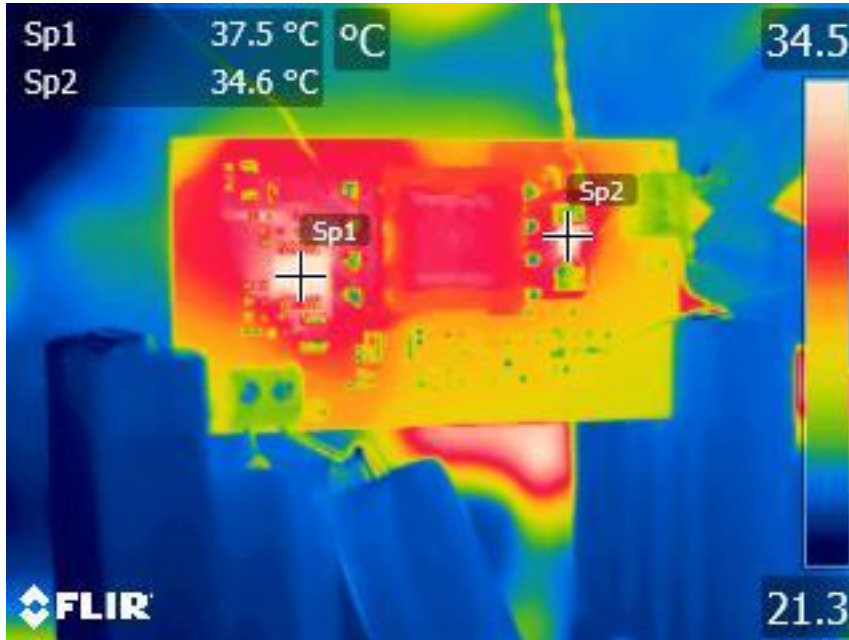

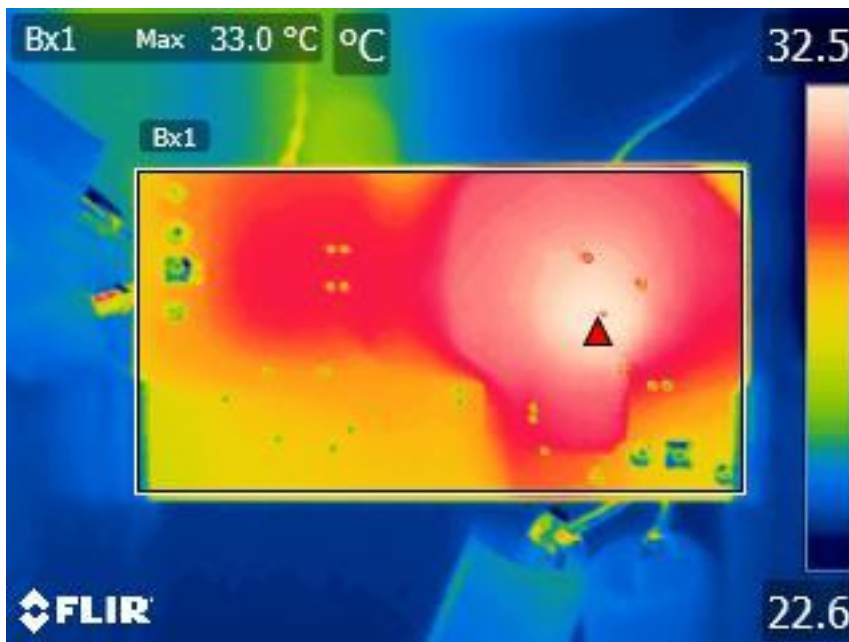
### 2.3.4 5VDC Input, Bottom, 5V/0.5A Output




### 3 Waveforms

#### 3.1 Switching
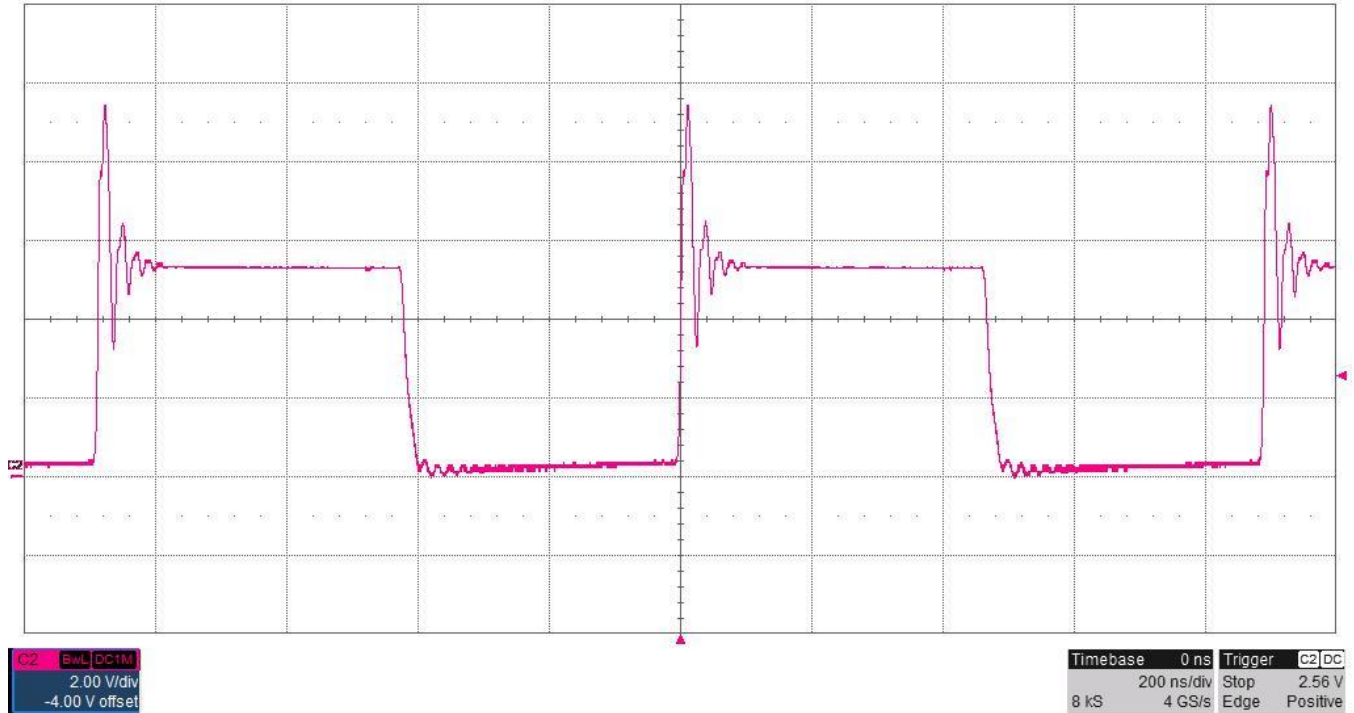
##### 3.1.1 SW to GND, 3VDC Input, 5V/0.5A Output



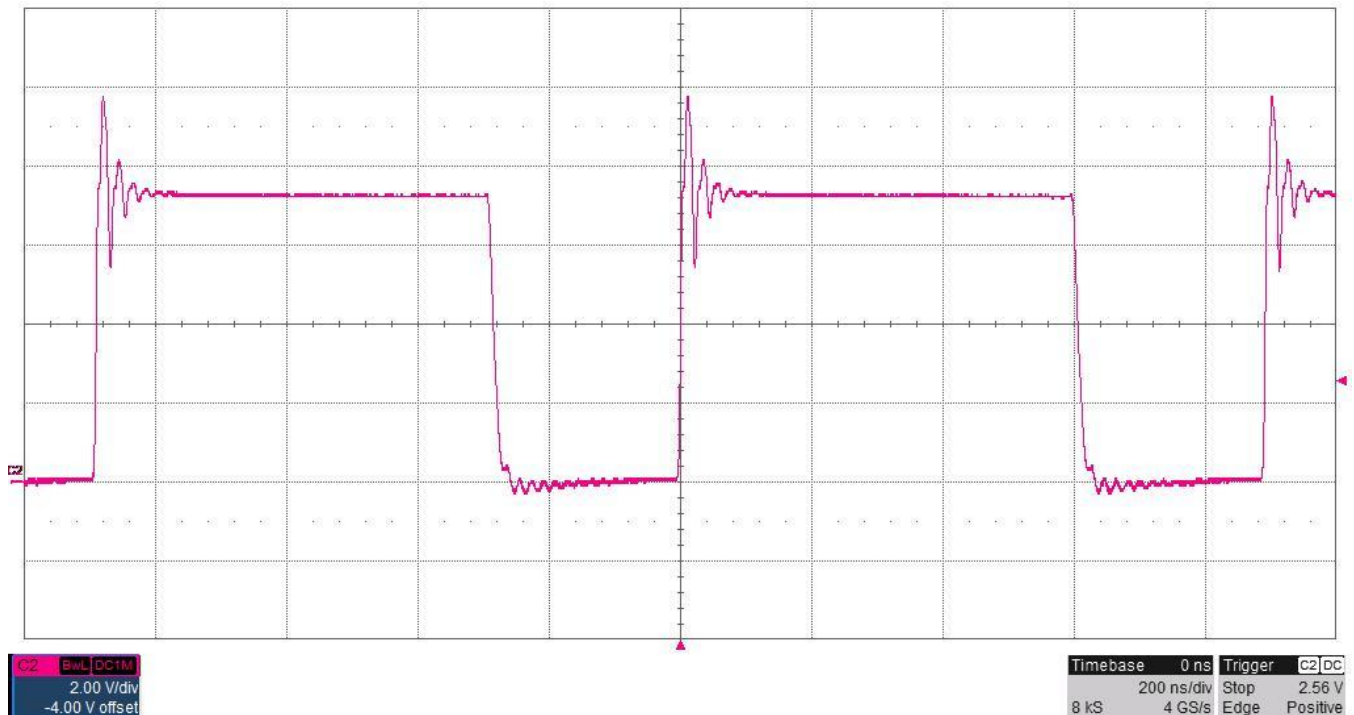
##### 3.1.2 SW to GND, 5VDC Input, 5V/0.5A Output




### 3.2 Output Voltage Ripple

#### 3.2.1 5V/0.5A Output, 3VDC Input

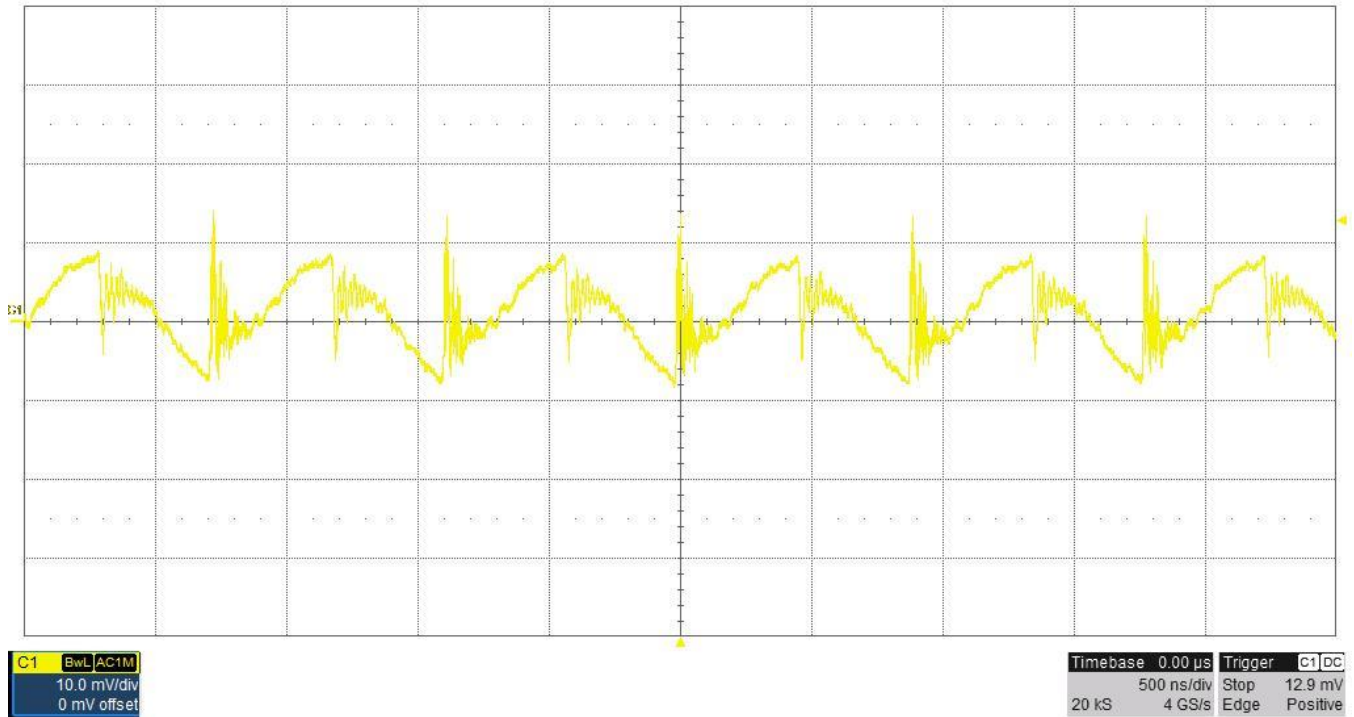


#### 3.2.2 5V/0.5A Output, 5VDC Input

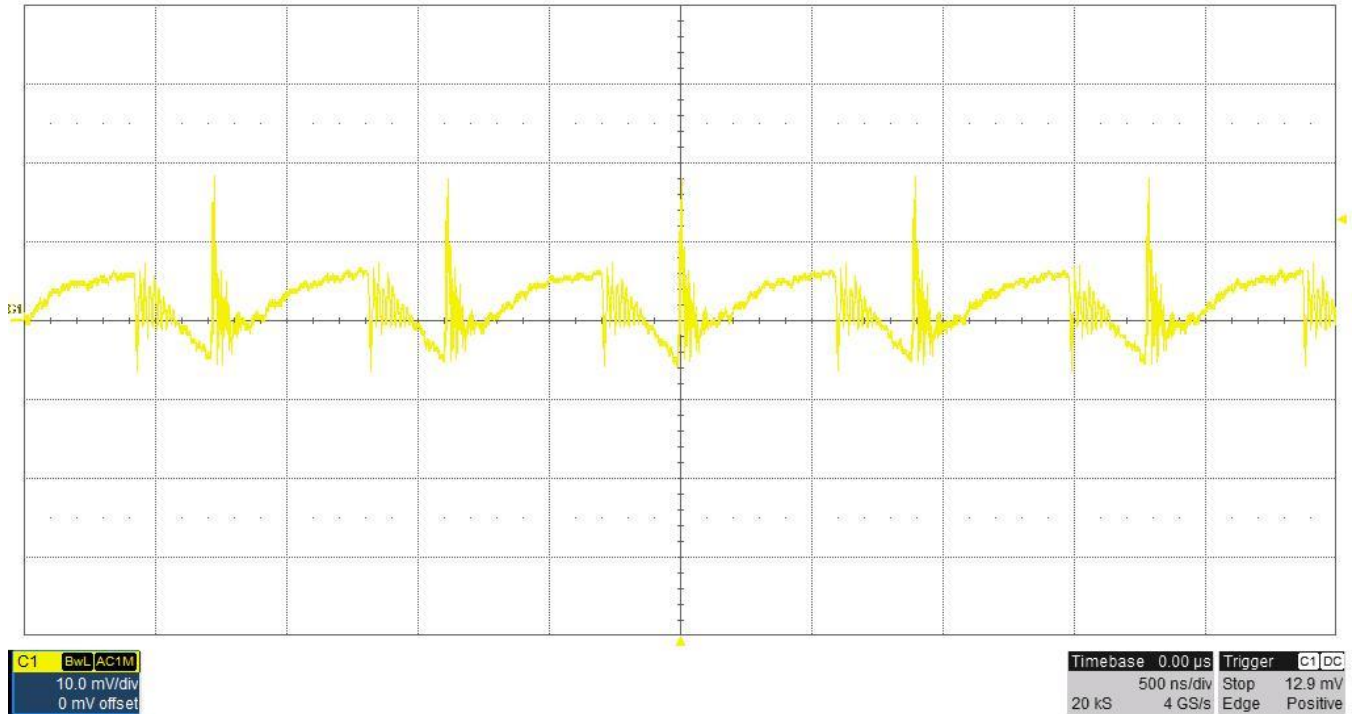

### 3.3 Bode Plot
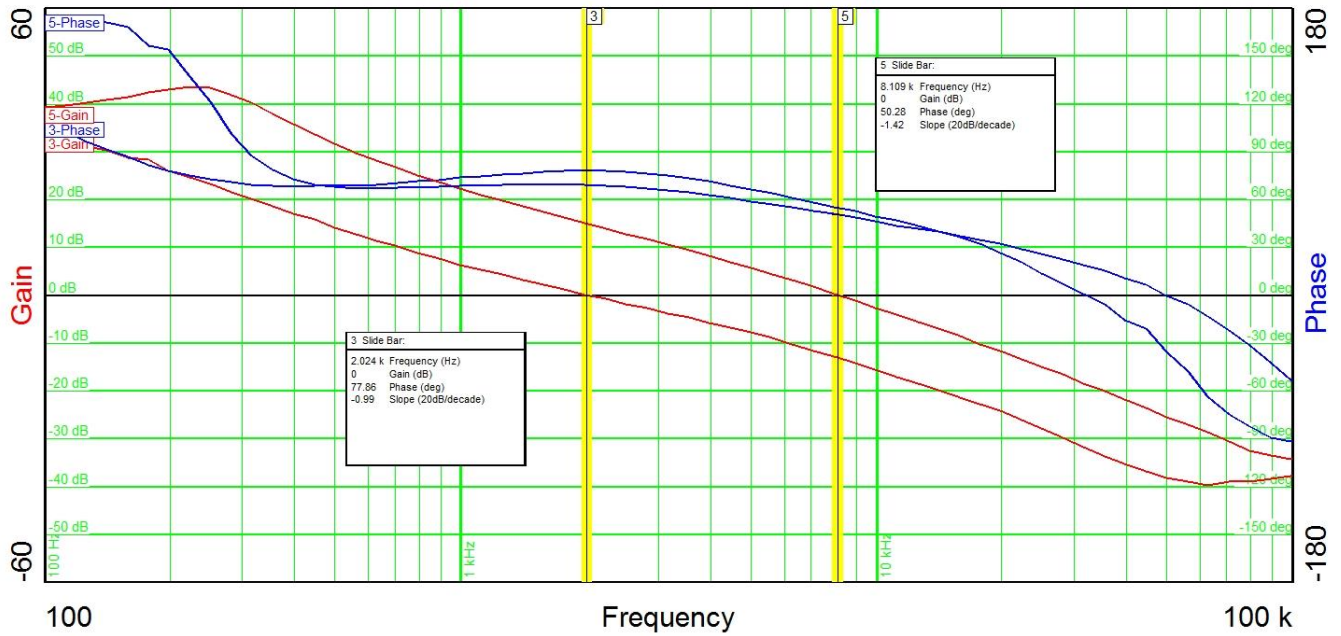
#### 3.3.1 5V/0.5A Output, 3VDC (3-Gain/3-Phase) and 5VDC (5-Gain/5-Phase) Input






### 3.4 Load Transients


#### 3.4.1 5V Output, 0A to 0.25A, 3VDC Input

C1 – Vout  
C4 – Iout

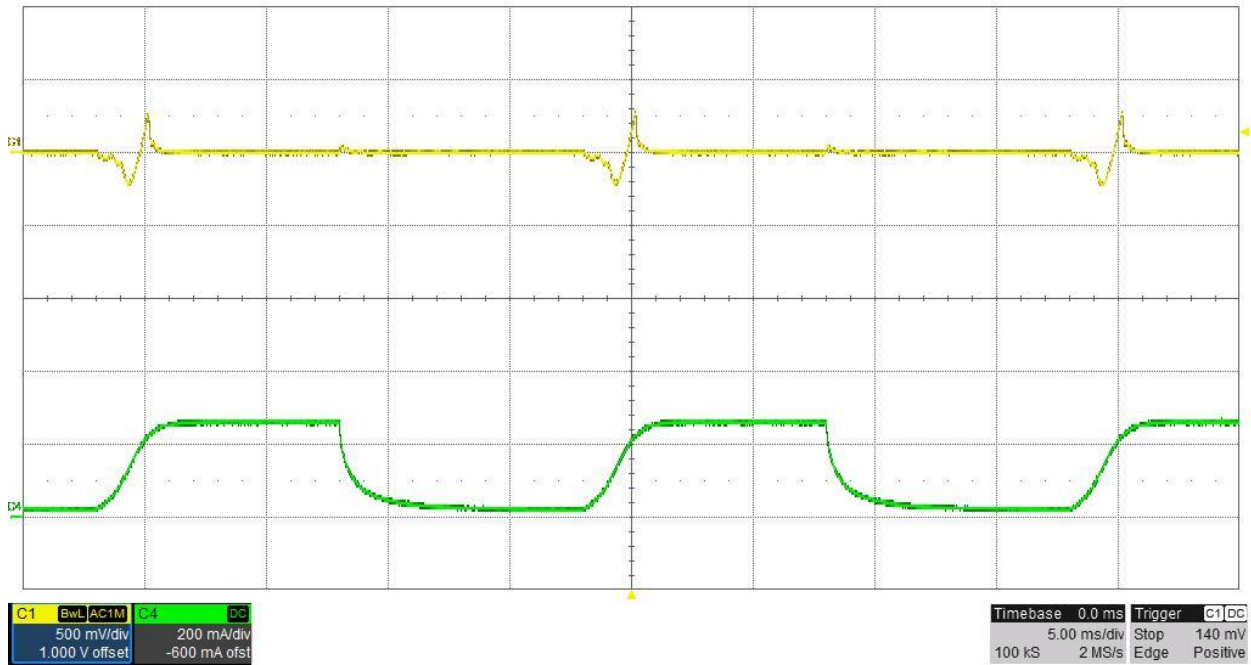

#### 3.4.2 5V Output, 0A to 0.25A, 5VDC Input


C1 – Vout  
C4 – Iout

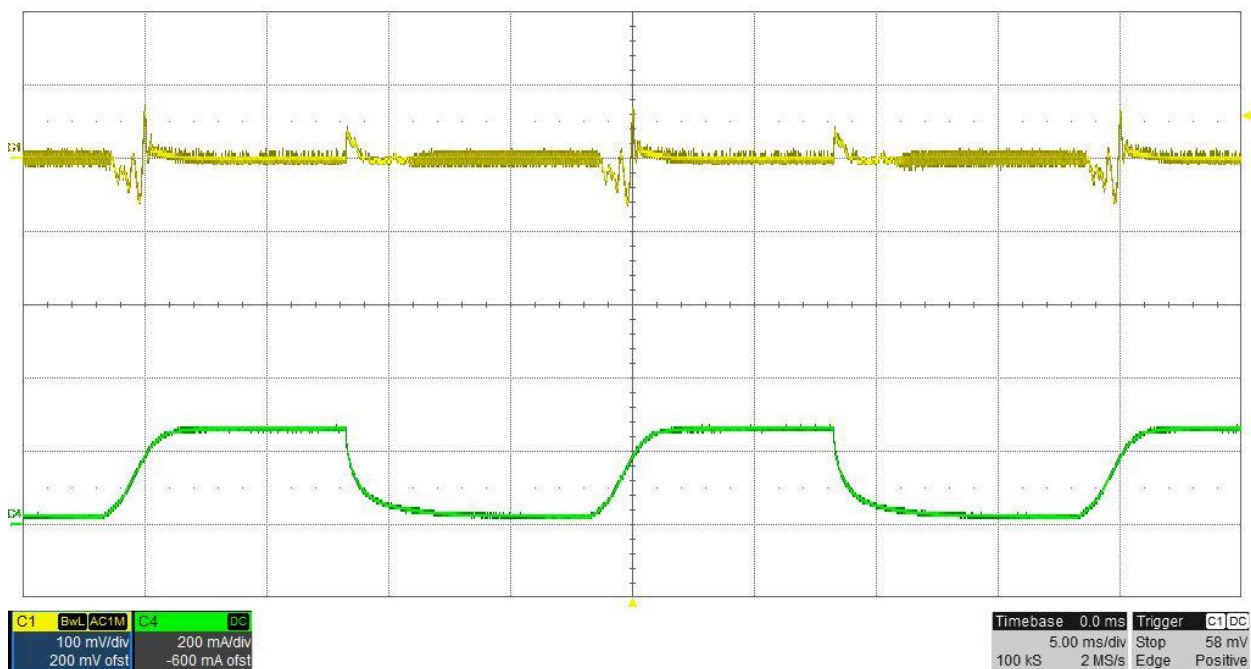

### 3.4.3 5V Output, 0.25A to 0.50A, 3VDC Input

C1 – Vout


C4 – Iout

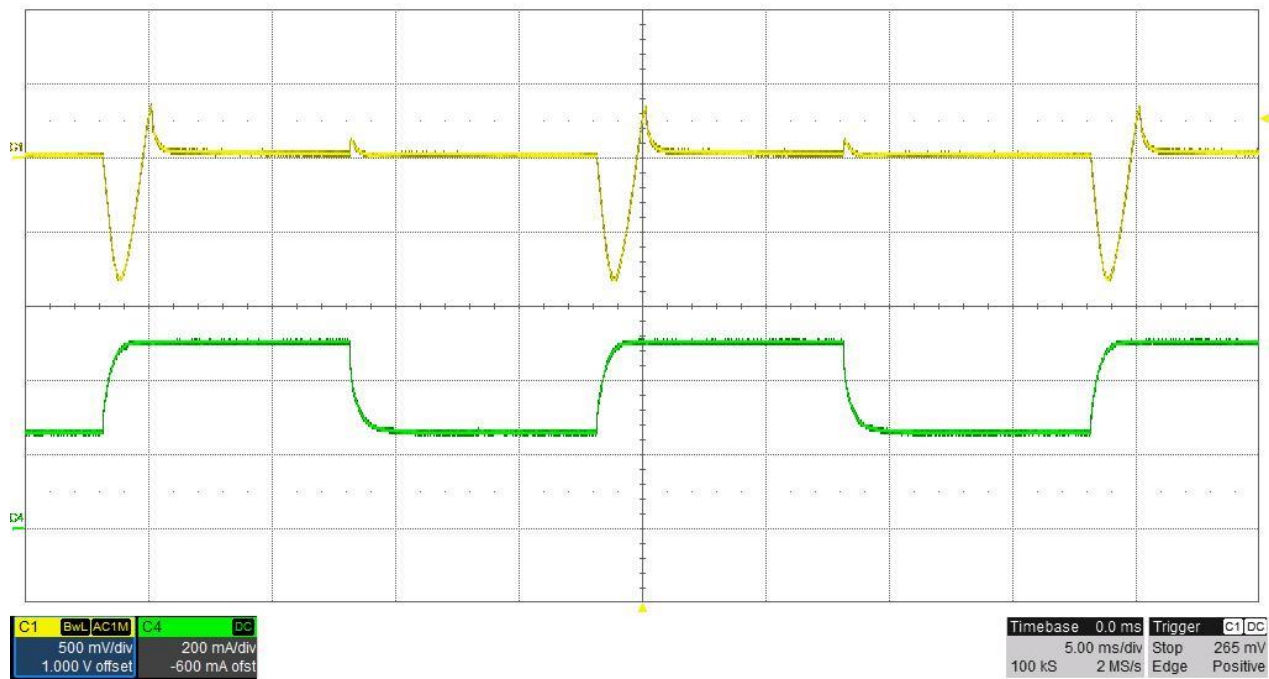

### 3.4.4 5V Output, 0.25A to 0.50A, 5VDC Input

C1 – Vout


C4 – Iout

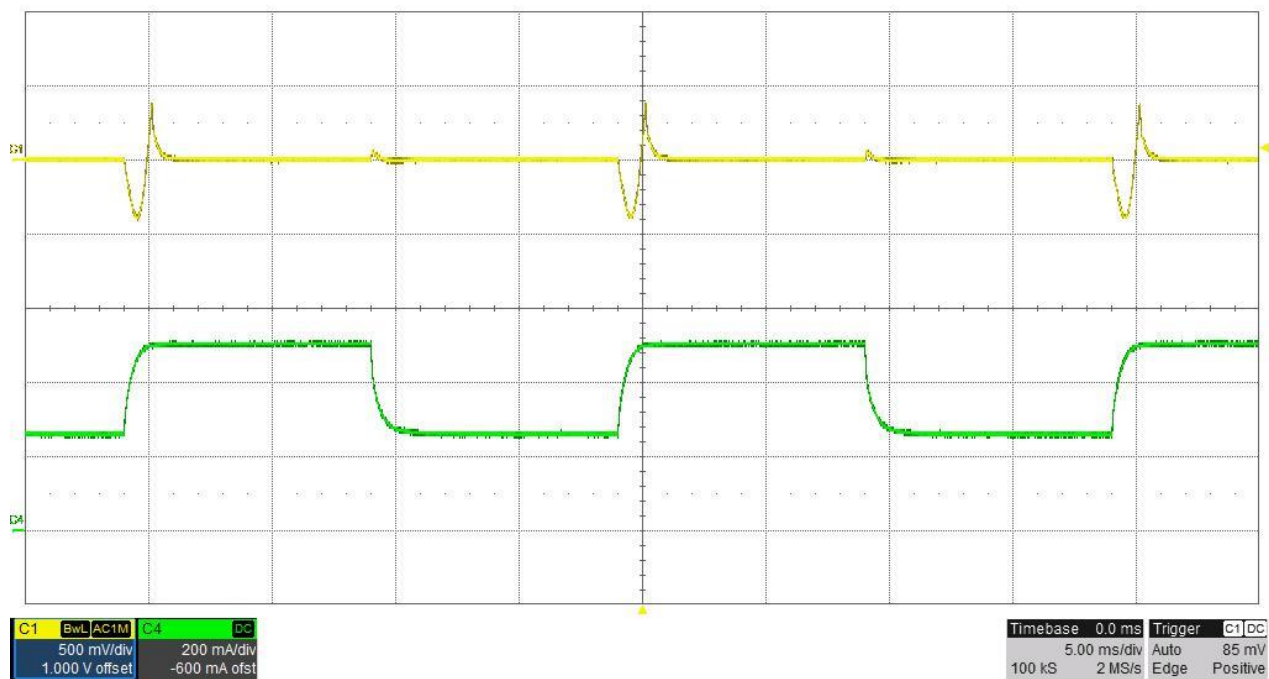

### 3.5 Start up


#### 3.5.1 5V Output, No Load

C1 – Vout  
C3 – Vin

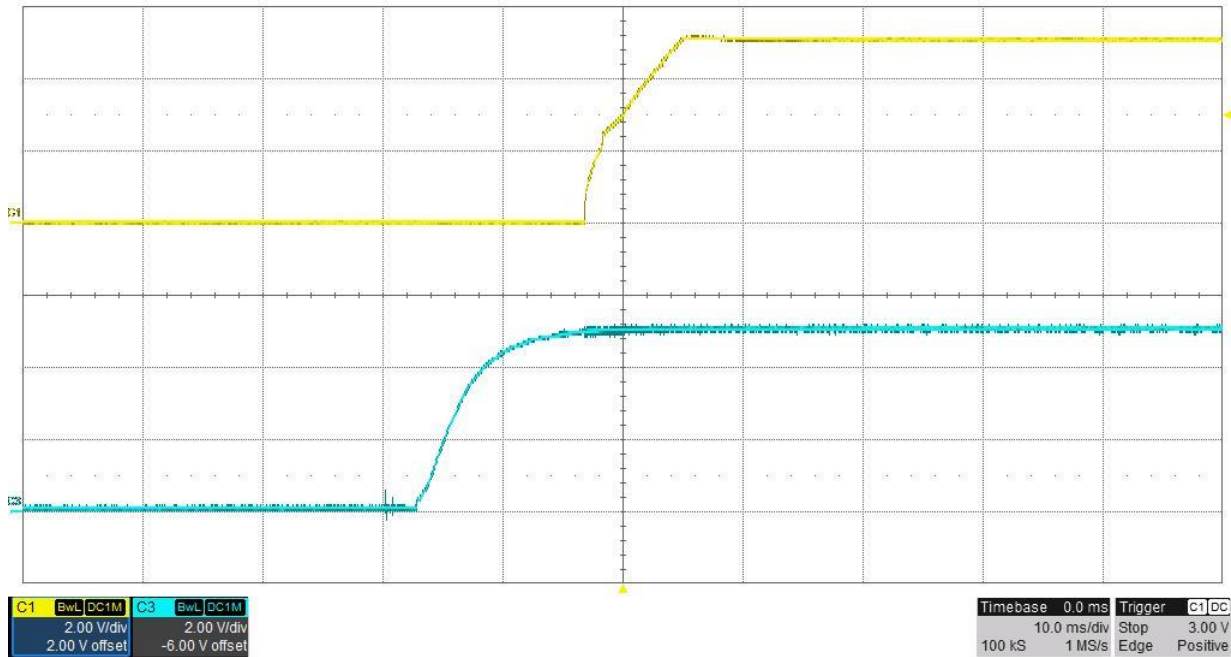

#### 3.5.2 5V Output, 0.5A,


C1 – Vout  
C3 – Vin

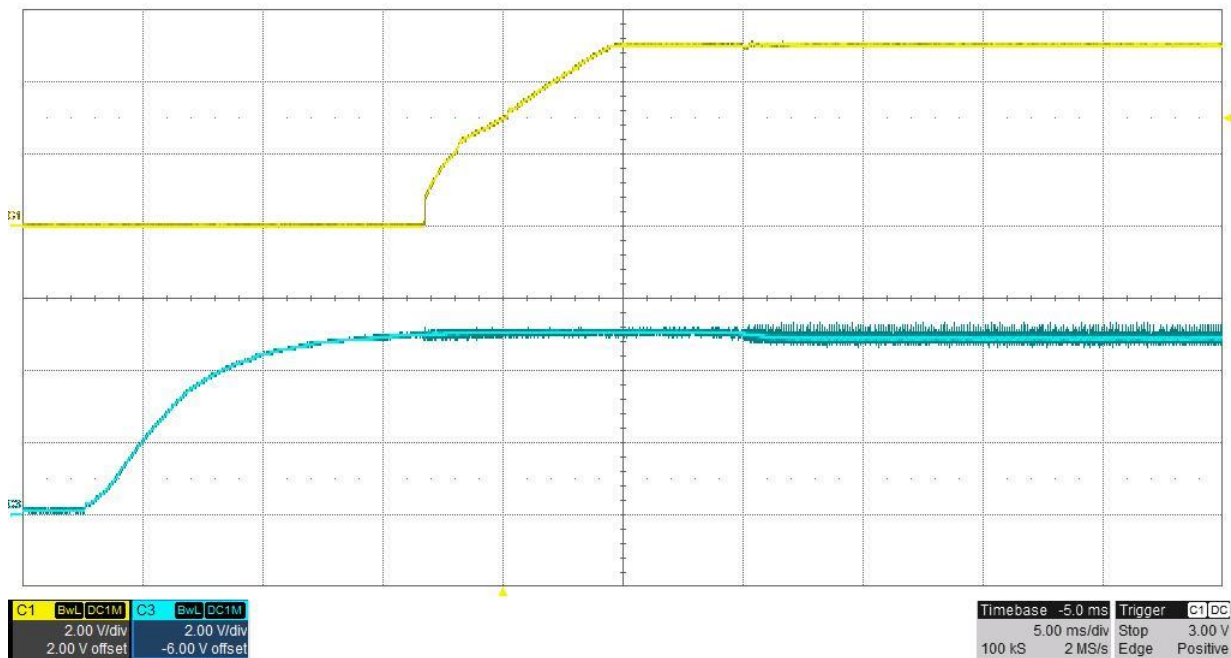

### 3.6 Shutdown


#### 3.6.1 5V Output, No Load

C1 – Vout  
C3 – Vin

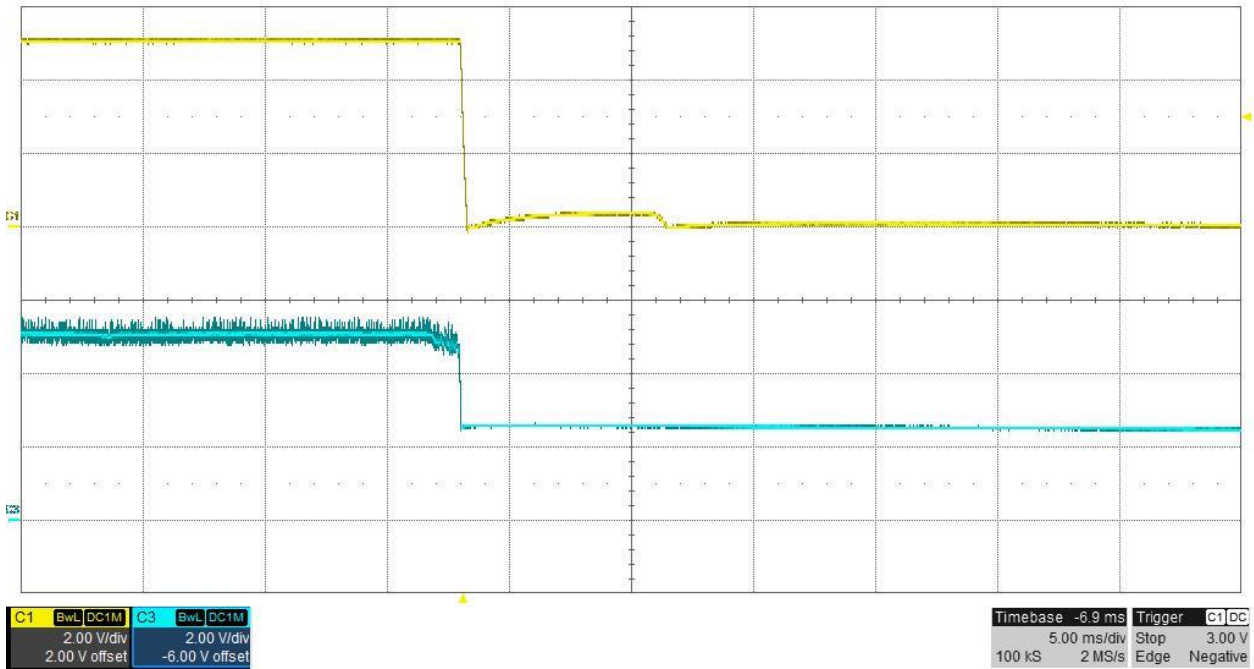

#### 3.6.2 5V Output, 0.5A,

C1 – Vout  
C3 – Vin

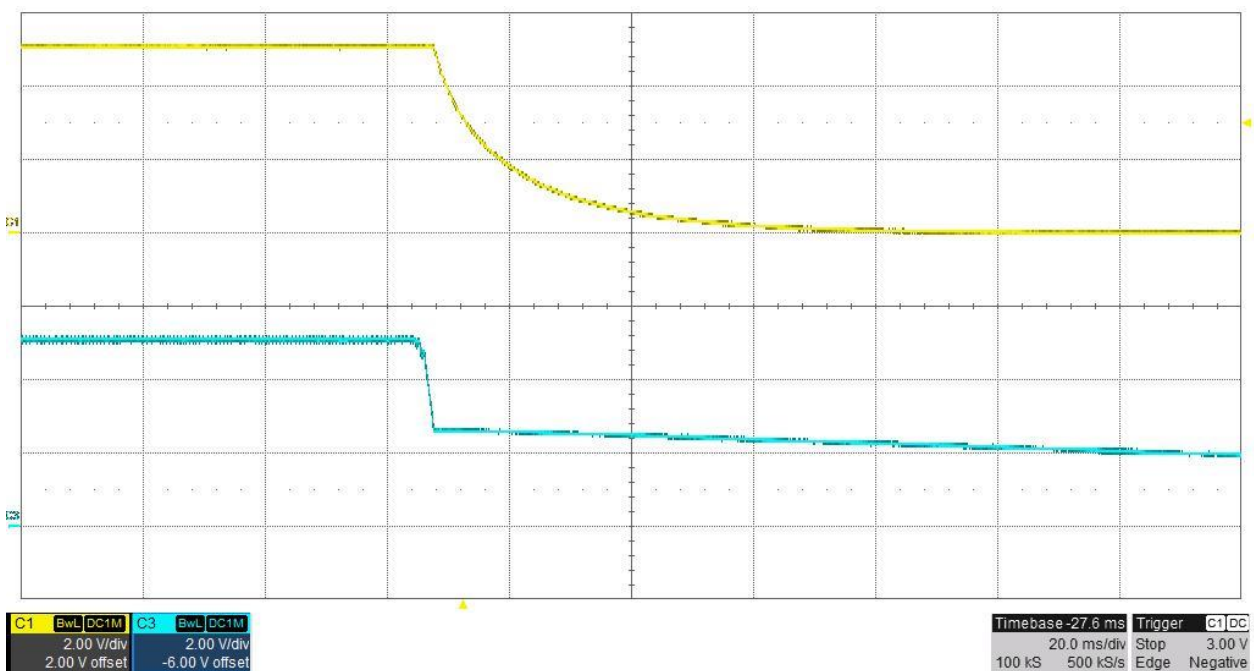

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated