

# Power Tips: in the Quest for No Standby Power, Where Do We Declare Victory?



Brian King

The U.S. and Europe’s energy-conservation programs are demanding standby power loss below 75mW and 100mW. Some industry-led initiatives are rewarding products that keep standby power consumption below 30mW. In the quest for no standby power, where do we declare victory?

It is becoming established in the industry that anything below 5mW is considered “zero-power” standby loss. This definition has been put forth by the International Electrotechnical Commission (IEC) 62301 clause 4.5.

Operating at very low switching frequencies is critical to achieving the lowest standby power consumption possible. In-between switching pulses, the AC/DC controller goes to sleep. Each time it switches, the controller awakens just long enough to monitor the loading conditions and determine the frequency at which it should continue to operate.

What happens if a load step occurs while the controller is asleep? Obviously, the output voltage drops until the next switching event, which can be a very long time. This limits the minimum switching frequency of controllers in standby mode to around 200Hz, without requiring inordinately huge output capacitors. At this frequency, standby power consumption levels can easily be kept below 20mW.

A minimum switching frequency in the tens of hertz is required to achieve standby power-consumption levels below 5mW. By using a simple wakeup monitor, the primary controller can operate at these incredibly low switching frequencies without sacrificing load-step response. Figure 1 shows a simplified schematic.

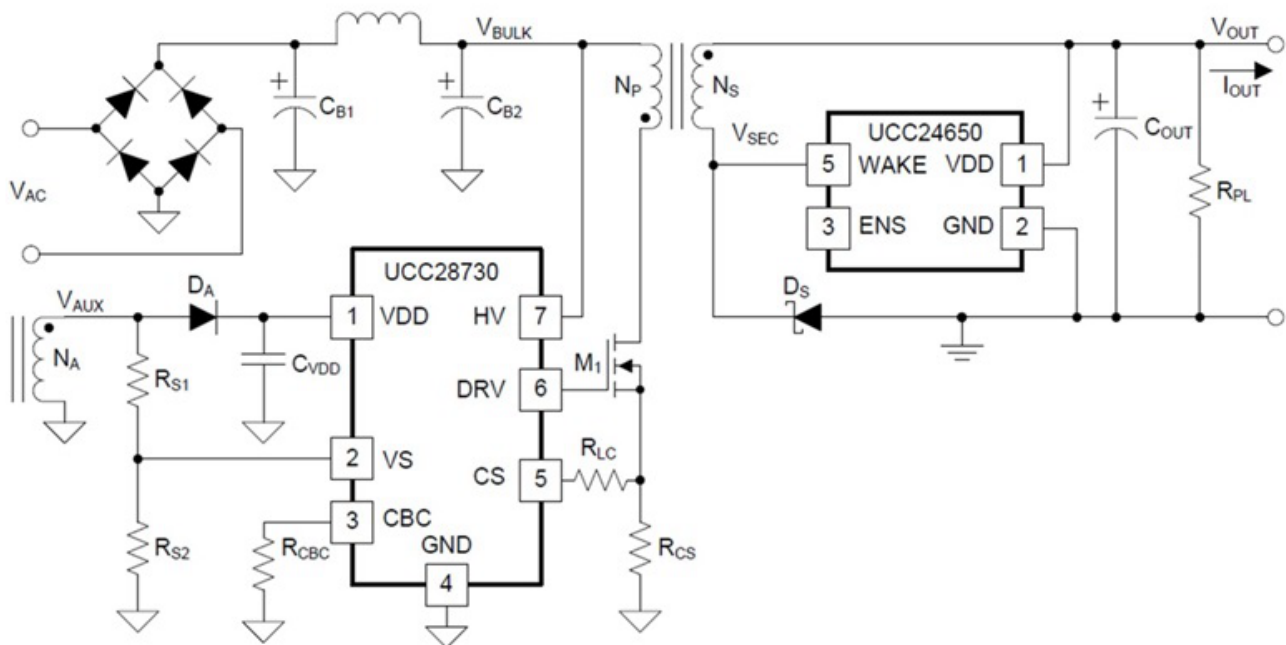


Figure 1. A Wakeup Monitor Enables Extremely Low Switching Frequencies, Minimizing Standby Power Loss

---

The wakeup monitor is located on the secondary side of the transformer and keeps continual watch on the output. Once it detects a load, the wakeup IC pulls the transformer secondary winding low for a short time, telling the primary-side controller to wake up immediately and respond to the increased load demand.

Minimizing standby power consumption requires implementing many other features as well – I discuss a few more details in my latest Power Tips [post](#) on EE Times. Find previous posts from TI's previous [Power Tips posts](#).

In addition, here are a couple of examples of AC/DC converters that use a wakeup monitor to minimize no-load power consumption from our TI Designs power reference designs:

- 5V/10W Off-Line DCM Flyback Converter Optimized for Zero-Power at No-Load: [PMP9561](#)
- 24V/12W Off-Line DCM Flyback Converter Optimized for Zero-Power at No-Load: [PMP10927](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated