



## Design Steps


1. Select  $R_{set}$  and check  $I_{LMin}$  based on voltage compliance.

$$I_{LMax} = \frac{V_{oOPAMax}}{R_{set} + R_{LMax}}$$

$$10\mu A = \frac{4.9V}{R_{set} + 390k\Omega} \rightarrow R_{set} = 100k\Omega$$

$$I_{LMin} = \frac{V_{oOPAMin}}{R_{set} + R_{LMin}}$$
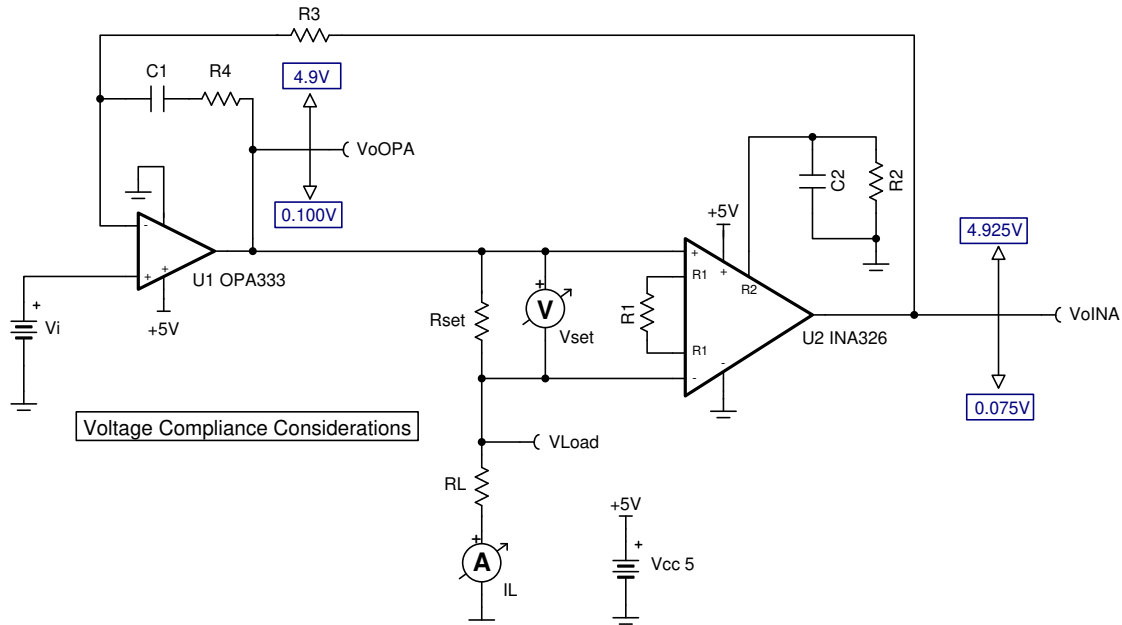
$$I_{LMin} = \frac{0.1V}{100k\Omega + 0\Omega} = 1\mu A$$



2. Compute instrumentation amplifier gain,  $G$ .

$$V_{setMin} = I_{LMin} \times R_{set} = 1\mu A \times 100k\Omega = 0.1V$$

$$V_{setMax} = I_{LMax} \times R_{set} = 10\mu A \times 100k\Omega = 1V$$

$$G = \frac{V_{iMax} - V_{iMin}}{V_{setMax} - V_{setMin}}$$

$$G = \frac{4.9V - 0.49V}{1V - 0.1V} = 4.9$$

3. Choose  $R_1$  for INA326 instrumentation amplifier gain,  $G$ . Use data sheet recommended  $R_2 = 200k\Omega$  and  $C_2 = 510pF$ .

$$G = 2 \times \left( \frac{R_2}{R_1} \right)$$

$$R_1 = \frac{2 \times R_2}{G}$$

$$R_1 = \left( \frac{2 \times 200k\Omega}{4.9} \right) = 81.6327k\Omega \approx 81.6k\Omega$$

4. The final transfer function of the circuit follows:

$$I_L = \frac{V_i}{G \times R_{set}}$$

$$I_L = \frac{V_i}{4.9 \times 100k\Omega} = \frac{V_i}{490k\Omega}$$


$$V_i = 0.49V \rightarrow I_L = 1\mu A$$

$$V_i = 4.9V \rightarrow I_L = 10\mu A$$

## Design Simulations

### DC Simulation Results

$V_i$	$R_L$	$I_L$	$V_{oOPA}$	$V_{oOPA}$ Compliance	$V_{oINA}$	$V_{oINA}$ Compliance
0.49V	0Ω	0.999627μA	99.982723mV	100mV to 4.9V	490.013346mV	75mV to 4.925V
0.49V	390kΩ	0.999627μA	489.837228mV	100mV to 4.9V	490.013233mV	75mV to 4.925V
4.9V	0Ω	9.996034μA	999.623352mV	100mV to 4.9V	4.900016V	75mV to 4.925V
4.9V	390kΩ	9.996031μA	4.898075V	100mV to 4.9V	4.900015V	75mV to 4.925V

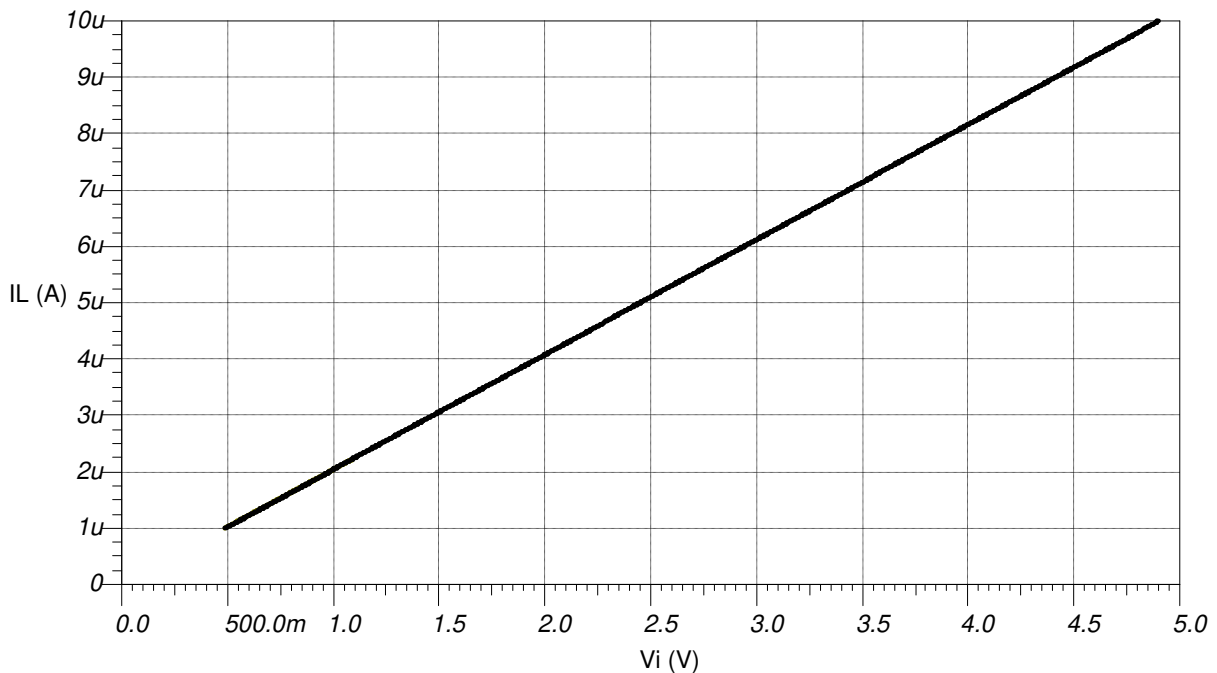

### Design References

Texas Instruments, [SBOMAT8 TINA-TI™ circuit simulation](#), file download

Texas Instruments, [Low-Level V-to-I Converter Reference Design, 0V to 5V Input and 0μA to 5μA Output](#), product page

Texas Instruments, [Solving Op Amp Stability Issues](#), E2E™ amplifiers forum

## Design Featured Op Amp

OPA333	
$V_{SS}$	1.8V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	2 $\mu$ V
$I_q$	17 $\mu$ A/Ch
$I_b$	70pA
UGBW	350kHz
SR	0.16V/ $\mu$ s
#Channels	1 and 2
<a href="#">OPA333</a>	

## Design Featured Instrumentation Amplifier

INA326	
$V_{SS}$	2.7V to 5.5V
$V_{inCM}$	Rail-to-rail
$V_{out}$	Rail-to-rail
$V_{os}$	20 $\mu$ V
$I_q$	2.4mA
$I_b$	0.2nA
UGBW	1kHz (set by 1kHz filter)
SR	0.012V/ $\mu$ s (set by 1kHz filter)
#Channels	1
<a href="#">INA326</a>	

## Trademarks

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated