

# Analog Engineer's Circuit

## Inverting attenuator circuit




### Amplifiers

#### Design Goals

Input		Output		BW	Gain	Supply	
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$f_p$	G	$V_{cc}$	$V_{ee}$
-200V	200V	-2V	2V	1MHz	-40dB	2.5V	-2.5V
 
#### Design Description

This circuit inverts the input signal,  $V_i$ , and applies a signal gain of  $-40\text{dB}$ . The common-mode voltage of an inverting amplifier is equal to the voltage applied to the non-inverting input, which is ground in this design.



#### Design Notes

1. The common-mode voltage in this circuit does not vary with input voltage.
2. The input impedance is determined by the input resistor. Make sure this value is large when compared to the output impedance of the source.
3. Using high-value resistors can degrade the phase margin of the circuit and introduce additional noise in the circuit. The capacitor in parallel with  $R_2$  provides filtering and improves stability of the circuit if high-value resistors are used for both the input and feedback resistances.
4. Avoid placing capacitive loads directly on the output of the amplifier to minimize stability issues.
5. Small-signal bandwidth is determined by the noise gain (or non-inverting gain) and op amp gain-bandwidth product (GBP).
6. Large signal performance may be limited by slew rate. Therefore, check the maximum output swing versus frequency plot in the data sheet to minimize slew-induced distortion.
7. For more information on op amp linear operating region, stability, slew-induced distortion, capacitive load drive, driving ADCs, and bandwidth see the [Design References](#) section.
8. Note that higher input voltage levels may require the use of multiple resistors in series to help reduce the voltage drop across the individual resistors. For more information, see the [Design References](#) section.

## Design Steps

The transfer function of this circuit follows:

$$V_o = V_i \times \left( -\frac{R_2}{R_1} \right)$$

1. Calculate the gain required for the circuit.

$$G = \frac{V_{oMax} - V_{oMin}}{V_{iMax} - V_{iMin}} = \frac{2V - (-2V)}{200V - (-200V)} = 0.01 \frac{V}{V} = -40dB$$

2. Choose the starting value of  $R_1$ .

$$R_1 = 100k\Omega$$

3. Calculate for a desired signal attenuation of 0.01 V/V.

$$G = \frac{R_2}{R_1} \rightarrow R_2 = R_1 \times G = 0.01 \frac{V}{V} \times 100k\Omega = 1k\Omega$$

4. Select the feedback capacitor,  $C_1$ , to meet the circuit bandwidth.

$$C_1 \leq \frac{1}{2\pi \times R_2 \times f_p} \rightarrow C_1 \leq \frac{1}{2\pi \times 1k\Omega \times 1MHz} \leq 159.15pF \approx 160pF \text{ (Standard Value)}$$

5. Calculate the minimum slew rate required to minimize slew-induced distortion.

$$V_p < \frac{SR}{2\pi \times f_p} \rightarrow SR > 2\pi \times f \times V_p \rightarrow SR > 2\pi \times 1 \text{ MHz} \times 2 \text{ V} = 12.6 \frac{V}{\mu S}$$

- $SR_{LMV861} = 18V/\mu s$ ; therefore, it meets this requirement.

6. Calculate the circuit bandwidth to ensure it meets the 1-MHz requirement. Be sure to use the noise gain, NG, or non-inverting gain, of the circuit.

$$NG = 1 + \frac{R_2}{R_1} = 1.01 \frac{V}{V} \rightarrow BW = \frac{GBP}{NG} = \frac{30MHz}{1.01 \frac{V}{V}} = 29.7MHz$$

- $BW_{LMV861} = 30MHz$ ; therefore, it meets this requirement.


7. If  $C_1$  is not used to limit the circuit bandwidth, to avoid stability issues ensure that the zero created by the gain setting resistors and input capacitance of the device is greater than the bandwidth of the circuit.

$$\frac{1}{2\pi \times (C_{cm} + C_{diff}) \times (R_2 \parallel R_1)} > \frac{GBP_{LMV861}}{NG}$$


- $C_{cm}$  and  $C_{diff}$  are the common-mode and differential input capacitance of the LMV861, respectively.

## Design Simulations

### DC Simulation Results

 


### AC Simulation Results

 
 
## Transient Simulation Results

A 1-kHz, 400-Vpp input sine wave yields a 4-Vpp output sine wave.



## Design References

1. See [Analog Engineer's Circuit Cookbooks](#) for the comprehensive TI circuit library.
2. SPICE Simulation File [SBOC522](#).
3. [TI Precision Labs](#)
4. For more information on circuits with larger input voltages, see [Considerations for High-Voltage Measurements](#).

## Design Featured Op Amp

LMV861	
$V_{SS}$	2.7V to 5.5V
$V_{inCM}$	(V <sub>ee</sub> – 0.1V) to (V <sub>cc</sub> – 1.1V)
$V_{out}$	Rail-to-rail
$V_{os}$	0.273mV
$I_q$	2.25mA
$I_b$	0.1pA
UGBW	30MHz
SR	18V/μs
#Channels	1, 2
<a href="http://www.ti.com/product/LMV861">www.ti.com/product/LMV861</a>	

## Design Alternate Op Amp

	TLV9002	OPA377
$V_{SS}$	1.8V to 5.5V	2.2V to 5.5V
$V_{inCM}$	Rail-to-rail	Rail-to-rail
$V_{out}$	Rail-to-rail	Rail-to-rail
$V_{os}$	0.4mV	0.25mV
$I_q$	0.06mA	0.76mA
$I_b$	5pA	0.2pA
UGBW	1MHz	5.5MHz
SR	2V/μs	2V/μs
#Channels	1, 2, 4	1, 2, 4
	<a href="http://www.ti.com/product/TLV9002">www.ti.com/product/TLV9002</a>	<a href="http://www.ti.com/product/OPA377">www.ti.com/product/OPA377</a>

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated