

## High Voltage Power Supply Using the TPS61040


Michael Day

Power Management Products/Portable Power DC-DC Applications

### ABSTRACT

The TPS61040 is a highly integrated, low power, boost converter capable of delivering output voltages up to 28 V. The addition of two small diodes and two small capacitors enables the TPS61040 to deliver output voltages up to 50 V.

The maximum allowable voltage on the SW pin of the TPS61040 limits the output voltage to 28 V. The addition of C2, C5, D2, and D3 allow the supply to deliver output voltages over 50 V. The circuit shown in Figure 1 generates a 50 V output at up to 15 mA, depending upon input voltage. The portion of the circuit within the dotted line is a basic boost topology based upon the TPS61040. Steady state operation of the supply is described below.

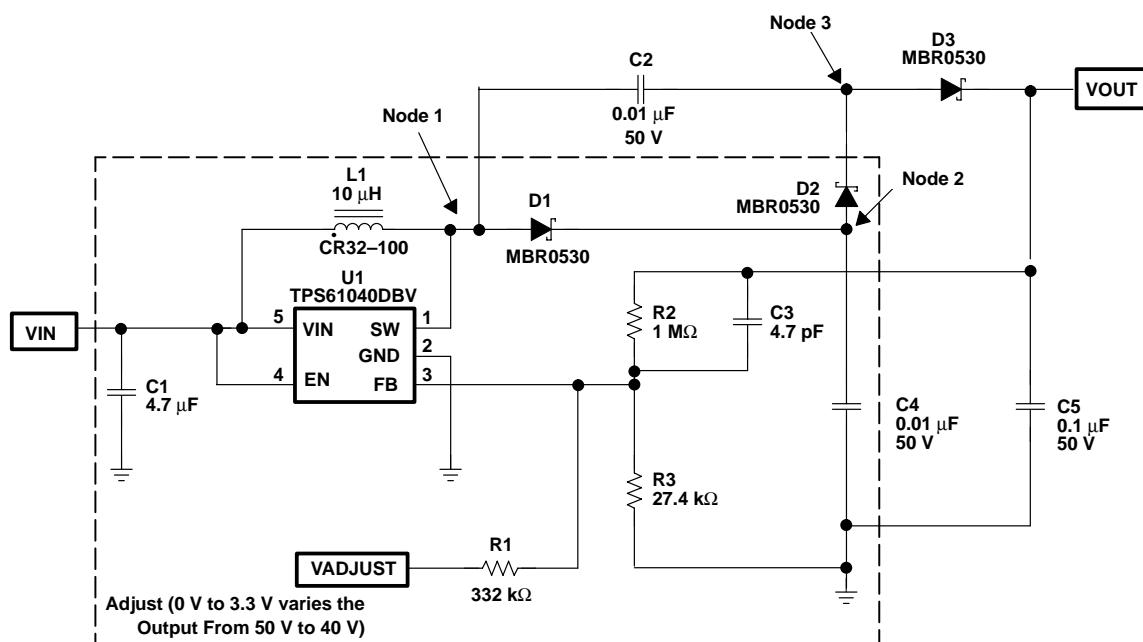

**Figure 1. Example Power Supply Using the TPS61040**

When the internal power switch of the TPS61040 is closed, current flows from the input, through L1, through the internal switch, to ground. During this time, the voltage at node 1 is 0 V and the voltage at node 2 is equal to 25 V ( $V_{out}/2$ ). D2 is forward biased, so the voltage at node 3 is also 25 V. This charges C2 up to 25 V. D3 is reverse biased during this time, so the output current is supplied by the output capacitor, C5.

When the power switch opens, current flows through L1 and D1 into C4. D1 is now forward biased; therefore, the voltage at node 1 is equal to the voltage on C4 (25 V). C2, which was previously charged to 25 V is now referenced to node 1. The voltage across C2 remains at 25 V, but the left side is 25 V with respect to ground and the right side is 50 V with respect to ground. As node 3 is forced to 50 V, D3 becomes forward biased and C5 is charged to 50 V. D2 is reverse biased during this time period.

The output is regulated to 50 V through the feedback divider that goes back to the FB pin of the TPS61040. An unregulated output voltage of 1/2  $V_{out}$  is available from node 2 in this configuration. If desired, the feedback can be recalculated for a 25 V output and connected to node 2. This provides a regulated 25-V output and an unregulated 50-V output.

D1, D2, and D3 must be rated for at least 1/2 the output voltage. The peak current ratings for the diodes must be greater than 1/2 the peak switch current of the TPS61040 (400 mA for the TPS61040 and 250 mA for the TPS61041). C2 and C3 must have voltage ratings greater than 1/2 the output voltage, while C5 must be rated for the full output voltage. The required capacitance of C2 and C3 can be roughly calculated by the equation shown below. A higher value capacitance may be chosen with no adverse effects on the power supply; however, reducing the capacitance may cause excessive ringing and jitter in the output voltage waveform.

$$C_{2,4} \equiv \frac{I_{pk} \times I_{pk} \times L1}{0.1 \times V_{out} \times (V_{out} - V_{in})}$$

Where:  $I_{pk}$  = peak switch current of the TPS61040 (400mA),  
 $L1$  = inductor value,  
 $V_{out}$  = output voltage, and  $V_{in}$  = input voltage.

Injecting a *voltage control* signal through R1 into the FB pin varies the output voltage of the supply. With the values shown in Figure 1, a 0 V control signal generates a 50 V output voltage and a 3.3 V signal generates a 40 V output voltage. More information about varying the output voltage of a TPS61040 controlled boost converter may be found in TI literature number SLVU065.

## References

1. *TPS61040 data sheet* (Texas Instruments literature number SLVS413)
2. *TPS61040EVM-001 Users Guide* (Texas Instruments literature number SLVU065)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

### Mailing Address:

Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265