

TPS25830, TPS25831-Q1, and TPS25840-Q1 Short-to-Battery Application



Pioneer Li

ABSTRACT

In the automotive USB application system, USB port short to battery is a common issue, which can damage the equipment. This application report focuses on how to solve the problem of USB port short to battery through circuit design with TPS25830/31/40.

Table of Contents

| | |
|--|----|
| 1 Introduction | 3 |
| 2 Short-to-Battery Conventional Application | 3 |
| 2.1 External FET VBUS/DP_IN/DM-IN Short-to-VBAT Application..... | 4 |
| 2.2 Without External FET VOUT/DP_IN/DM-IN Short-to-VBAT Application..... | 5 |
| 2.3 CC1/CC2 Short-to-VBAT Application..... | 7 |
| 3 Short-to-Battery Special Application | 9 |
| 3.1 External FET VBUS/DP_IN/DM-IN Short-to-VBAT Application..... | 10 |
| 3.2 Without External FET VOUT/DP_IN/DM-IN Short-to-VBAT Application..... | 12 |
| 4 Short-to-Battery Connect to TVS Application | 16 |
| 4.1 VBUS Short-to-VBAT Connect to TVS Application..... | 16 |
| 4.2 VOUT Short-to-VBAT Connect to TVS Application..... | 16 |
| 4.3 DP/DM Short-to-VBAT Connect to TVS Application..... | 17 |
| 4.4 CC1/CC2 Short-to-VBAT Connect to TVS Application..... | 17 |
| 5 Revision History | 18 |

List of Figures

| | |
|---|----|
| Figure 2-1. Cigarette Lighter Application..... | 3 |
| Figure 2-2. Short-to-Battery System Test Setup..... | 3 |
| Figure 2-3. Power On VBUS Short-to-VBAT Test Setup..... | 4 |
| Figure 2-4. Power on VBUS Short-to-VBAT Test..... | 4 |
| Figure 2-5. Power On DP_IN/DM_IN Short-to-VBAT Test Setup..... | 5 |
| Figure 2-6. Power On DP_IN Short-to-VBAT Test..... | 5 |
| Figure 2-7. Power On VOUT Short-to-VBAT Test Setup..... | 6 |
| Figure 2-8. Power On VOUT Short-to-VBAT Test..... | 6 |
| Figure 2-9. Power On DP_IN/DM_IN Short-to-VBAT Test Setup..... | 6 |
| Figure 2-10. Power On DM_IN Short-to-VBAT Test..... | 7 |
| Figure 2-11. Power On CC1/CC2 Short-to-VBAT Test Setup..... | 7 |
| Figure 2-12. Power On CC1 Short-to-VBAT Test..... | 8 |
| Figure 2-13. Power On CC2 Short-to-VBAT Test..... | 8 |
| Figure 3-1. VBUS/DP_IN/DM_IN Short-to-VBAT Test Setup..... | 9 |
| Figure 3-2. VBUS/DP_IN/DM_IN Short-to-VBAT Test Setup..... | 9 |
| Figure 3-3. VBUS/DP_IN/DM_IN Short-to-VBAT Test Setup..... | 10 |
| Figure 3-4. Power Off VBUS Short-to-VBAT Test..... | 10 |
| Figure 3-5. VBUS Short to VBAT, then Power On Test..... | 10 |
| Figure 3-6. VBUS Short to VBAT and Power On, then Enable On Test..... | 11 |
| Figure 3-7. Power Off, DP_IN Short-to-VBAT Test..... | 11 |
| Figure 3-8. Power Off, DM_IN Short-VBAT Test..... | 11 |
| Figure 3-9. DP_IN Short to VBAT, then Power On Test..... | 12 |
| Figure 3-10. DM_IN Short to VBAT, then Power On Test..... | 12 |
| Figure 3-11. DM_IN Short to VBAT and Power On, then Enable On Test..... | 12 |

| | |
|---|----|
| Figure 3-12. DP_IN Short to VBAT and Power On, then Enable On Test..... | 12 |
| Figure 3-13. VOUT/DP_IN/DM_IN Short-to-VBAT Test Setup..... | 13 |
| Figure 3-14. VOUT/DP_IN/DM_IN Short-to-VBAT Test Setup..... | 13 |
| Figure 3-15. VOUT/DP_IN/DM_IN Short-to-VBAT Test Setup..... | 13 |
| Figure 3-16. Power Off, DP_IN Short-to-VBAT Test..... | 14 |
| Figure 3-17. Power Off, DM_IN Short-to-VBAT Test..... | 14 |
| Figure 3-18. DP_IN Short to VBAT, then Power On Test..... | 14 |
| Figure 3-19. DM_IN Short to VBAT, then Power On Test..... | 14 |
| Figure 3-20. DM_IN Short to VBAT and Power On, then Enable On Test..... | 15 |
| Figure 3-21. DP_IN Short to VBAT and Power On, then Enable On Test..... | 15 |
| Figure 4-1. VBUS Short-to-VBAT Connect to TVS Setup..... | 16 |
| Figure 4-2. VOUT Short-to-VBAT Connect to TVS Setup..... | 16 |
| Figure 4-3. DP_IN/DM_IN Short-to-VBAT Connect to TVS Setup..... | 17 |
| Figure 4-4. CC1/CC2 Short-to-VBAT Connect to TVS Setup..... | 17 |

List of Tables

| | |
|---|----|
| Table 2-1. VBUS /DP_IN/DP_IN Short-to-VBAT Application Summary..... | 5 |
| Table 2-2. VOUT/DP_IN/DP_IN Short-to-VBAT Application Summary..... | 7 |
| Table 3-1. VBUS/DP_IN/DM-IN Short-to-VBAT Application Summary..... | 12 |
| Table 3-2. VOUT/DP_IN/DM-IN Short to VBAT Application Summary..... | 15 |

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

TPS2583x-Q1 is a highly-integrated USB Type-C and BC1.2 charging port controller that includes a synchronous DC/DC converter. It also supports DP_IN/DM_IN/CC1/CC2 short-to-battery protect. During the assembly, manufacturing, and maintenance of a car, there is a common problem where the USB port randomly shorts to the car battery, causing chip damage, or the USB lightning port accidentally hits the cigarette lighter during the daily application, which also causes chip damage. The TPS25830, TPS25831-Q1, and TPS25840-Q1 provide DP_IN/DM_IN/CC1/ CC2 short-to-battery protection, and supports 18-V maximum protection voltage, thus avoiding chip damage. All the following tests are based on the TPS25830Q1EVM-040. A power supply plus an external 30-mF electrolytic capacitor was used to simulate the car battery. The test input voltage was 14.5 V, R3 external. The recommended value for External FET is 10R/0603. The recommended value for External FET without External R3 is 100R/0805.

2 Short-to-Battery Conventional Application

After the car is started, the exposed USB lightning cable usually accidentally touches the positive pole of the cigarette lighter (see Figure 2-1). The equivalent test condition is $V_{IN} = 14.5\text{ V}$, $V_{OUT} = 5.1\text{ V}$, and $I_{OUT} = 0\text{ A}$. Turn on the power supply, then test VBUS/Vout/DP_IN/DM_IN/CC1/CC2 short to battery, respectively (battery VBAT) (see Figure 2-2).

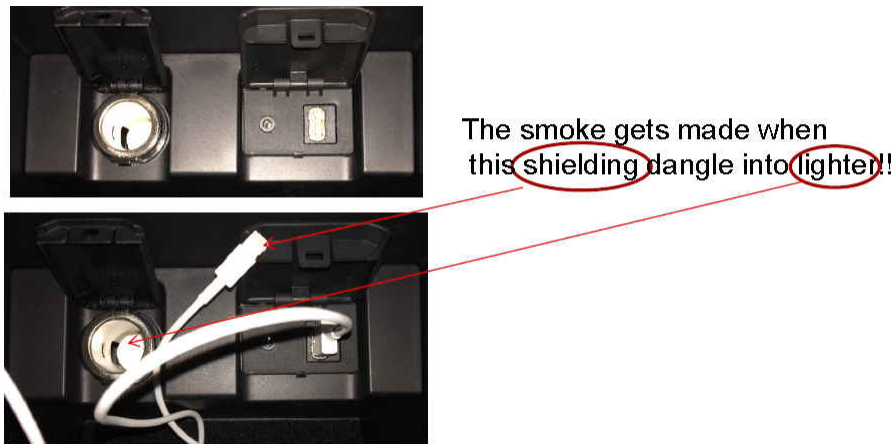


Figure 2-1. Cigarette Lighter Application

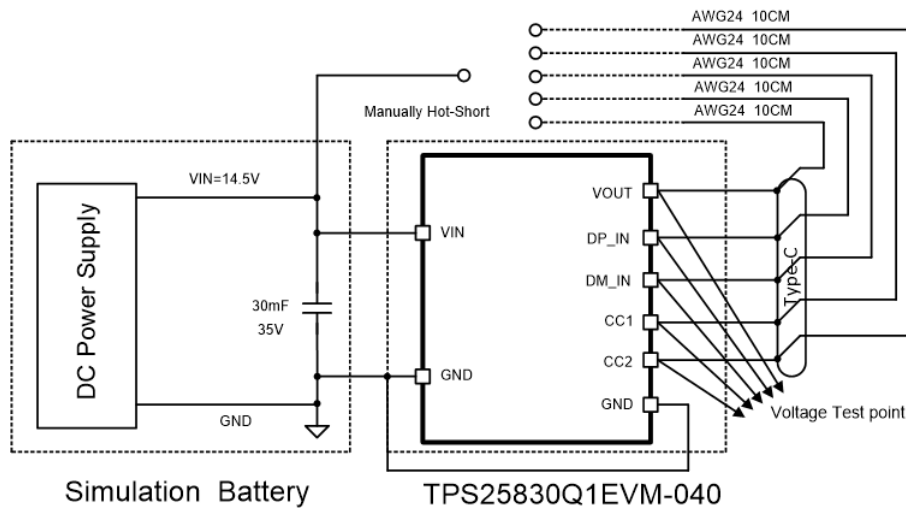


Figure 2-2. Short-to-Battery System Test Setup

2.1 External FET VBUS/DP_IN/DM-IN Short-to-VBAT Application

For short-to-battery protection, TI recommends connecting an N-channel back-to-back MOS FET between the CSN PIN and VBUS as seen in Figure 2-3.

2.1.1 VBUS Short-to-VBAT Application

When the output VBUS is short circuited to VBAT, the VBAT voltage charges the output capacitor C4, and at the same time charges C3 through R3. When the voltage of BUS pin exceeds 7 V, the external FET is closed, and the LS_GD is set from high to low. Figure 2-4 shows the test results.


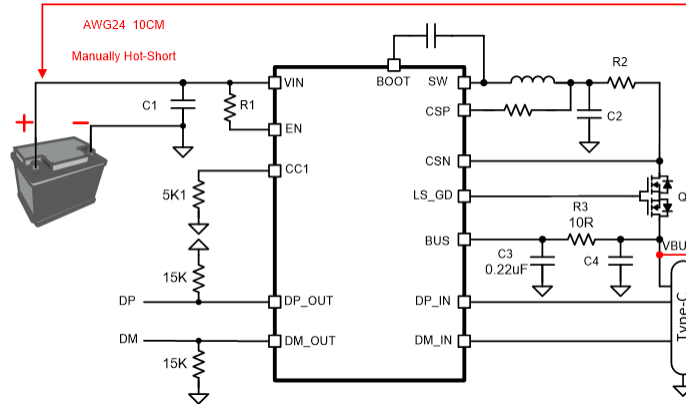


Figure 2-3. Power On VBUS Short-to-VBAT Test Setup

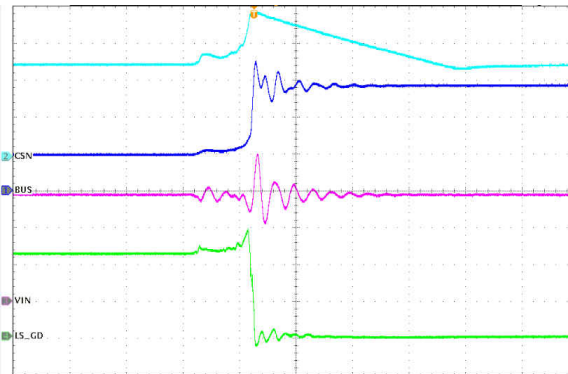

CH1 = 5 V/div, CH2 = 2 V/div, CH3 = 5 V/div, CH4 = 5 V/div, 20 μ S/div

Figure 2-4. Power on VBUS Short-to-VBAT Test

2.1.2 DP_IN/DM_IN Short-to-VBAT Application

DP_IN/DM_IN shorts to the VBAT protection function, which is realized by the internal protection circuit and external capacitance, C3 (see Figure 2-5). When DP_IN/DM_IN shorts to VBAT, some voltage spikes are clamped by an internal protection circuit, and the other part is absorbed by the external C3 through the internal diode Z1 or Z2. At the same time, output capacitance C4 and C2 are also charged to effectively absorb voltage spikes. Figure 2-6 shows the test results.


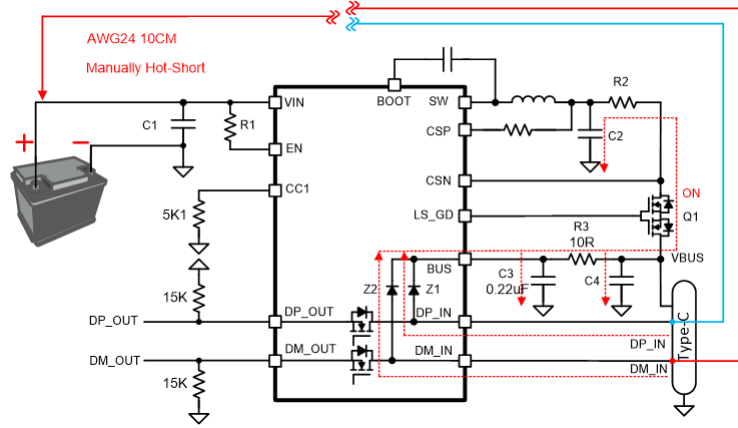


Figure 2-5. Power On DP_IN/DM_IN Short-to-VBAT Test Setup

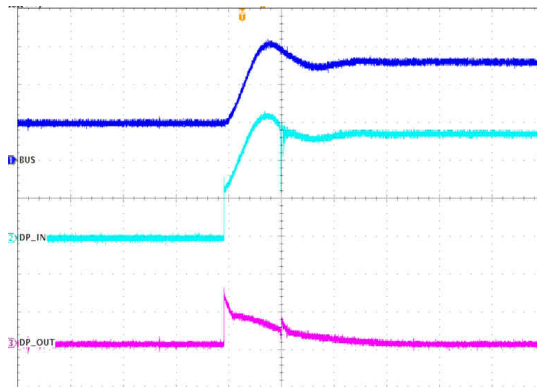

CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 1 μs/div

Figure 2-6. Power On DP_IN Short-to-VBAT Test

2.1.3 VBUS /DP_IN/DP_IN Short-to-VBAT Application Summary

Table 2-1. VBUS /DP_IN/DP_IN Short-to-VBAT Application Summary

| TEST ITEM | DP_IN SHORT-TO-VBAT | DM_IN SHORT-TO-VBAT | VBUS SHORT-TO-VBAT |
|--|---------------------|---------------------|--------------------|
| Fist the power on ,then VBUS/DP_IN/DM_IN short to VBAT | PASS | PASS | PASS |

2.2 Without External FET VOUT/DP_IN/DM-IN Short-to-VBAT Application

Sometimes, to save costs, customers omit external FET (see [Figure 2-7](#)). For special applications without external FET, refer to [Section 3](#).

2.2.1 VOUT/CSN Short-to-VBAT Application

When there is no back-to-back MOSFET, VOUT and CSN are directly connected. At this time, short VOUT to VBAT and VBAT charges the output capacitors C4 and C2. When the voltage of BUS pin exceeds 7 V, the fault is set from high to low. When the Vout/CSN pin voltage exceeds 7.5 V, the converter stops switching. [Figure 2-8](#) shows the test results.


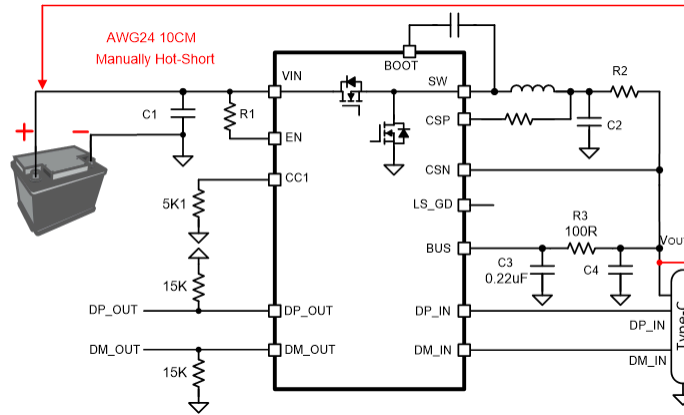


Figure 2-7. Power On VOUT Short-to-VBAT Test Setup

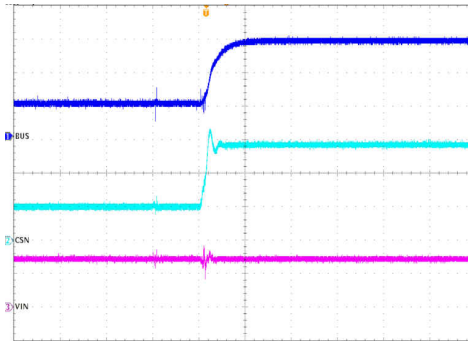

CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 10 V/div, 100 μ S/div

Figure 2-8. Power On VOUT Short-to-VBAT Test

2.2.2 DP_IN/DM_IN Short-to-VBAT Application

DP_IN/DM_IN shorts to VBAT without an external MOSFET (see [Figure 2-9](#)). Its working principle is described in [Section 2.1.2](#). [Figure 2-10](#) shows the results.


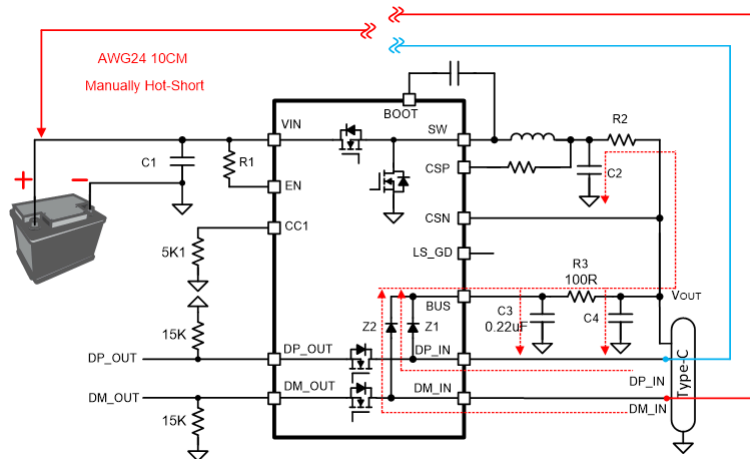


Figure 2-9. Power On DP_IN/DM_IN Short-to-VBAT Test Setup

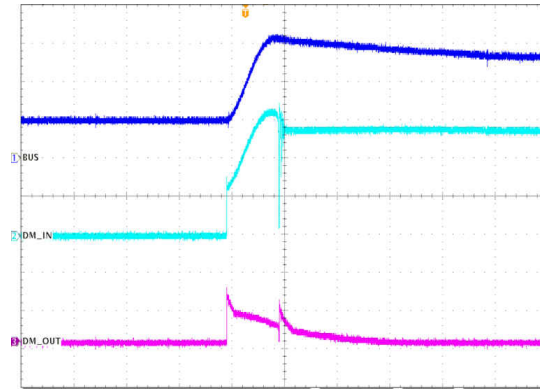

CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 1 μ S/div

Figure 2-10. Power On DM_IN Short-to-VBAT Test

2.2.3 VOUT/DP_IN/DP_IN Short-to-VBAT Application Summary

Table 2-2. VOUT/DP_IN/DP_IN Short-to-VBAT Application Summary

| ITEM | DP_IN SHORT-TO-VBAT | DM_IN SHORT-TO-VBAT | VOUT (CSN) SHORT-TO-VBAT |
|--|---------------------|---------------------|--------------------------|
| Fist the power on, then VOUT/DP_IN/DM_IN short to VBAT | PASS | PASS | PASS |

2.3 CC1/CC2 Short-to-VBAT Application

The result of CC1/CC2 shorting to VBAT has nothing to do with the external MOSFET Q1. Figure 2-11 shows the test setup. Figure 2-12 and Figure 2-13 show the test results.



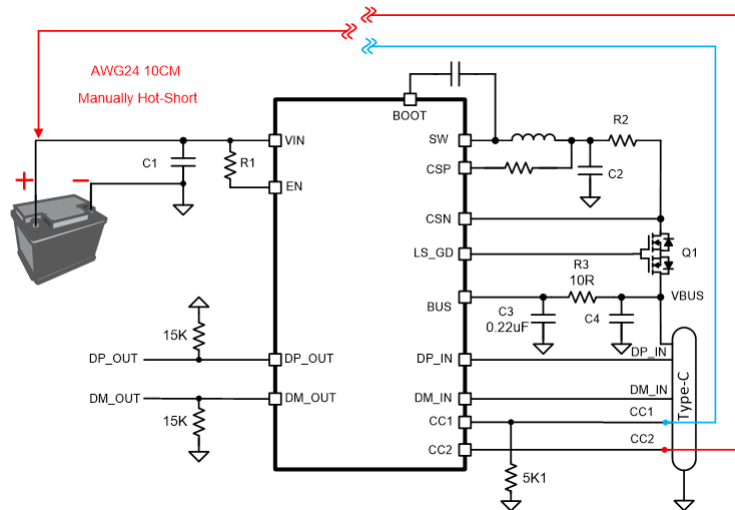


Figure 2-11. Power On CC1/CC2 Short-to-VBAT Test Setup

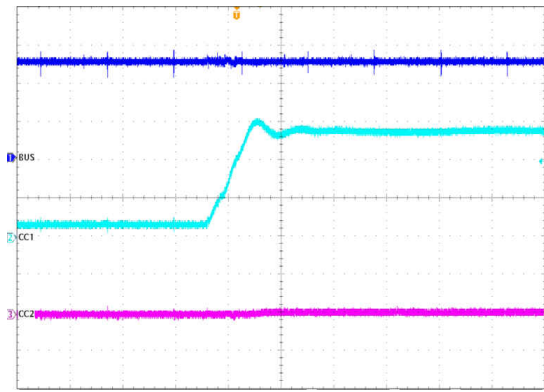

CH1 = 2 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 4 μ S/div, CC1 = Rd

Figure 2-12. Power On CC1 Short-to-VBAT Test

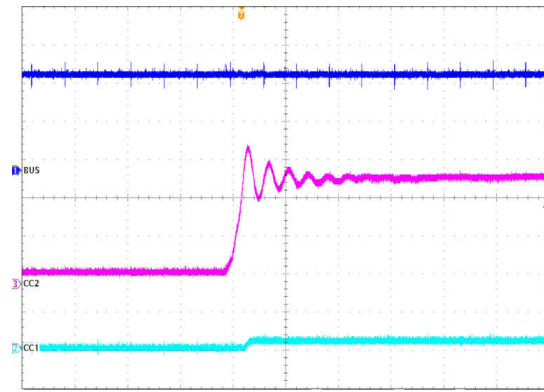

CH1 = 2 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 4 μ S/div, CC2 = Rd

Figure 2-13. Power On CC2 Short-to-VBAT Test

3 Short-to-Battery Special Application

In the customer applications, there are usually some special applications, which can be summarized as the following:

Application 1: Customers usually add a MOSFET Q2 protection circuit before the TPS25830, TPS25831-Q1, or TPS25840-Q1 system to realize overvoltage, undervoltage, and anti-reverse connection functions. When input voltage is overvoltage or undervoltage, Q2 is closed. When Q2 is closed, the USB lighting output port can accidentally touch the positive pole of the cigarette lighter. This is a possible situation that needs to be tested. Equivalent test conditions are power off, then VBUS/DP_IN/DM_IN short-to-battery VBAT (see Figure 3-1):

- VBAT = 14.5 V
- VIN = 0 V
- EN = VIN
- Vout = 0 V
- IOU = 0 A

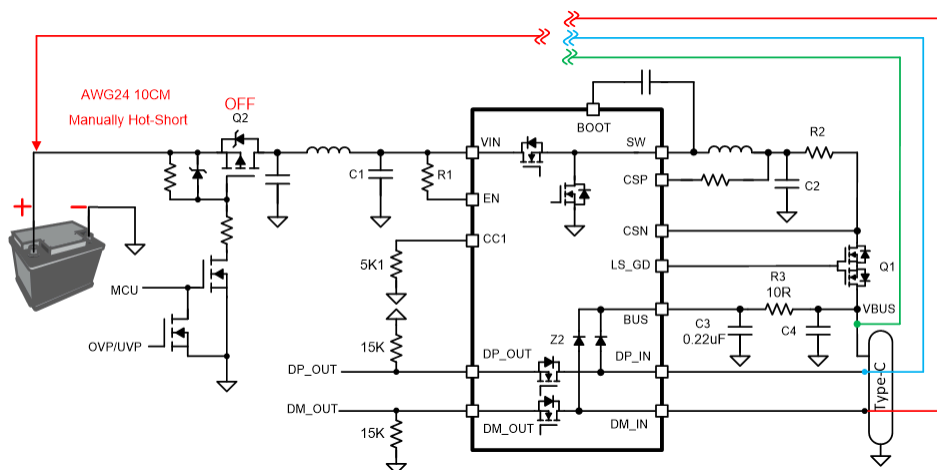


Figure 3-1. VBUS/DP_IN/DM_IN Short-to-VBAT Test Setup

Application 2: After the end user drives to the destination, they shut down the car engine and pull out the USB lightning port from their device. If the USB lightning port accidentally touches the positive pole of the cigarette lighter at this time, the next time the car starts, it has a short circuit between VBUS and VBAT. Equivalent test conditions are: VBUS/DP_IN/DM_IN shorts to the VBAT, then the power on TPS25830, TPS25831-Q1, or TPS25840-Q1 (Figure 3-2).

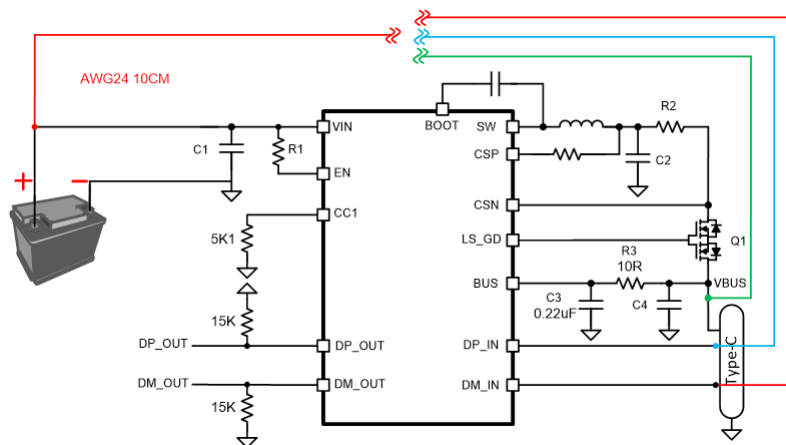


Figure 3-2. VBUS/DP_IN/DM_IN Short-to-VBAT Test Setup

Application 3 is similar to application 2. The only difference is that EN is controlled by an external MCU or other control signals due to customer timing requirements. Equivalent test conditions are to first, VBUS/DP_IN/DM_IN short to VBAT and power on, then EN enable. [Figure 3-3](#) shows the test setup.

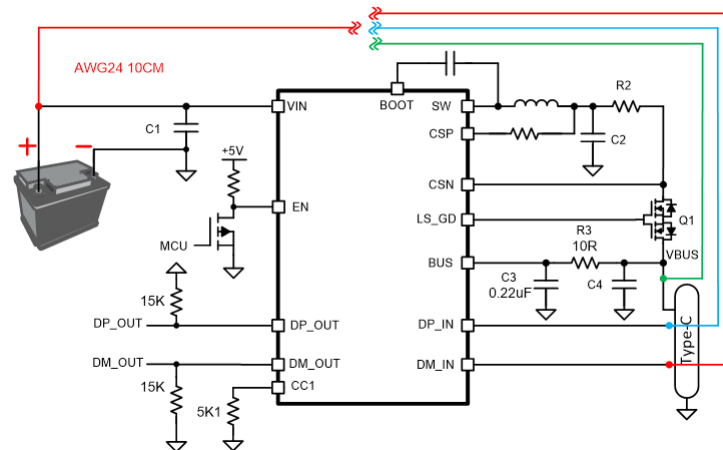


Figure 3-3. VBUS/DP_IN/DM_IN Short-to-VBAT Test Setup


3.1 External FET VBUS/DP_IN/DM-IN Short-to-VBAT Application

3.1.1 VBUS Short-to-VBAT Application

Application 1: [Figure 3-1](#) shows the test setup. The state at each point is power supply off (VBUS = 0 V, LS_GD is low, and Q1 is off). Short VBUS to VBAT. The voltage of VBUS rushes to the same height as VBAT. [Figure 3-4](#) shows the test results.


Application 2: [Figure 3-2](#) shows the test setup. VBUS shorts to VBAT. The input voltage and VBUS are rushed to the same height as VBAT together. [Figure 3-5](#) shows the test results.

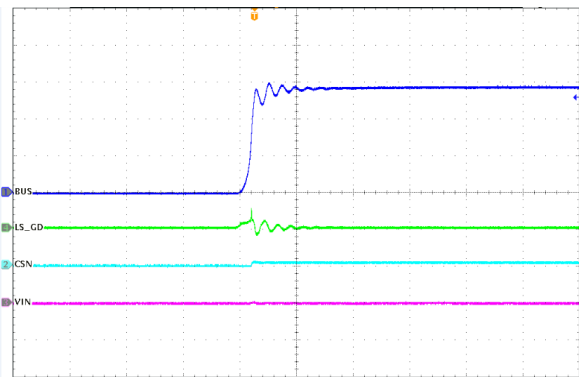Application 3: [Figure 3-3](#) shows the test setup. First, short VBUS to VBAT and power on the power supply, then enable EN. [Figure 3-6](#) shows the test results.




CH1 = 5 V/div, CH2 = 2 V/div, CH3 = 5 V/div, CH4 = 5 V/div,
20 μ S/div

Figure 3-4. Power Off VBUS Short-to-VBAT Test

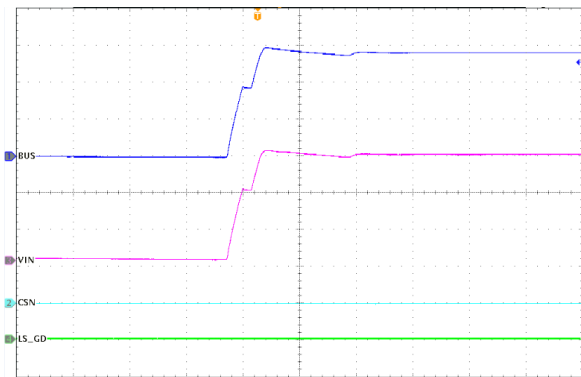

CH1 = 5 V/div, CH2 = 2 V/div, CH3 = 5 V/div, CH4 = 5 V/div, 10
mS/div

Figure 3-5. VBUS Short to VBAT, then Power On Test

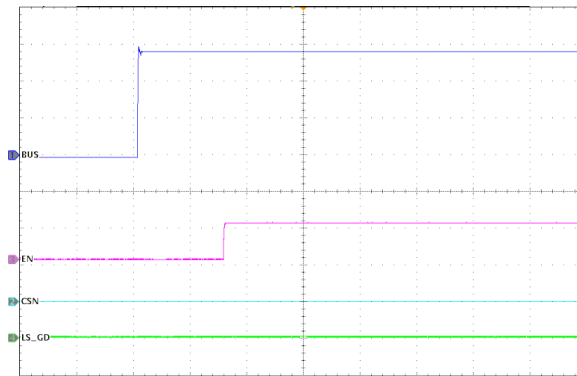

CH1 = 5 V/div, CH2 = 2 V/div, CH3 = 5 V/div, CH4 = 2 V/div, 400 ms/div


Figure 3-6. VBUS Short to VBAT and Power On, then Enable On Test

3.1.2 DP_IN/DM_IN Short-to-VBAT Application

Application 1: [Figure 3-1](#) shows the test setup. The state at each point is power supply off ($V_{out} = 0\text{ V}$, LS_GD is low, and Q1 is off). Short DP_IN/DM_IN to VBAT. The voltage of DP_IN/DM_IN rushes to the same height as VBAT. [Figure 3-7](#) and [Figure 3-8](#) show the test results.


Application 2: [Figure 3-2](#) shows the test setup. DP_IN/DM_IN shorts to VBAT. The input voltage and DP_IN/DM_IN voltage are rushed to the same height as VBAT together. [Figure 3-9](#) and [Figure 3-10](#) show the test results.

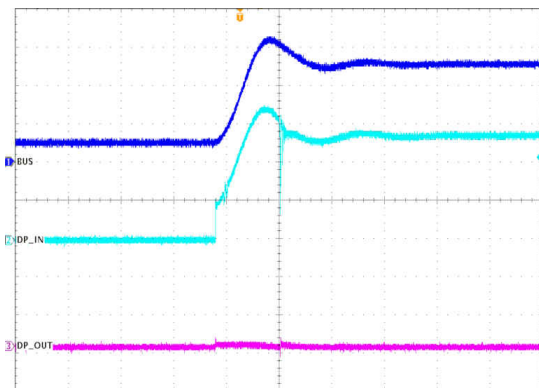Application 3: [Figure 3-3](#) shows the test setup. First, short DP_IN/DM_IN to VBAT and power on the power supply, then enable EN. [Figure 3-11](#) and [Figure 3-12](#) show the test results.




CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 2 μS /div

Figure 3-7. Power Off, DP_IN Short-to-VBAT Test

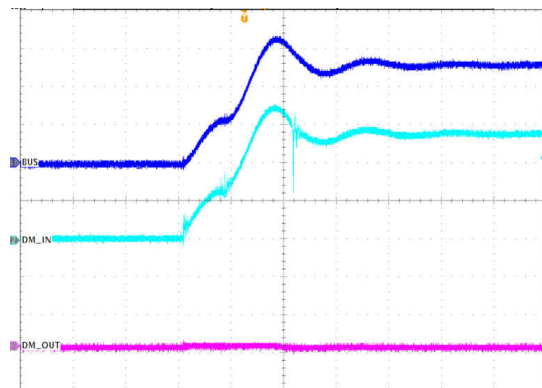


CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 2 μS /div

Figure 3-8. Power Off, DM_IN Short-VBAT Test

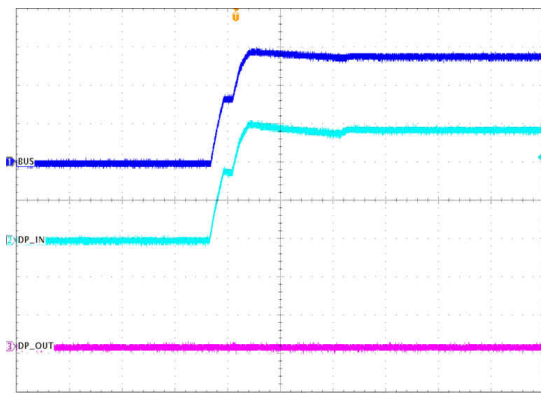

CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 10 mS/div

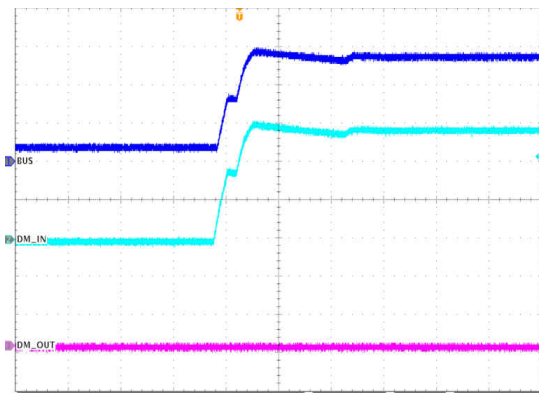Figure 3-9. DP_IN Short to VBAT, then Power On Test


CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 10 mS/div


Figure 3-10. DM_IN Short to VBAT, then Power On Test

 CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, CH3 = 5 V/div,
400 mS/div


Figure 3-11. DM_IN Short to VBAT and Power On, then Enable On Test

 CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, CH3 = 5 V/div,
400 mS/div

Figure 3-12. DP_IN Short to VBAT and Power On, then Enable On Test

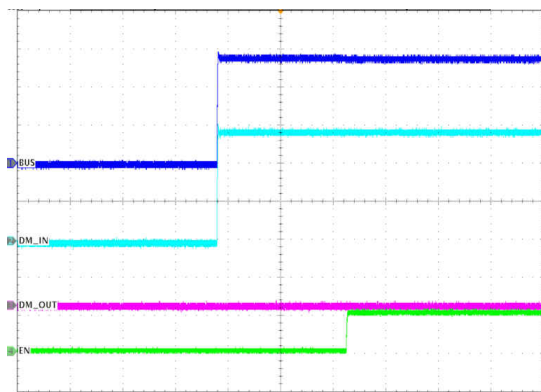3.1.3 VBUS/DP_IN/DM-IN Short-toVBAT Application Summary

Table 3-1. VBUS/DP_IN/DM-IN Short-to-VBAT Application Summary
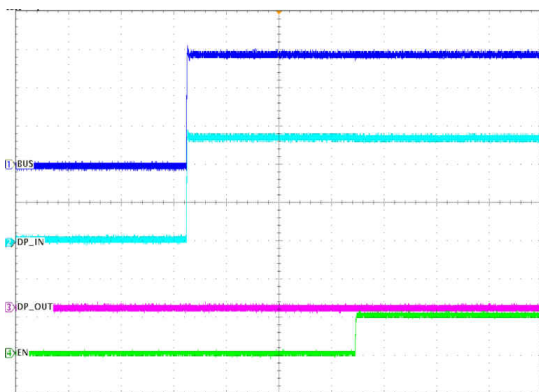
| ITEM | DP_IN SHORT-TO-VBAT | DM_IN SHORT-TO-VBAT | VBUS SHORT-TO-VBAT |
|--|---------------------|---------------------|--------------------|
| Fist the power off, then VBUS/DP_IN/DM_IN Short to VBAT | PASS | PASS | PASS |
| Fist the VBUS/DP_IN/DM_IN Short to VBAT, then Power on | PASS | PASS | PASS |
| Fist the VBUS/DP_IN/DM_IN Short to VBAT and Power on, then EN on | PASS | PASS | PASS |

3.2 Without External FET VOUT/DP_IN/DM-IN Short-to-VBAT Application

This application is the same as the application in [Section 3.1](#), this case also can be summarized as the following:

Application 1: [Figure 3-13](#) shows the test setup. First, power off the power supply, then short VOUT/DP_IN/DM_IN to VBAT. The state at each point is the following:

- VBAT = 14.5 V
- VIN = 0 V
- EN = VIN
- VOUT = 0 V
- IOUT = 0 A

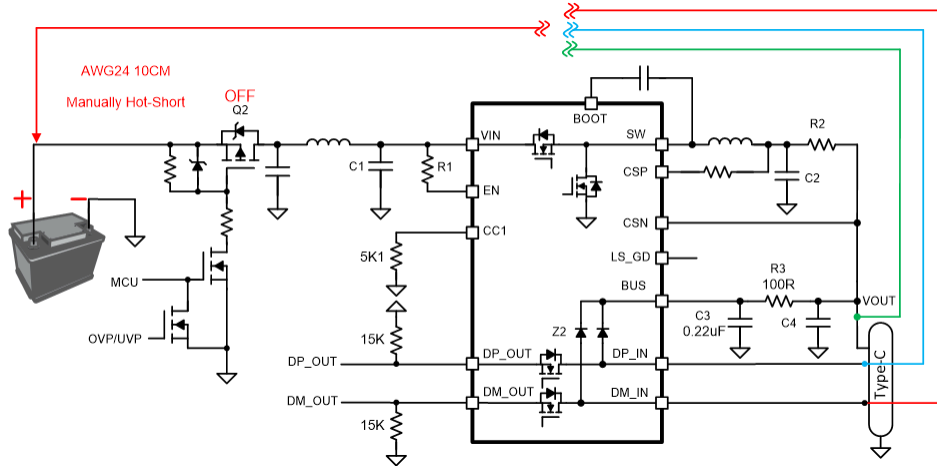


Figure 3-13. VOUT/DP_IN/DM_IN Short-to-VBAT Test Setup

Application 2: Figure 3-14 shows the test setup. First, short VOUT/DP_IN/DM_IN to VBAT, then power on the power supply.

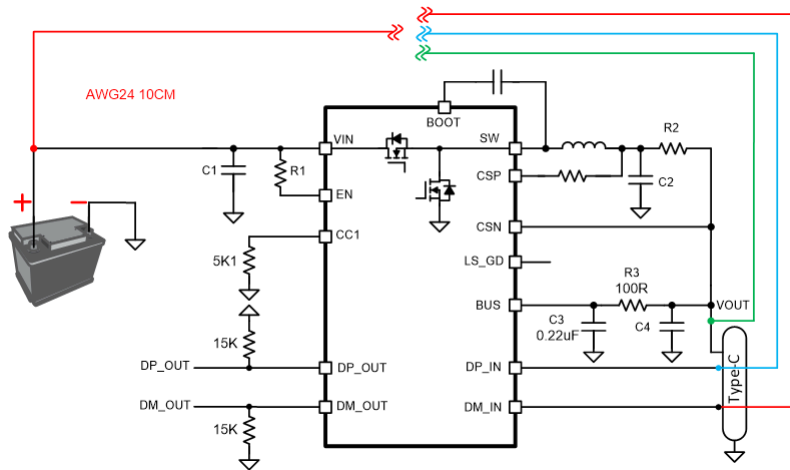


Figure 3-14. VOUT/DP_IN/DM_IN Short-to-VBAT Test Setup

Application 3: Figure 3-15 shows the test setup. Short VOUT/DP_IN/DM_IN to VBAT and power on the power supply, then enable EN.

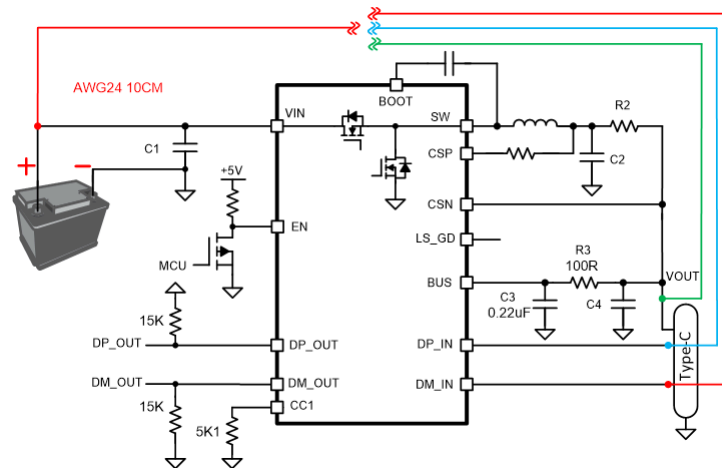


Figure 3-15. VOUT/DP_IN/DM_IN Short-to-VBAT Test Setup

3.2.1 VOUT Short-to-VBAT Application

- Application 1: Power off the power supply, then short CSN to VBAT. TPS25830, TPS25831-Q1, and TPS25840-Q1 do not support short-to-battery protection in this case.
- Application 2: Short CSN to VBAT, then power on the power supply. TPS25830, TPS25831-Q1, and TPS25840-Q1 do not support short-to-battery protection in this case.
- Application 3: Short CSN to VBAT and power on the power supply, then enable EN. TPS25830, TPS25831-Q1, and TPS25840-Q1 do not support short-to-battery protection in this case.

3.2.2 DP_IN/DM_IN Short-to-VBAT Application

- Application 1: Power off the power supply, then short DP_IN/DM_IN to VBAT. [Figure 3-16](#) and [Figure 3-17](#) show the test results.
- Application 2: Short DP_IN/DM_IN to VBAT, then power on the power supply. [Figure 3-18](#) and [Figure 3-19](#) show the test results.
- Application 3: Short DP_IN/DM_IN to VBAT, power on the power supply, then enable EN. [Figure 3-20](#) and [Figure 3-21](#) show the test results.

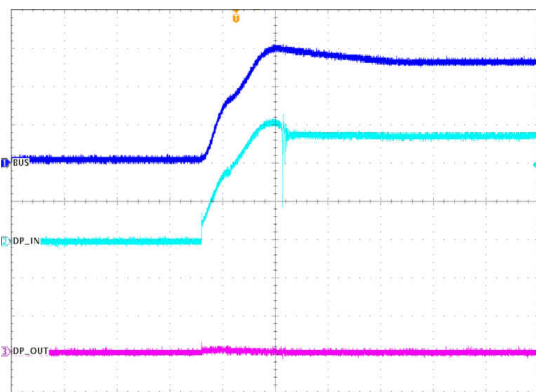

 CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 2 μ S/div




Figure 3-16. Power Off, DP_IN Short-to-VBAT Test

 CH1 = 5V/div, CH2 = 5 V/div, CH3 = 5 V/div, 2 μ S/div


Figure 3-17. Power Off, DM_IN Short-to-VBAT Test


CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 10 mS/div

Figure 3-18. DP_IN Short to VBAT, then Power On Test

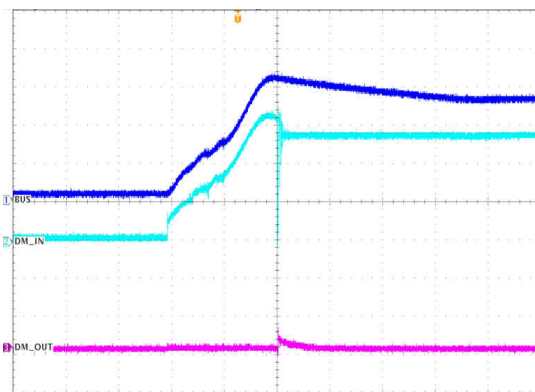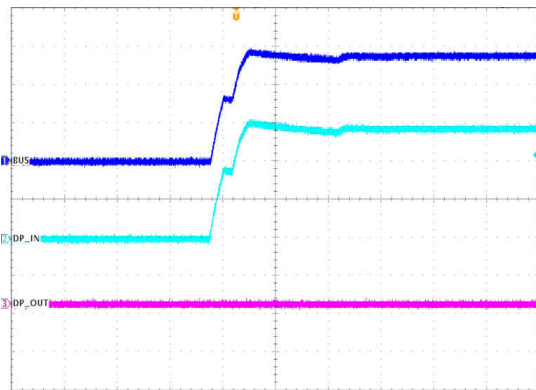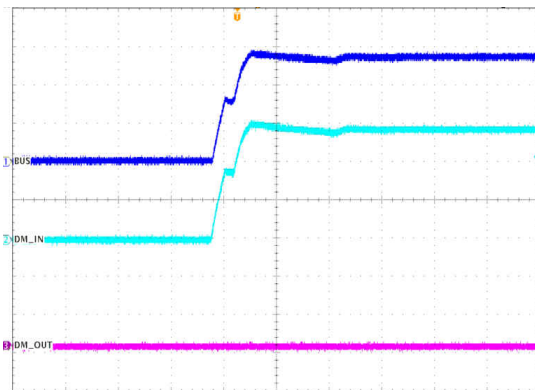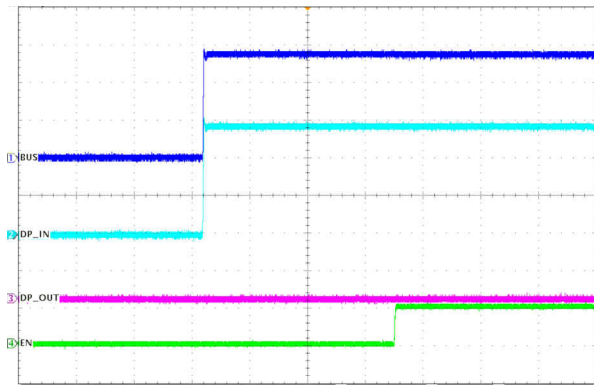
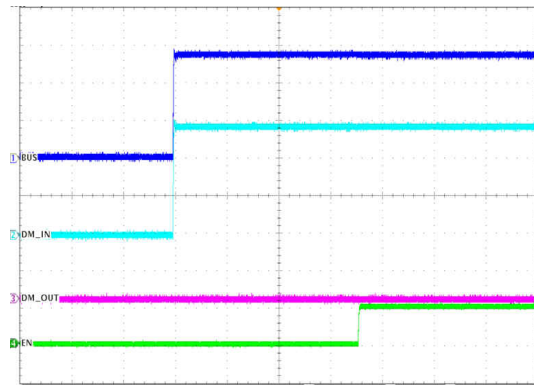
CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, 10 mS/div

Figure 3-19. DM_IN Short to VBAT, then Power On Test



CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, CH3 = 5 V/div, 400 mS/div

Figure 3-20. DM_IN Short to VBAT and Power On, then Enable On Test



CH1 = 5 V/div, CH2 = 5 V/div, CH3 = 5 V/div, CH3 = 5 V/div, 400 mS/div

Figure 3-21. DP_IN Short to VBAT and Power On, then Enable On Test

3.2.3 VOUT /DP_IN/DM-IN Short-to-VBAT Application Summary

Table 3-2. VOUT/DP_IN/DM-IN Short to VBAT Application Summary

| ITEM | DP_IN SHORT-TO-VBAT | DM_IN SHORT-TO-VBAT | VOUT SHORT-TO-VBAT |
|--|---------------------|---------------------|--------------------|
| Fist the power off, then VOUT/DP_IN/DM_IN Short to VBAT | PASS | PASS | Does not support |
| Fist the VOUT /DP_IN/DM_IN Short to VBAT, then Power on | PASS | PASS | Does not support |
| Fist the VOUT/DP_IN/DM_IN Short to VBAT and Power on, then EN on | PASS | PASS | Does not support |

4 Short-to-Battery Connect to TVS Application

During the actual process of shorting to VBAT, the parasitic inductance and capacitance of PCB generate resonance. The resonance voltage usually exceeds 18 V. The maximum voltage of the following on the TPS25830-Q1, TPS25831-Q1, and TPS25840-Q1 is 18 V:

- VBUS
- Vout
- DP_IN
- DM_IN
- CC1 and CC2 pins

If the voltage of those pins exceeds 18 V, you need to add a TVS diode. The TVS diode TI used in the demo is SMAJ18A with the TVS PCB Layout as close as possible to the IC PIN.

4.1 VBUS Short-to-VBAT Connect to TVS Application

If the voltage exceeds 18 V when VBUS shorts to VBAT, TI recommends connecting a 18-V TVS diode between VBUS and GND, as shown with Z3 in Figure 4-1.

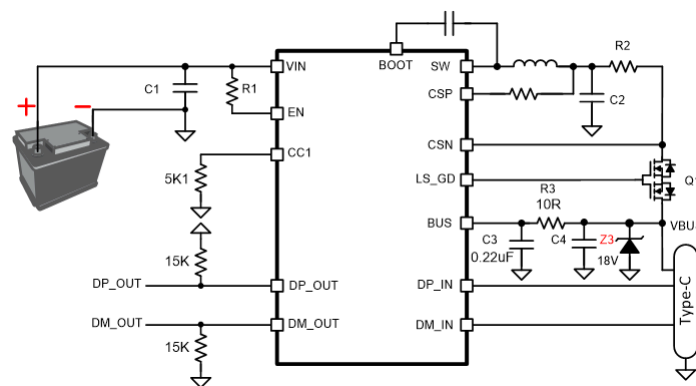


Figure 4-1. VBUS Short-to-VBAT Connect to TVS Setup

4.2 VOUT Short-to-VBAT Connect to TVS Application

If the voltage exceeds 18 V when Vout shorts to VBAT, TI recommends connecting a 18-V TVS diode between VBUS and GND, as shown with Z3 in Figure 4-2.

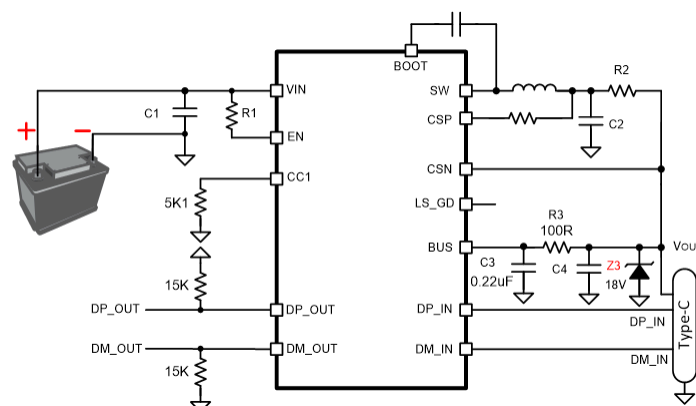


Figure 4-2. VOUT Short-to-VBAT Connect to TVS Setup

4.3 DP/DM Short-to-VBAT Connect to TVS Application

If the voltage exceeds 18 V when DP_IN/DM_IN shorts to VBAT, TI recommends connecting a 18-V TVS diode between VBUS and GND, as shown with Z3 in Figure 4-3.

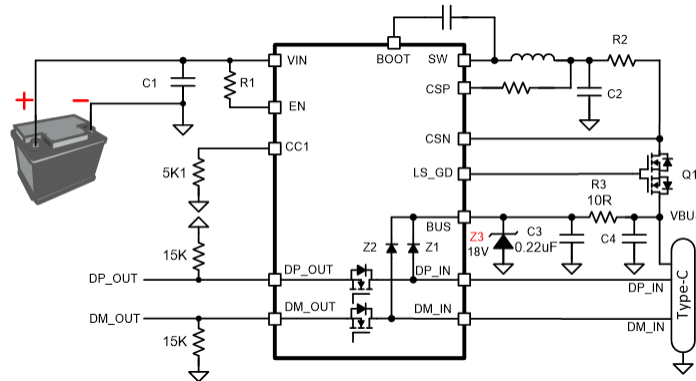


Figure 4-3. DP_IN/DM_IN Short-to-VBAT Connect to TVS Setup

4.4 CC1/CC2 Short-to-VBAT Connect to TVS Application

If the voltage exceeds 18 V when CC1/CC2 shorts to VBAT, TI recommends connecting a 18-V TVS diode between VBUS and GND, as shown with Z3 in Figure 4-4.

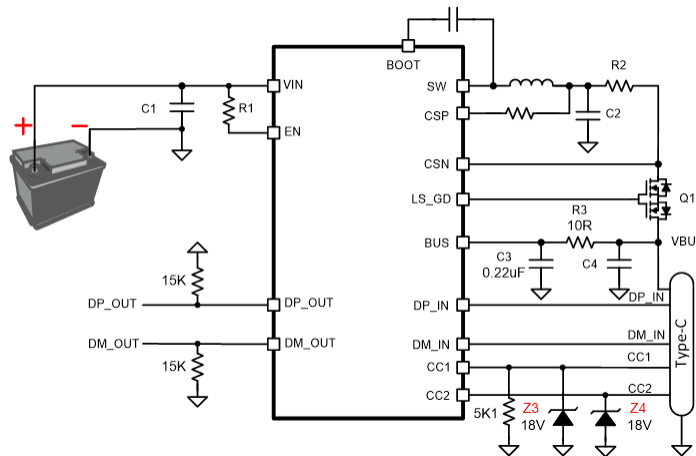


Figure 4-4. CC1/CC2 Short-to-VBAT Connect to TVS Setup

5 Revision History

| Changes from Revision * (September 2019) to Revision A (May 2023) | Page |
|---|-------------|
| • Updated the numbering format for tables, figures, and cross-references throughout the document..... | 1 |

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated