

Ammarah Aziz

Power Management ICs

This application brief details two optimized power-tree designs for the Horizon Robotics Journey 3 (J3) system-on-chip (SoC). Design A is a power-management IC (PMIC) and Design B is a discrete power design. Designs support operation from a car battery (40V absolute maximum) using the primary regulator LM63635-Q1 to step the voltage down to 5V. All components in the design are AEC-Q100-qualified.

Design A: PMIC reference design leverages TPS6593-Q1 (ASILD compliant), TPS628502-Q1, or TPS628503-Q1 synchronous buck converters and TPS745-Q1 low-dropout (LDO) regulators. The TPS6593-Q1 IC has five buck converters and four LDOs. This PMIC has a non-volatile memory (NVM) programmable, meaning the default register values are set in the TI production line to the desired values for this platform without further need for the customer to change settings. The full orderable part number for this one-time-programmable (OTP) spin is TPS6593C3C0RWERQ1.

Design B: Discrete power reference design with the TPS62812-Q1, TPS624421-Q1, TPS62873-Q1, and TPS62813-Q1 synchronous buck converters and LP5907-Q1 LDOs.

Power Design

Figure 1 shows the block diagram for design (A) using the TPS6593-Q1, TPS62850x-Q1, and TPS745-Q1.

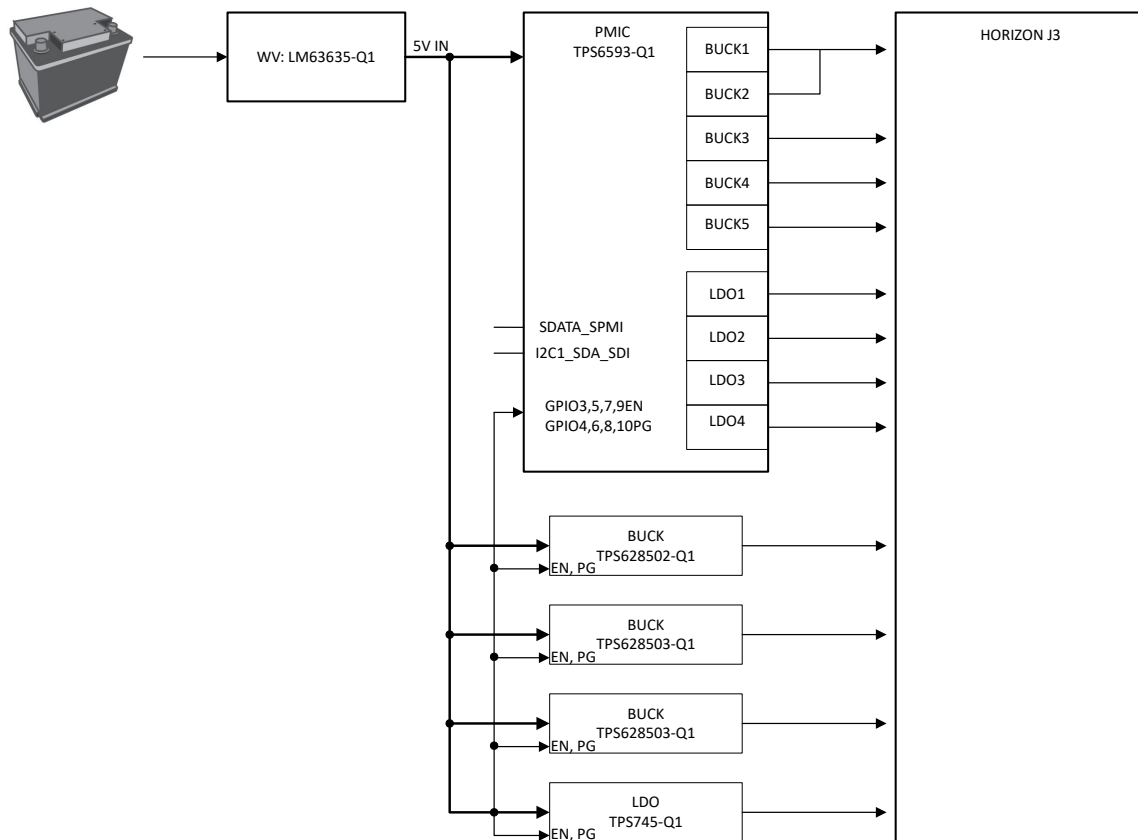


Figure 1. Design A: PMIC Design for J3

Figure 2 shows a block diagram design (B) using the TPS62812-Q1, TPS624421-Q1, TPS62873-Q1, TPS62813-Q1 and LP5907-Q1.

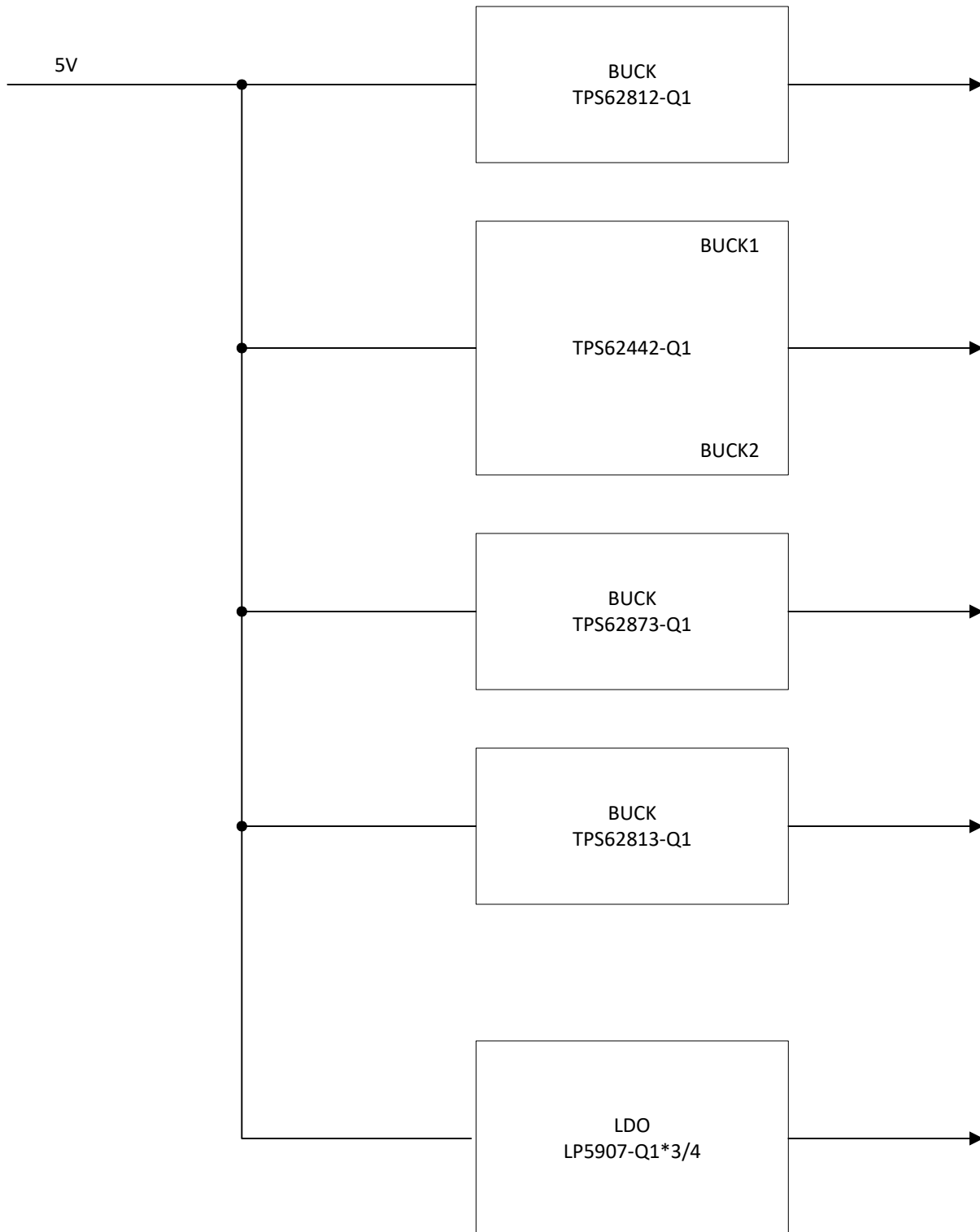


Figure 2. Design B: Discrete Design for J3

For a more detailed power design application note, contact China-reference-design-team@list.ti.com for further details.

References

1. Texas Instruments, [TPS6593-Q1 Automotive 2.8 V to 5.5 V 5 buck and 4 LDO Power Management IC \(PMIC\) product folder](#)
2. Texas Instruments, [LM63635-Q1 3.5-V to 32-V 3.25-A step-down voltage converter with spread spectrum product folder](#)
3. Texas Instruments, [TPS628502-Q1 2.7-V to 6-V, 2-A adjustable-frequency, step-down converter in SOT583 package product folder](#)
4. Texas Instruments, [TPS628503-Q1 2.7-V to 6-V, 3-A automotive step-down converter in SOT583 package product folder](#)
5. Texas Instruments, [TPS745-Q1 Automotive 500-mA, low- \$I_Q\$, high-PSRR, low-dropout \(LDO\) voltage regulator with power good product folder](#)
6. Texas Instruments, [TPS62812-Q1 Automotive 2.75-V to 6-V, 2-A step-down converter in a 2mm x 3mm wettable-flanks QFN package product folder](#)
7. Texas Instruments, [TPS62442-Q1 Automotive 2.75-V to 6-V, dual 2-A or 3-A and 1-A output, adjustable frequency, step-down converter product folder](#)
8. Texas Instruments, [TPS62873-Q1 Automotive 2.7-V to 6-V input, 15-A, stackable, synchronous buck converter product folder](#)
9. Texas Instruments, [TPS62813-Q1 Automotive 2.75-V to 6-V, 3-A step-down converter with fixed \$F_{SW}\$ and SYNC in 2x3mm wettable-flanks product folder](#)
10. Texas Instruments, [LP5907-Q1 Automotive, 250-mA, low-noise, high-PSRR, ultra-low-dropout voltage regulator with low \$I_Q\$ and enable product folder](#)

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated