

# Level Shift No More: Support Low Voltage I/O Signals into a FPGA, Processor, or ASIC



Amy Weatherby

## Background

Low voltage differential signaling (LVDS) interfaces are often internally integrated into data processing platforms such as field programmable gate arrays (FPGAs). The development of these platforms on smaller geometry CMOS processes has reduced voltage requirements for both the core supply and input/output (I/O) channels. These I/O requirements are defined by lower voltage standards designated by an LV (low voltage) prefix. Single-ended, 5V CMOS signals, for example, now come in lower voltage (LVCMOS) flavors, such as 3.3V, 2.5V, 1.8V, and 1.2V. Smaller geometry processes reach a limitation and cannot support the entire LVDS standard, requiring an external LVDS receiver solution. This application brief spotlights the [DS90LVRA2-Q1](#), an external LVDS receiver solution that supports I/O voltages as low as 1.8V.

## Point-to-Point LVDS Topology

LVDS is a differential physical (PHY) layer protocol that offers gigabits of data throughput using only milliwatts. A point-to-point LVDS application consists of an LVDS driver that sources a constant 3.5mA of drive current along a bus medium terminated by a 100-ohm resistor. The LVDS receiver determines a high or low data bit based on a positive or negative voltage swing across the bus termination of  $\pm 350\text{mV}$ . The LVDS driver translates LVCMOS or LVTTTL single-ended inputs into an LVDS output. The LVDS receiver translates LVDS inputs into single-ended LVCMOS or LVTTTL outputs.

 


Figure 1. Point-to-Point LVDS Topology

## Lower I/O Voltage Requirements

The development of smaller process technologies has reduced the core supply voltages for data capture platforms to 2.5V, 1.8V, and 1.2V. These platforms generally only send and receive signals that match the supply voltage. Most devices in the TI LVDS portfolio run at 3.3V and only accept and output 3.3V single-ended signals. This means that the I/O channels of these devices does not support the lower voltage signaling requirements these platforms require without the need for a level shifter. The TI application brief, [How to Support 1.8-V Signals Using a 3.3-V LVDS Driver/Receiver + Level-Shifter](#) details how this is achieved. The application note also provides practical tips and considerations for design implementation. The TI [Logic Guide](#) is another helpful resource to select the best level shifter for any application.

 



Figure 2. LVDS Receiver and Level Shifter to Support Low Voltage Signals

As an example, the [DS90LV028A](#) dual-channel 3.3V receiver supports up to two LVDS inputs and two single-ended 3.3V LVCMOS outputs. The outputs must be level shifted for a low power processing platform. One option is implementing a dual-channel level-shifter, such as the [SN74AVC2T45-Q1](#). Level shifters can limit receiver performance for metrics such as signaling rates and this must be considered in device selection.

## Level Shift No More with TI LVDS Receivers


Level shifters increase design complexity and can limit receiver performance. The use of two devices, driver or receiver and a level shifter, plus associated discrete components take up more PCB area and requires the use of a 3.3V supply in the design.

For a more integrated solution, Texas Instruments offers the [DS90LVRA2-Q1](#). This device is a dual-channel automotive grade LVDS receiver that operates at signaling rates up to 600Mbps. The DS90LVRA2-Q1 offers the flexibility to operate at 3.3V, 2.5V, and 1.8V to drive LVCMOS output signals to these voltage levels, thus eliminating the need for a separate level shifter device to meet lower voltage input signal specifications.

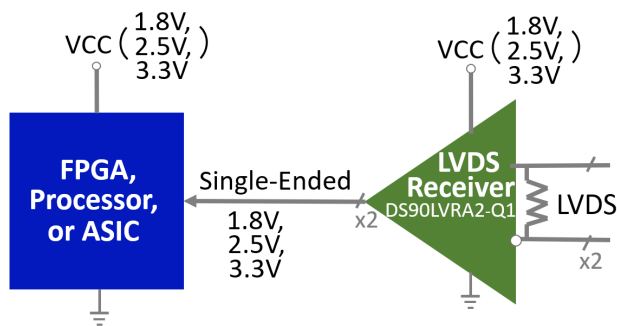


**Figure 3. DS90LVRA2-Q1 Dual-Channel LVDS Receiver to Support Low Voltage Output Signals**

The [DS90LVRA2](#) is the non-automotive grade version of the DS90LVRA2-Q1. This device operates only as a 1.8V LVDS receiver with a 1.8V LVCMOS output.

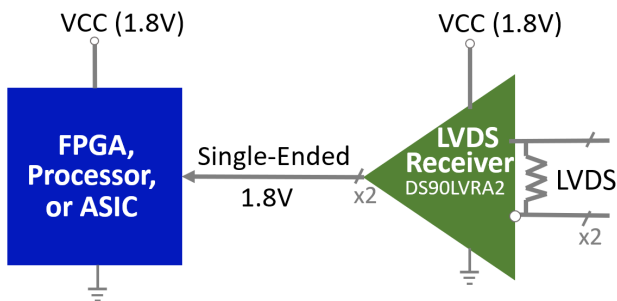

**Figure 4. DS90LVRA2 Dual-Channel LVDS Receiver to Support 1.8V Output Signals**

The [SN65LVDS4](#) is a non-automotive grade, single-channel LVDS receiver. It operates at signaling rates up to 500Mbps. The device drives 3.3V LVTTTL, 2.5V LVCMOS, 1.8V LVCMOS outputs based on the output drive voltage pin (VDD), eliminating the need for a separate level shifter device to meet lower voltage input signal specifications. However, the SN65LVDS4 requires two voltage supply pins (VCC and VDD), whereas the DS90LVRA2-Q1 and DS90LVRA2 offer the advantage of a single voltage supply pin.

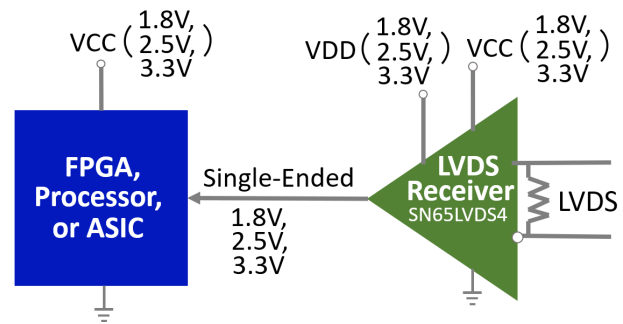

**Figure 5. SN65LVDS4 Single-Channel LVDS Receiver to Support Low Voltage Output Signals**


## Lower Voltage Solutions for TI LVDS Drivers

The TI LVDS portfolio does not currently offer a lower voltage LVDS driver. The automotive-grade [DS90LV027AQ-Q1](#) dual-channel 3.3V LVDS driver is the recommended pair for the DS90LVRA2-Q1. See the TI application brief, [How to Use a 3.3-V LVDS Buffer as a Low-Voltage LVDS Driver](#), for applications requiring lower voltage input signals. A LVDS driver does not require a level shifter when a simple biasing network is implemented.

## System Advantages of External LVDS Interfaces

### 1: Optimize FPGA Performance

FPGAs commonly have internally integrated programmable LVDS interfaces. Designing with an external LVDS receiver offloads the interface, meaning that FPGA power and performance are not sacrificed. This is highlighted in the TI application brief [Enabling LVDS Links for Low Power FPGAs, Processors, and ASIC Implementations](#).

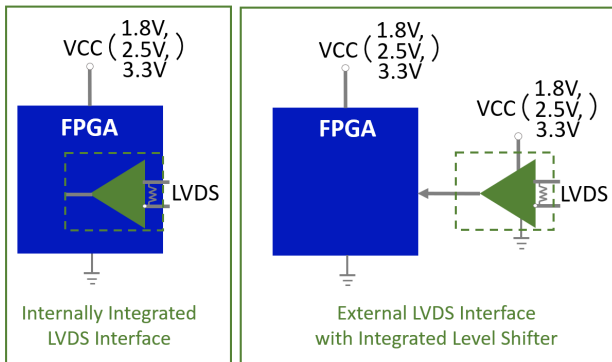

**Figure 6. Optimize FPGA Performance by Offloading the LVDS Interface**

### 2: Design Flexibility and Lower Cost FPGAs

Smaller geometry CMOS processes are a limiting factor in the feasibility of offering an internally integrated LVDS receiver and are unable to support entire common-mode voltage (VCM) range of the LVDS standard. The standard allows for a  $\pm 1$ -V common-mode ground shift, meaning that the VCM is as high as 2.2V. Additionally, system designs with the potential for large ground shifts further benefit from external LVDS interfaces that offer extended common-mode range voltages as high as 5V. FPGAs with integrated LVDS interfaces are typically more expensive. In some designs, an external LVDS interface offers system design flexibility and reduces complexity and cost.

### 3: Reduced Power Budget

Using lower power data capture platforms helps optimize power consumption, allowing for smaller systems that are cheaper, more reliable, and reduce thermal design complexity by reducing the need for fans or heat sinks. Application-specific integrated circuits (ASICs) are non-programmable logic devices with fixed logic sources, allowing for predictable power consumption, while modern FPGAs require three separate power supplies and the overall power consumption is design-dependent.

The TI application note, [Fast Forward Your FPGA Power Design with TI Designs](#), highlights the use of power-management integrated circuits (PMICs) as integrated power solutions. [This link](#) provides a comprehensive overview of power solutions using Texas Instruments processors. The site also includes power solutions compatible with other popular processors and FPGAs, such as [Altera](#) and [Xilinx](#).

### Conclusion

Smaller geometry CMOS processes have reduced core and I/O voltage requirements and limited the feasibility of internally integrated LVDS receiving solutions in data capture platforms. The DS90LVRA2-Q1 dual-channel LVDS receiver is an external solution with integrated features that eliminate the need for a separate level shifting device for platforms requiring inputs as low as 1.8V. This solution increases design flexibility while reducing component count and supports the lower voltage signal requirements of many smaller geometry CMOS processes. The DS90LVRA2 dual-channel 1.8-V receiver and the SN65LVDS4 single-channel receiver offer similar benefits.

### References

1. Texas Instruments, [How to Support 1.8-V Signals Using a 3.3-V LVDS Driver/Receiver and Level-Shifter](#), Application Brief
2. Texas Instruments, [How to Use a 3.3-V LVDS Buffer as a Low-Voltage LVDS Driver](#), Application Brief
3. Texas Instruments, [Enabling LVDS Links for Low Power FPGAs, Processors, and ASIC Implementations](#), Application Brief
4. Texas Instruments, [Fast Forward Your FPGA Power Design with TI Designs](#), Technical Article

### Trademarks

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated