

**Test Data  
For PMP10666  
08/011/2015**



## Table of Contents

1. Design Specifications .....	3
2. Circuit Description .....	3
3. PMP10666 Board Photos .....	4
4. Thermal Data .....	5
5. Test results .....	6
5.1 Efficiency Chart .....	6
5.2 Efficiency Data .....	7
6. Test results .....	8
6.1 Startup .....	8
6.2 Output Voltage Ripple and Switch Node Voltage .....	12
7. Frequency Response .....	14

## 1. Design Specifications

<b>Vin Minimum</b>	<b>4V- Full Load 3.3V Start up at 50% Load</b>
<b>Vin Maximum</b>	<b>5.5V</b>
<b>Vin Nominal</b>	<b>5V</b>
<b>Vout</b>	<b>120V</b>
<b>Iout</b>	<b>100mA</b>
<b>Switching Frequency(SMPS)</b>	<b>130 KHz</b>
<b>Isolation</b>	<b>2KVAC</b>


## 2. Circuit Description

PMP10666 is a 12W isolated flyback design that supports very low Vin of 3.3V-6V and is capable of delivering 100mA at 120V output. The design uses LM3481 Boost controller IC which works on current mode operation and can be synchronized to any frequency between 100KHz to 1 MHz.


This design was built on a 2 layer board and is a simple, low-BOM-count, and low-cost design providing an isolated output.

### 3. PMP10666 Board Photos

Board Dimensions: 2125 mil \*5150 mil

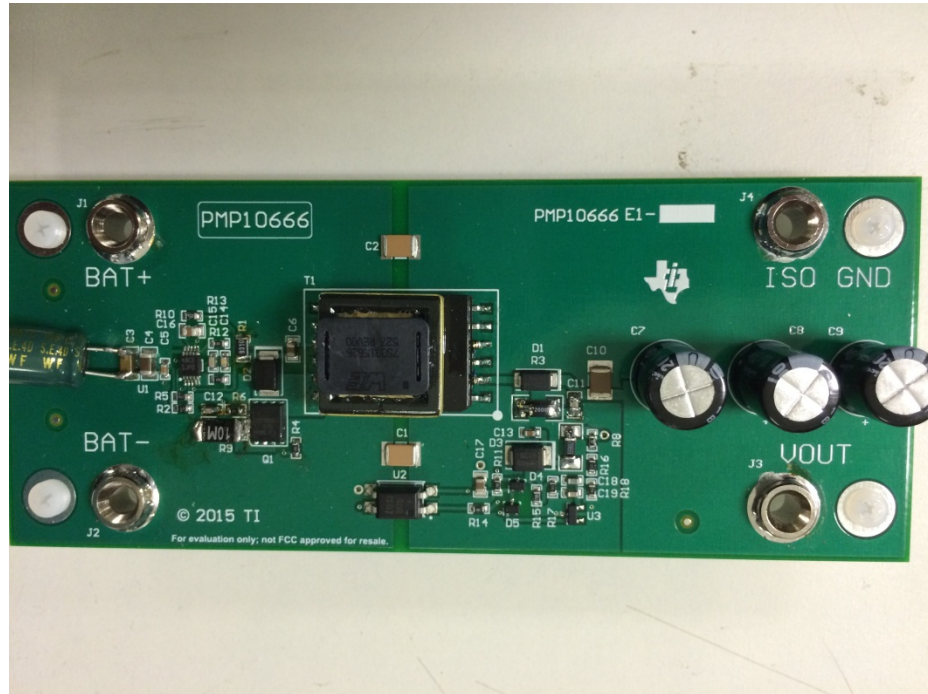


Board Photo (Top)

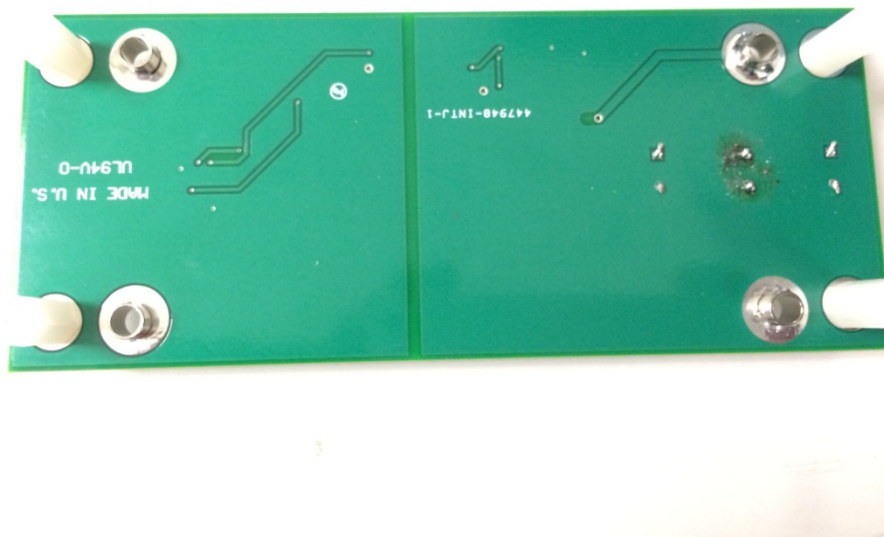

Board Photo (Bottom)


#### 4. Thermal Data

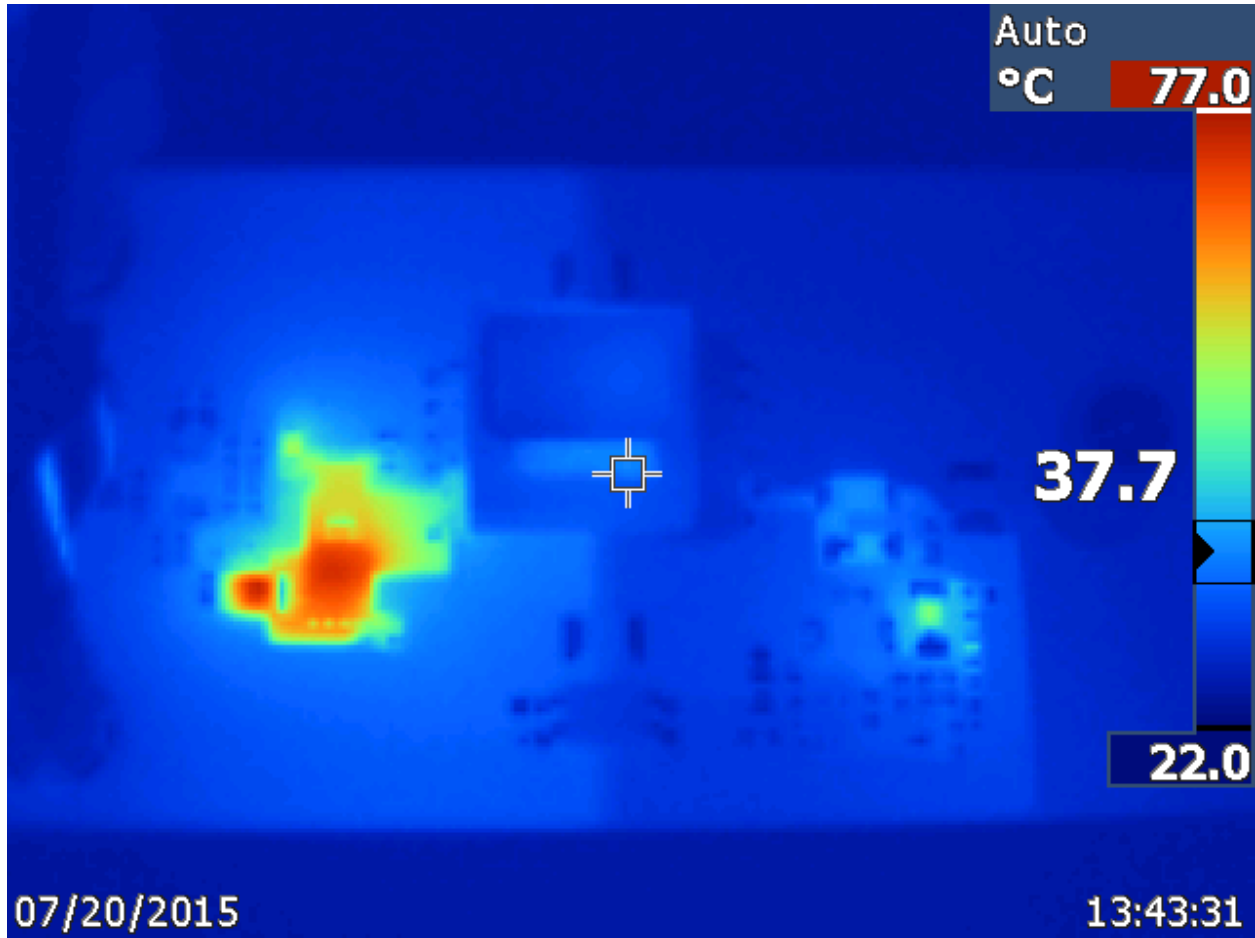

IR thermal image taken at steady state with 4 Vin and 120V@100mA output

## 5. Test results

### 5.1 Efficiency Chart

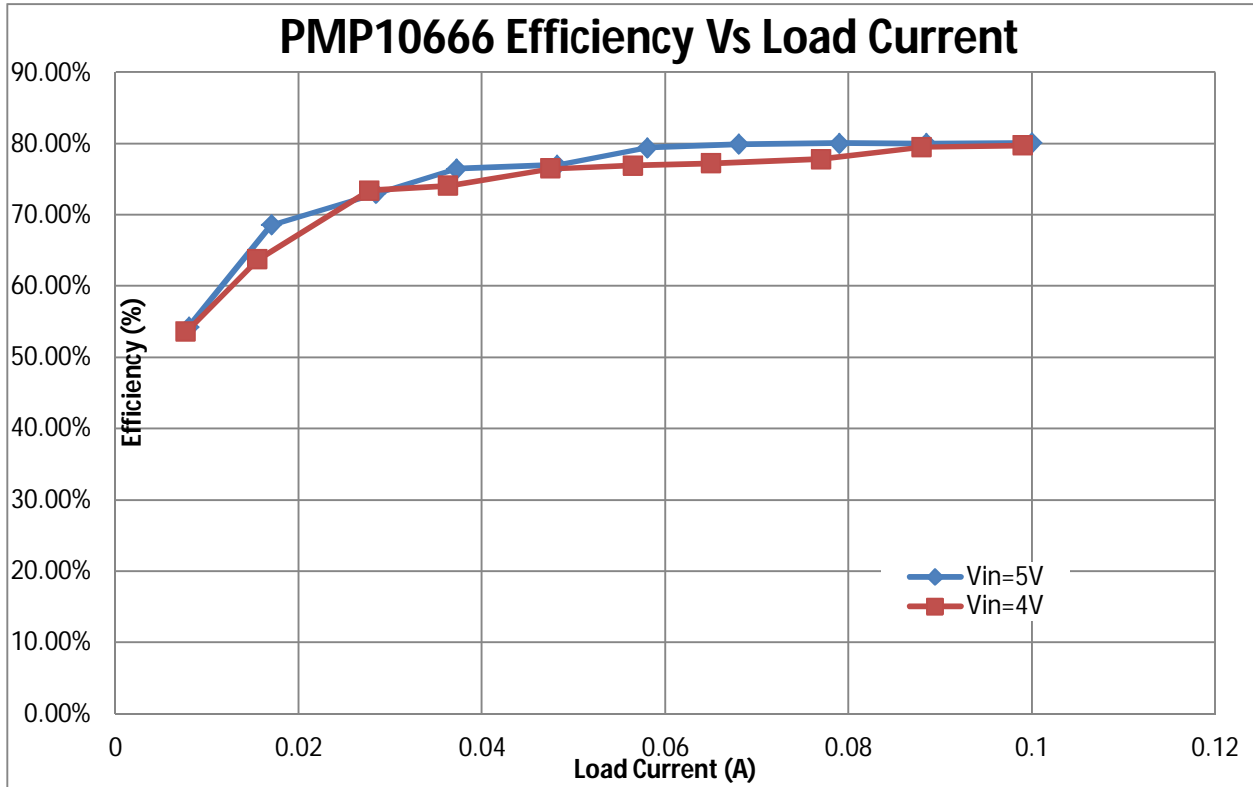


## 5.2 Efficiency Data

Vin (V)	Iin (A)	Vout (V)	Iout (A)	Pin (W)	Pout (W)	Efficiency (%)
5.21	0.332	117.3	0.008	1.72972	0.9384	54.25%
5.19	0.56	117.3	0.017	2.9064	1.9941	68.61%
5.17	0.883	117.3	0.0284	4.56511	3.33132	72.97%
5.15	1.108	117.3	0.0372	5.7062	4.36356	76.47%
5.12	1.434	117.3	0.0482	7.34208	5.65386	77.01%
5.1	1.68	117.3	0.058	8.568	6.8034	79.40%
5.08	1.965	117.3	0.068	9.9822	7.9764	79.91%
5.05	2.2919	117.3	0.079	11.5741	9.2667	80.06%
5.03	2.58	117.3	0.0885	12.9774	10.38105	79.99%
5	2.93	117.3	0.1	14.65	11.73	80.07%
Vin (V)	Iin (A)	Vout (V)	Iout (A)	Pin (W)	Pout (W)	Efficiency (%)
4.1	0.411	117.3	0.0077	1.6851	0.90321	53.60%
4.08	0.699	117.3	0.0155	2.85192	1.81815	63.75%
4.04	1.096	117.3	0.0277	4.42784	3.24921	73.38%
4.02	1.43	117.3	0.0363	5.7486	4.25799	74.07%
3.98	1.83	117.3	0.0475	7.2834	5.57175	76.50%
3.98	2.165	117.3	0.0565	8.6167	6.62745	76.91%
3.95	2.5	117.3	0.065	9.875	7.6245	77.21%
3.91	2.97	117.3	0.077	11.6127	9.0321	77.78%
4.02	3.23	117.3	0.088	12.9846	10.3224	79.50%
3.99	3.65	117.3	0.099	14.5635	11.6127	79.74%

## 6. Test results

### 6.1 Startup

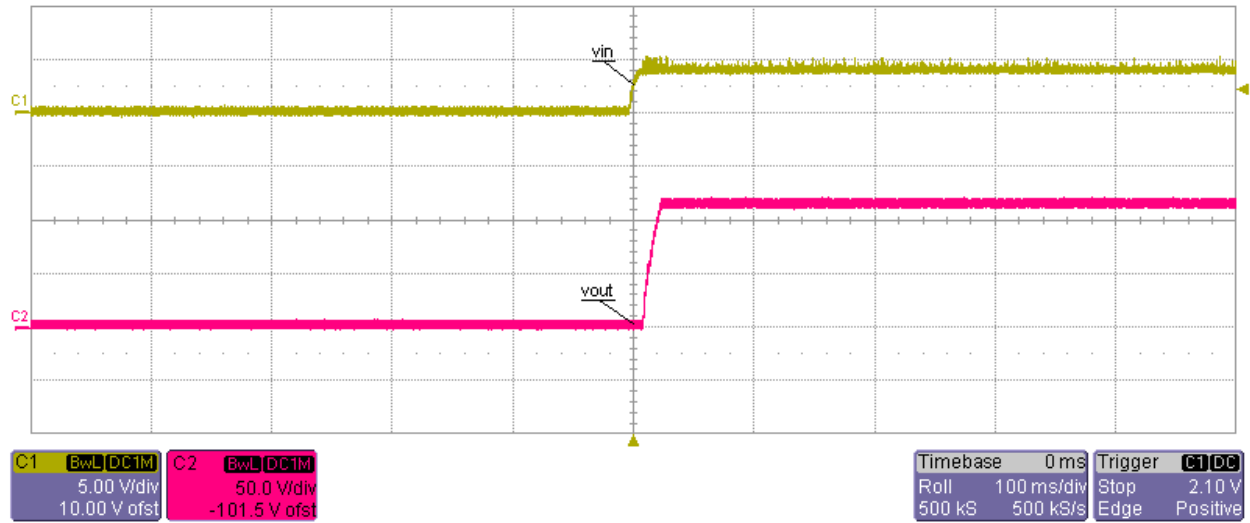


Startup into No Load at 4 Vin

C1- Vin

C2-Vout




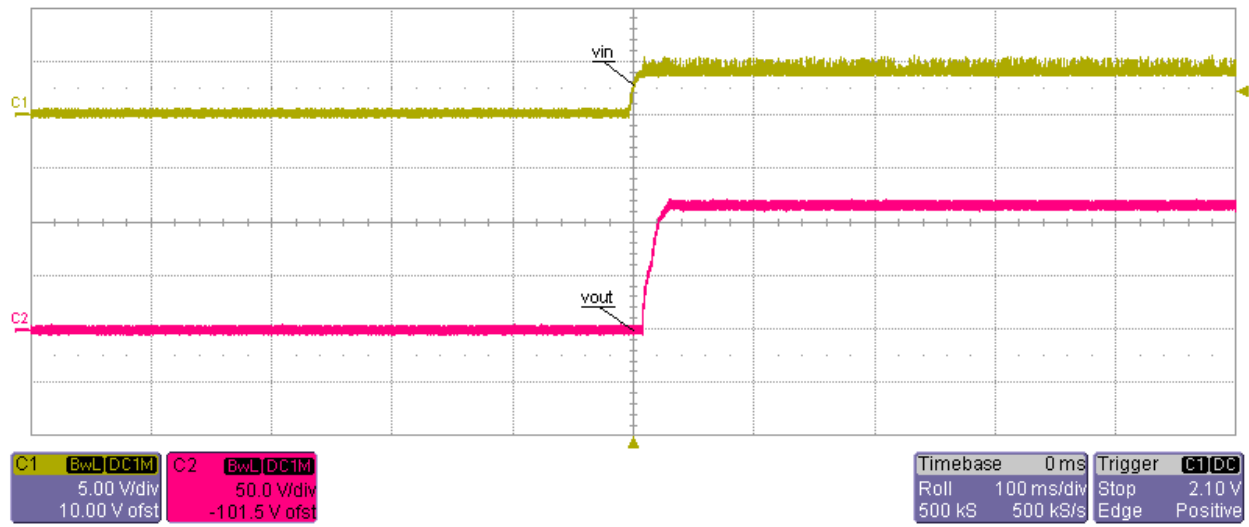

**Startup into Full Load(100mA) at 4 Vin**

**C1- Vin**


**C2-Vout**

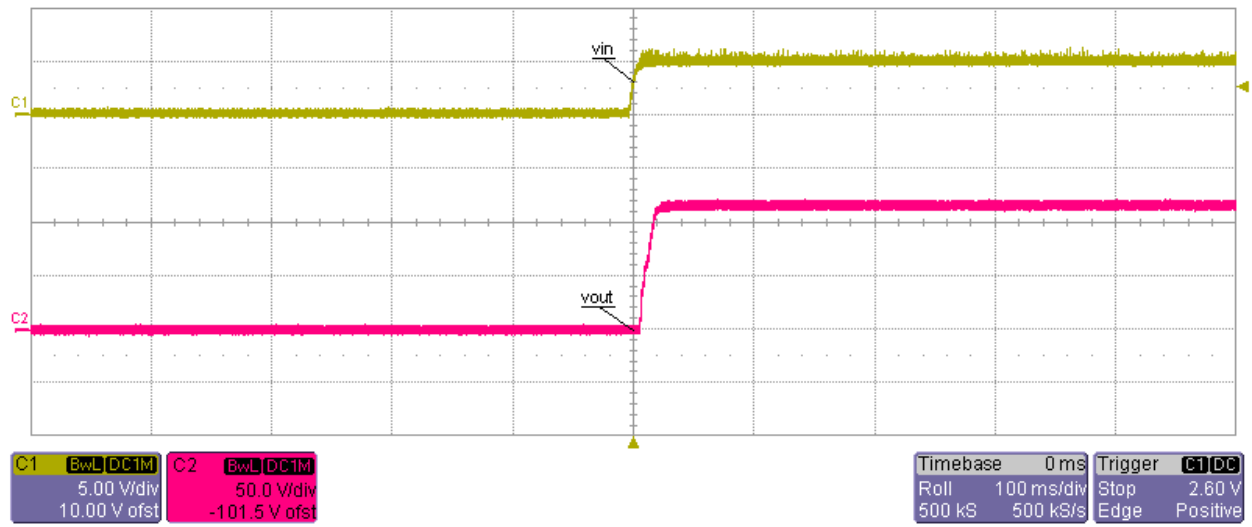

### Startup into No Load at 5 Vin

C1- Vin

C2-Vout

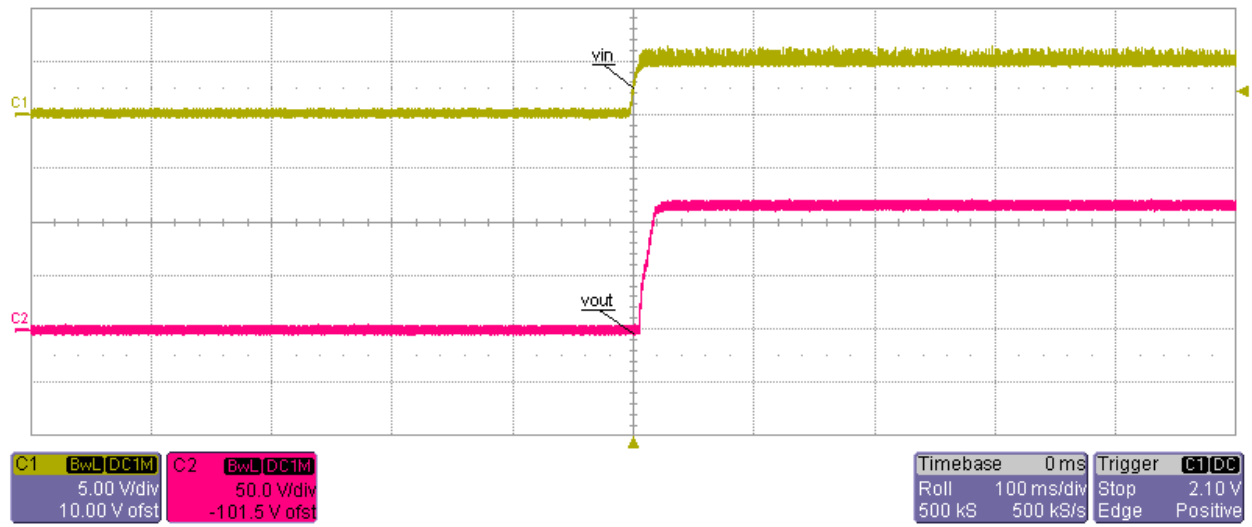


**Startup into Full Load(100mA) at 5 Vin**

**C1- Vin**


**C2-Vout**

## 6.2 Output Voltage Ripple and Switch Node Voltage

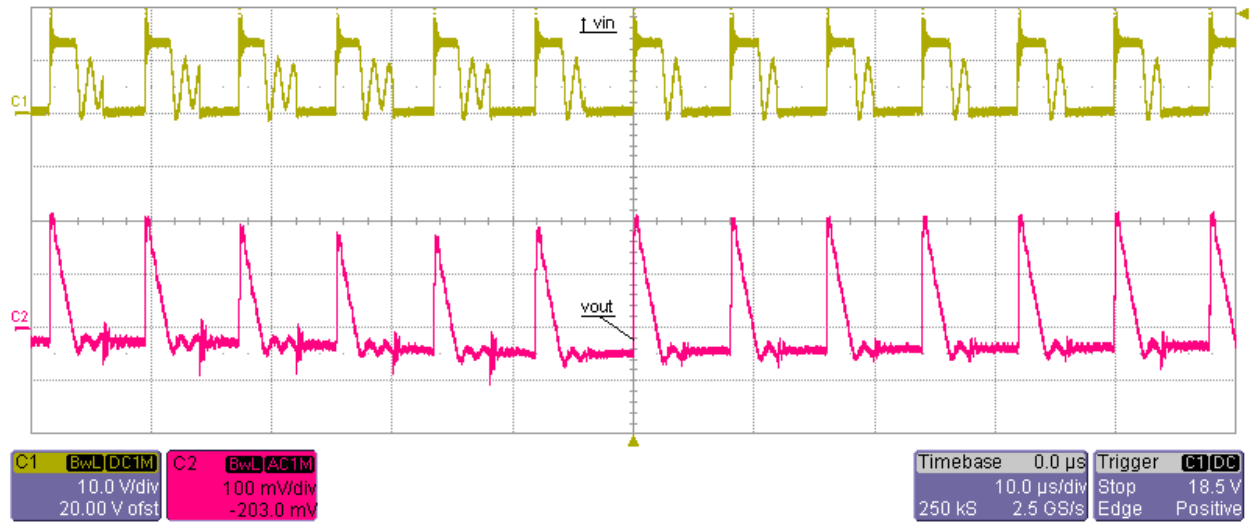

**Ch1 - Switch Node Voltage**

**Ch2-Output Voltage Ripple at 5Vin @ 100mA output**

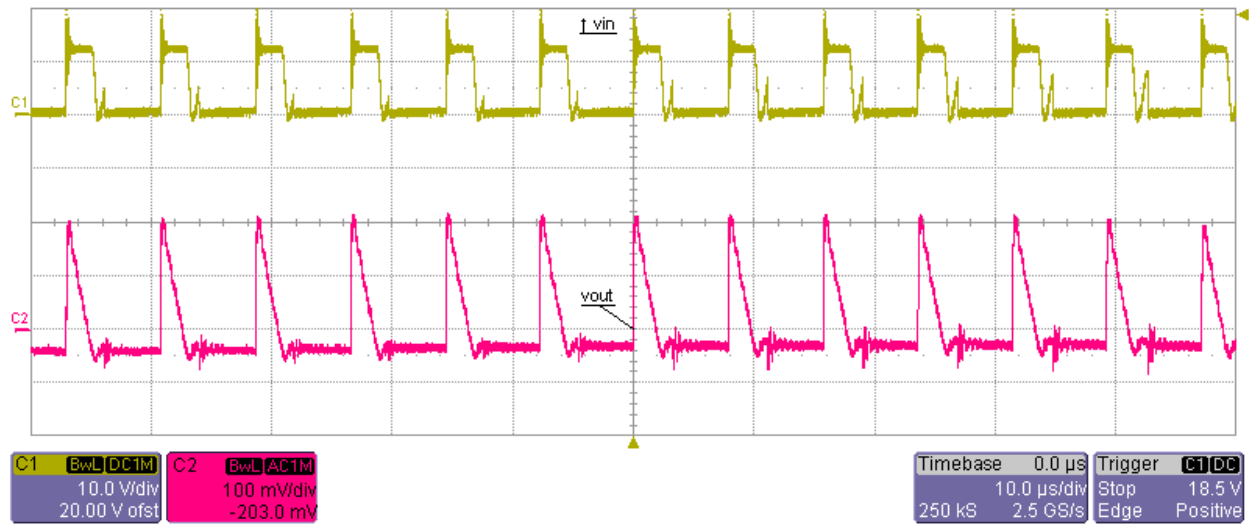


**Ch1 - Switch Node Voltage**


**Ch2-Output Voltage Ripple at 4Vin @ 100mA output**
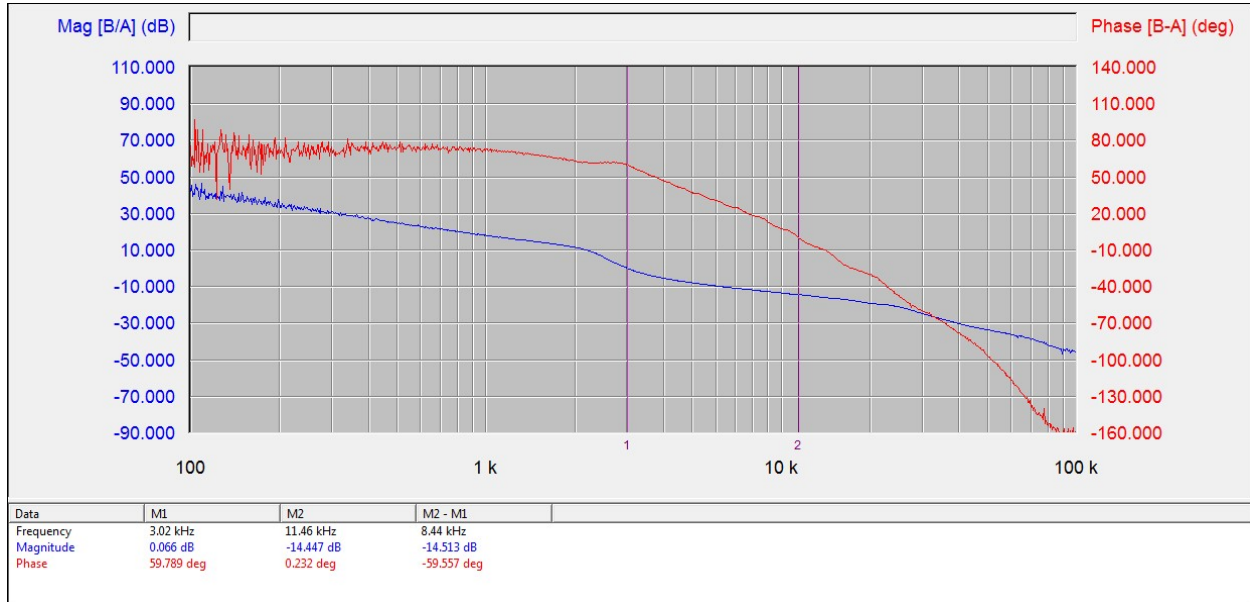
## 7. Frequency Response

The output was loaded with full load 100mA .For gain/phase plot 1 , the input was 3.7V and for gain/phase plot 2 , the input was 4.7V



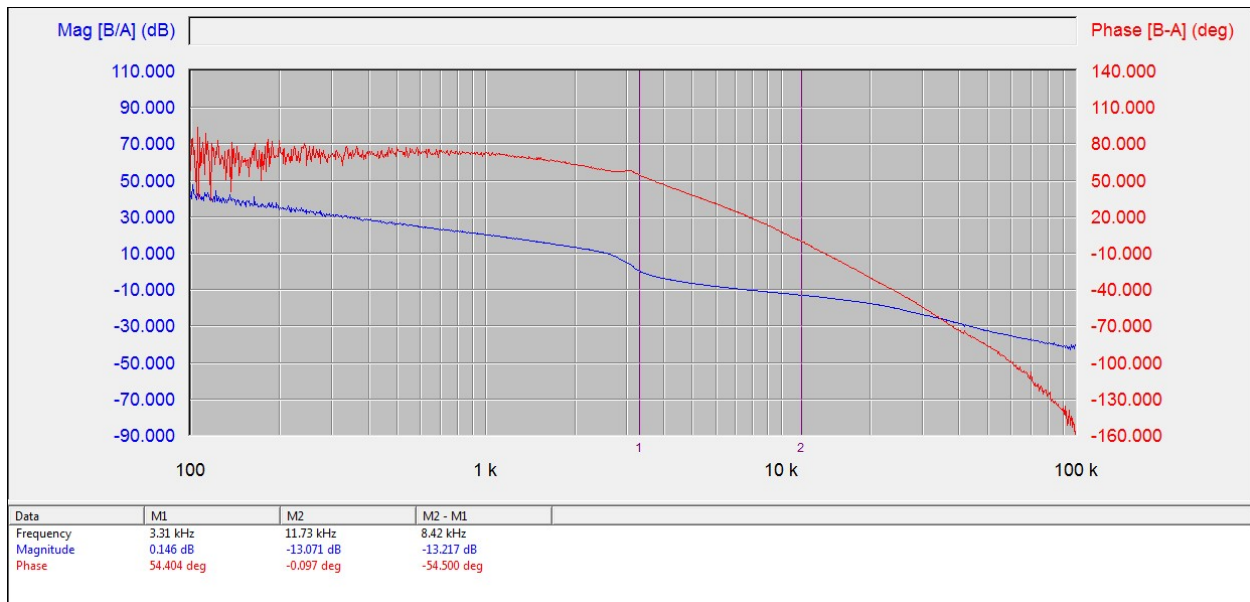Gain/Phase plot 1 at  $V_{in} = 3.7V$  ,  $V_{out} = 120V@100mA$



Gain/Phase plot 2 at  $V_{in} = 4.7V$  ,  $V_{out} = 120V@100mA$

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated