

How to Get the Most Benefits Out of WCSPs for Portable Electronics



Linhong Qin

Wafer chip-scale packages (WCSPs) are becoming more popular in portable electronics due to their smaller footprint, lighter weight, better electrical parameters and lower manufacturing costs. WCSPs enable a direct interconnection between the silicon chip and the printed circuit board (PCB). Their minimal footprint frees up a lot of space on the PCB for other components. [Figure 1](#) illustrates a WCSP.

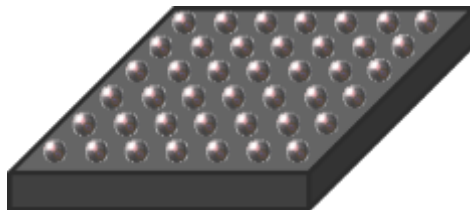


Figure 1. WCSP Illustration

A WCSP also reduces parasitic resistance, inductance and weight by eliminating the extra bond wires, lead frames and encapsulation found in other packages. The lowered resistance in the power-conversion integrated circuit (IC) results in higher efficiency. As [Figure 2](#) shows, the power loss is lower in bq25898x WCSP than in a competing IC family, while also providing 13% more charging current for the same 1W power-loss budget. This is very significant for maintaining the same equipment case temperature at a higher charging current, as discussed in the blog post, [“How 1.2% more efficiency can help you charge faster and cooler.”](#)

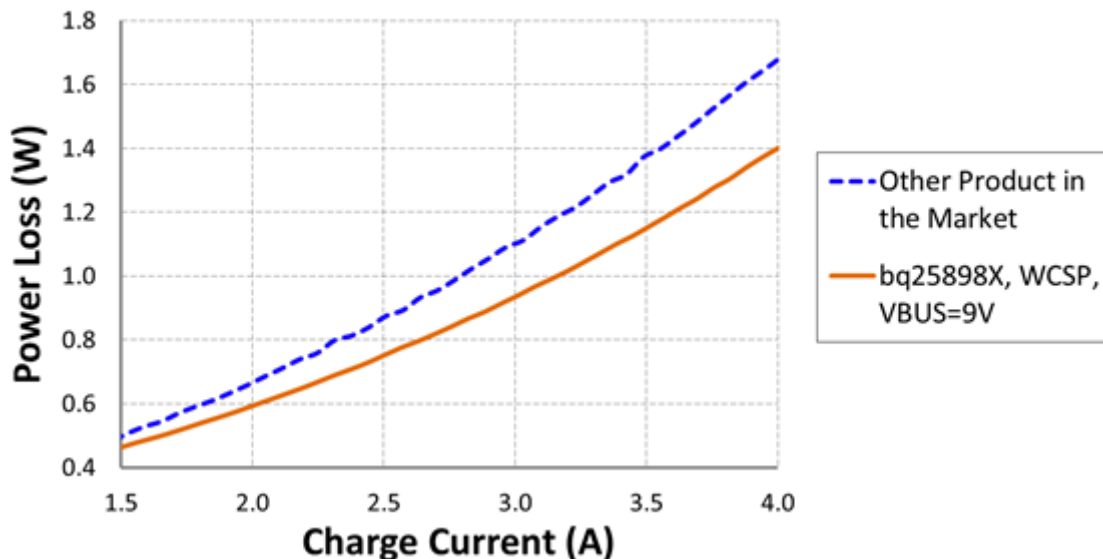


Figure 2. Power Loss of bq25898 in WCSP


For the same power loss, however, the IC temperature increase is usually higher in WCSPs due to their higher junction-to-ambient thermal resistance ($R_{\theta JA}$). The smaller footprint also leaves little room for component placement and wire routing. Optimizing PCB layout and maintaining good thermal performance are therefore big challenges.

Figure 3a is an example layout of the bq25898. All critical components, input (PMID and VBUS), system (SYS) and battery (BAT) capacitors are placed next to the device pins, keeping the high-frequency current loop at a minimum. All power lines use the maximum copper pours; almost the entire PCB is covered by copper. A big ground copper pour is created at device GND, and well connected to other GNDs.

Figure 3b is a thermal image of the bq25898 taken at 3A Charging current with a 9V input and a 3.9V battery . As you can see, heat is evenly distributed across the IC, with no excessive heat buildup or hot spots.

This experiment shows that a PCB layout like that shown in Figure 3 can reduce the IC temperature from 55°C to 52°C compared to a “normally” laid-out PCB. For more details about layout optimization, see the application note, “Achieving the Optimal Thermal Performance for Chip Scale Package.”

(a)

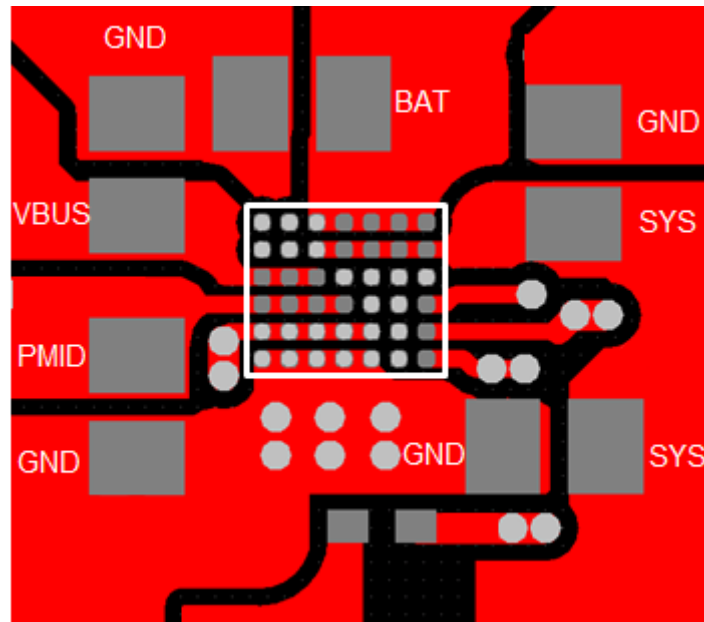

(b)

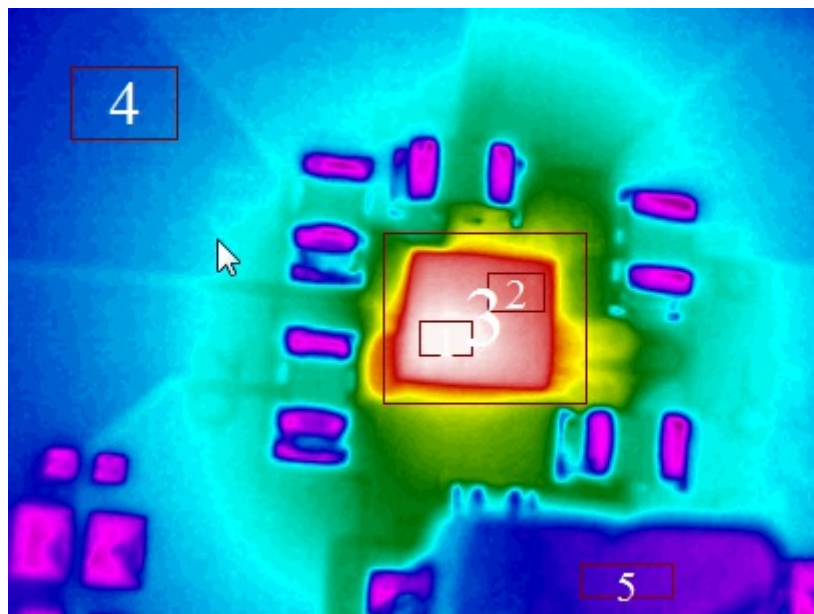


Figure 3. PCB Top-layer Layout (a); and Thermal Image (b)

As you can see, it's possible to highly enhance thermal performance with an optimized PCB layout to avoid hot spots. If done properly, WCSPs provide a lighter, faster and cooler charger, with a better customer experience.

Additional Resources:

- Read the application note: [Achieving the Optimal Thermal Performance for Chip Scale Package](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated