

Ultra-Wide Input Non-Isolated High-Side Buck Converter Reference Design



Description

This reference design is an ultra-wide input, offline, high-side buck reference design that provides a 13V output at a maximum of 0.6A. The input voltage range is between 85V_{AC} to 485V_{AC}. The reference design uses the UCC28750 current-mode flyback controller without opto-coupler feedback. There is no isolation, the design uses a low cost current mirror to regulate the output. The design is developed to be resistant to magnetic fields up to 200mT near the inductor.

Features


- Wide input range: 100V_{DC} to 630V_{DC}
- Resistant to external magnetic fields
- Output short-circuit (OSC) protection
- Frequency dithering for improved electromagnetic interference (EMI)
- Frequency foldback and burst mode for improved light load efficiency
- [UCC28750](#) controller with low cost current mirror

Applications


- [Electricity meter](#)
- [DC-input BLDC motor drive](#)
- [String inverter](#)
- [Refrigerator and freezer](#)
- [Washer and dryer](#)



Top Photo

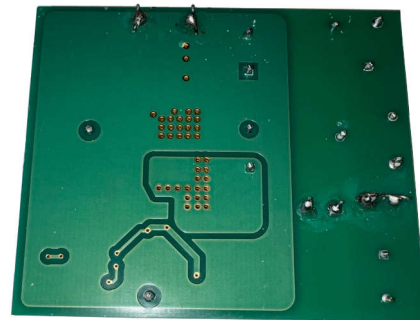

Bottom Photo

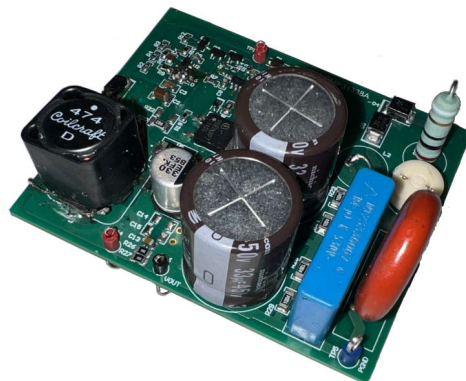

Angled Board Photo

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Maximum DC input voltage	100V _{DC} to 630V _{DC}
Output Voltage	13V
Output Current	0.6A

1.2 Dimensions

The reference design is built on board PMP31338RevA. The outline of the two-layer board is 69.9mm × 59.2mm.

2 Testing and Results

2.1 Efficiency Graph

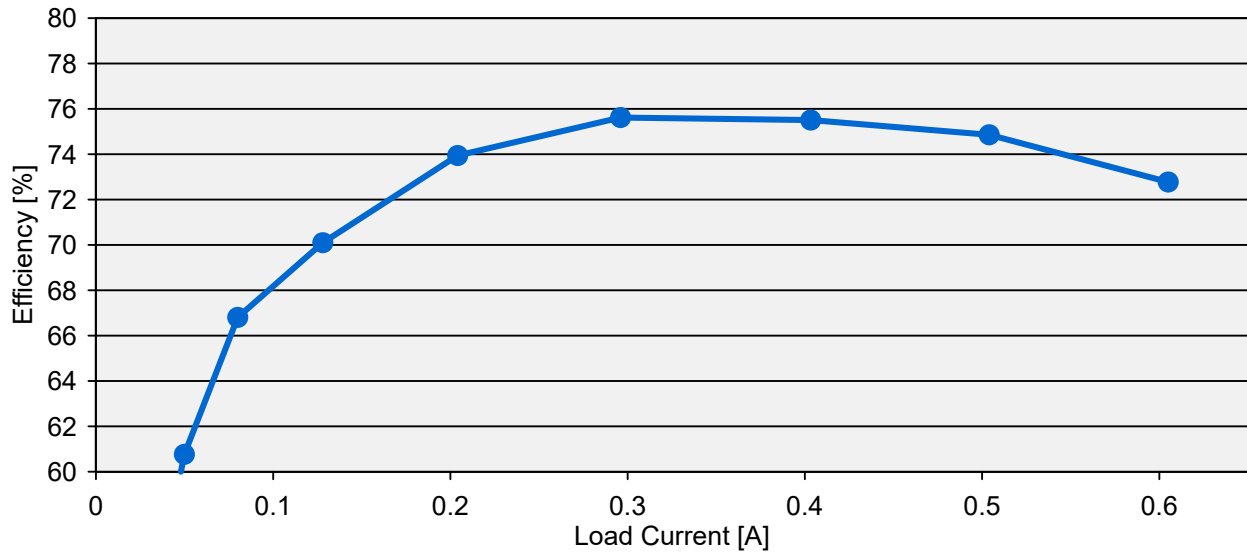


Figure 2-1. Efficiency versus Load Current (at 230V_{AC} Input Voltage)

2.2 Load Regulation

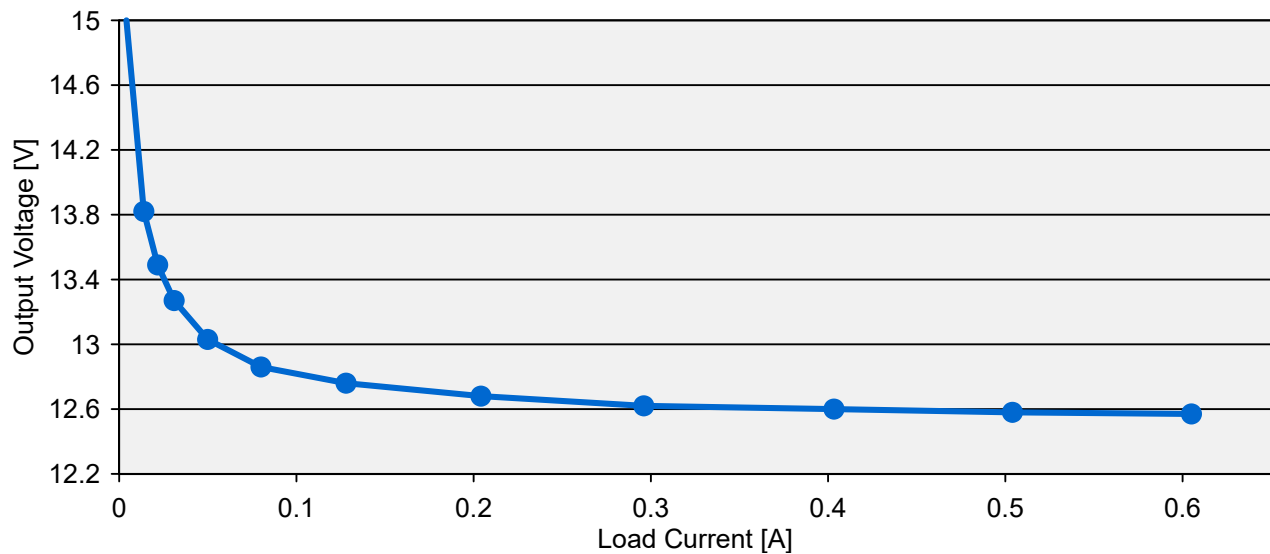


Figure 2-2. Output Voltage versus Load Current (at 230V_{AC} Input Voltage)

2.3 Line Regulation

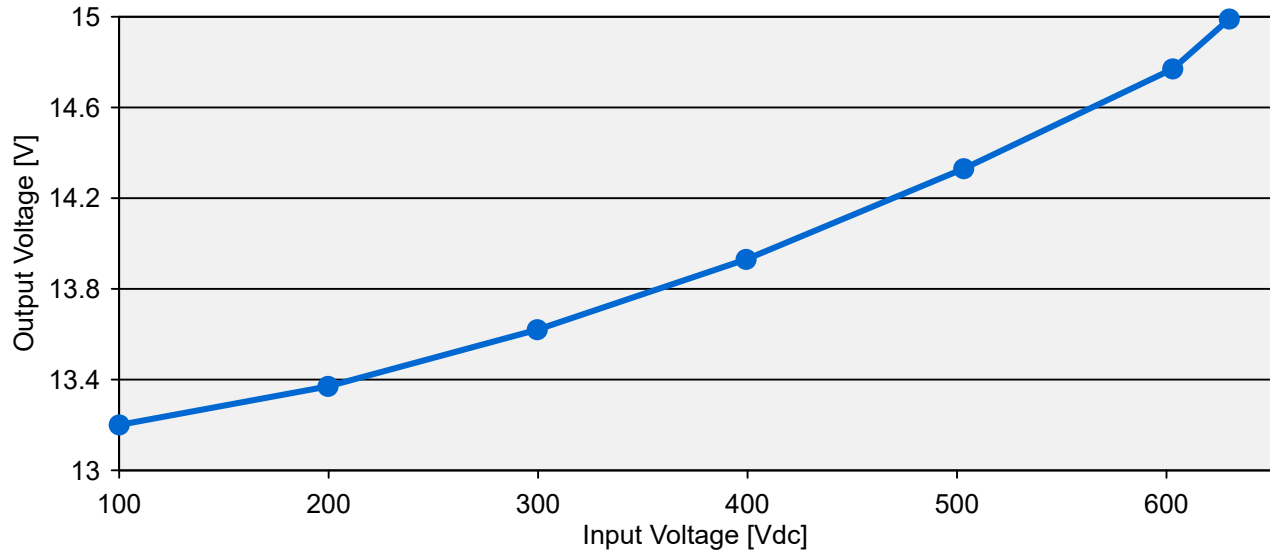


Figure 2-3. Output Voltage versus Input Voltage

3 Waveforms

3.1 Switching

3.1.1 325V_{DC} Input Voltage

3.1.1.1 0A Load Current

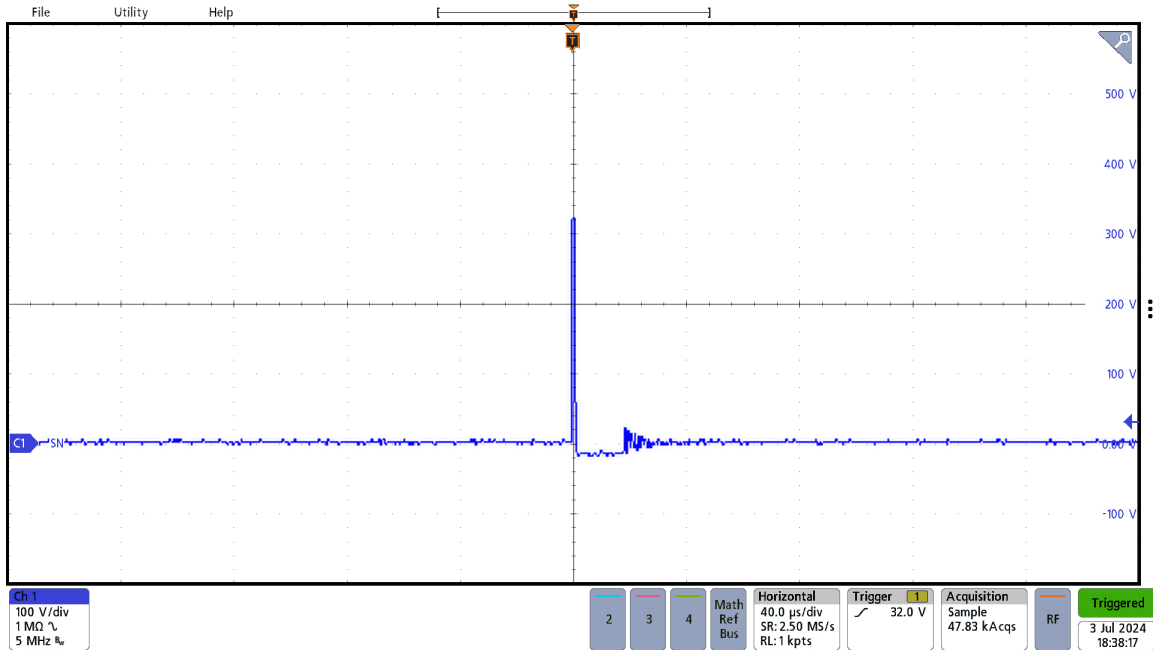


Figure 3-1. Load Current = 0mA

3.1.1.2 30mA Load Current

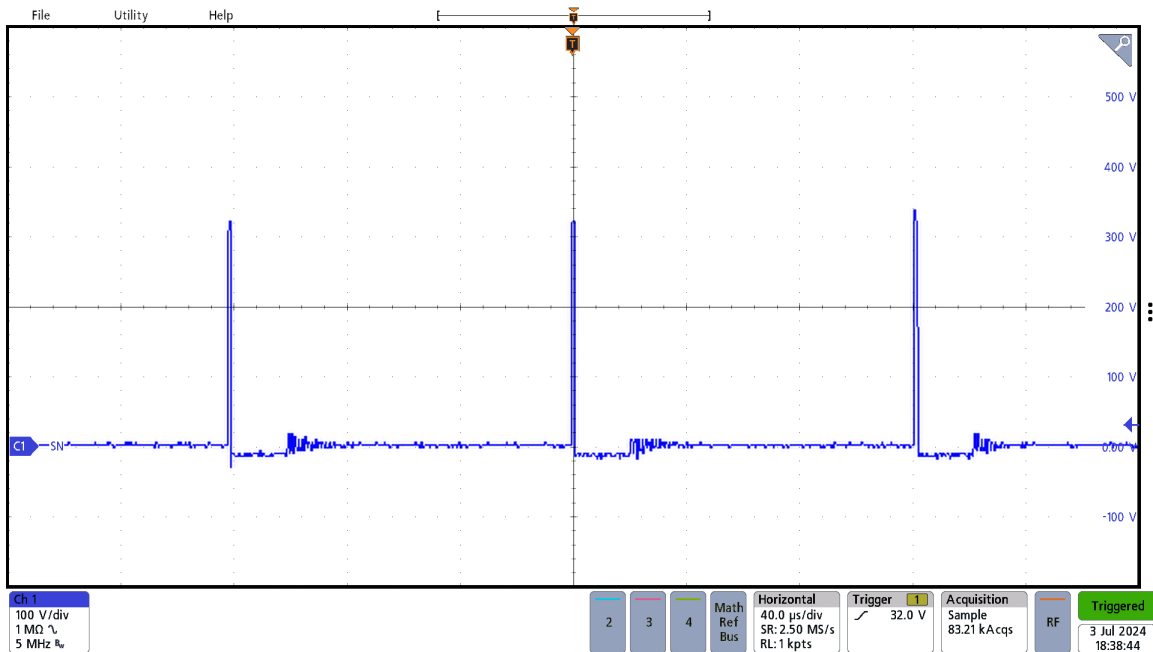


Figure 3-2. Load Current = 30mA

3.1.1.3 130mA Load Current

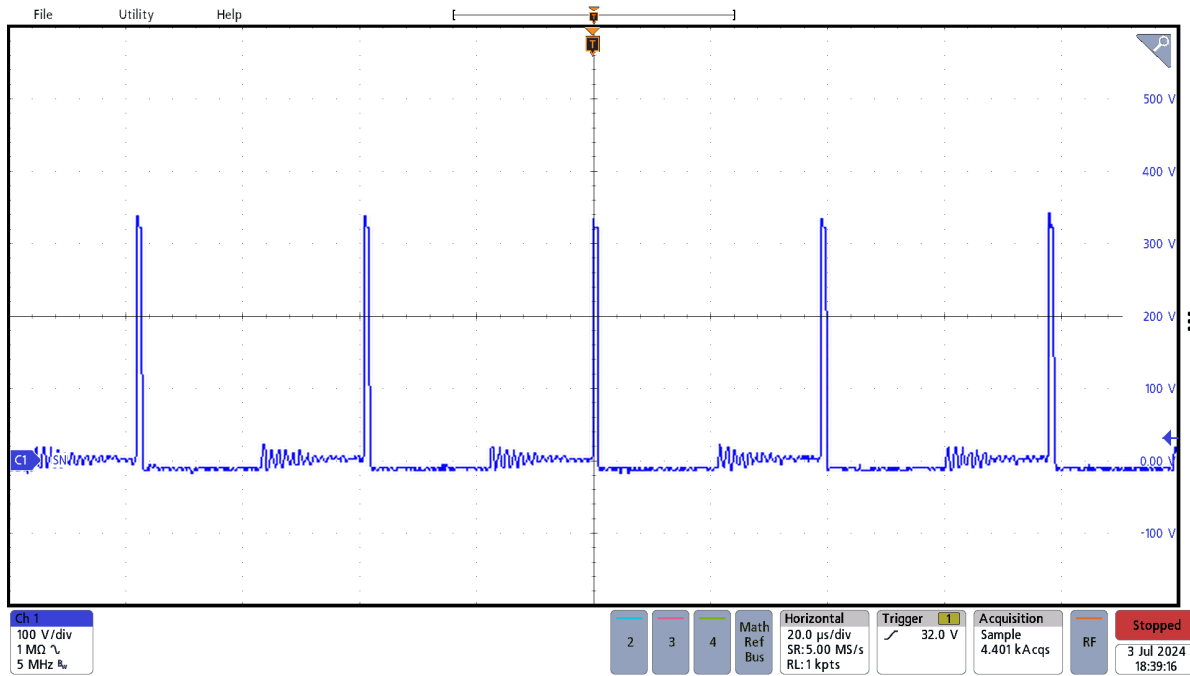


Figure 3-3. Load Current = 130mA

3.1.1.4 340mA Load Current

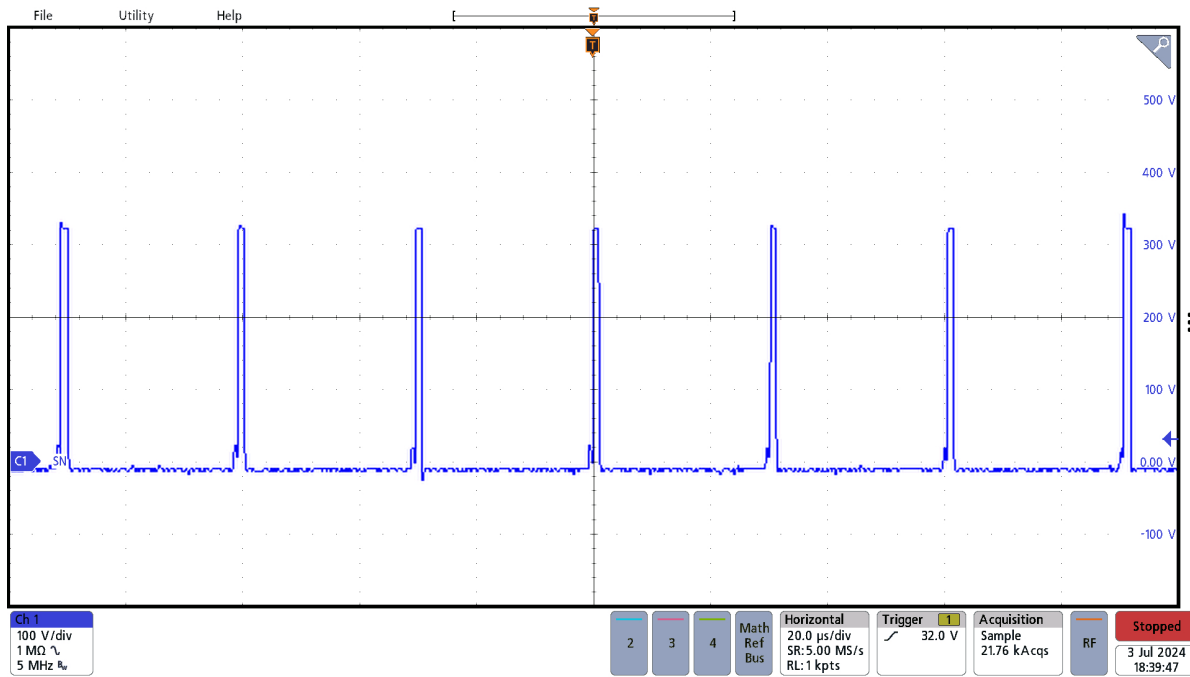


Figure 3-4. Load Current = 340mA

3.1.1.5 600mA Load Current

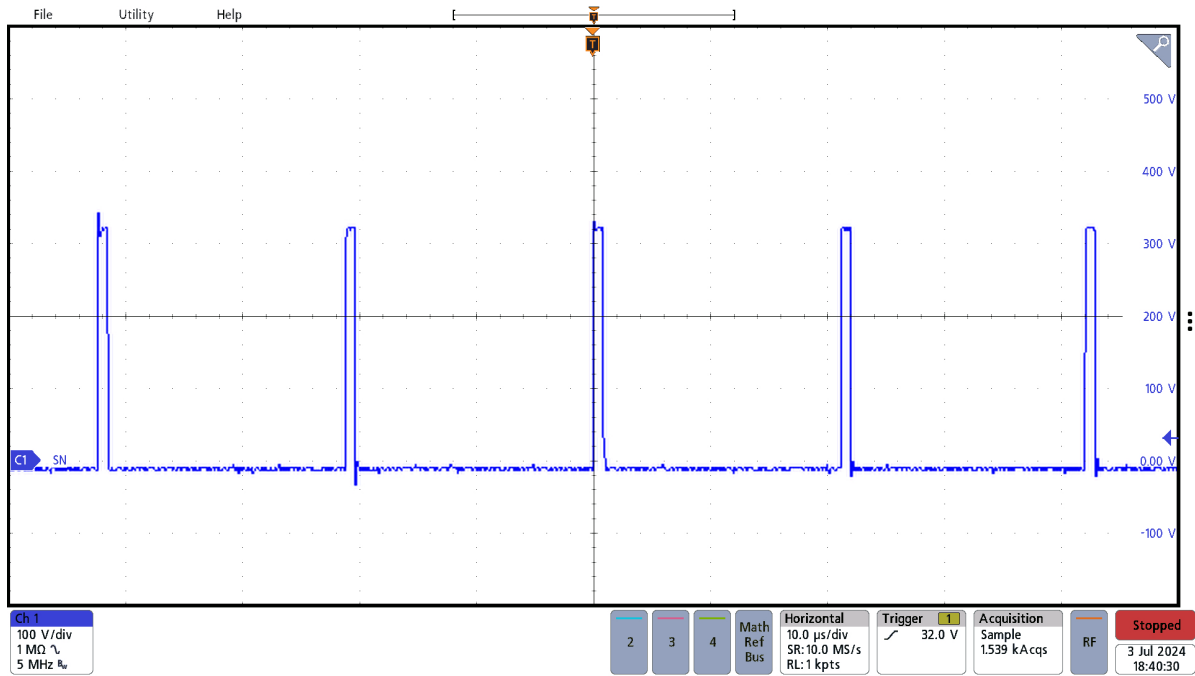


Figure 3-5. Load Current = 600mA

3.1.2 630V_{DC} Input Voltage

3.1.2.1 600mA Load Current

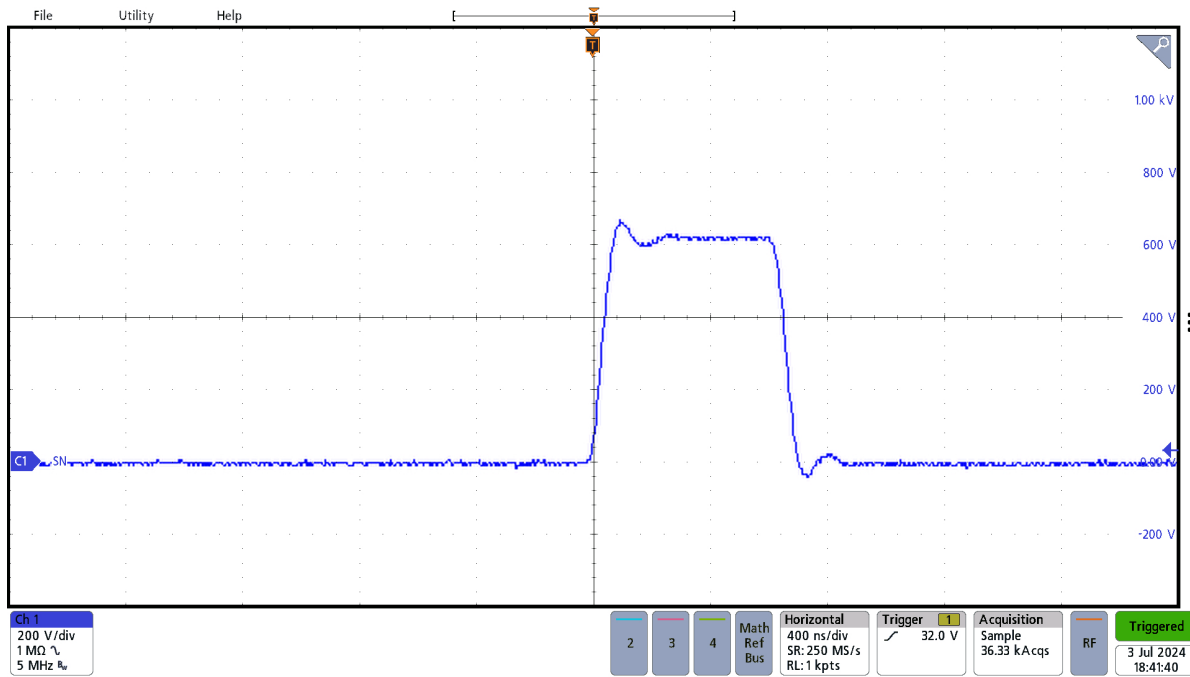


Figure 3-6. Load Current = 600mA

3.2 Output Voltage Ripple

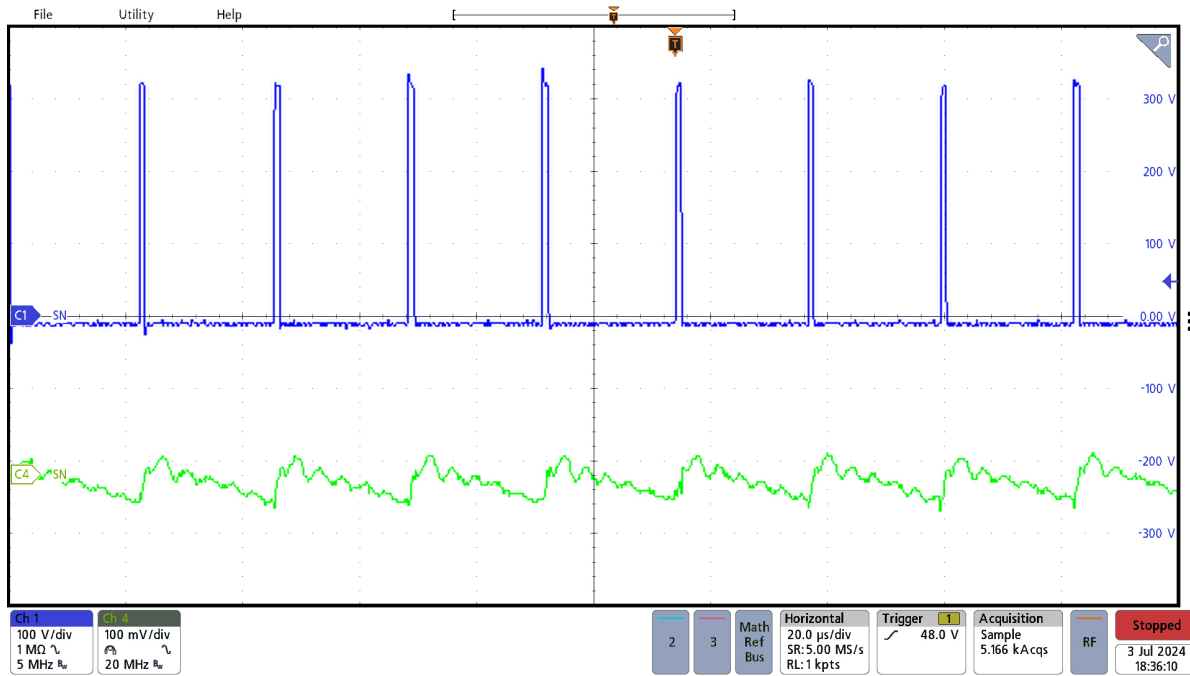


Figure 3-7. 325V_{DC} Input Voltage, Full Load

3.3 Load Transients

3.3.1 100V_{DC} Input Voltage

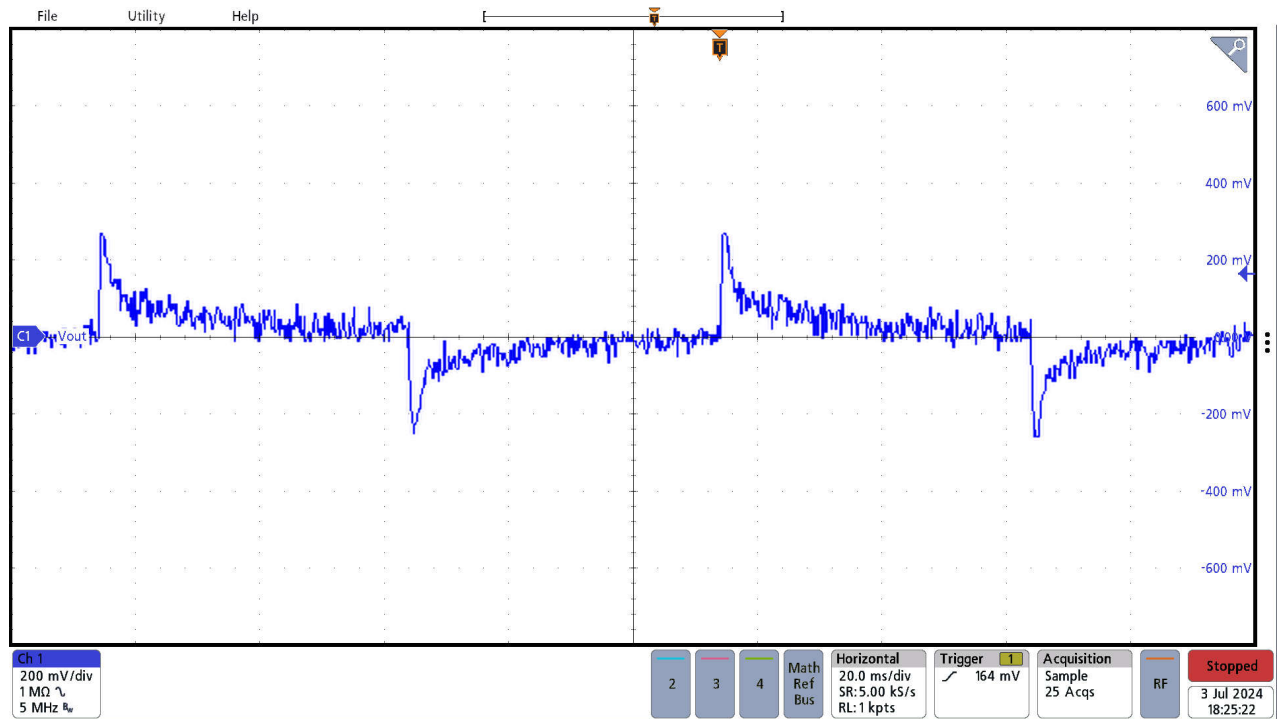


Figure 3-8. 100V_{DC} Input Voltage, Loadstep = 300mA to 600mA

3.3.2 250V_{DC} Input Voltage

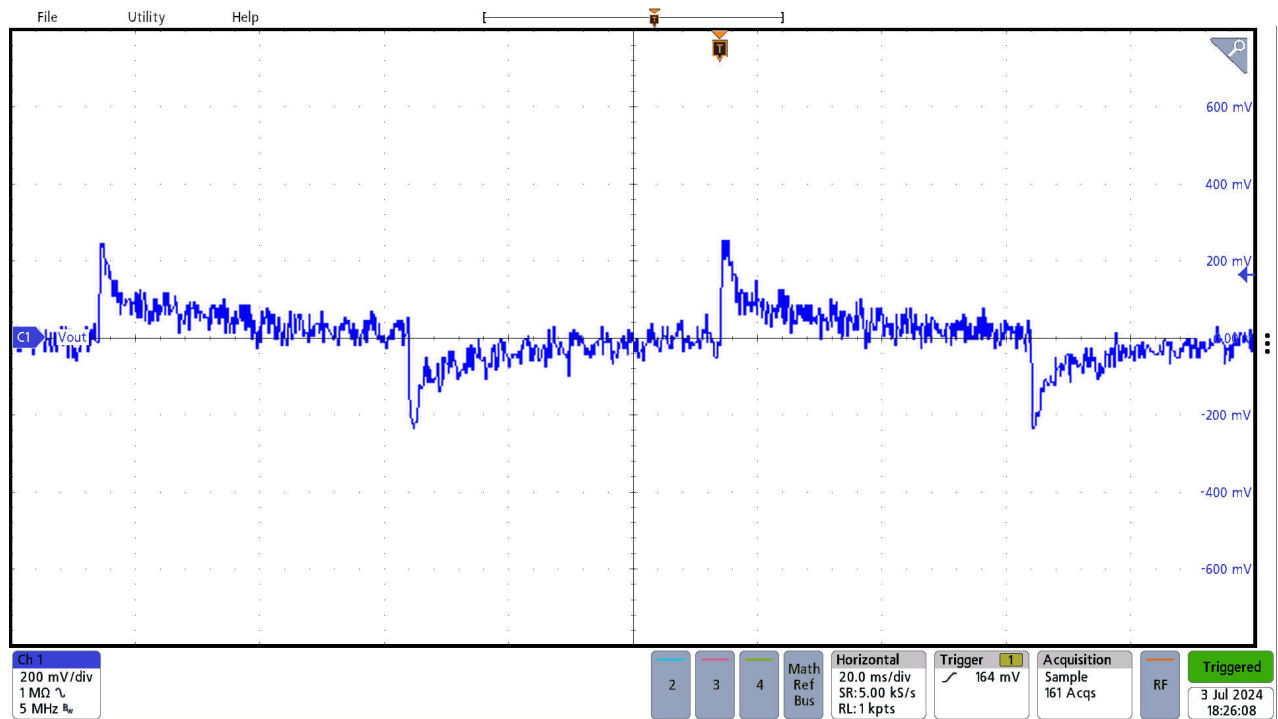


Figure 3-9. 250V_{DC} Input Voltage, Loadstep = 300mA to 600mA

3.3.3 450V_{DC} Input Voltage

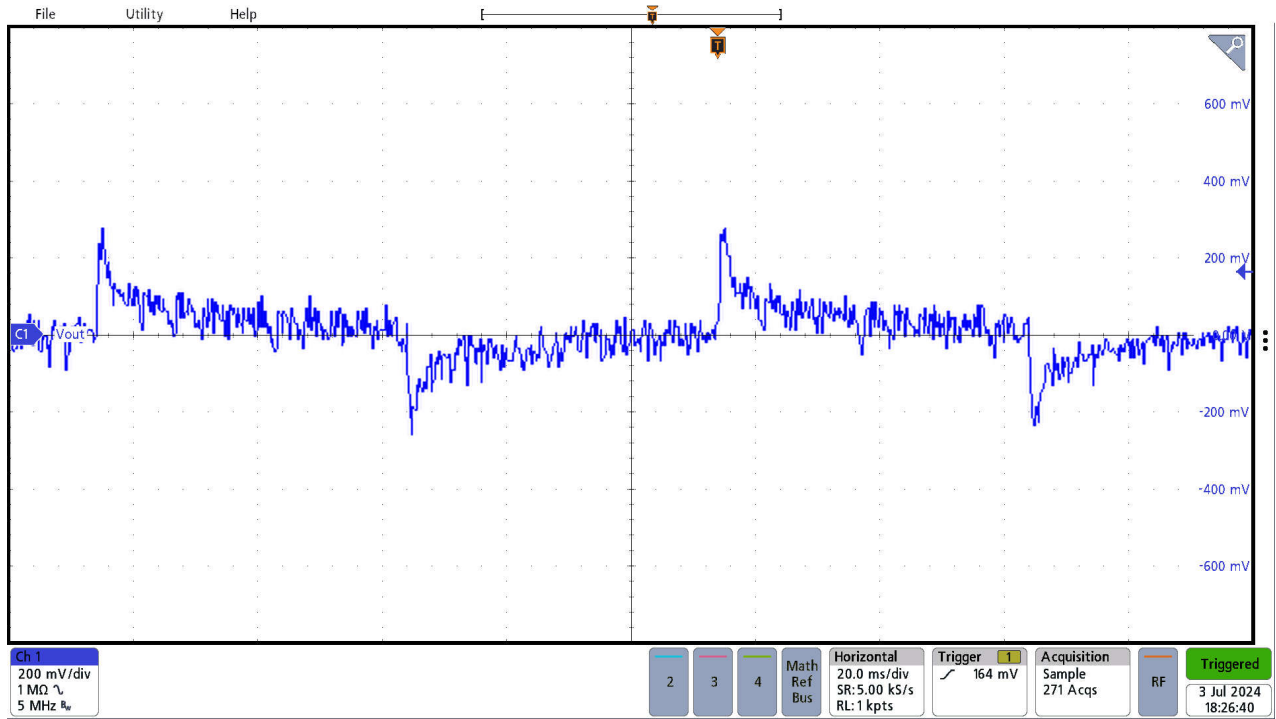


Figure 3-10. 450V_{DC} Input Voltage, Loadstep = 300mA to 600mA

3.3.4 630V_{DC} Input Voltage

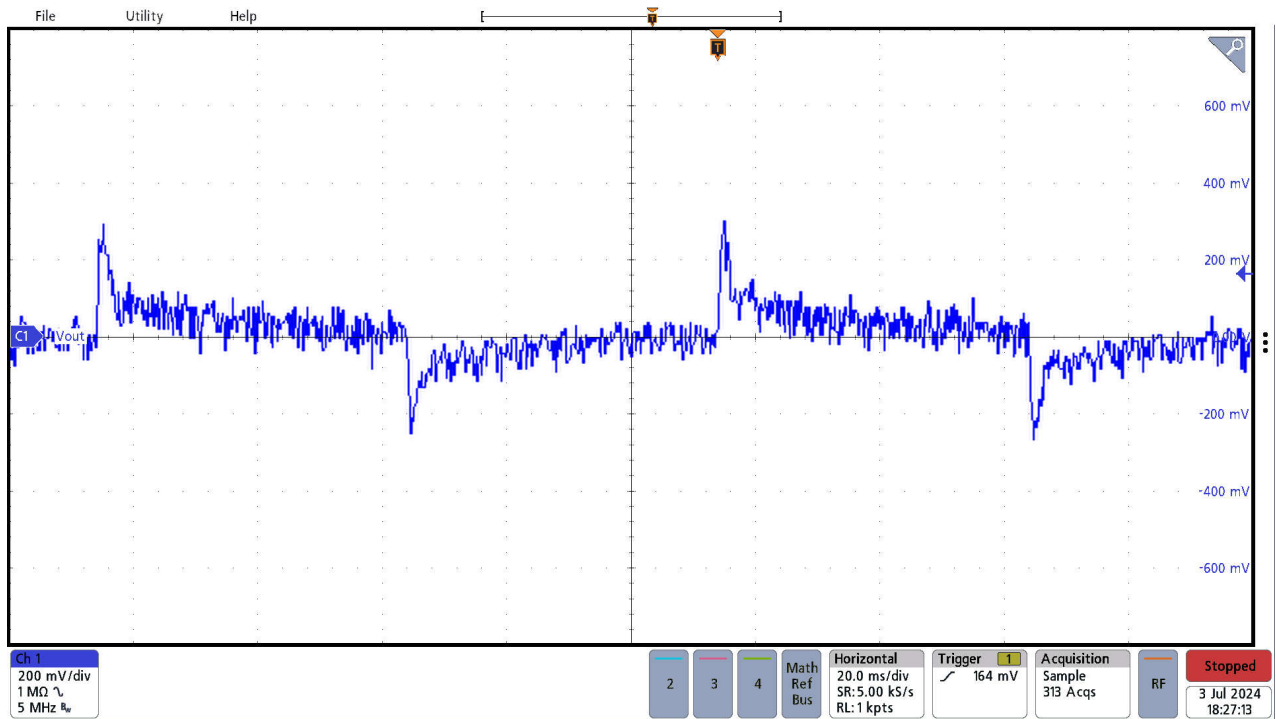


Figure 3-11. 630V_{DC} Input Voltage, Loadstep = 300mA to 600mA

3.4 Start-up Sequence

3.4.1 150V_{DC} Input Voltage and 600mA Load Current

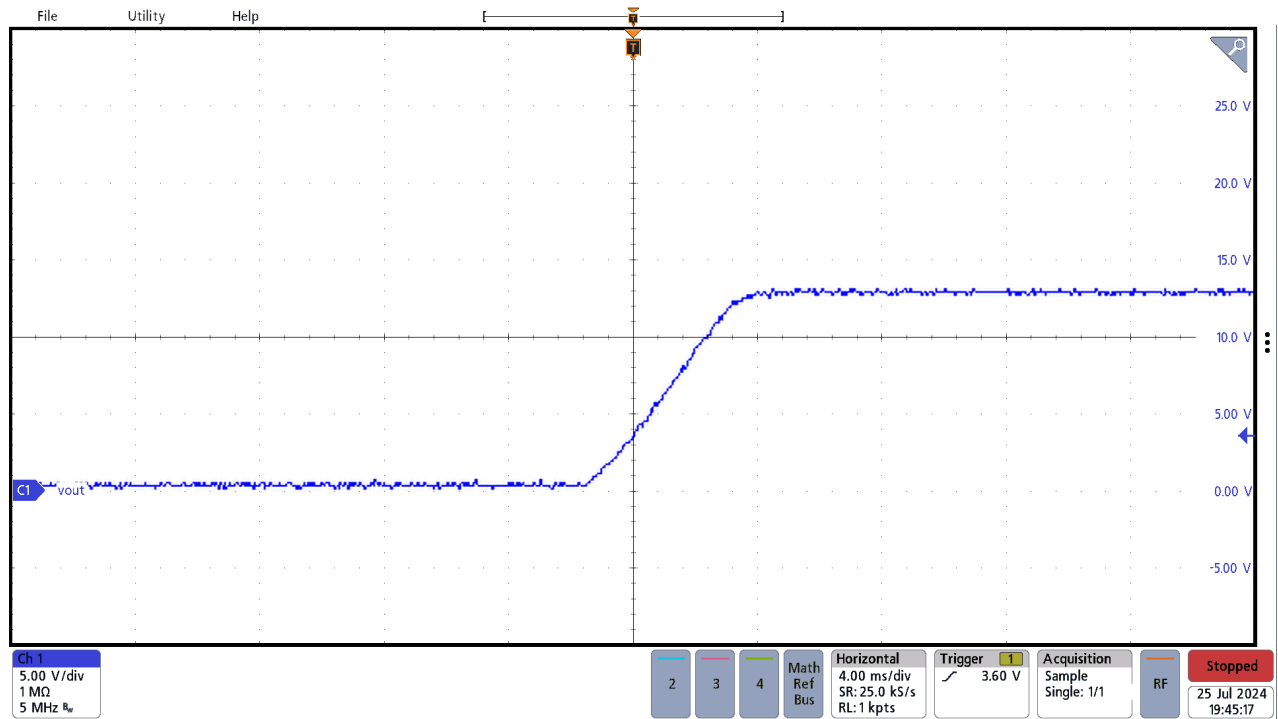


Figure 3-12. 150V_{DC} Input Voltage, Load Current = 600mA

3.4.2 325V_{DC} Input Voltage and No Load

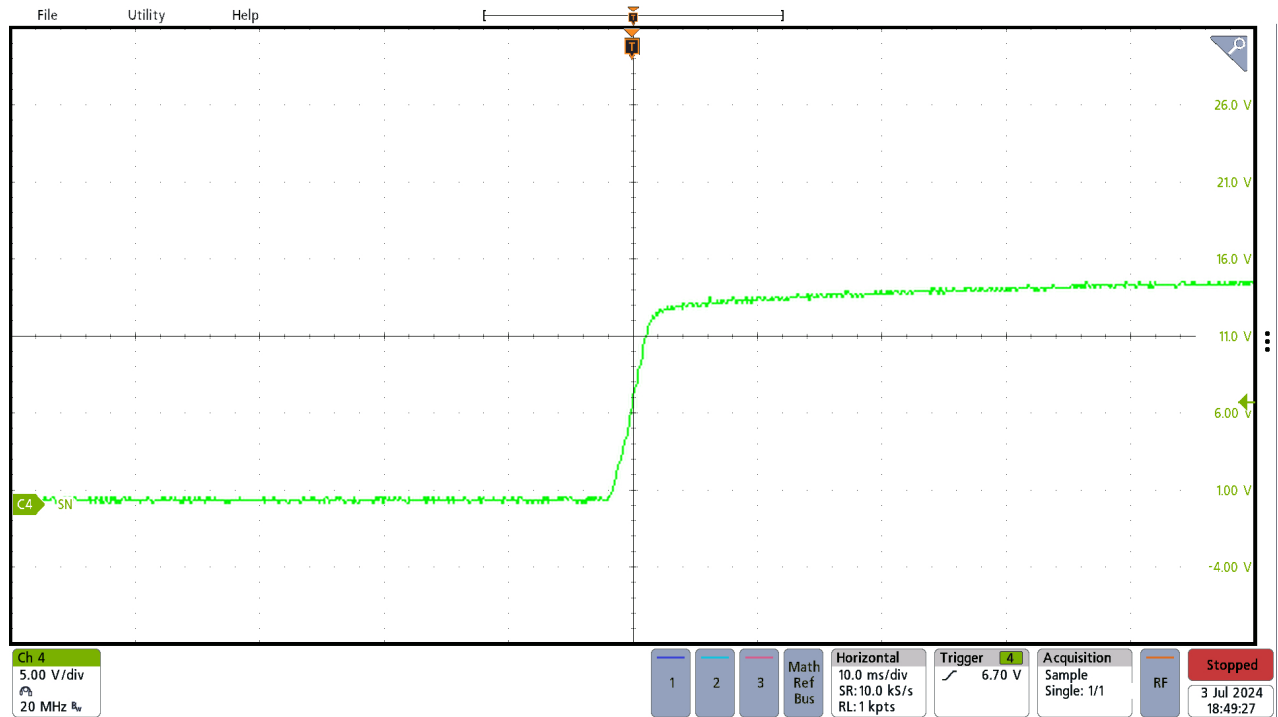


Figure 3-13. 325V_{DC} Input Voltage, Load Current = 0A

3.4.3 630V_{DC} Input Voltage and 600mA Load Current

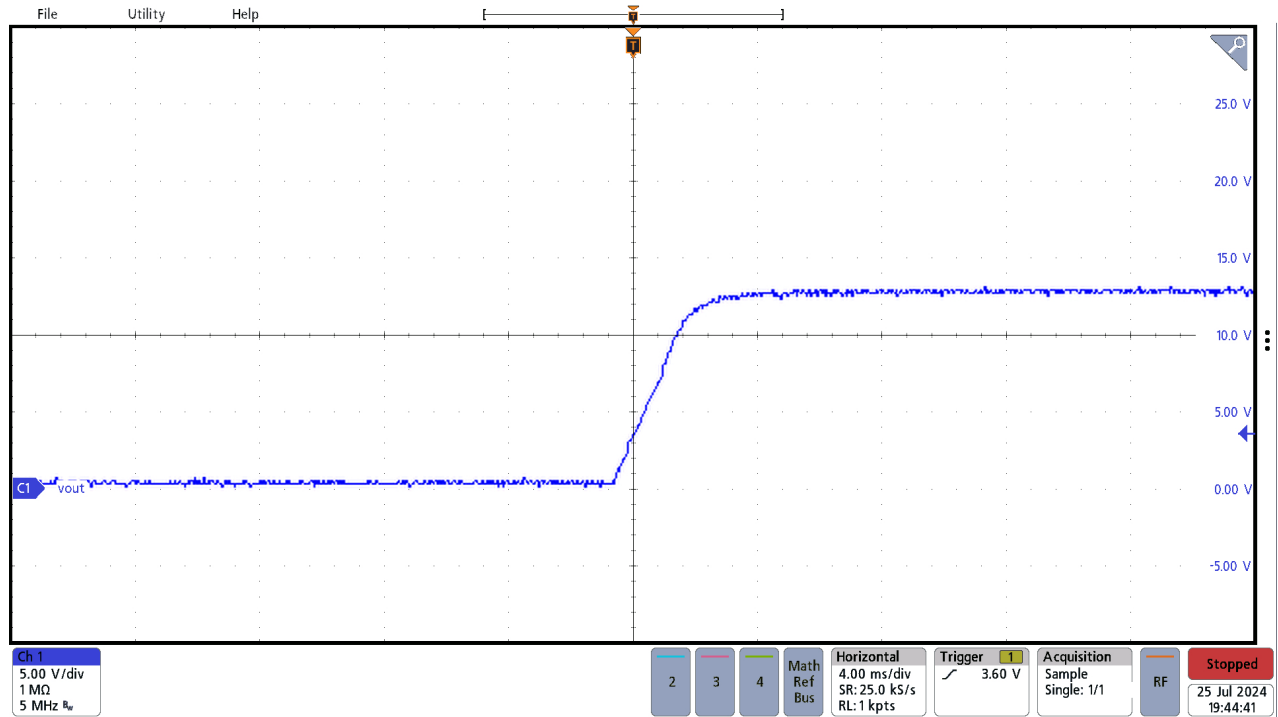


Figure 3-14. 630V_{DC} Input Voltage, Load Current = 600mA

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated