

PMP40294 Test Results

1 General

1.1 Purpose

This test report is to provide the detailed data for evaluating and verifying the PMP40294 which performs a battery powered bi-directional system. It employs a bidirectional Buck-Boost Controller ---- BQ25703A with a user command switch. It can support any adaptor input within 5V-20V. And the system can also output multiple output options including 5/9/12/14.5/15/16/19/20V.the max output power is designed as 45W and valid battery voltage is from 9V to 13.2V.

1.2 Reference Documentation

Schematic: PMP40294_Sch.pdf

Gerber: PMP40294_GerberNCdrills.zip

Layer Plot: PMP40294_PCBlayers.pdf

Assembly Drawing: PMP40294_Assy.pdf

CAD File: PMP40294_CAD.zip

BOM: PMP40294_BOM.pdf

1.3 Test Equipment

Multi-meter (current): Fluke 287C

Multi-meter (voltage): Fluke 287C

DC Source: Chroma 62006P-100-25

E-Load: Chroma 63105A module

Oscilloscope: Tektronix DPO3054


Electrical Thermography: Fluke Ti9

2 Performance Data and Waveform

2.1 Efficiency

2.1.1 5V Input in Forward Mode


$V_{IN}(V)$	$I_{IN}(A)$	$V_{BAT}(V)$	$I_{BAT}(A)$	Efficiency
5.077	0.409	9.294	0.194	86.83%
5.057	0.878	9.294	0.436	91.24%
5.016	1.842	9.294	0.938	94.39%
4.975	2.823	9.294	1.403	92.81%
5.073	0.496	11.095	0.194	85.59%
5.050	1.056	11.095	0.436	90.70%
5.001	2.205	11.096	0.931	93.67%
4.970	2.938	11.096	1.209	91.90%
5.070	0.565	12.523	0.194	84.86%
5.044	1.196	12.523	0.434	90.12%
4.989	2.486	12.523	0.923	93.23%
4.970	2.938	12.523	1.063	91.17%

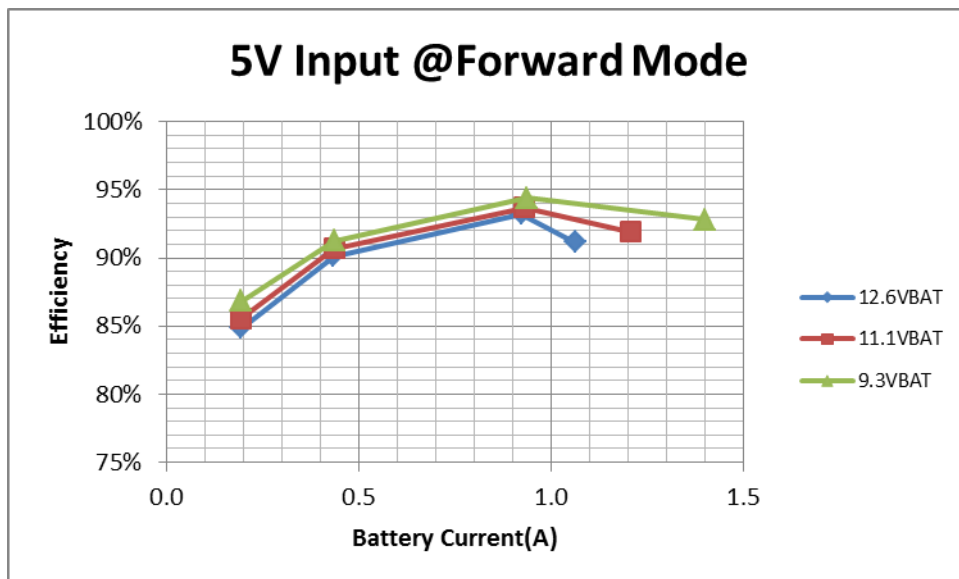

2.1.2 9V Input in Forward Mode

$V_{IN}(V)$	$I_{IN}(A)$	$V_{BAT}(V)$	$I_{BAT}(A)$	Efficiency
9.091	0.226	9.294	0.193	87.35%
9.079	0.510	9.294	0.462	92.77%


9.058	1.017	9.294	0.959	96.76%
9.035	1.558	9.294	1.447	95.51%
9.012	2.107	9.294	1.969	96.36%
8.990	2.612	9.294	2.431	96.21%
9.089	0.275	11.095	0.190	84.47%
9.075	0.616	11.095	0.464	92.11%
9.049	1.221	11.095	0.956	96.03%
9.022	1.863	11.095	1.438	94.93%
8.994	2.525	11.095	1.961	95.82%
8.976	2.940	11.095	2.277	95.74%
9.088	0.307	12.523	0.192	86.27%
9.071	0.703	12.523	0.468	91.87%
9.042	1.387	12.523	0.958	95.67%
9.012	2.102	12.524	1.432	94.65%
8.980	2.857	12.524	1.956	95.46%
8.977	2.939	12.524	2.010	95.41%

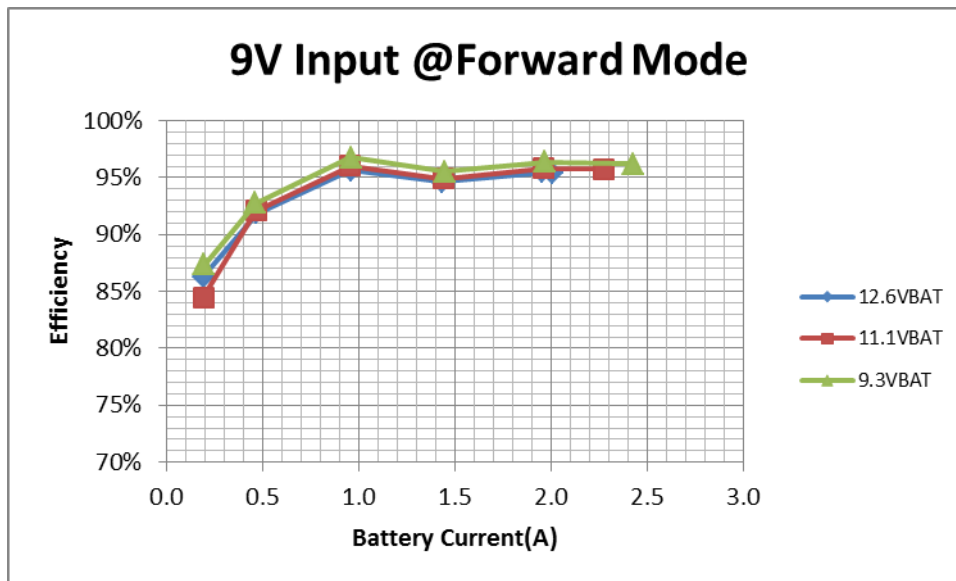

2.1.3 12V Input in Forward Mode

$V_{IN}(V)$	$I_{IN}(A)$	$V_{BAT}(V)$	$I_{BAT}(A)$	Efficiency
12.095	0.174	9.294	0.200	88.19%
12.085	0.392	9.294	0.457	89.58%
12.068	0.803	9.294	0.985	94.50%
12.051	1.223	9.294	1.500	94.59%


12.033	1.627	9.294	2.017	95.75%
12.016	2.039	9.294	2.523	95.70%
12.001	2.395	9.294	2.978	96.28%
12.093	0.206	11.095	0.201	89.34%
12.082	0.457	11.095	0.446	89.68%
12.062	0.947	11.095	0.981	95.25%
12.042	1.435	11.096	1.484	95.30%
12.021	1.923	11.096	2.005	96.26%
12.000	2.389	11.095	2.491	96.40%
11.982	2.824	11.095	2.958	96.98%
12.092	0.225	12.523	0.197	90.58%
12.080	0.499	12.523	0.448	93.09%
12.057	1.051	12.523	0.968	95.61%
12.036	1.577	12.523	1.448	95.56%
12.013	2.122	12.523	1.966	96.58%
11.991	2.626	12.523	2.427	96.53%
11.977	2.938	12.523	2.726	97.02%

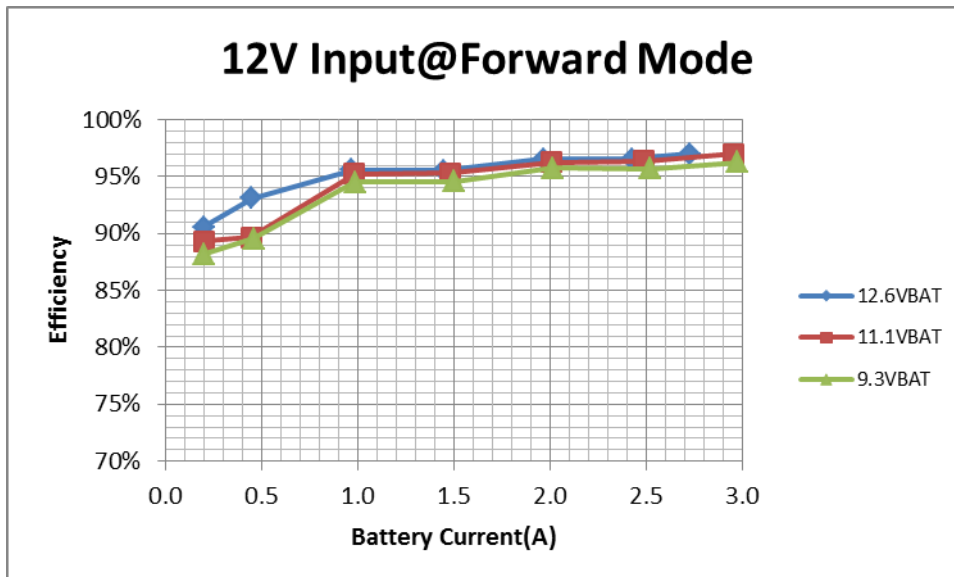

2.1.4 15V Input in Forward Mode

$V_{IN}(V)$	$I_{IN}(A)$	$V_{BAT}(V)$	$I_{BAT}(A)$	Efficiency
15.093	0.144	9.294	0.201	85.78%
15.086	0.321	9.294	0.456	87.44%
15.073	0.645	9.294	0.977	93.39%


15.058	0.991	9.294	1.499	93.36%
15.044	1.315	9.294	2.017	94.74%
15.030	1.642	9.294	2.520	94.90%
15.018	1.928	9.294	2.975	95.48%
15.093	0.169	11.095	0.201	87.26%
15.084	0.375	11.095	0.456	89.36%
15.068	0.759	11.096	0.977	94.78%
15.050	1.174	11.095	1.500	94.19%
15.033	1.559	11.096	2.018	95.52%
15.018	1.947	11.096	2.521	95.66%
15.002	2.286	11.096	2.977	96.31%
15.092	0.187	12.524	0.201	89.02%
15.082	0.418	12.524	0.457	90.71%
15.064	0.850	12.524	0.977	95.55%
15.044	1.318	12.523	1.500	94.74%
15.026	1.751	12.524	2.019	96.12%
15.007	2.188	12.524	2.522	96.19%
14.991	2.568	12.524	2.977	96.84%

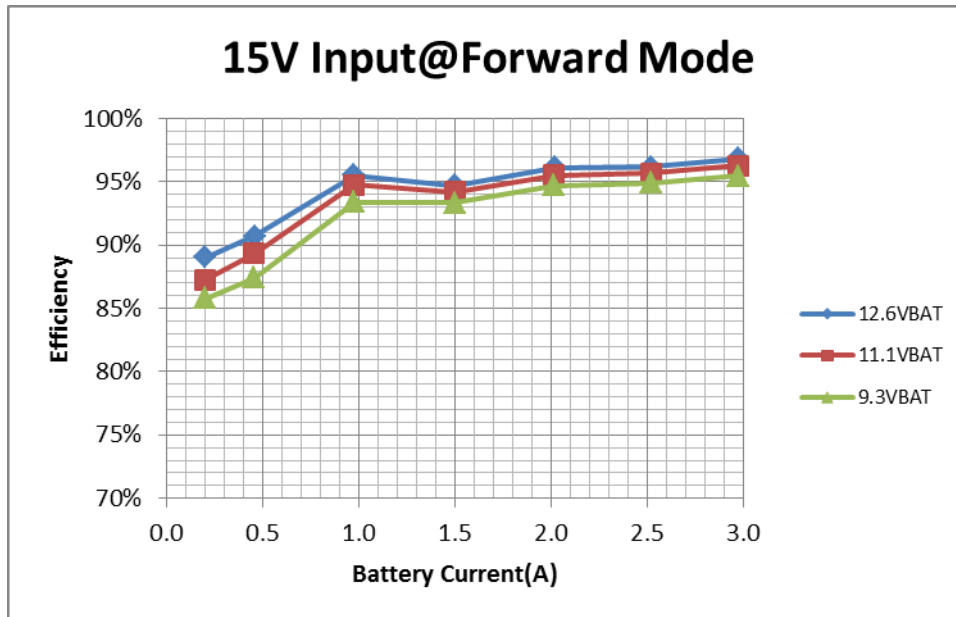

2.1.5 20V Input in Forward Mode

$V_{IN}(V)$	$I_{IN}(A)$	$V_{BAT}(V)$	$I_{BAT}(A)$	Efficiency
20.037	0.116	9.294	0.201	80.21%


20.088	0.255	9.294	0.454	82.33%
20.076	0.520	9.294	0.971	86.47%
20.066	0.764	9.294	1.497	90.77%
20.055	1.009	9.294	2.017	92.62%
20.045	1.252	9.294	2.519	93.29%
20.036	1.467	9.294	2.974	94.03%
20.092	0.134	11.095	0.201	82.67%
20.085	0.297	11.095	0.454	84.40%
20.072	0.605	11.095	0.972	88.83%
20.060	0.902	11.095	1.500	91.98%
20.048	1.194	11.096	2.018	93.52%
20.036	1.481	11.095	2.520	94.22%
20.025	1.737	11.096	2.974	94.86%
20.092	0.148	12.523	0.201	84.48%
20.084	0.327	12.523	0.456	86.87%
20.070	0.672	12.524	0.972	90.28%
20.055	1.009	12.524	1.500	92.84%
20.041	1.338	12.524	2.018	94.27%
20.028	1.661	12.524	2.520	94.87%
20.016	1.949	12.524	2.974	95.47%

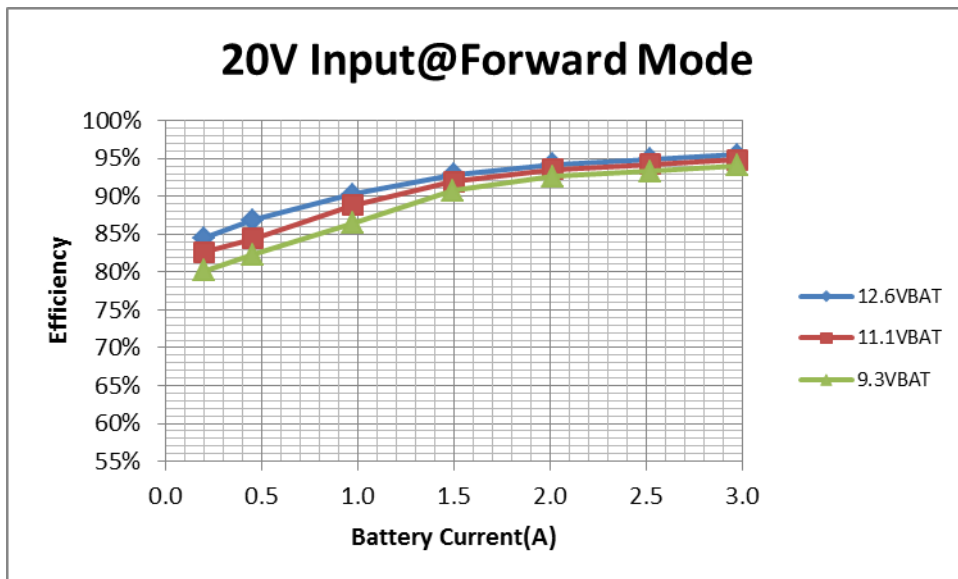

2.1.6 5V Output in Reverse Mode

$V_{BAT}(V)$	$I_{BAT}(A)$	$V_o(V)$	$I_o(A)$	Efficiency
9.292	0.305	5.033	0.498	88.40%


9.283	0.582	5.028	0.993	92.39%
9.274	0.868	5.021	1.502	93.69%
9.264	1.149	5.015	1.996	94.04%
9.255	1.432	5.009	2.490	94.11%
9.245	1.727	5.003	2.999	93.97%
11.093	0.262	5.030	0.497	86.00%
11.085	0.496	5.025	0.992	90.65%
11.077	0.736	5.019	1.501	92.40%
11.069	0.971	5.013	1.995	93.04%
11.061	1.208	5.005	2.490	93.27%
11.053	1.454	5.000	2.999	93.31%
12.593	0.236	5.030	0.497	84.10%
12.587	0.443	5.025	0.992	89.39%
12.580	0.655	5.019	1.501	91.42%
12.573	0.862	5.013	1.995	92.27%
12.566	1.071	5.005	2.490	92.60%
12.559	1.287	4.999	2.999	92.75%

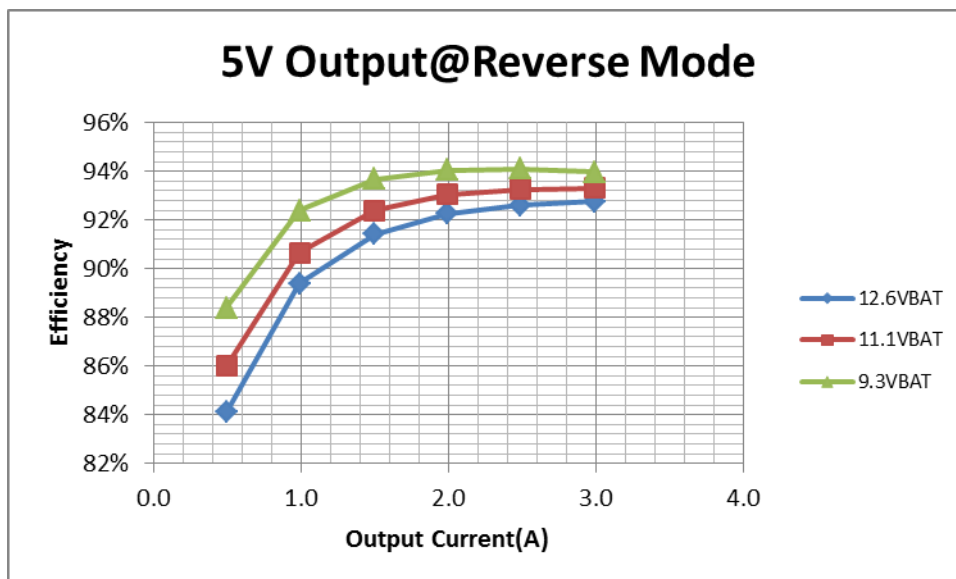

2.1.7 9V Output in Reverse Mode

$V_{BAT}(V)$	$I_{BAT}(A)$	$V_o(V)$	$I_o(A)$	Efficiency
9.285	0.521	9.104	0.496	93.32%
9.268	1.013	9.099	0.992	96.18%
9.251	1.526	9.088	1.500	96.56%
9.235	2.030	9.079	1.994	96.57%


9.218	2.538	9.070	2.488	96.46%
9.200	3.064	9.060	2.998	96.36%
11.086	0.443	9.106	0.496	91.95%
11.073	0.861	9.100	0.992	94.68%
11.058	1.292	9.095	1.501	95.55%
11.044	1.711	9.088	1.995	95.94%
11.030	2.135	9.080	2.490	96.01%
11.016	2.574	9.074	2.998	95.94%
12.588	0.396	9.105	0.497	90.76%
12.576	0.764	9.100	0.993	94.03%
12.563	1.143	9.095	1.501	95.06%
12.551	1.512	9.086	1.995	95.52%
12.539	1.885	9.078	2.490	95.63%
12.526	2.270	9.072	2.999	95.69%

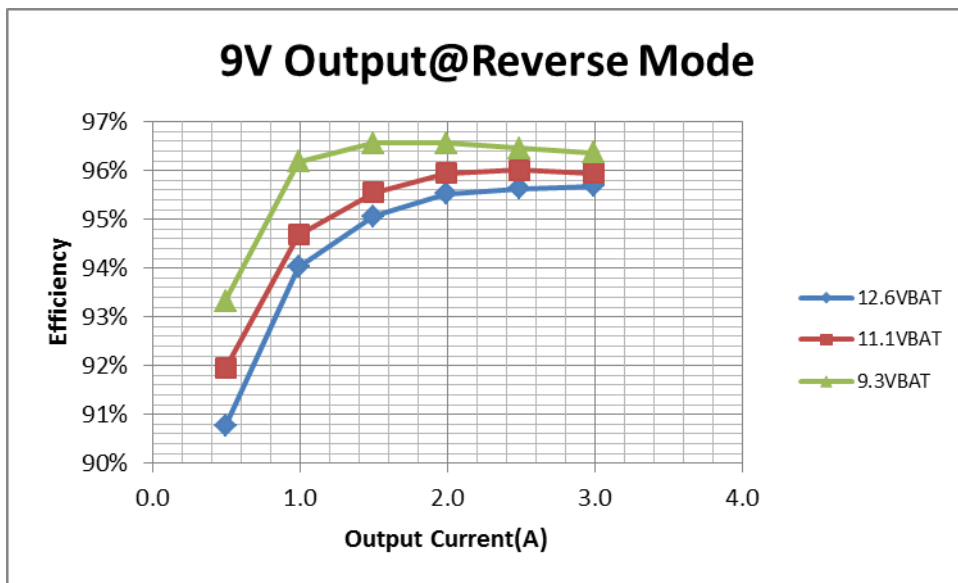

2.1.8 12V Output in Reverse Mode

$V_{BAT}(V)$	$I_{BAT}(A)$	$V_o(V)$	$I_o(A)$	Efficiency
9.278	0.705	12.231	0.496	92.73%
9.256	1.373	12.218	0.990	95.18%
9.233	2.072	12.205	1.498	95.58%
9.211	2.756	12.194	1.992	95.70%
9.187	3.452	12.185	2.486	95.53%
9.163	4.177	12.173	2.996	95.30%


11.082	0.587	12.229	0.495	93.06%
11.063	1.143	12.213	0.989	95.53%
11.044	1.721	12.201	1.497	96.11%
11.026	2.286	12.190	1.991	96.30%
11.007	2.856	12.179	2.486	96.32%
10.987	3.449	12.171	2.996	96.24%
12.586	0.518	12.216	0.496	92.92%
12.568	1.008	12.204	0.991	95.46%
12.551	1.510	12.199	1.499	96.49%
12.535	2.003	12.190	1.993	96.76%
12.518	2.500	12.180	2.488	96.84%
12.501	3.016	12.170	2.997	96.74%

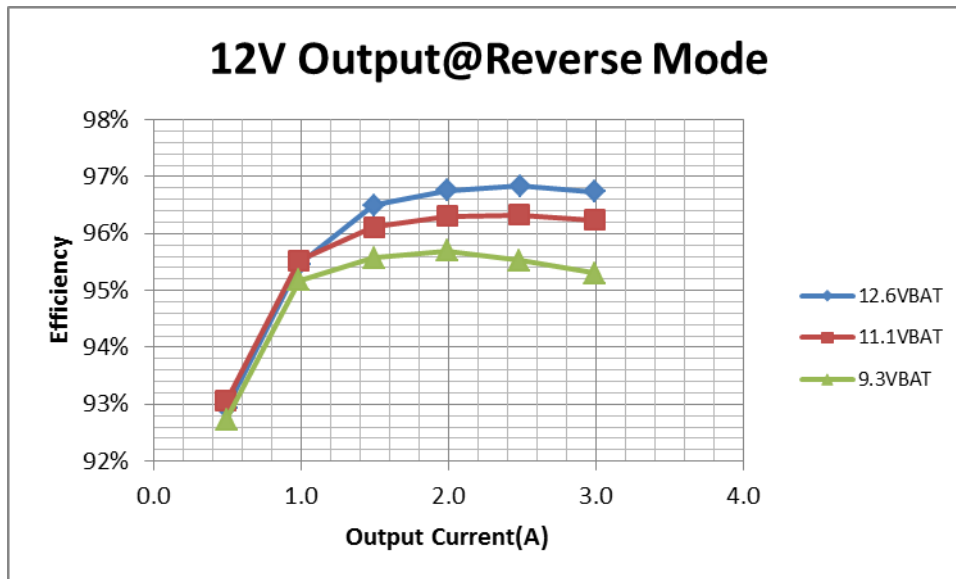

2.1.9 15V Output in Reverse Mode

$V_{BAT}(V)$	$I_{BAT}(A)$	$V_o(V)$	$I_o(A)$	Efficiency
9.272	0.885	15.213	0.495	91.77%
9.244	1.727	15.205	0.989	94.21%
9.215	2.607	15.193	1.497	94.69%
9.187	3.473	15.181	1.991	94.75%
9.158	4.356	15.165	2.486	94.52%
9.127	5.279	15.146	2.994	94.13%
11.077	0.737	15.210	0.494	92.06%
11.053	1.435	15.201	0.988	94.70%
11.029	2.162	15.191	1.497	95.38%


11.006	2.874	15.180	1.991	95.56%
10.982	3.594	15.169	2.485	95.52%
10.957	4.344	15.153	2.994	95.33%
12.580	0.647	15.211	0.495	92.51%
12.559	1.259	15.203	0.989	95.10%
12.538	1.893	15.194	1.497	95.85%
12.518	2.513	15.184	1.992	96.16%
12.497	3.140	15.170	2.485	96.08%
12.475	3.789	15.159	2.995	96.06%

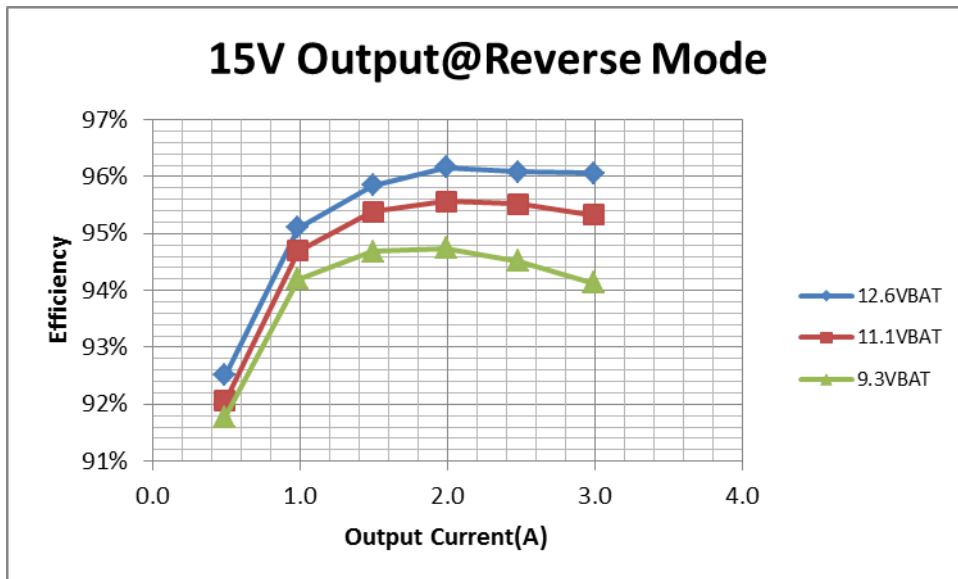

2.1.9 20V Output in Reverse Mode

V_{BAT} (V)	I_{BAT} (A)	V_o (V)	I_o (A)	Efficiency
9.262	1.200	20.235	0.495	90.12%
9.224	2.338	20.224	0.988	92.66%
9.184	3.536	20.206	1.496	93.10%
9.145	4.723	20.188	1.990	93.03%
9.125	5.349	20.174	2.243	92.69%
11.068	0.999	20.235	0.495	90.59%
11.037	1.941	20.224	0.983	92.81%
11.005	2.925	20.211	1.497	94.01%
10.973	3.892	20.195	1.991	94.16%
10.956	4.396	20.186	2.244	94.07%
12.573	0.875	20.235	0.495	91.05%


12.545	1.700	20.225	0.989	93.80%
12.517	2.557	20.214	1.497	94.56%
12.489	3.397	20.199	1.991	94.81%
12.474	3.833	20.193	2.244	94.79%

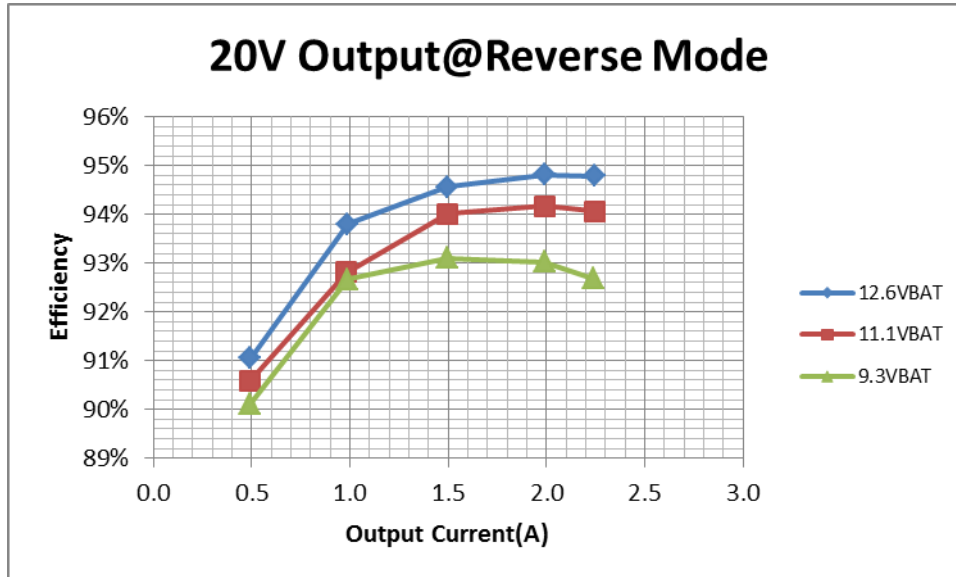

2.1.11 USB Type A

V _{BAT} (V)	I _{BAT} (A)	V _{VBUS} (V)	I _{VBUS} (A)	Efficiency
9.304	0.063	5.140	0.092	80.89%
9.299	0.297	5.108	0.495	91.48%
9.293	0.586	5.070	0.990	92.17%
9.286	0.894	5.028	1.498	90.72%
9.279	1.203	4.988	1.991	88.97%
9.278	1.271	4.978	2.096	88.51%
11.103	0.054	5.143	0.090	77.19%
11.099	0.255	5.108	0.495	89.50%
11.094	0.497	5.068	0.988	90.81%
11.088	0.756	5.028	1.498	89.85%
11.083	1.015	4.985	1.991	88.28%
11.081	1.072	4.978	2.096	87.84%
12.603	0.047	5.140	0.092	79.66%
12.599	0.226	5.108	0.495	88.67%
12.595	0.440	5.068	0.990	90.53%
12.590	0.669	5.028	1.498	89.42%
12.585	0.898	4.985	1.991	87.80%

12.584	0.949	4.978	2.096	87.37%
--------	-------	-------	-------	--------

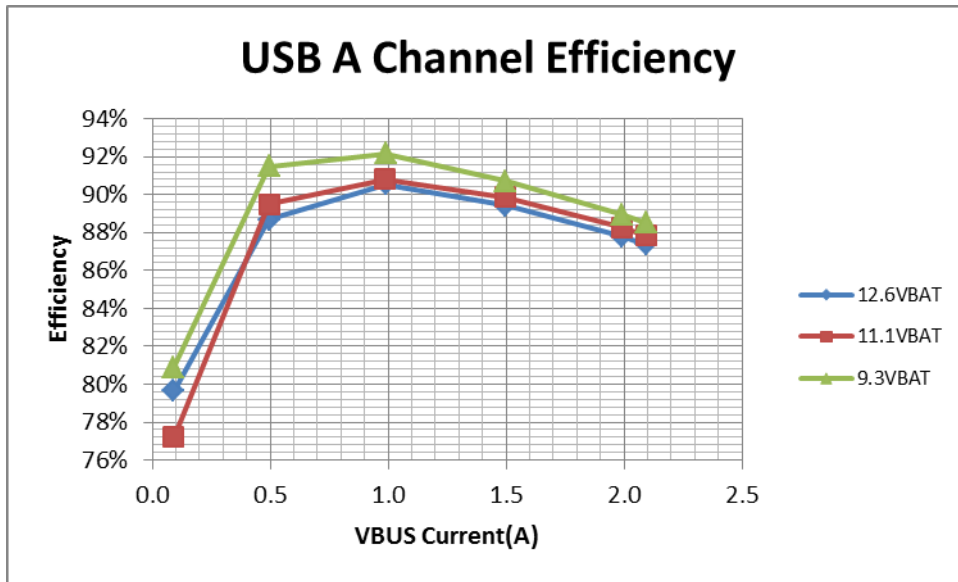


2.2 Standby Current


PARAMETER		TEST CONDITION	MIN	TYP	MAX	UNIT
I _{STD}	Standby current	V _{BAT} =9.3V, Connectors Unattached		100		uA
		V _{BAT} =11.1V, Connectors Unattached		102		uA
		V _{BAT} =12.6V, Connectors Unattached		103		uA

2.3 Start up


2.3.1 Forward Mode

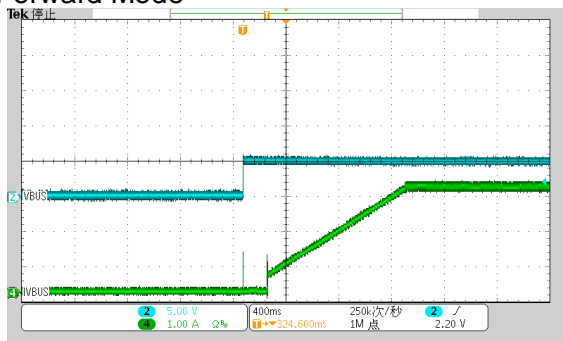

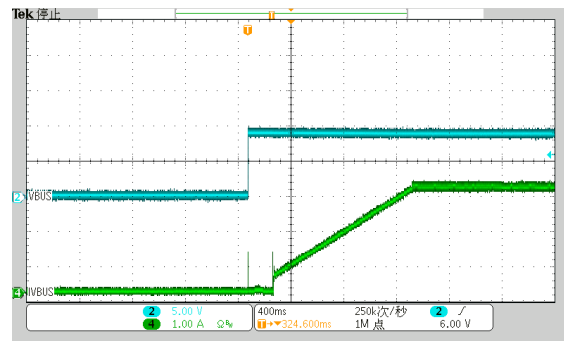
5V Input
CH2: Vin 5V/Div
CH4: Input Current 1A/Div



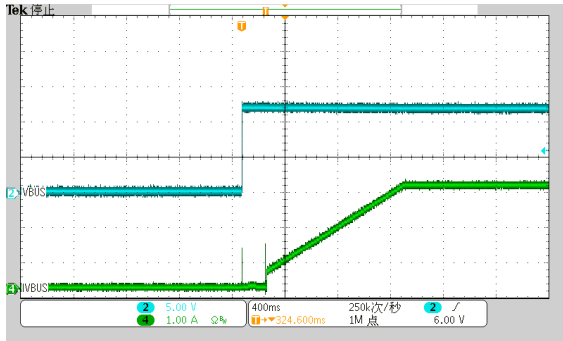
9V Input
CH2: Vin 5V/Div
CH4: Input Current 1A/Div



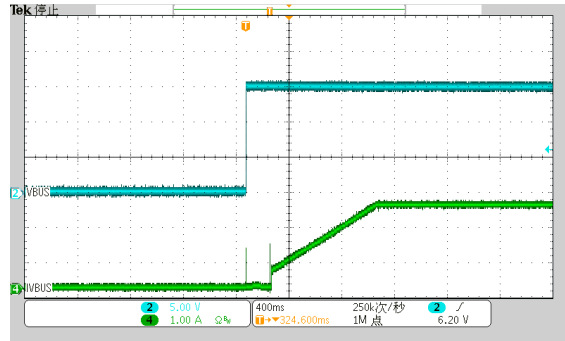12V Input
CH2: Vin 5V/Div
CH4: Input Current 1A/Div




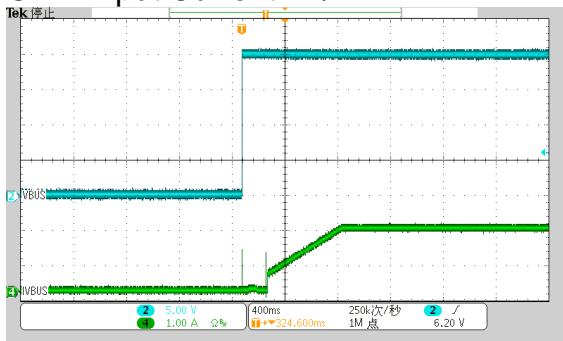15V Input
CH2: Vin 5V/Div
CH4: Input Current 1A/Div




20V Input
CH2: Vin 5V/Div
CH4: Input Current 1A/Div


2.3.2 Reverse Mode

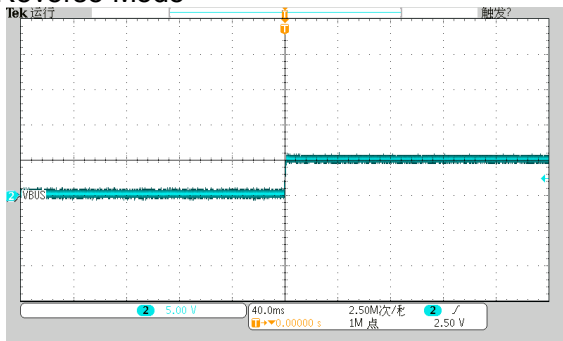


5V Output
CH2: Vo 5V/Div

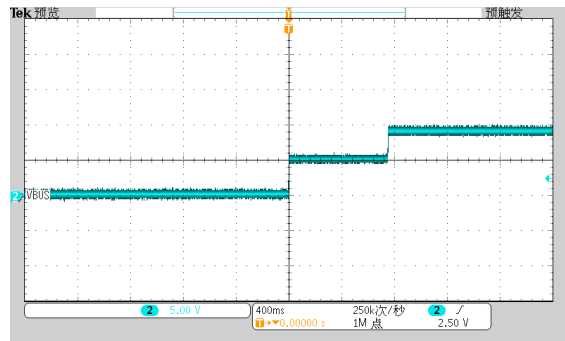


9V Output
CH2: Vo 5V/Div

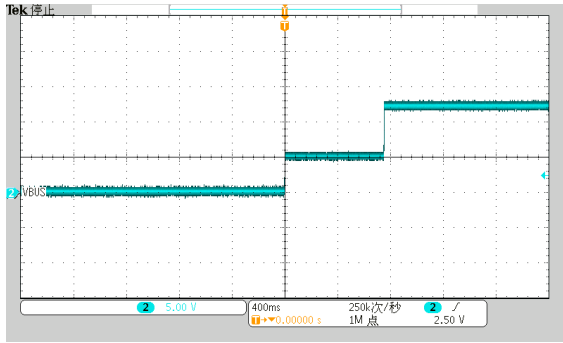


12V Output
CH2: Vo 5V/Div

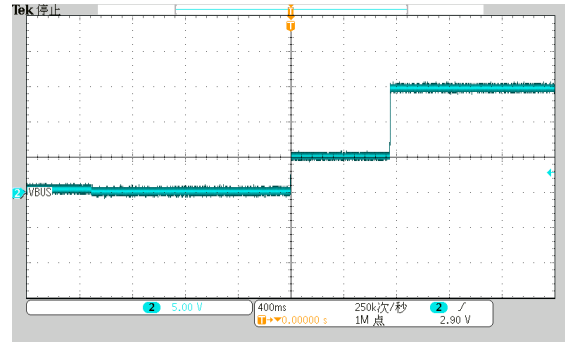


14.5V Output
CH2: Vo 5V/Div

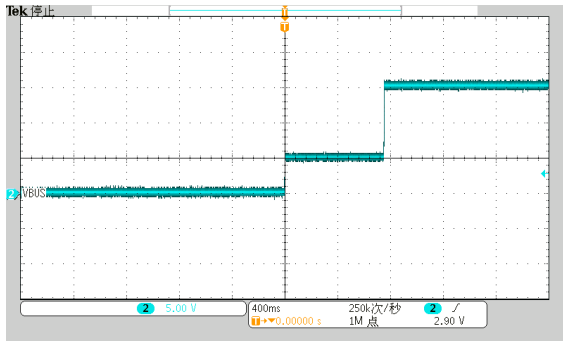


15V Output
CH2: Vo 5V/Div

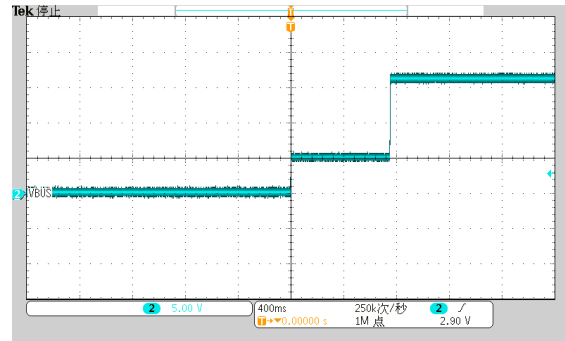

16V Output
CH2: Vo 5V/Div

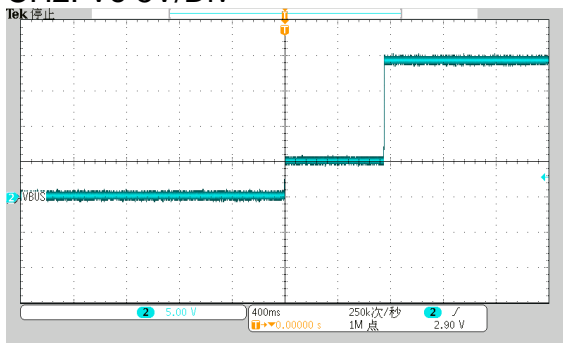


19V Output
CH2: Vo 5V/Div

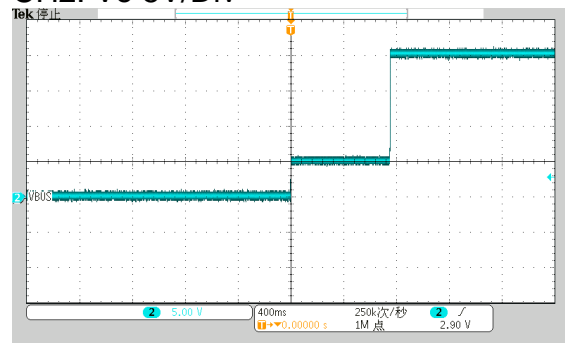


20V Output
CH2: Vo 5V/Div

2.4 Output Voltage Ripple in Reverse Mode


2.4.1 Output Voltage: 5V

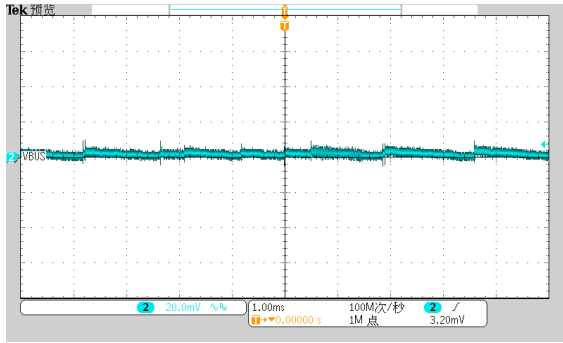

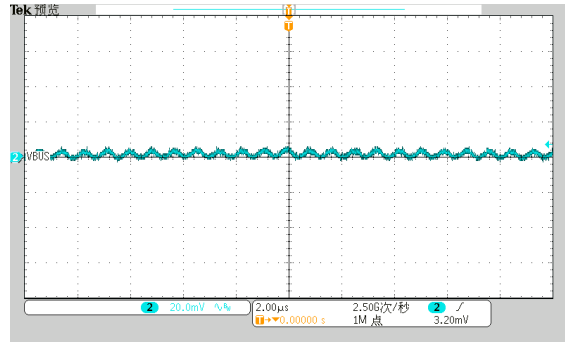
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



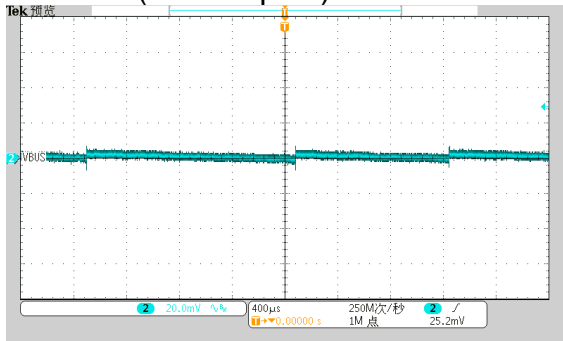
$V_{BAT}=9.3V$ and Full Load
CH2: V_o (AC Coupled) 20mV/Div



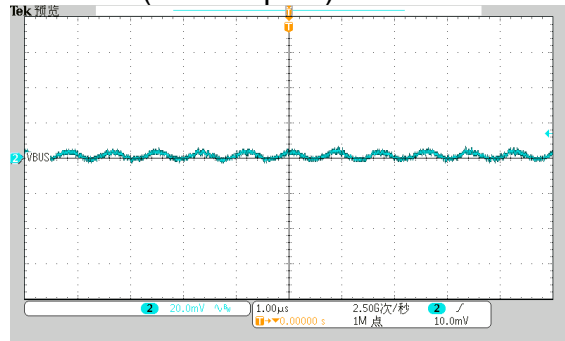
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



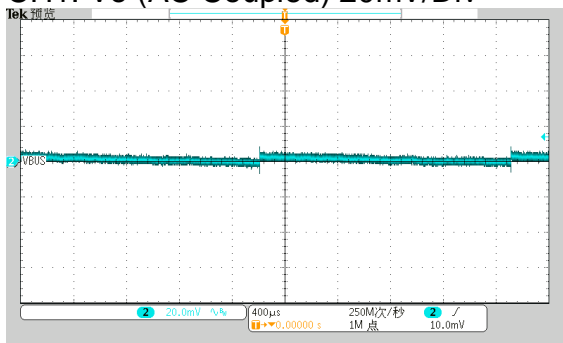$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 20mV/Div




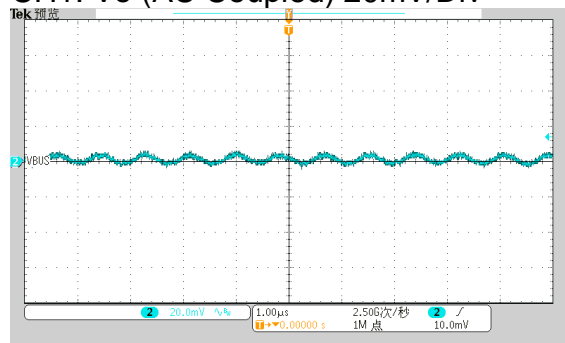$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 20mV/Div


2.4.2 Output Voltage: 9V

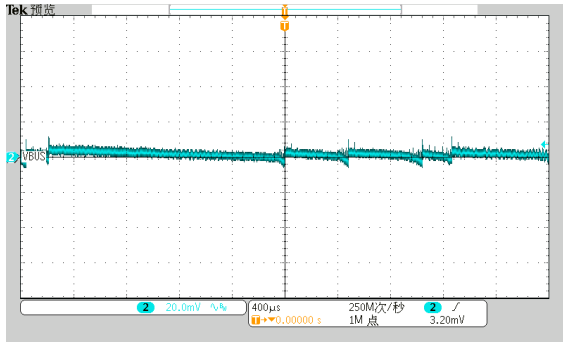

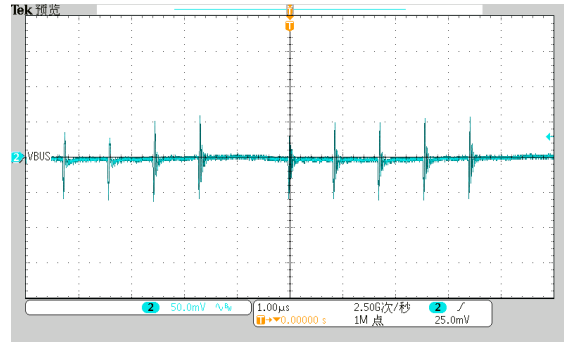
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



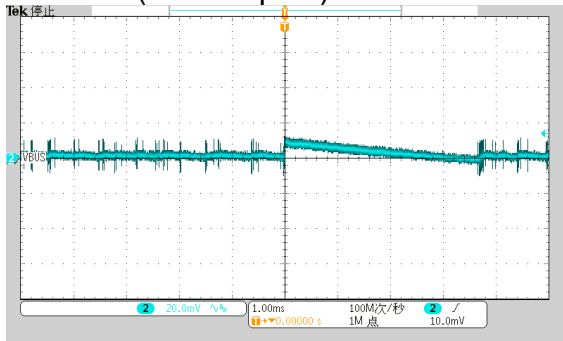
$V_{BAT}=9.3V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



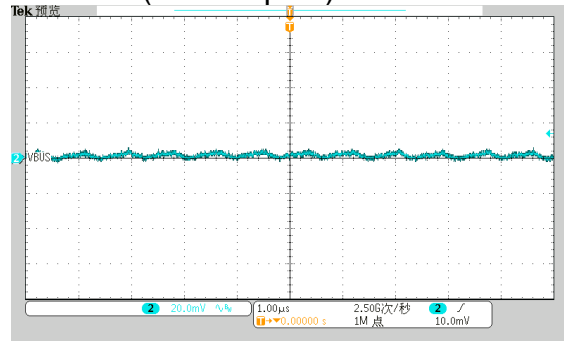
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



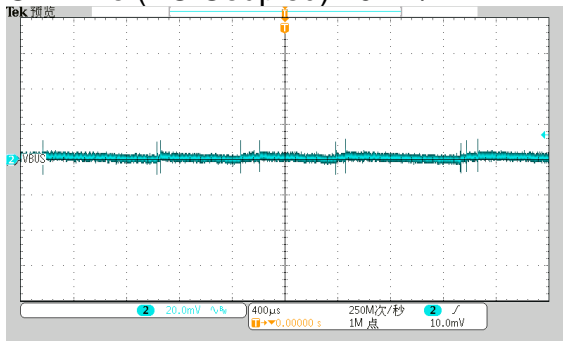$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 20mV/Div




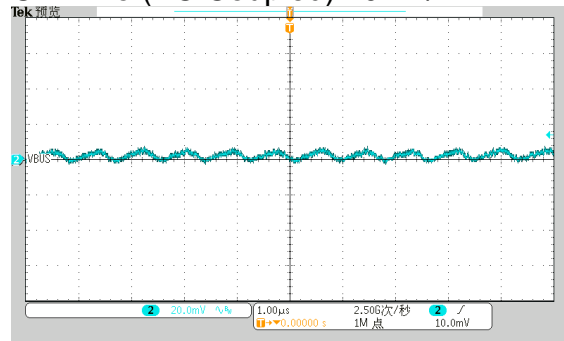$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 20mV/Div


2.4.3 Output Voltage: 12V

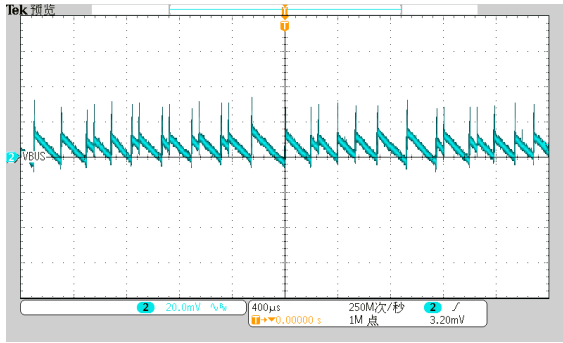

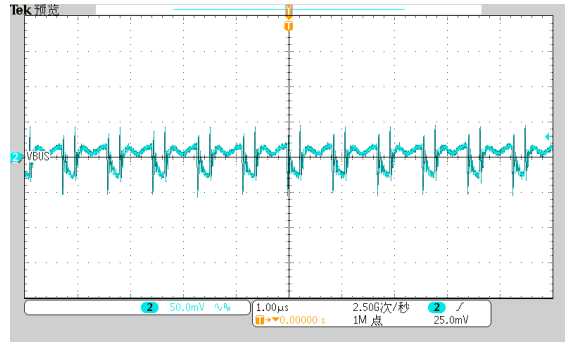
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



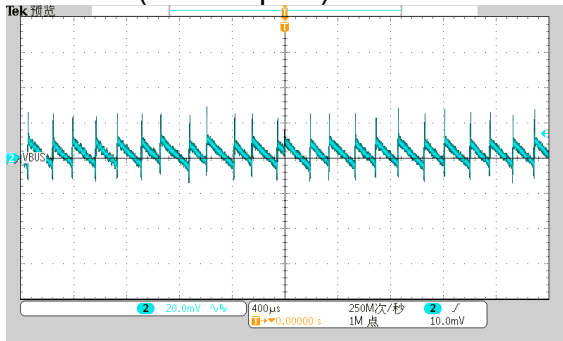
$V_{BAT}=9.3V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



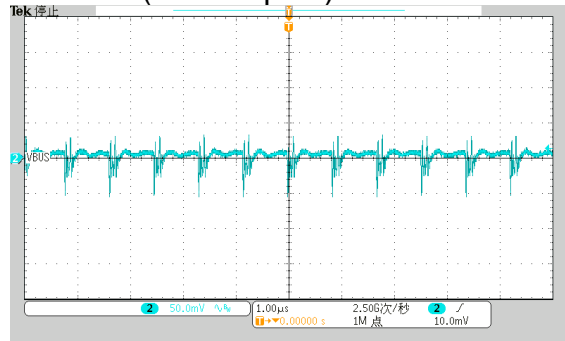
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



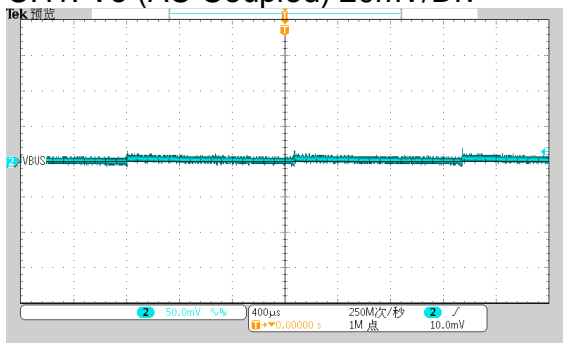$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div




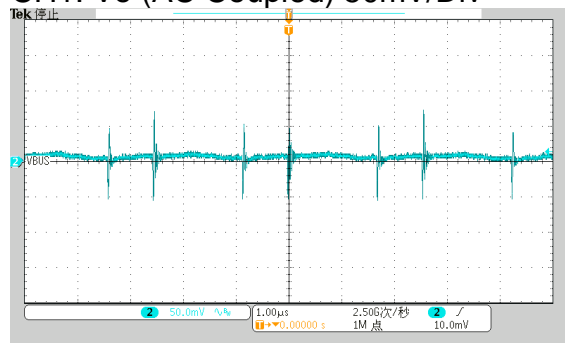$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 50mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div


2.4.4 Output Voltage: 14.5V

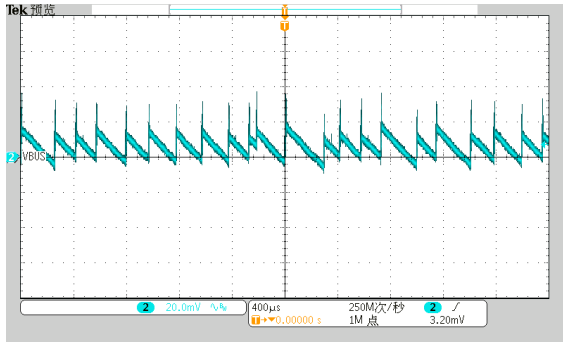

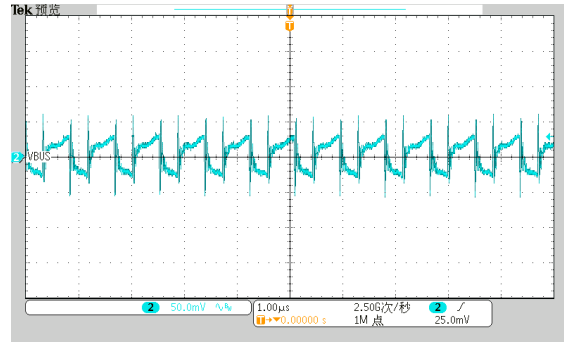
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



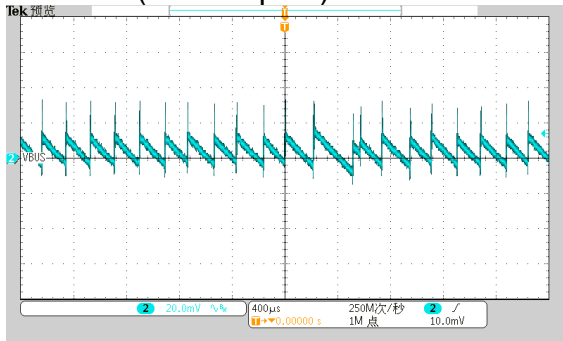
$V_{BAT}=9.3V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



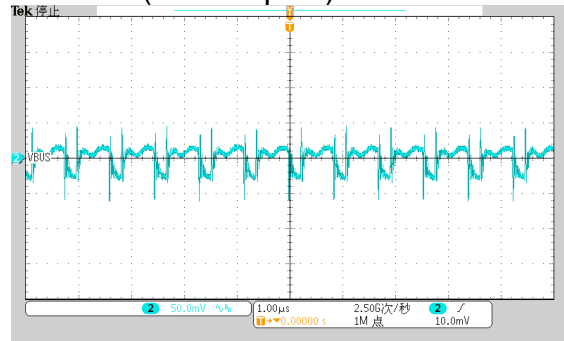
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



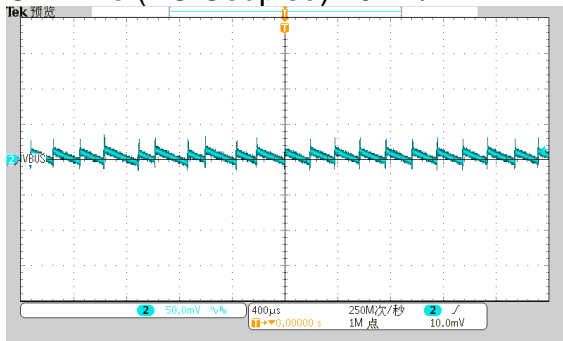$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div




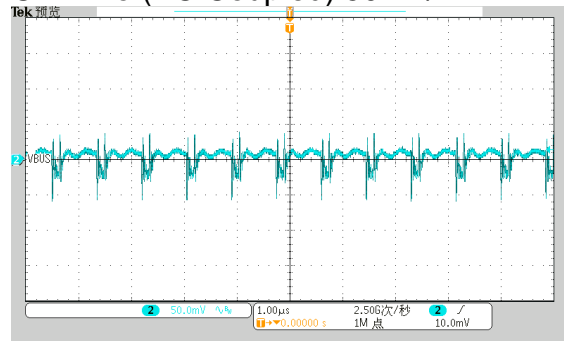$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 50mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div


2.4.5 Output Voltage: 15V

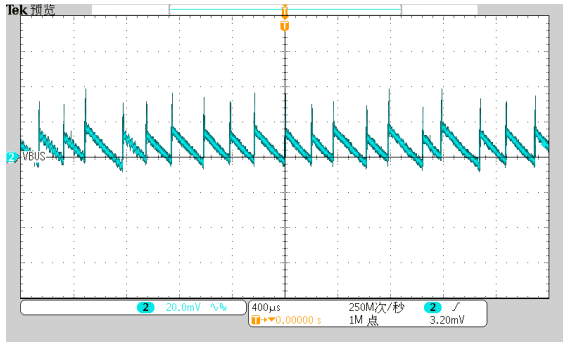

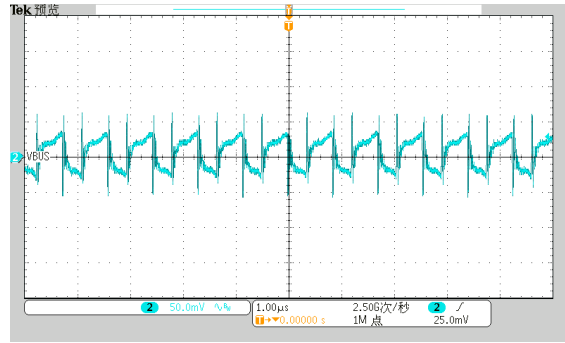
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



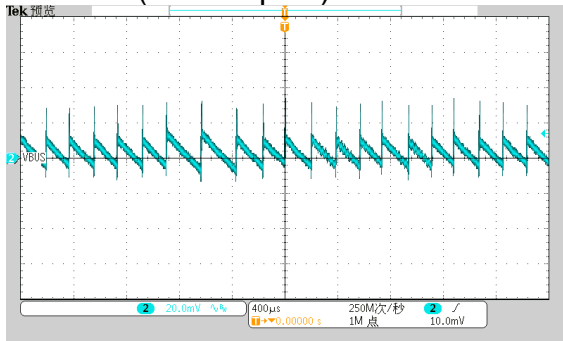
$V_{BAT}=9.3V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



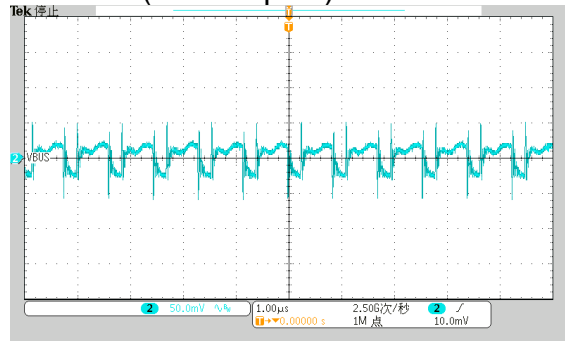
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



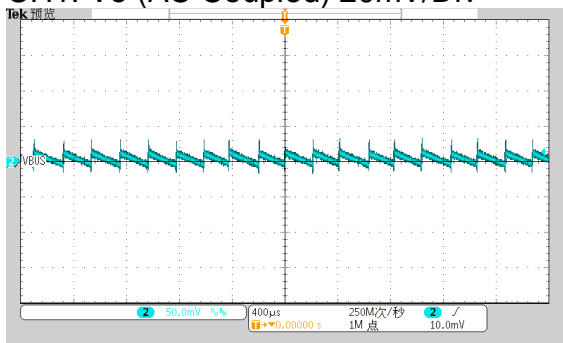$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div




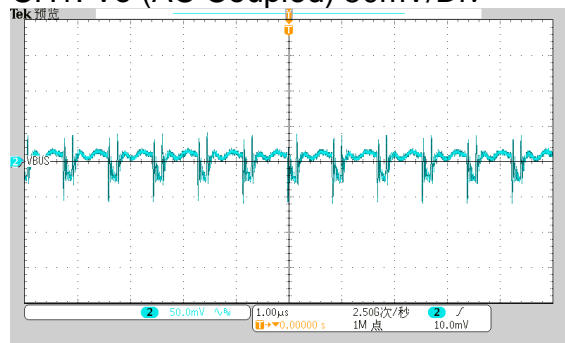$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 50mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div


2.4.6 Output Voltage: 16V

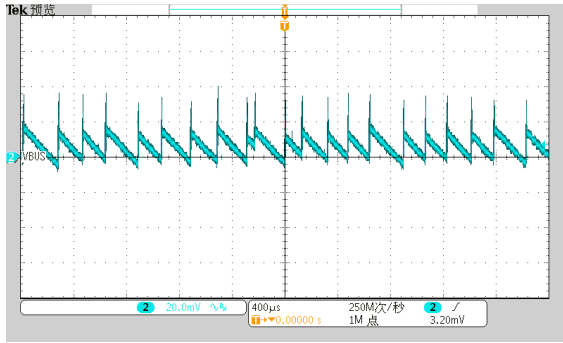

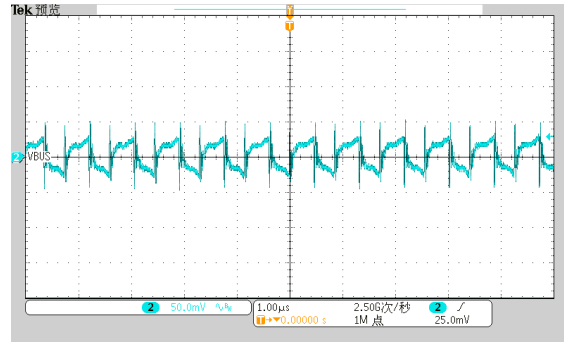
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



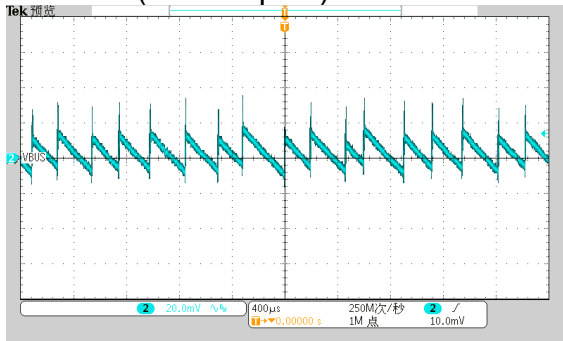
$V_{BAT}=9.3V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



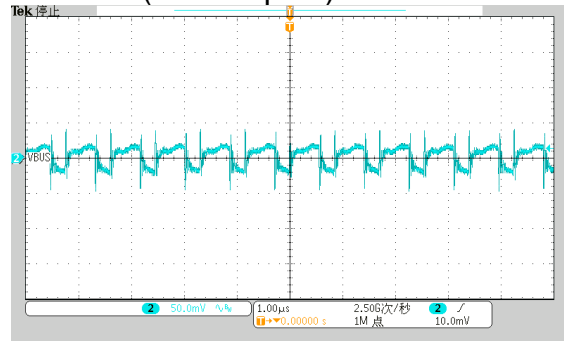
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



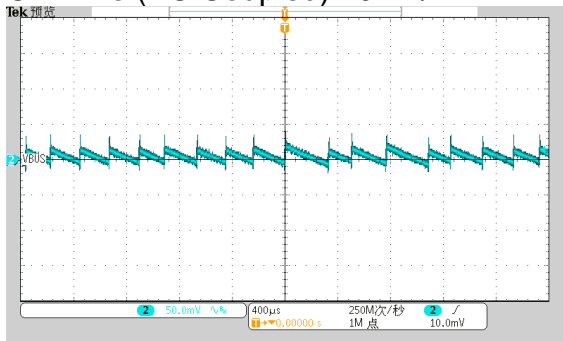$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div




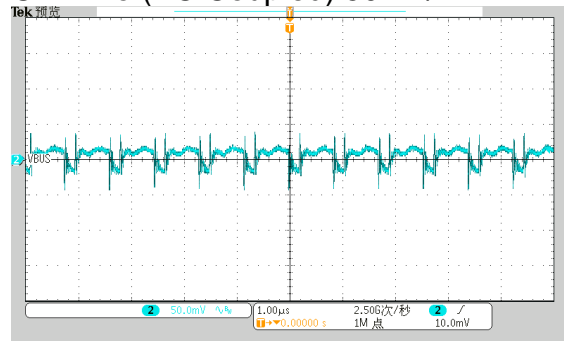$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 50mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div


2.4.7 Output Voltage: 19V

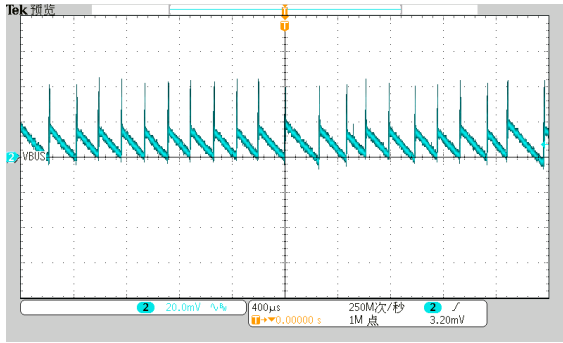

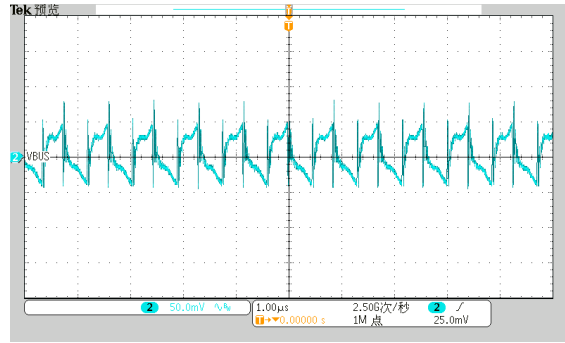
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



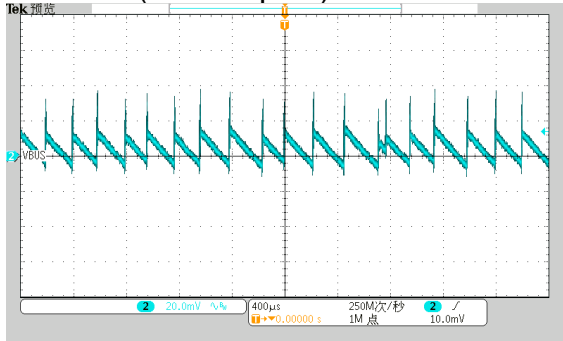
$V_{BAT}=9.3V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



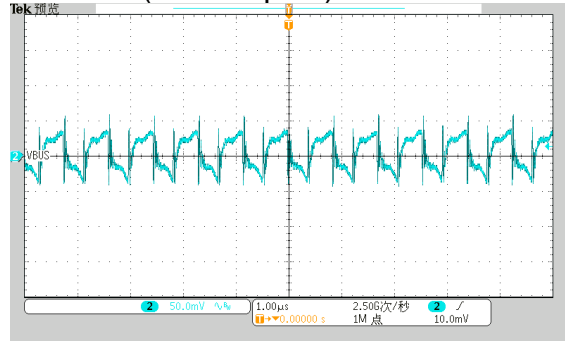
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



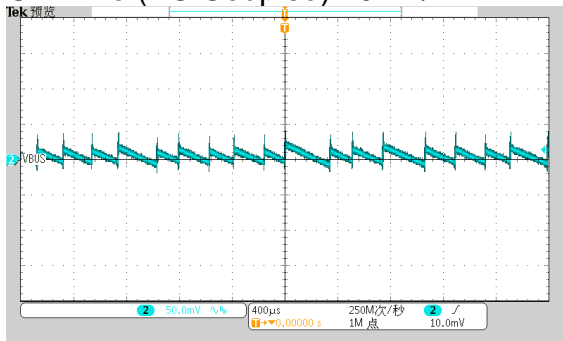$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div




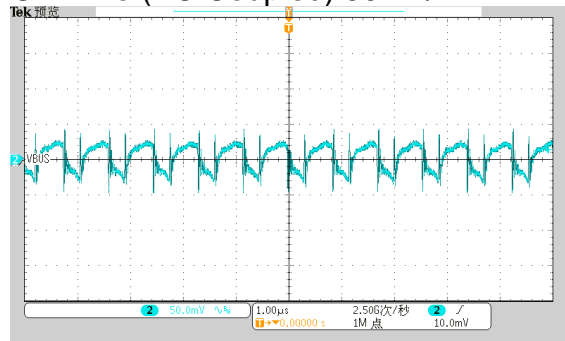$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 50mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div


2.4.8 Output Voltage: 20V

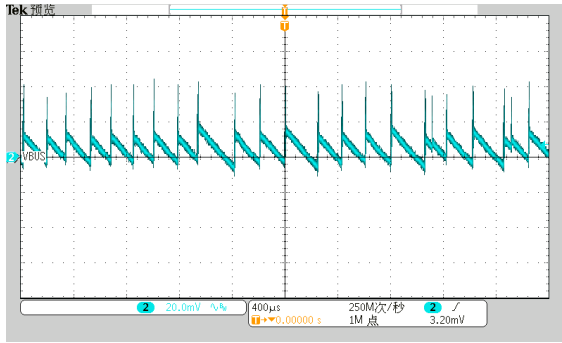

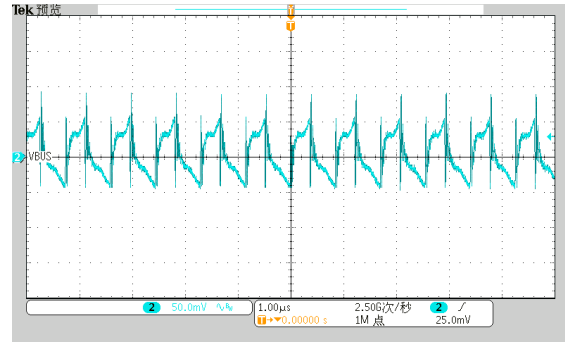
$V_{BAT}=9.3V$ and No Load
CH2: V_o (AC Coupled) 20mV/Div



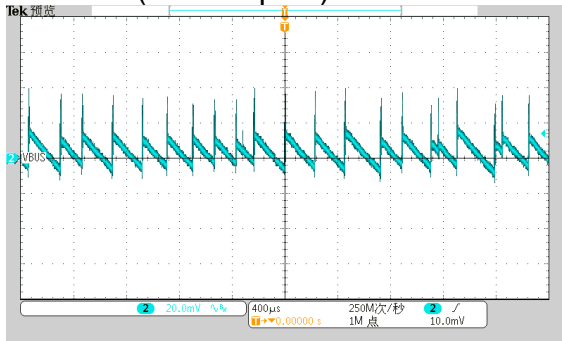
$V_{BAT}=9.3V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



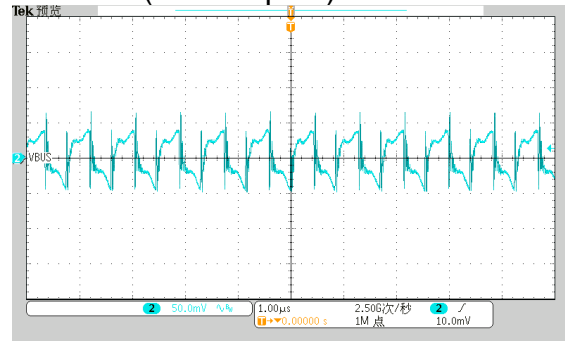
$V_{BAT}=11.1V$ and No Load
CH1: V_o (AC Coupled) 20mV/Div



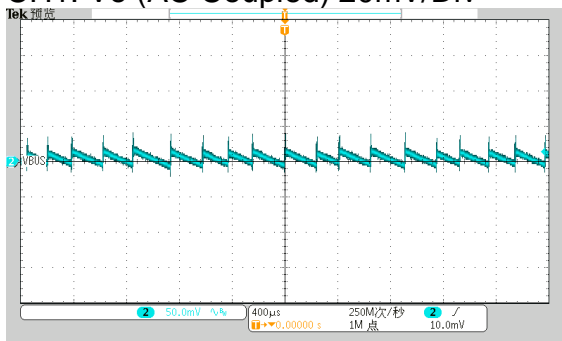$V_{BAT}=11.1V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div



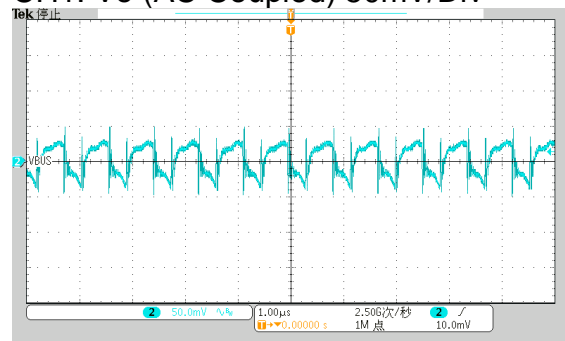
$V_{BAT}=12.6V$ and No Load
CH1: V_o (AC Coupled) 50mV/Div




$V_{BAT}=12.6V$ and Full Load
CH1: V_o (AC Coupled) 50mV/Div

2.5 Dynamic Performance

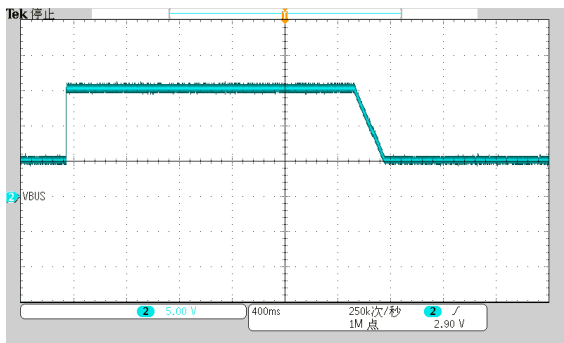
2.5.1 Output Voltage Transition in Reverse Mode



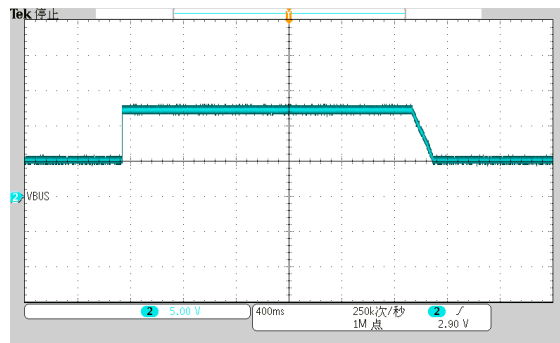User Command: 5V↔15V
 $V_{BAT}=11.1V$ and No Load
 CH2: V_o 5V/Div



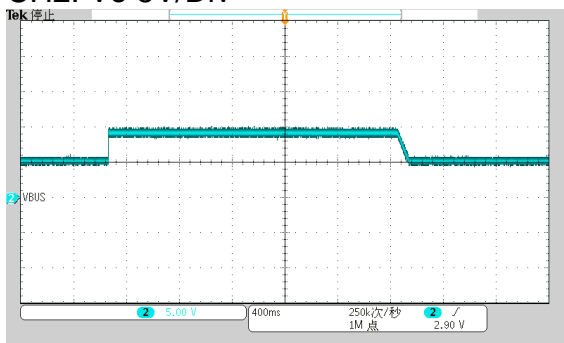
User Command: 5V↔12V
 $V_{BAT}=11.1V$ and No Load
 CH2: V_o 5V/Div




User Command: 5V↔9V
 $V_{BAT}=11.1V$ and No Load
 CH2: V_o 5V/Div

2.5.2 Output Current Transition in Reverse Mode


$V_o=5V$ & 100mA/us Current slew rate

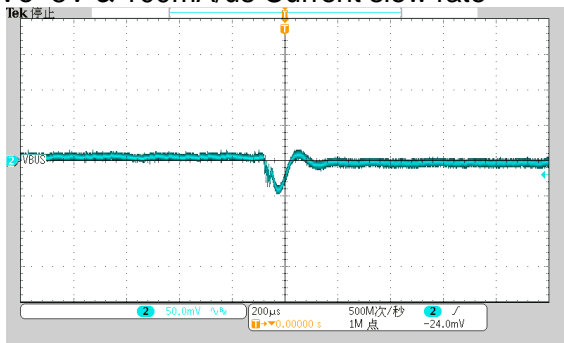

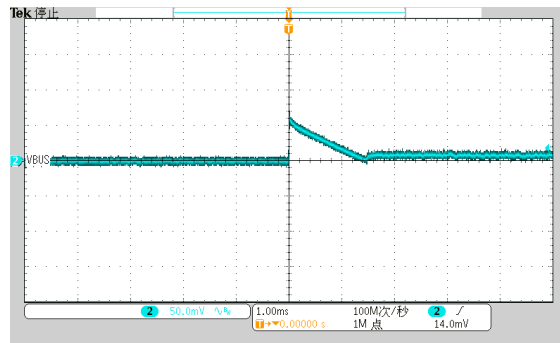
$V_{BAT}=9.3V$ and 0 to 25% load
 CH2: V_o (AC Coupled) 50mV/Div



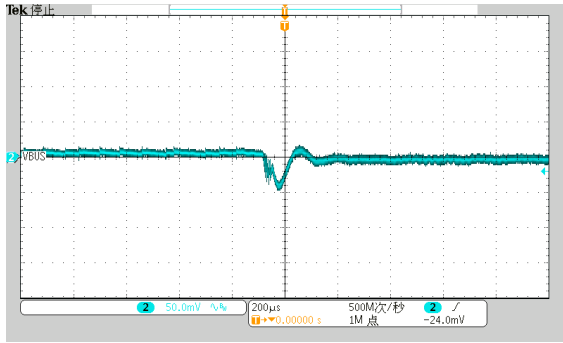
$V_{BAT}=9.3V$ and 25% to 0 load
 CH2: V_o (AC Coupled) 50mV/Div



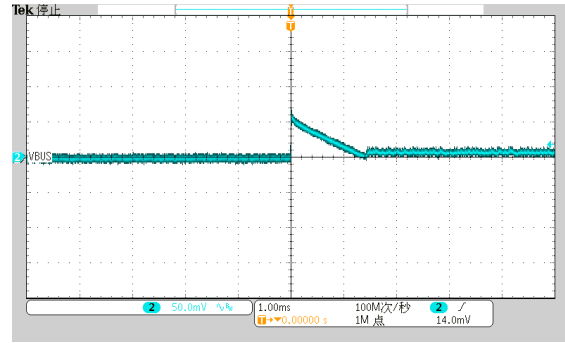
VBAT=11.1V and 0 to 25% load
CH2: Vo (AC Coupled) 50mV/Div



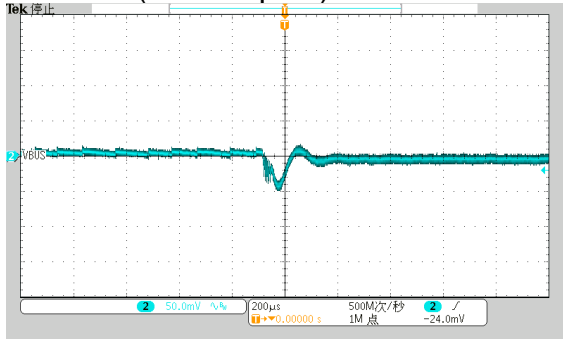
VBAT=11.1V and 25% to 0 load
CH2: Vo (AC Coupled) 50mV/Div



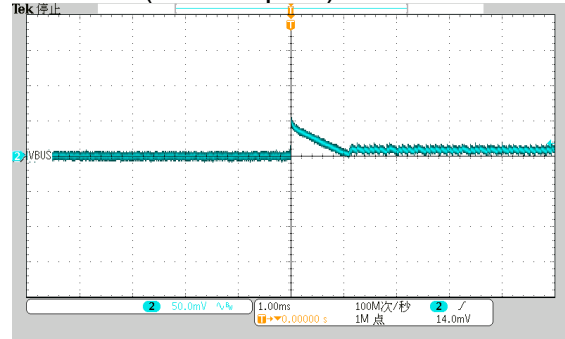
VBAT=12.6V and 0 to 25% load
CH2: Vo (AC Coupled) 50mV/Div



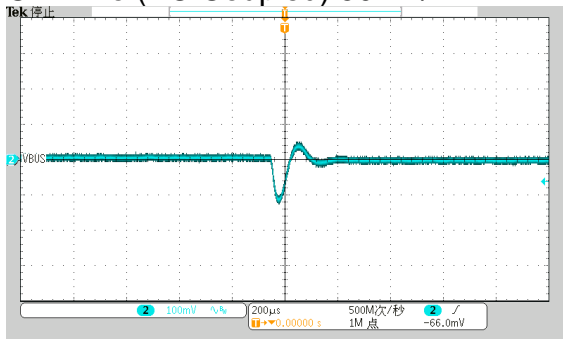
VBAT=12.6V and 25% to 0 load
CH2: Vo (AC Coupled) 50mV/Div



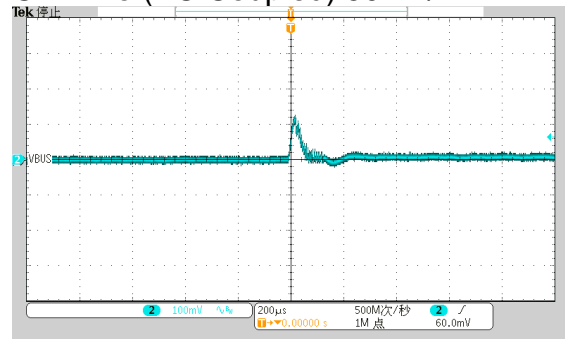
VBAT=9.3V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



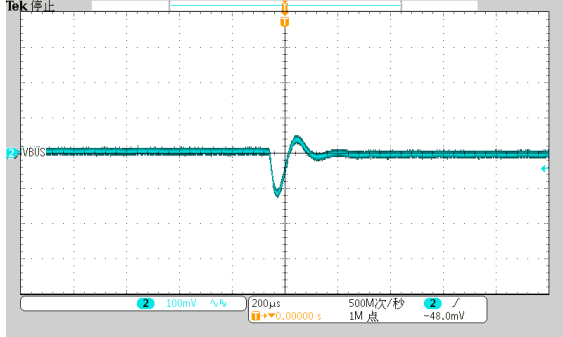
VBAT=9.3V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



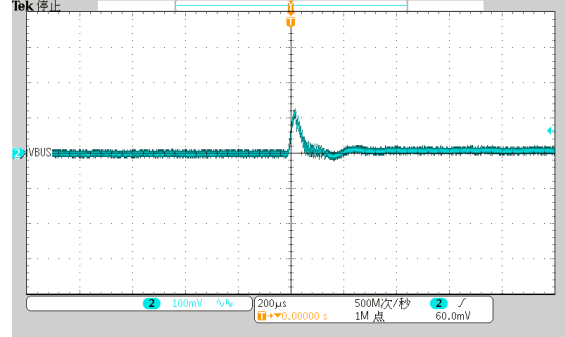
VBAT=11.1V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



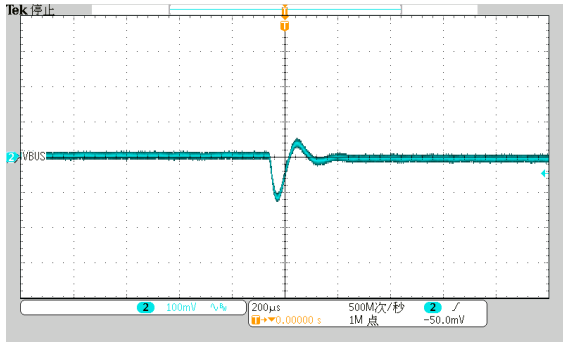
VBAT=11.1V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



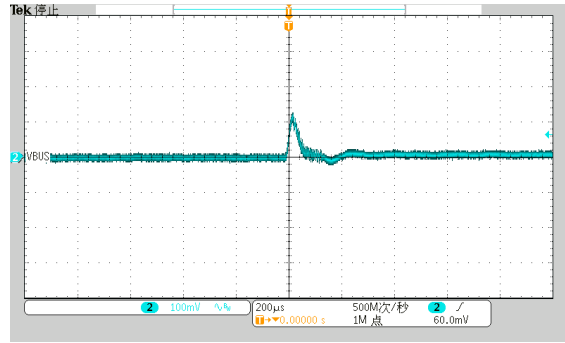
VBAT=12.6V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



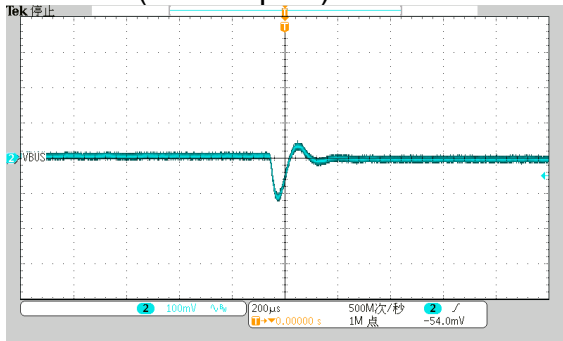
VBAT=12.6V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



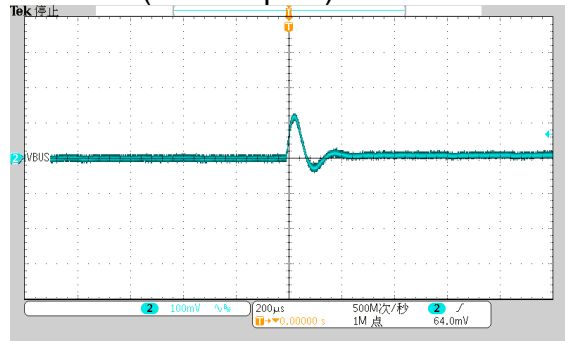
VBAT=9.3V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



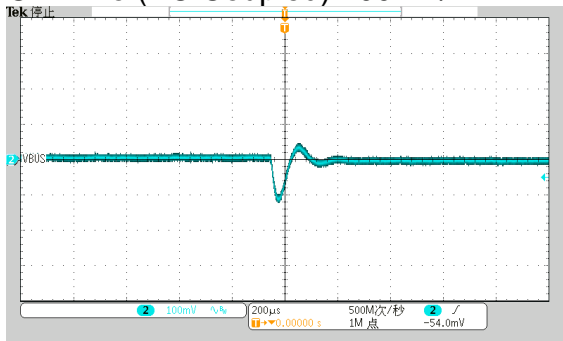
VBAT=9.3V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



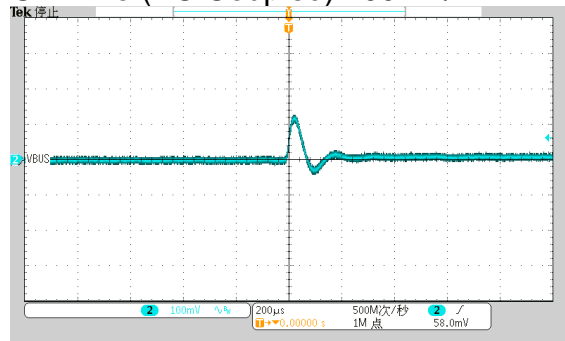
VBAT=11.1V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



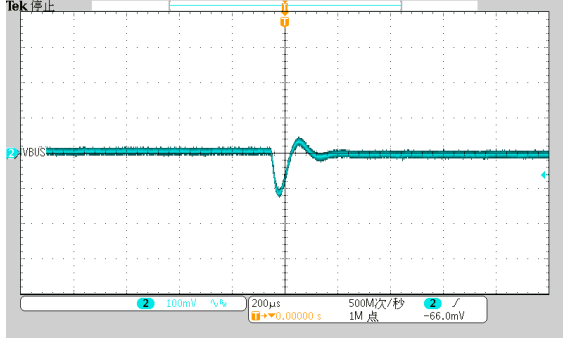
VBAT=11.1V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



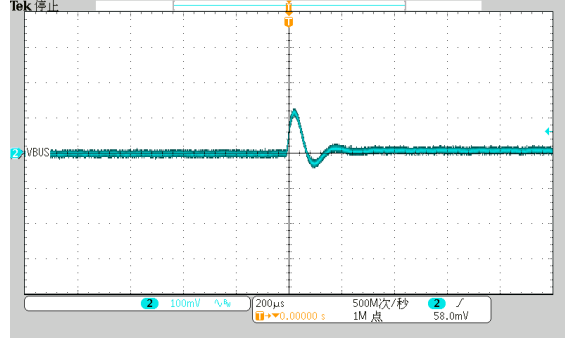
VBAT=12.6V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



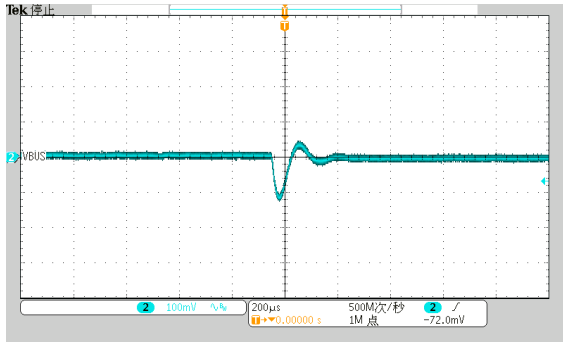
VBAT=12.6V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



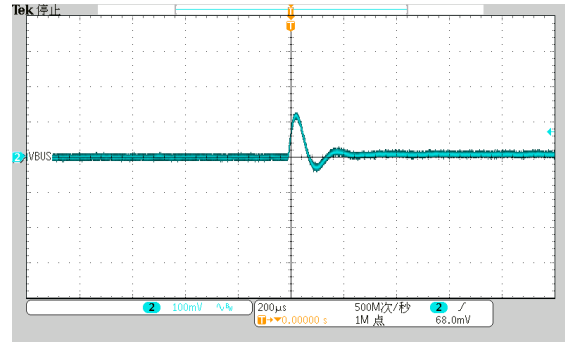
VBAT=9.3V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div



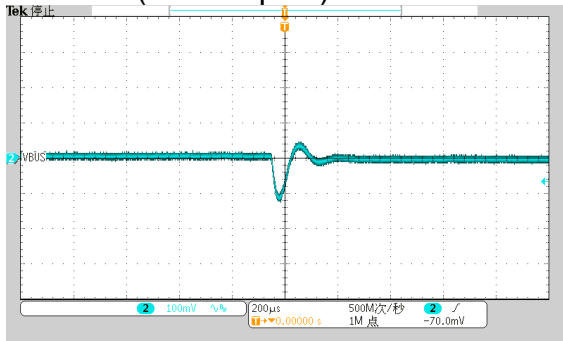
VBAT=9.3V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



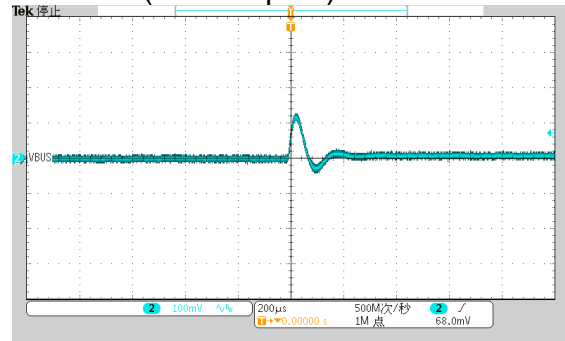
VBAT=11.1V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div



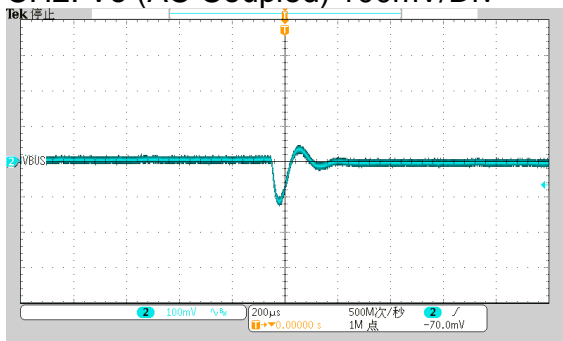VBAT=11.1V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div




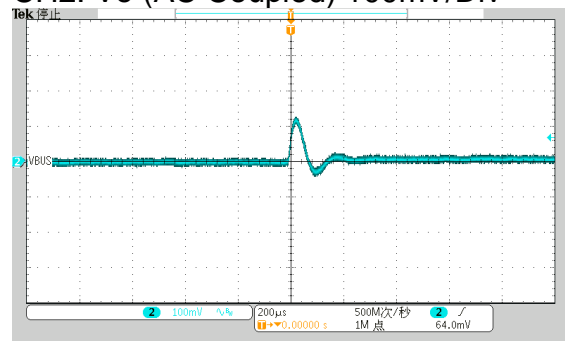VBAT=12.6V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div




VBAT=12.6V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div


Vo=9V & 100mA/us Current slew rate

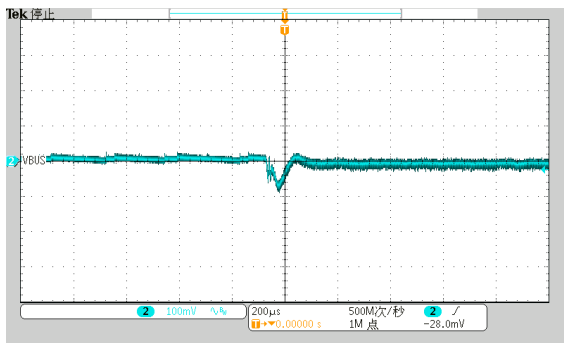

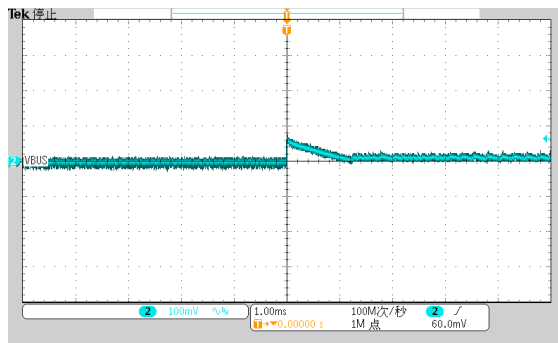
$V_{BAT}=9.3V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



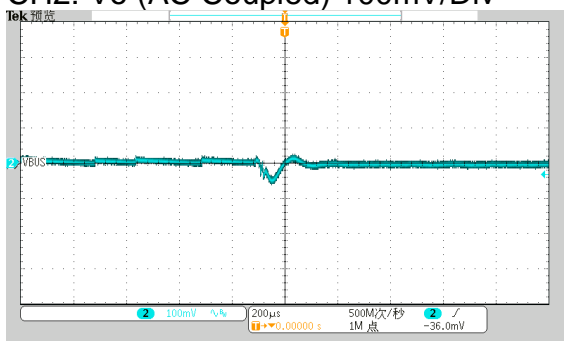
$V_{BAT}=9.3V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



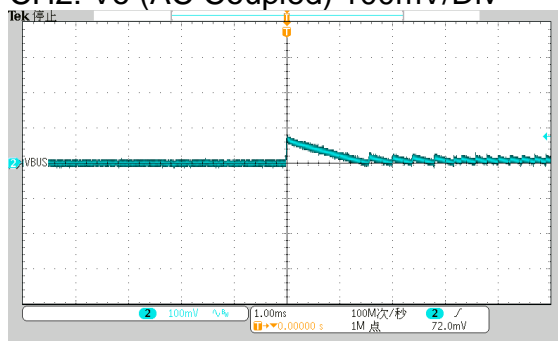
$V_{BAT}=11.1V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



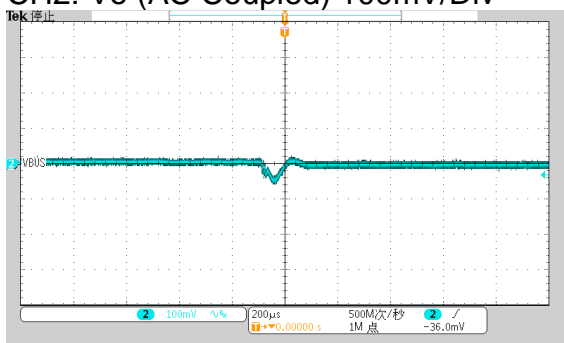
$V_{BAT}=11.1V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



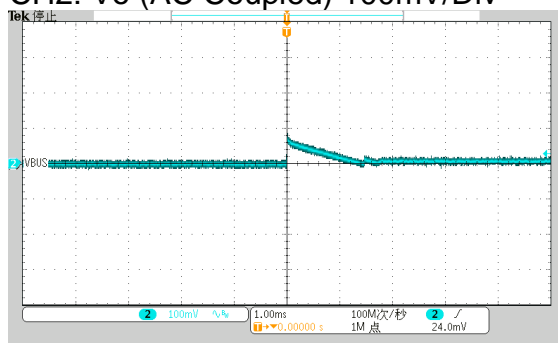
$V_{BAT}=12.6V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



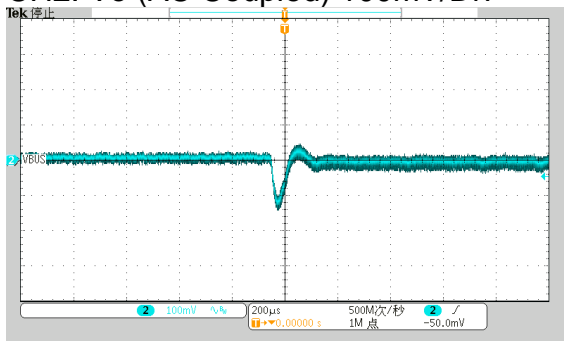
$V_{BAT}=12.6V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



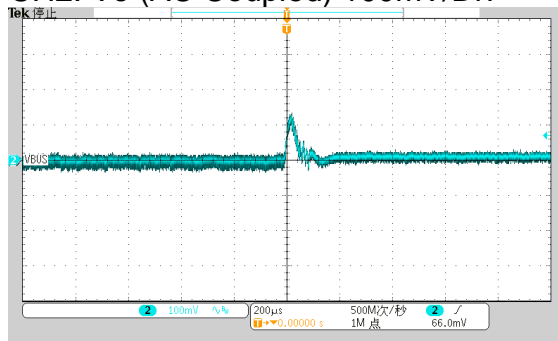
$V_{BAT}=12.6V$ and 25% to 50% load
CH2: V_o (AC Coupled) 100mV/Div



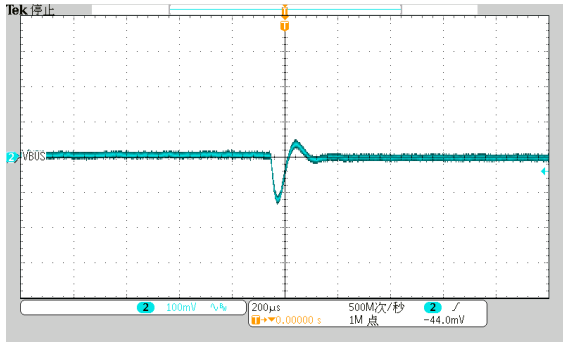
$V_{BAT}=9.3V$ and 50% to 25% load
CH2: V_o (AC Coupled) 100mV/Div



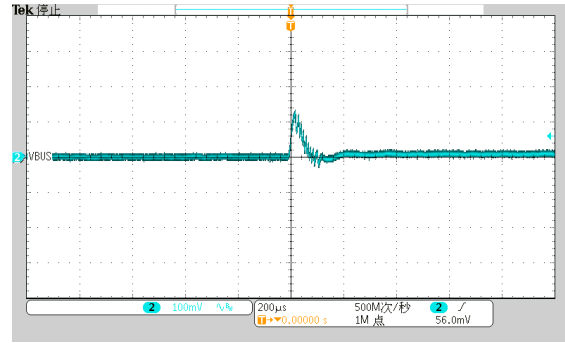
VBAT=11.1V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



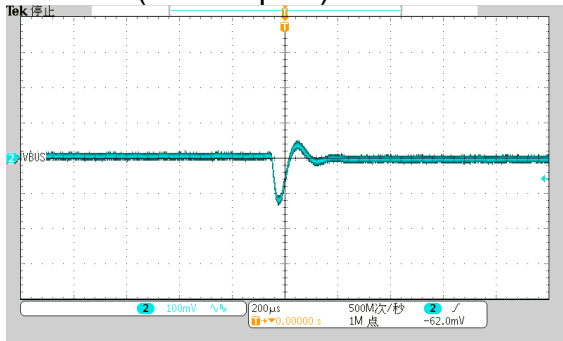
VBAT=11.1V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



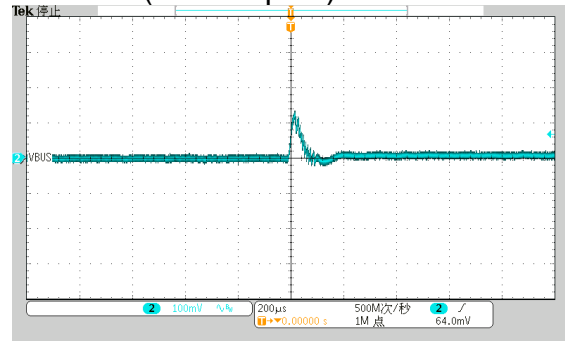
VBAT=12.6V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



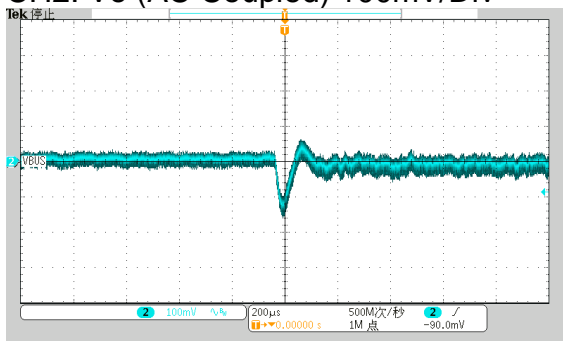
VBAT=12.6V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



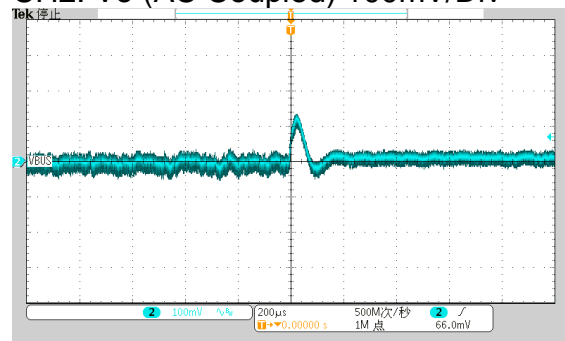
VBAT=9.3V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



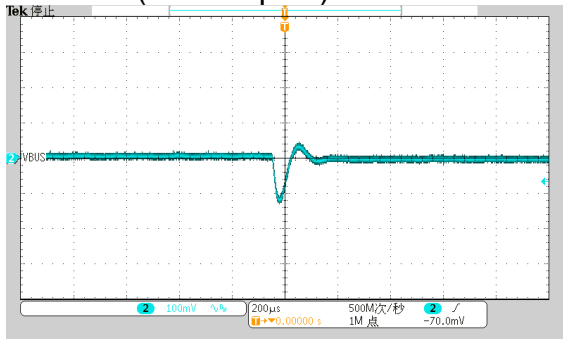
VBAT=9.3V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



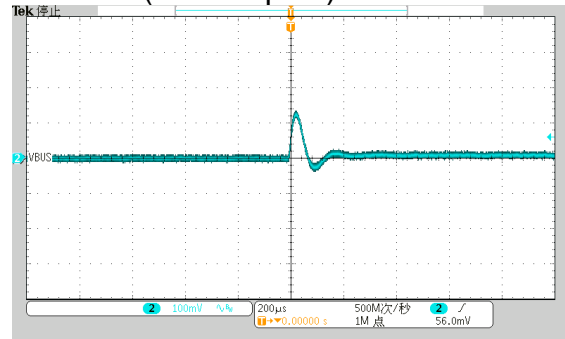
VBAT=11.1V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



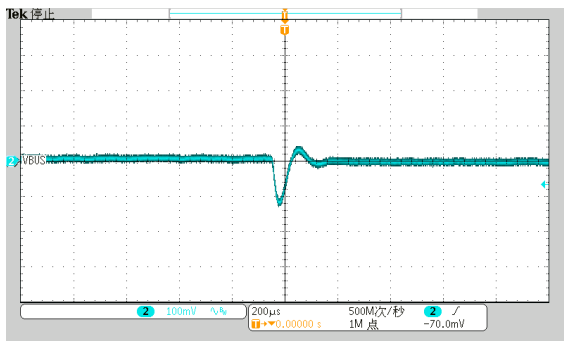
VBAT=11.1V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



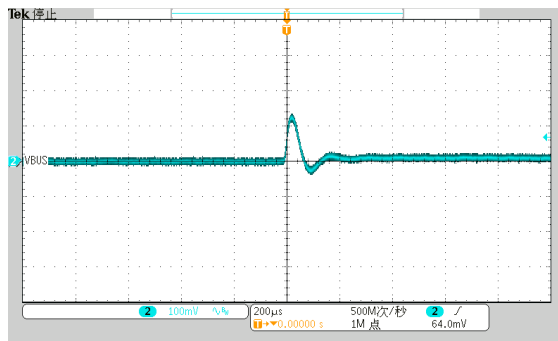
VBAT=12.6V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



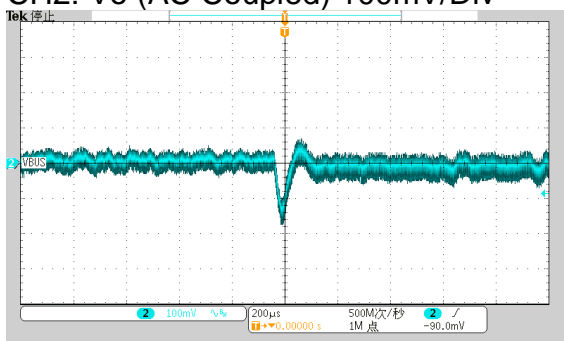
VBAT=12.6V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



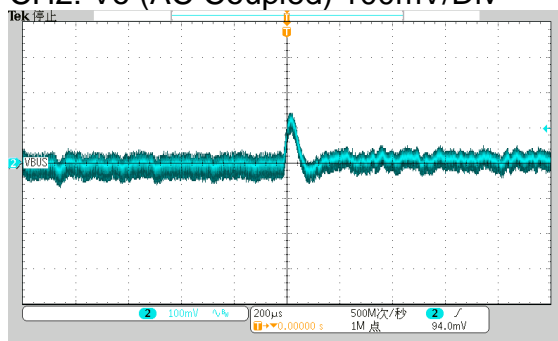
VBAT=9.3V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div



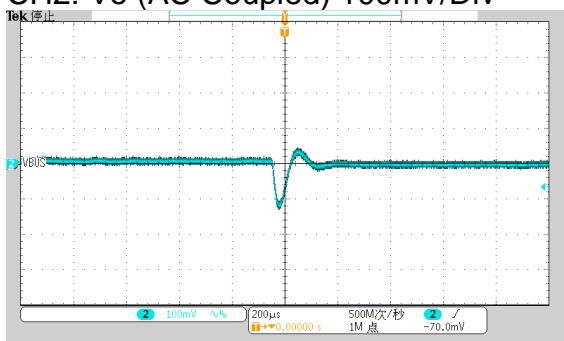
VBAT=9.3V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



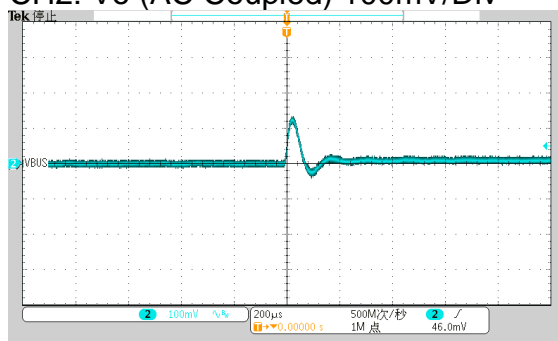
VBAT=11.1V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div



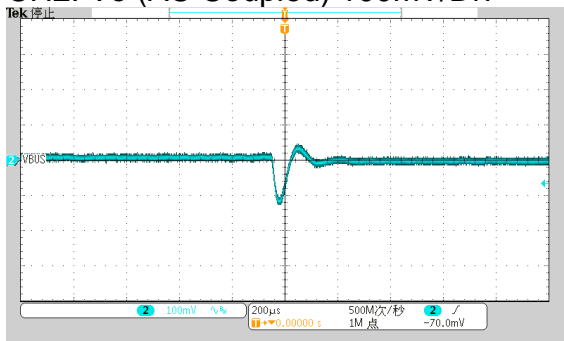VBAT=11.1V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div





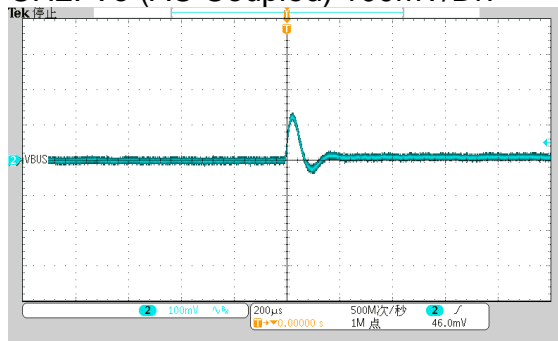VBAT=12.6V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div




VBAT=12.6V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div


Vo=12V & 100mA/us Current slew rate

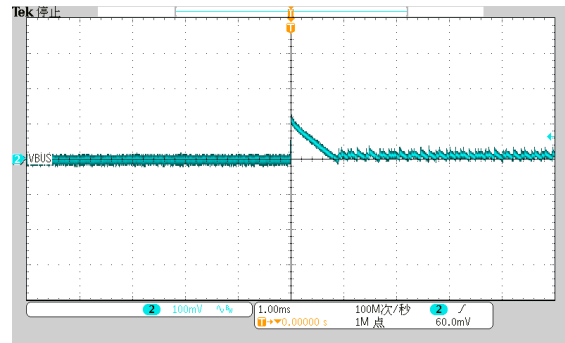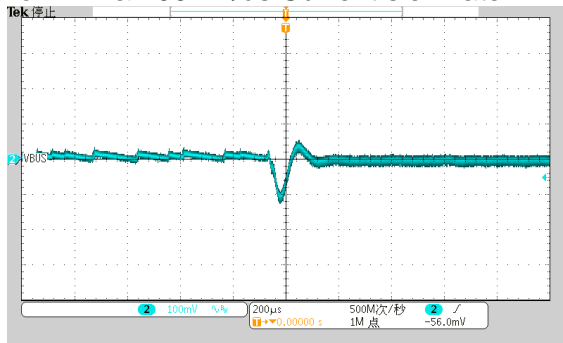

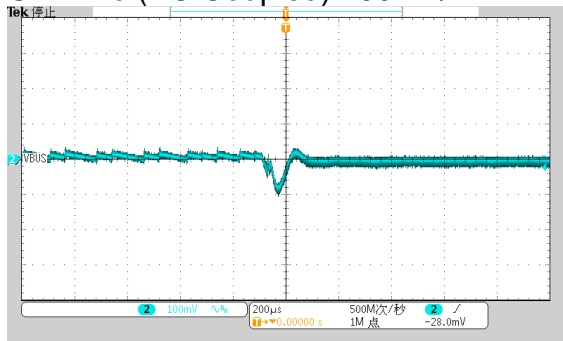
**V_{BAT}=9.3V and 0 to 25% load
CH2: Vo (AC Coupled) 100mV/Div**



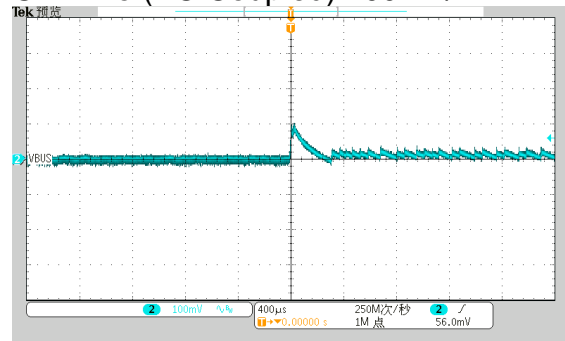
**V_{BAT}=9.3V and 25% to 0 load
CH2: Vo (AC Coupled) 100mV/Div**



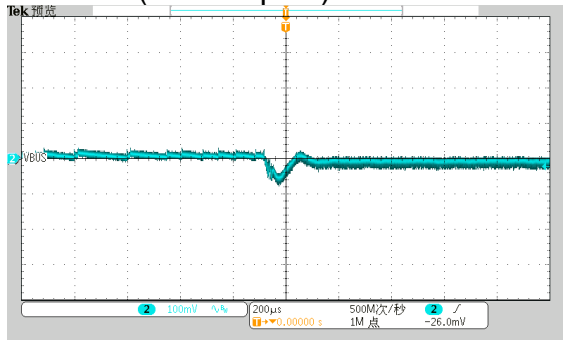
**V_{BAT}=11.1V and 0 to 25% load
CH2: Vo (AC Coupled) 100mV/Div**



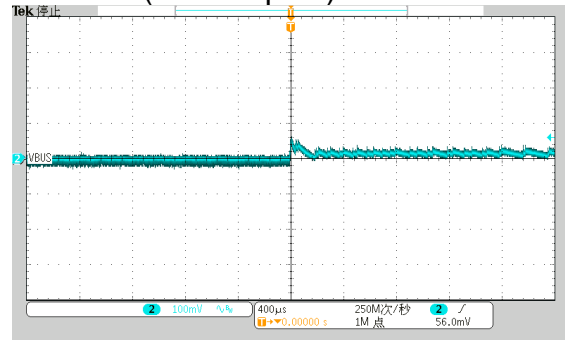
**V_{BAT}=11.1V and 25% to 0 load
CH2: Vo (AC Coupled) 100mV/Div**



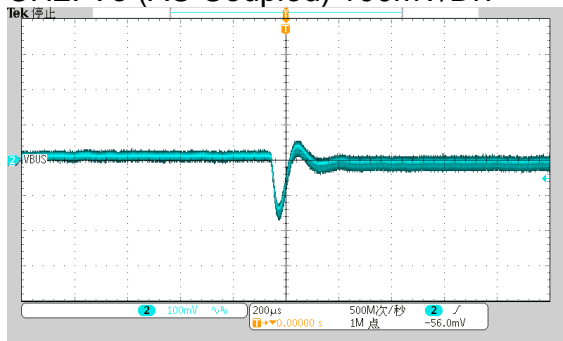**V_{BAT}=12.6V and 0 to 25% load
CH2: Vo (AC Coupled) 100mV/Div**




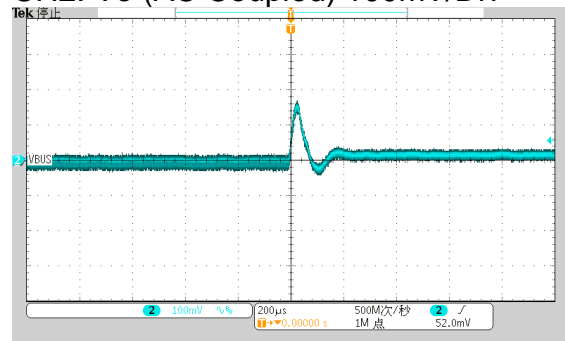**V_{BAT}=12.6V and 25% to 0 load
CH2: Vo (AC Coupled) 100mV/Div**




**V_{BAT}=9.3V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div**

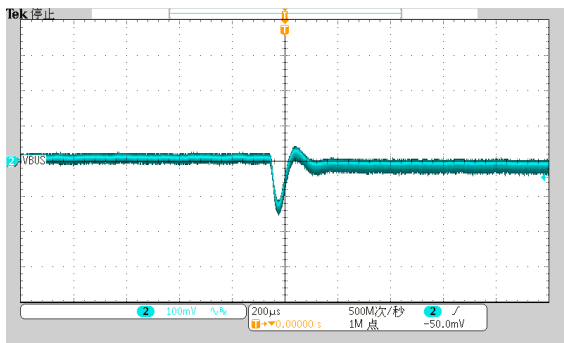
**V_{BAT}=9.3V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div**



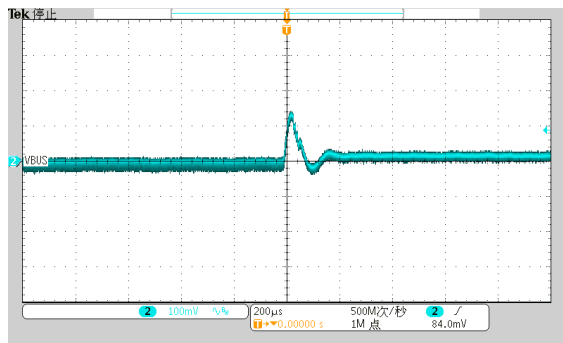
VBAT=11.1V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



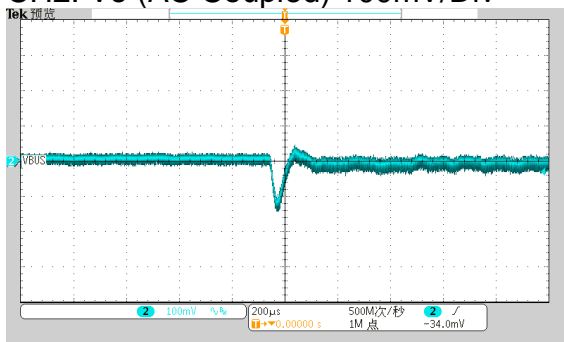
VBAT=11.1V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



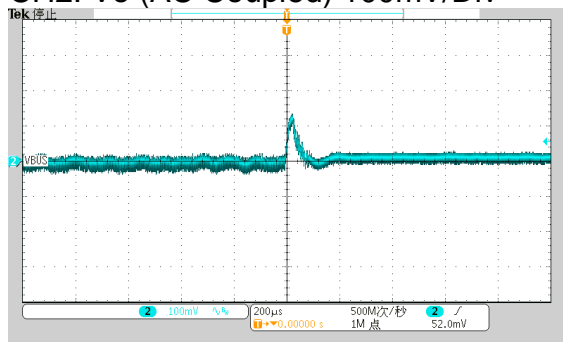
VBAT=12.6V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



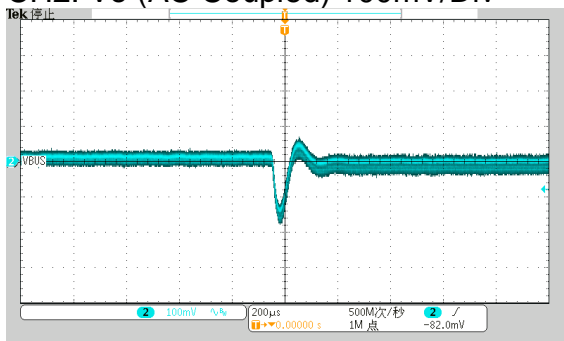
VBAT=12.6V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



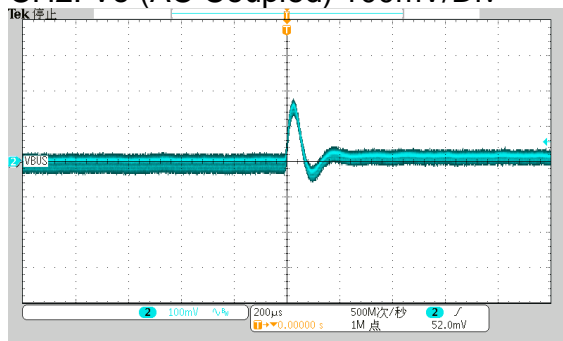
VBAT=9.3V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



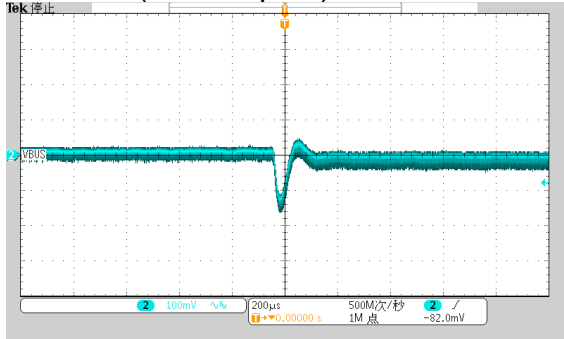
VBAT=9.3V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



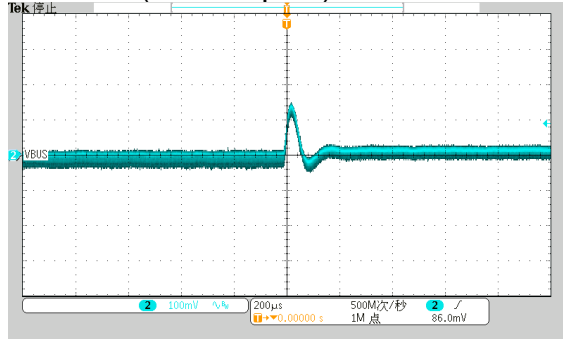
VBAT=11.1V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



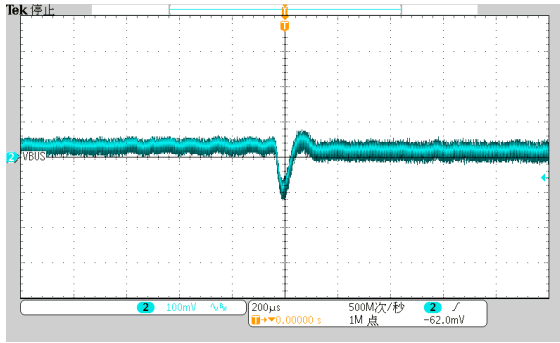
VBAT=11.1V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



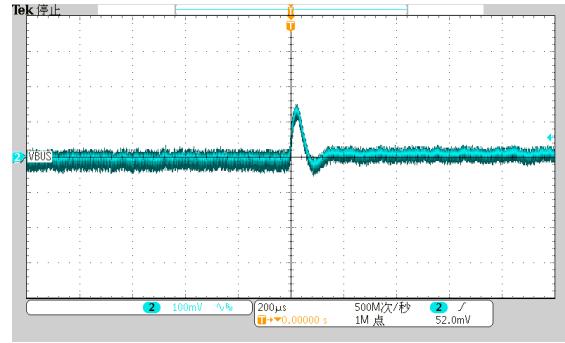
VBAT=12.6V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



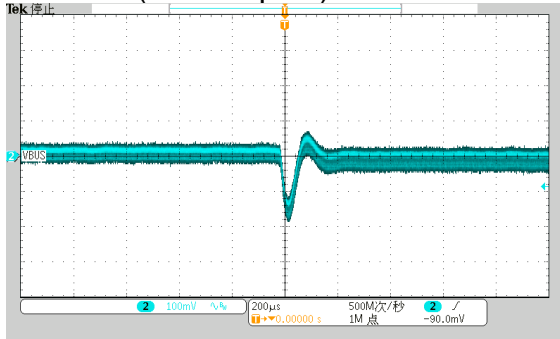
VBAT=12.6V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



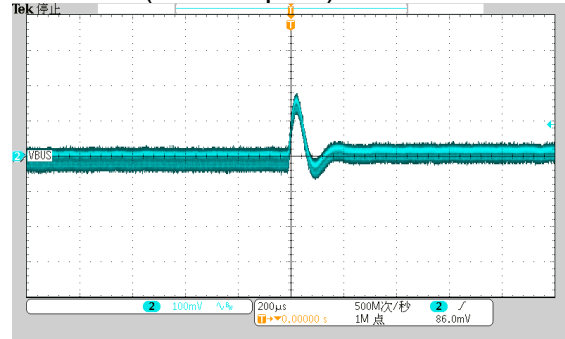
VBAT=9.3V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div



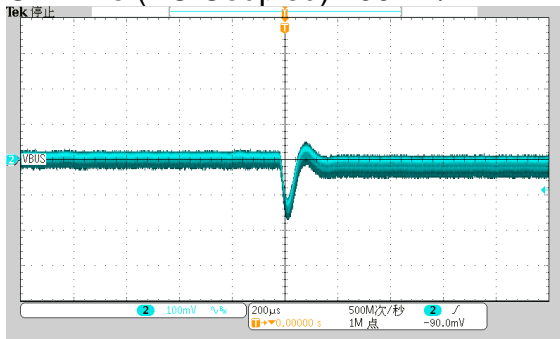
VBAT=9.3V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



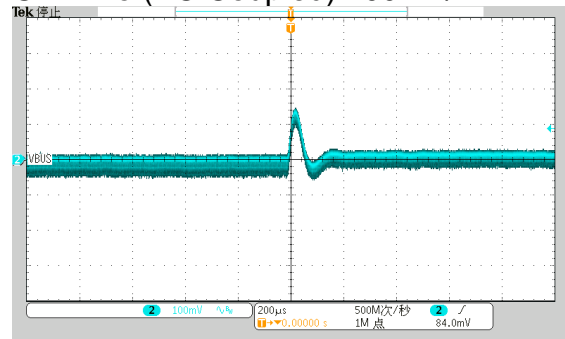
VBAT=11.1V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div



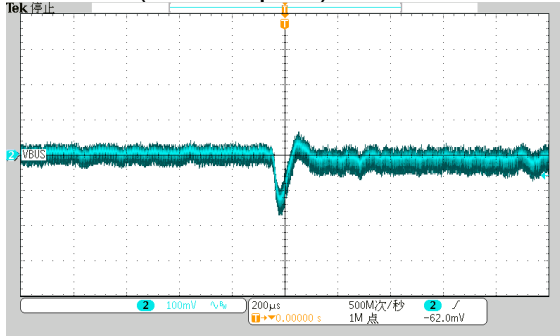VBAT=11.1V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div





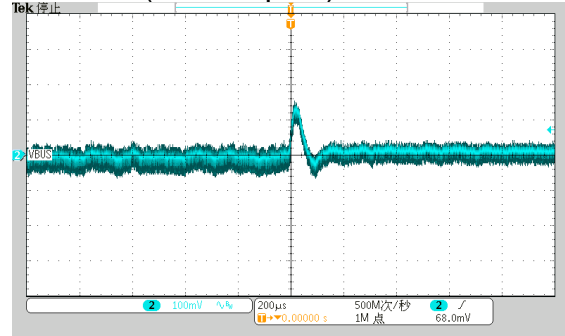VBAT=12.6V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div




VBAT=12.6V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div


$V_o=15V$ & 100mA/us Current slew rate

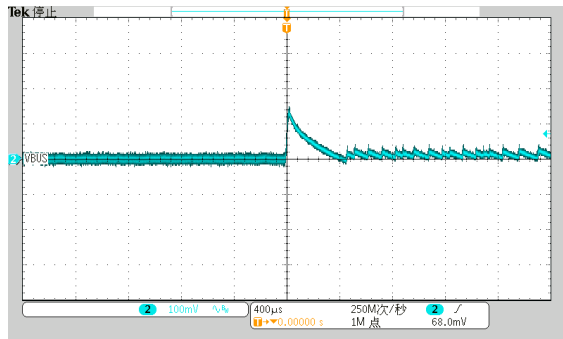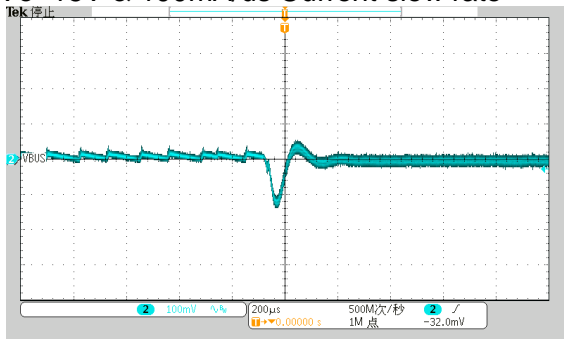

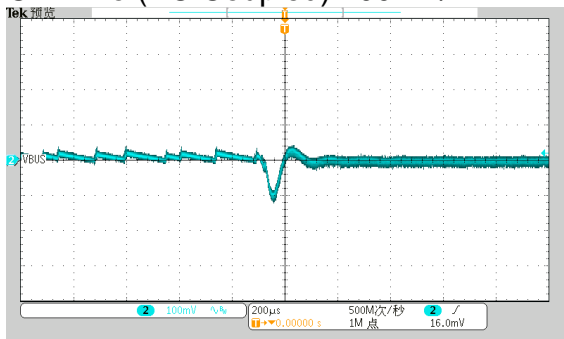
$V_{BAT}=9.3V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



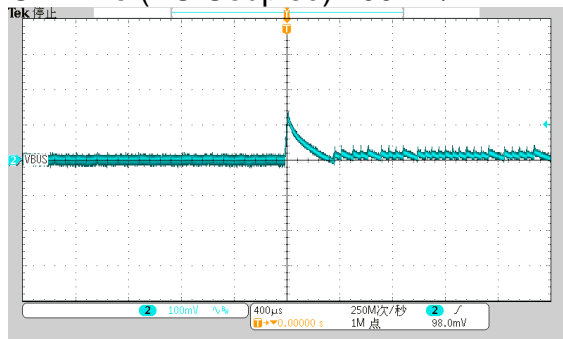
$V_{BAT}=9.3V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



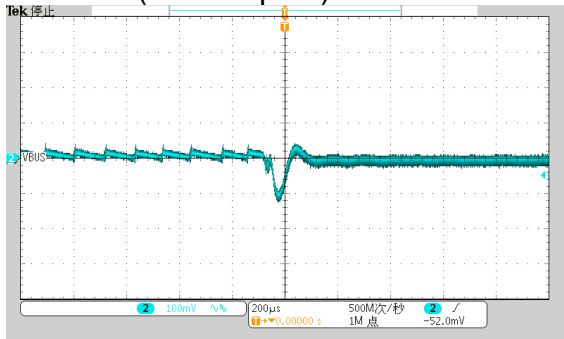
$V_{BAT}=11.1V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



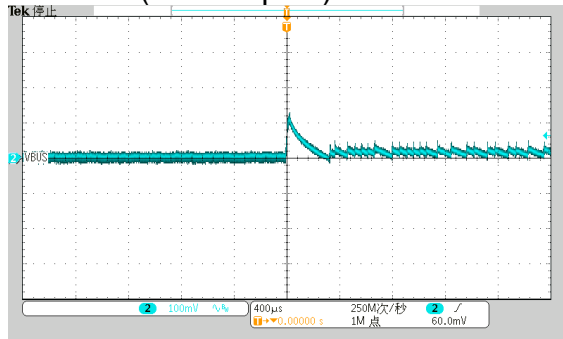
$V_{BAT}=11.1V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



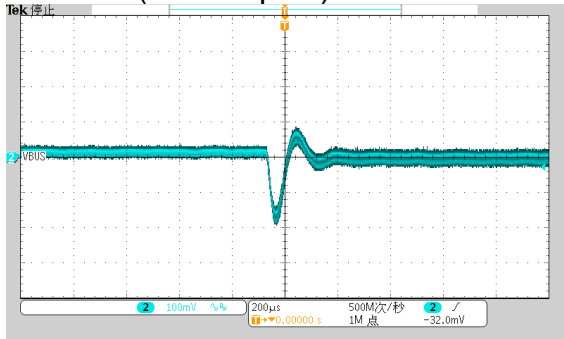
$V_{BAT}=12.6V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



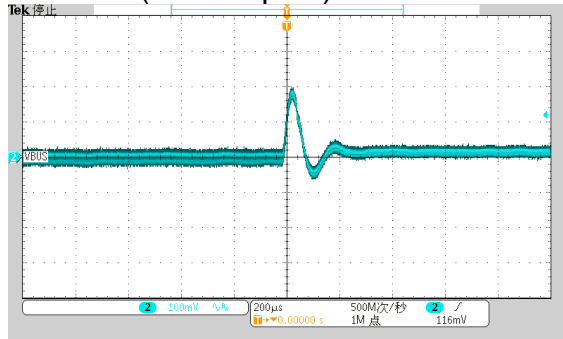
$V_{BAT}=12.6V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



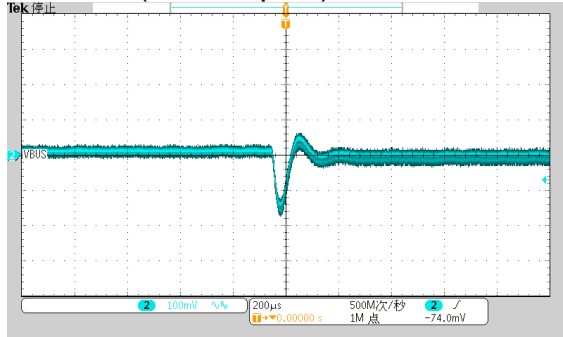
VBAT=9.3V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



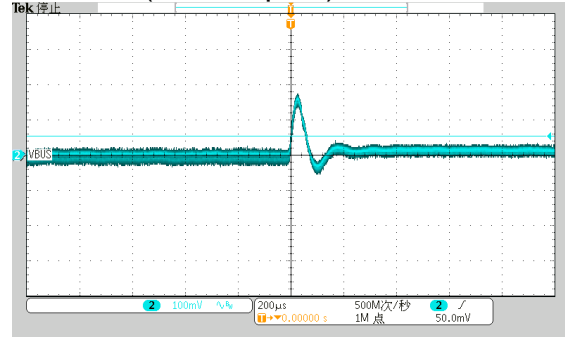
VBAT=9.3V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



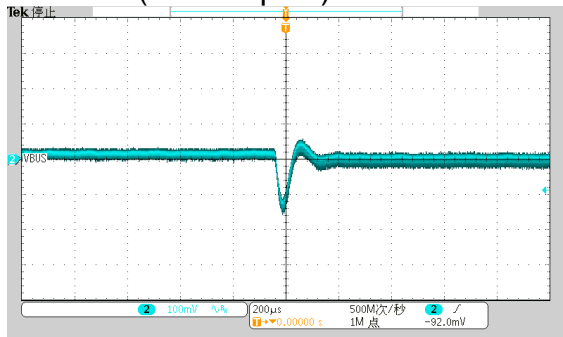
VBAT=11.1V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



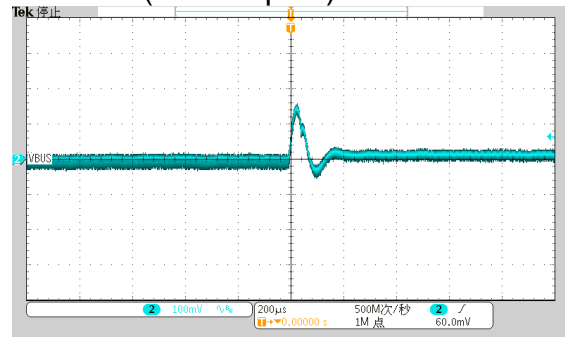
VBAT=11.1V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



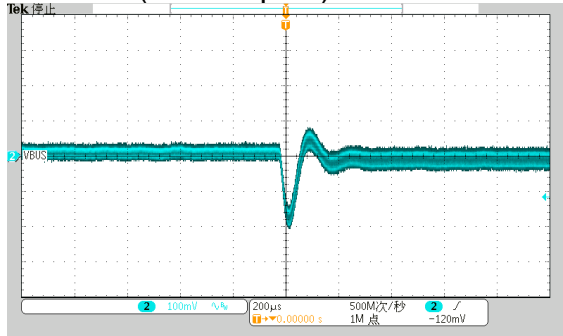
VBAT=12.6V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



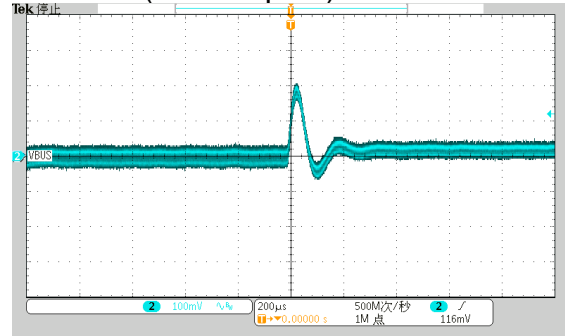
VBAT=12.6V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



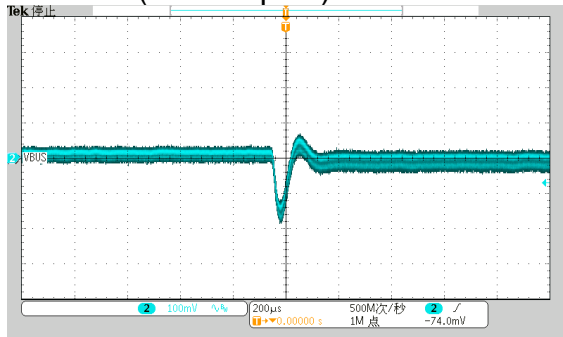VBAT=9.3V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



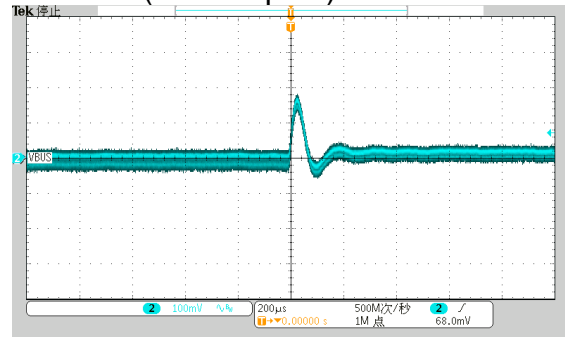
VBAT=9.3V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div




VBAT=11.1V and 50% to 75% load

VBAT=11.1V and 75% to 50% load


CH2: Vo (AC Coupled) 100mV/Div

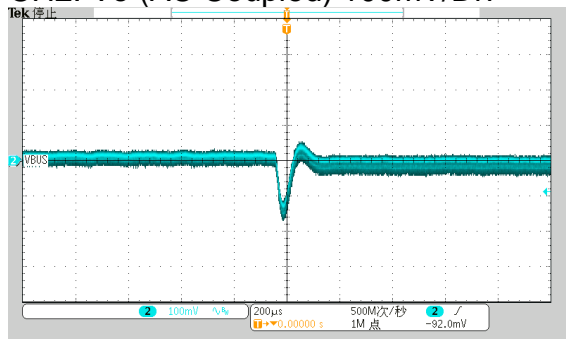


CH2: Vo (AC Coupled) 100mV/Div

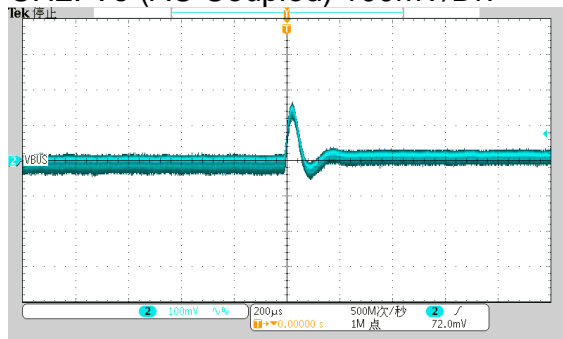

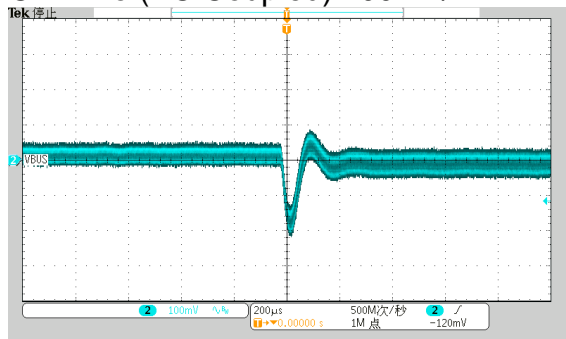
VBAT=12.6V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



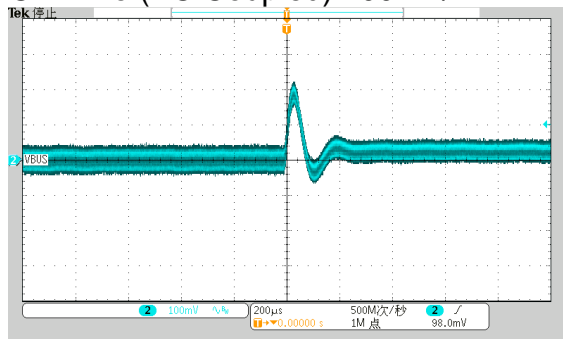
VBAT=12.6V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



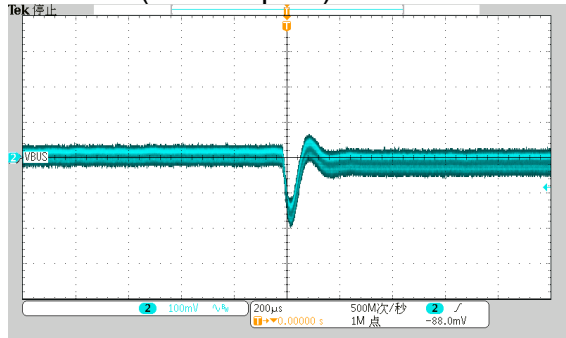
VBAT=9.3V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div



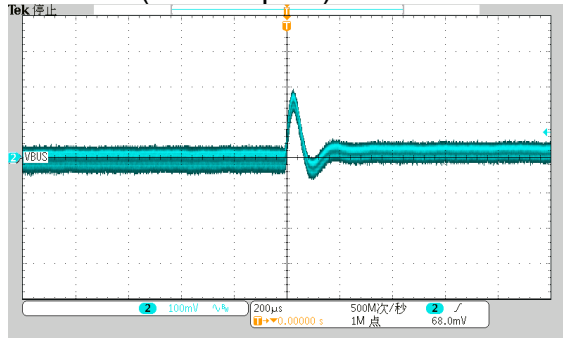
VBAT=9.3V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div



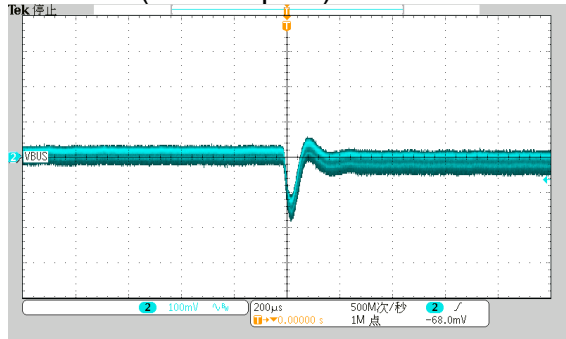VBAT=11.1V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div




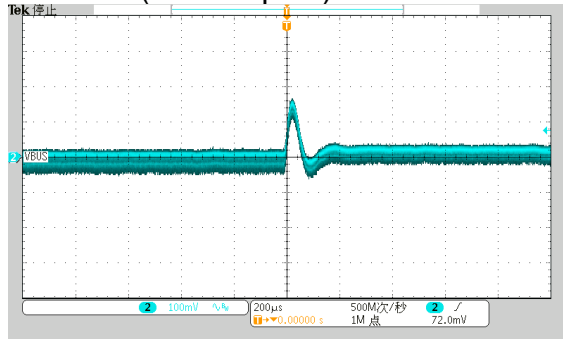
VBAT=11.1V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div




VBAT=12.6V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div

VBAT=12.6V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div

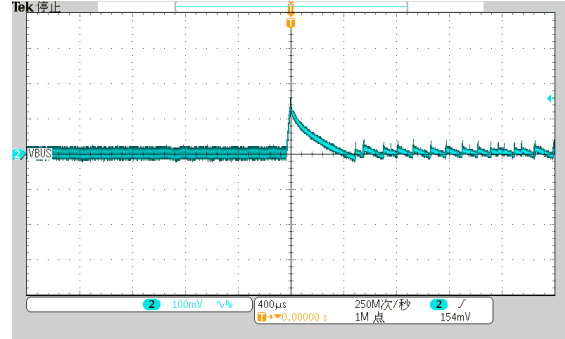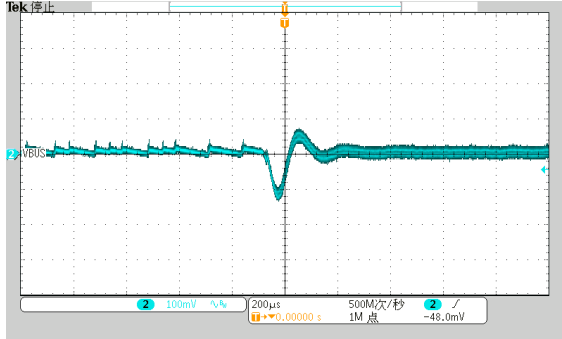
$V_o=20V$ & $100mA/\mu s$ Current slew rate



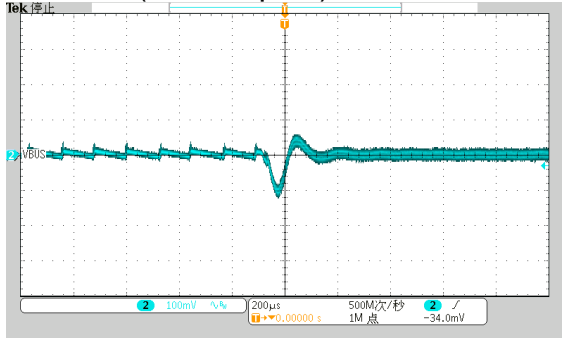
$V_{BAT}=9.3V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



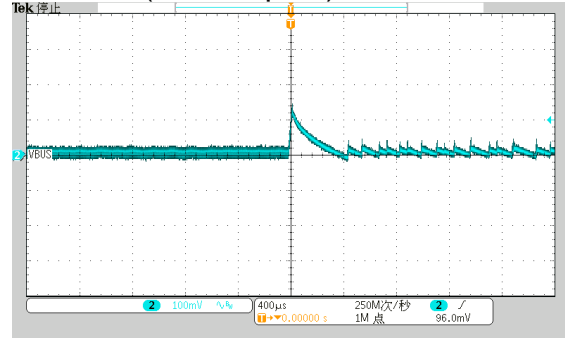
$V_{BAT}=9.3V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



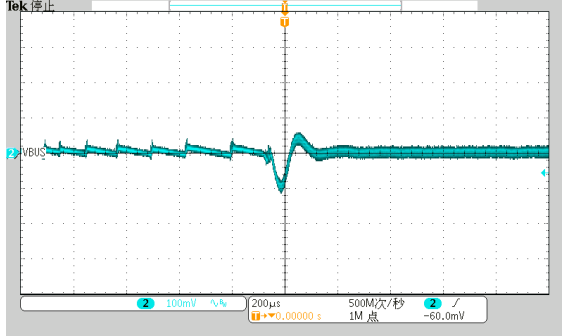
$V_{BAT}=11.1V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



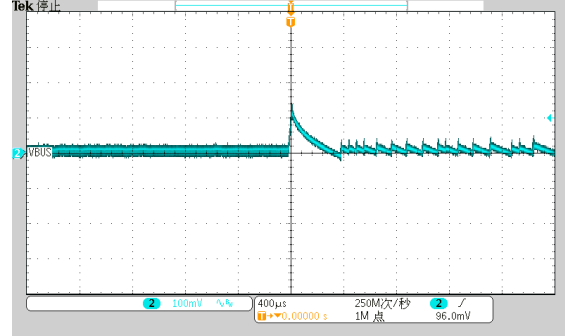
$V_{BAT}=11.1V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



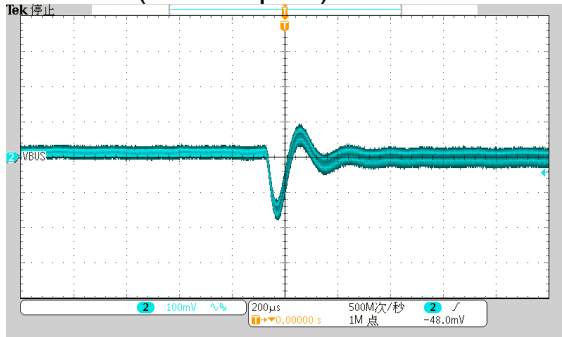
$V_{BAT}=12.6V$ and 0 to 25% load
CH2: V_o (AC Coupled) 100mV/Div



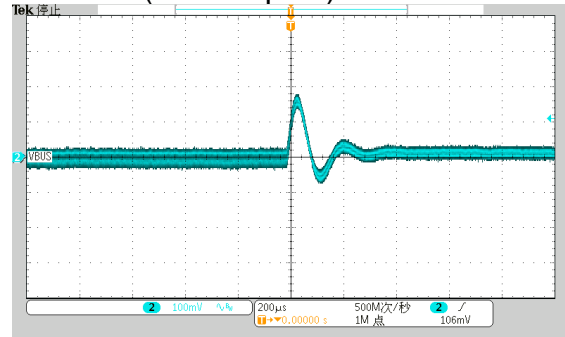
$V_{BAT}=12.6V$ and 25% to 0 load
CH2: V_o (AC Coupled) 100mV/Div



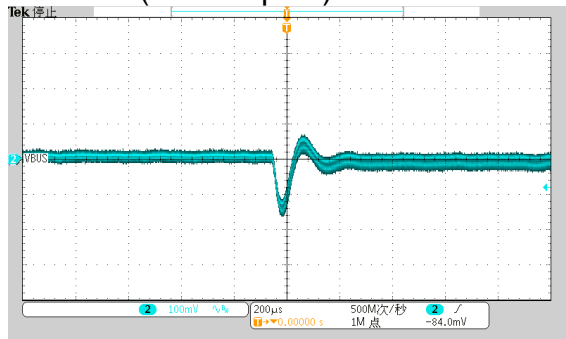
VBAT=9.3V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



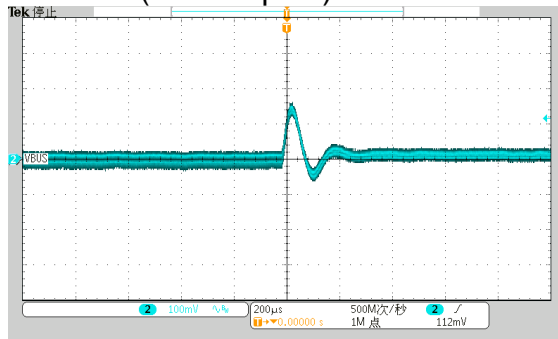
VBAT=9.3V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



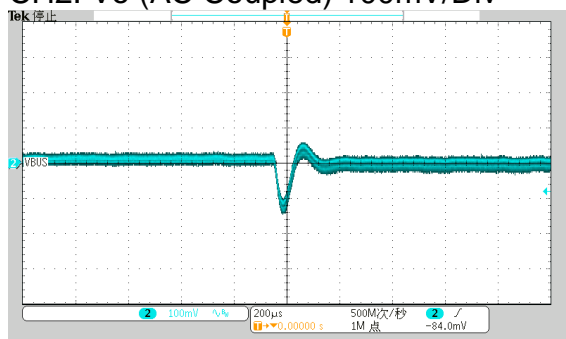
VBAT=11.1V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



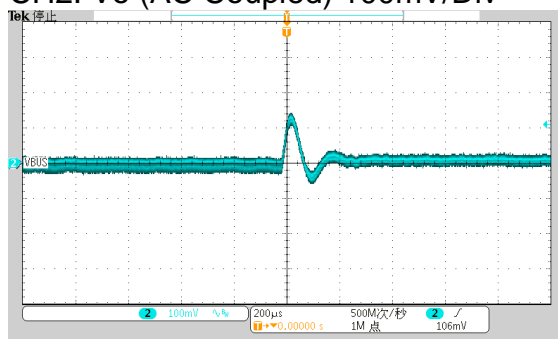
VBAT=11.1V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



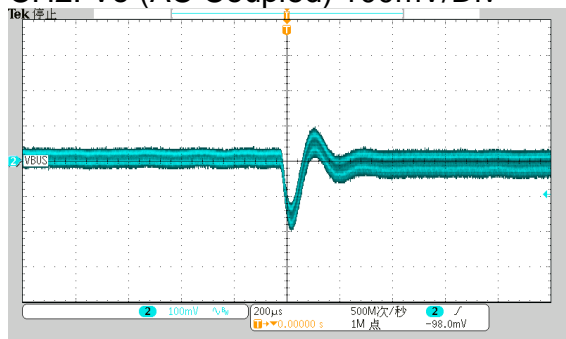
VBAT=12.6V and 25% to 50% load
CH2: Vo (AC Coupled) 100mV/Div



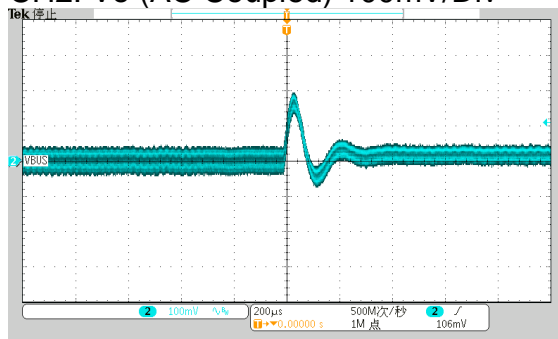
VBAT=12.6V and 50% to 25% load
CH2: Vo (AC Coupled) 100mV/Div



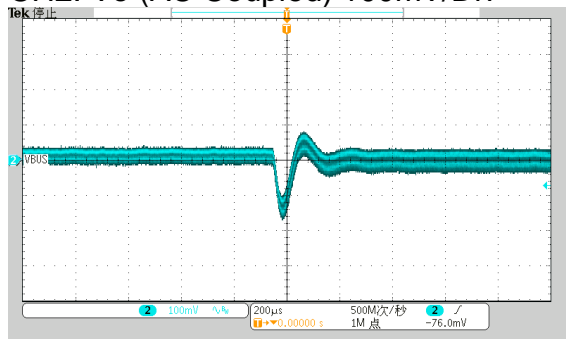VBAT=9.3V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div











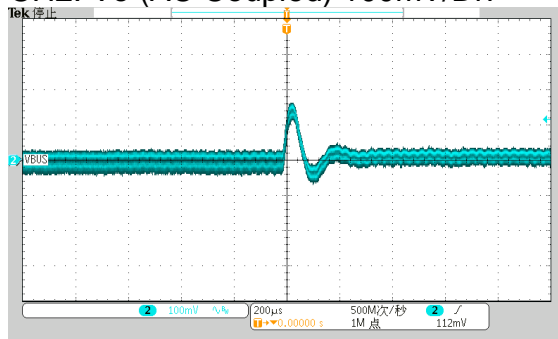VBAT=9.3V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div




VBAT=11.1V and 50% to 75% load

VBAT=11.1V and 75% to 50% load

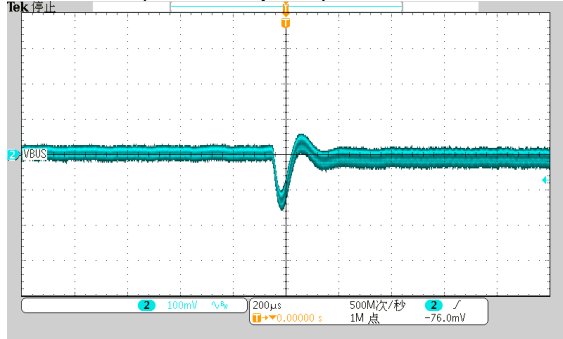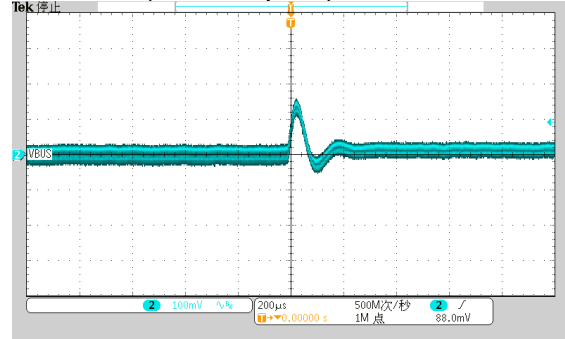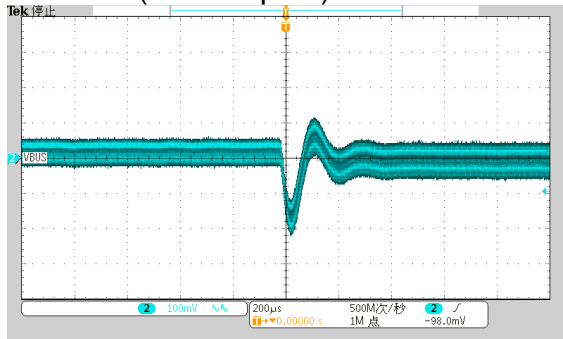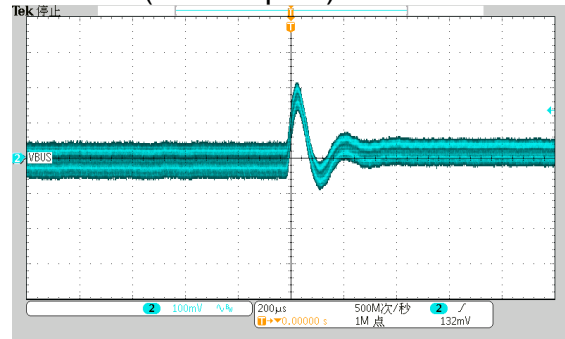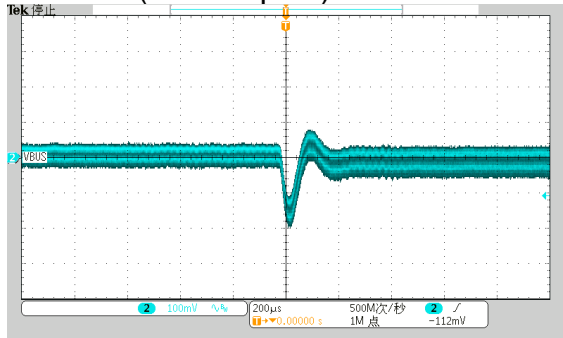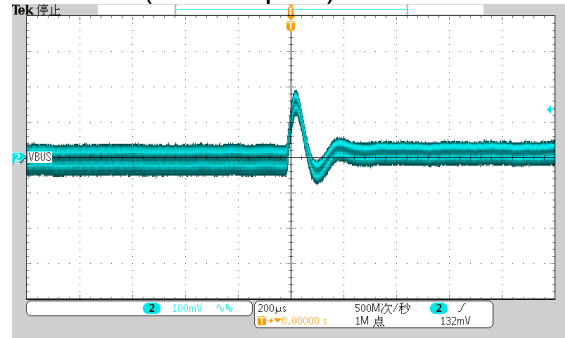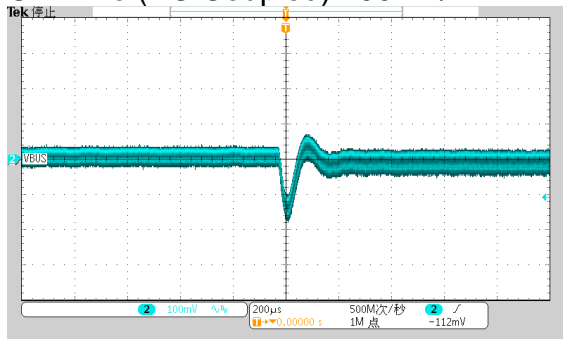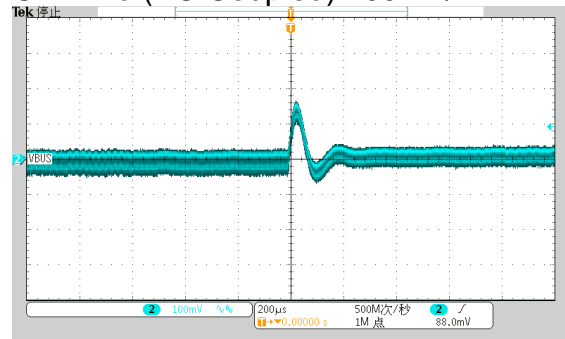CH2: Vo (AC Coupled) 100mV/Div

CH2: Vo (AC Coupled) 100mV/Div

**VBAT=12.6V and 50% to 75% load
CH2: Vo (AC Coupled) 100mV/Div**

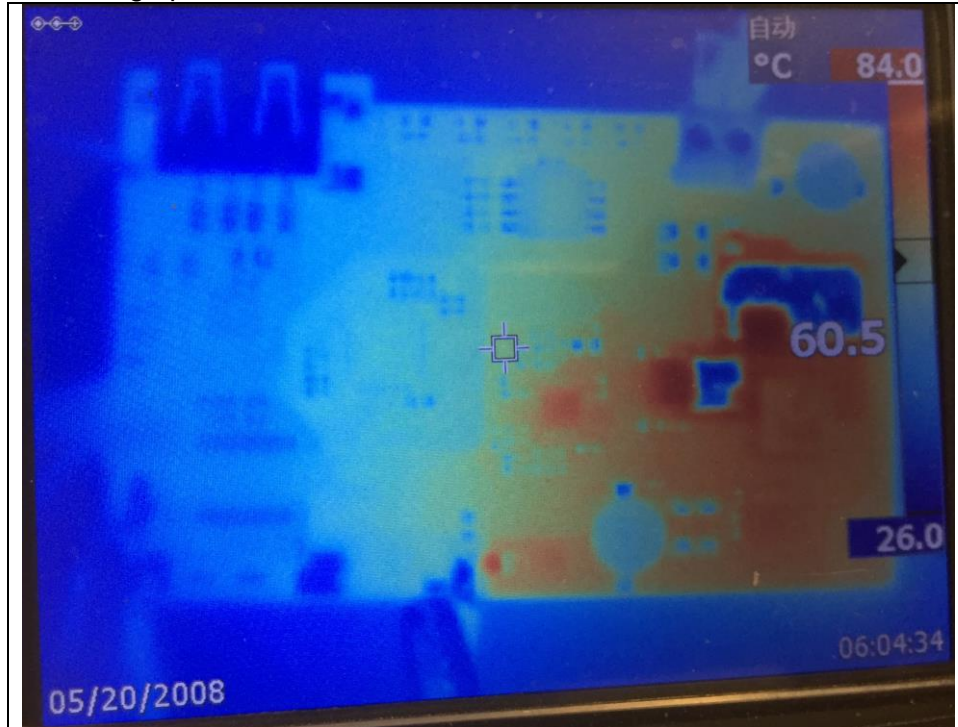**VBAT=12.6V and 75% to 50% load
CH2: Vo (AC Coupled) 100mV/Div**

**VBAT=9.3V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div**

**VBAT=9.3V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div**

**VBAT=11.1V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div**

**VBAT=11.1V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div**

**VBAT=12.6V and 75% to 100% load
CH2: Vo (AC Coupled) 100mV/Div**
**VBAT=12.6V and 100% to 75% load
CH2: Vo (AC Coupled) 100mV/Div**

2.6 Thermal Performance

The board is applied a 9.3V battery pack and output 20V/2.25A load at the connector. Run about 10min for warming up.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated