

Test Report


TIDA-00507

TPS53625 Intel[®] Atom[™] C2000 PVNN


PVNN- Configuration

- 1-phase mode
- MOSFET: TI Power Stage: CSD97374Q4M
- Inductor: 2.2uH,7mohm
- Output Capacitor:
 - Bulk: No Bulk
 - Ceramic: 4x47uF
- Max Current: 2.3A
- Frequency: 600KHz
- Zero Load-line
- Ramp 100mV
- SVID Address : 01h
- OSR disabled


Frequency Variation

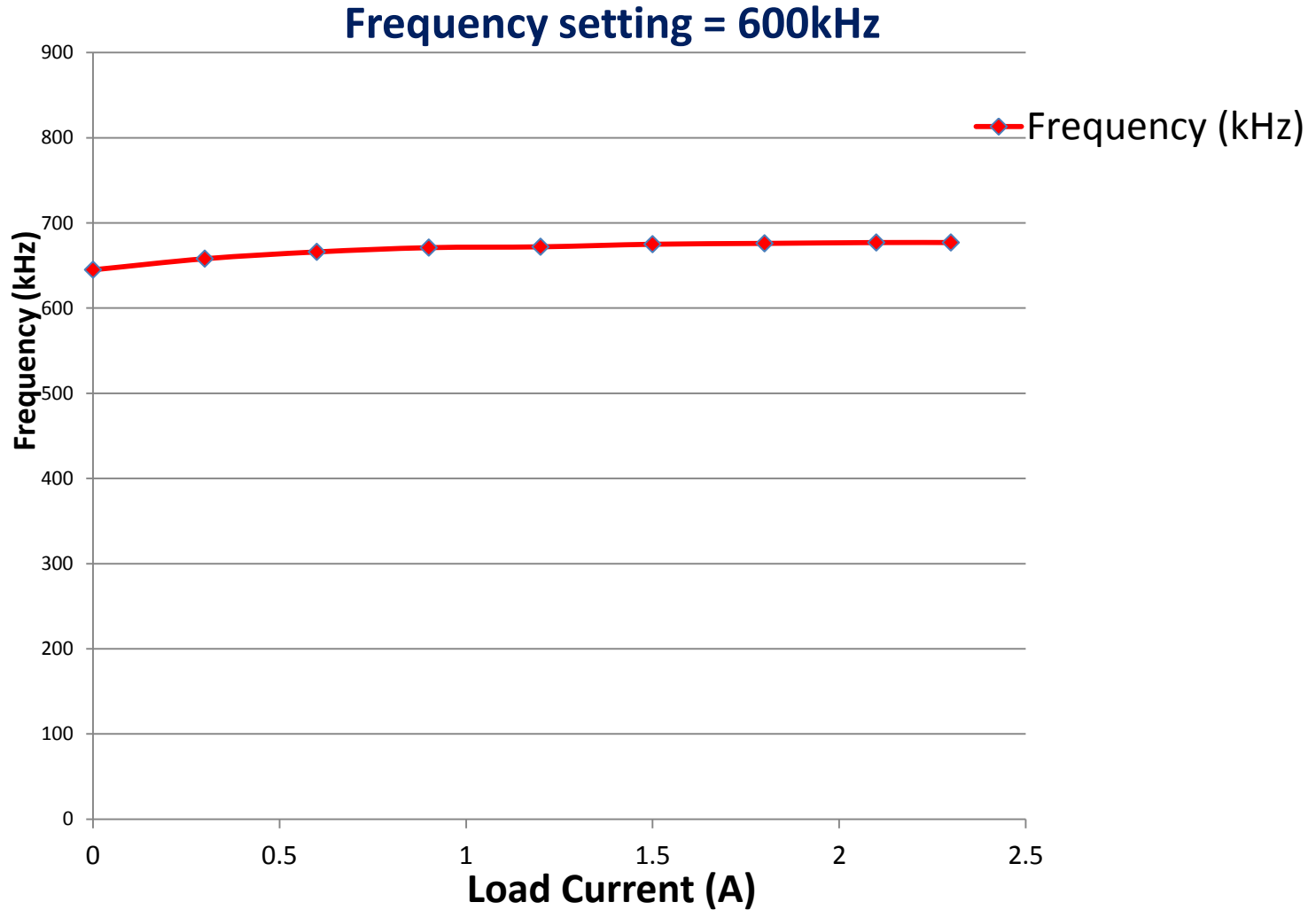


PSO Efficiency

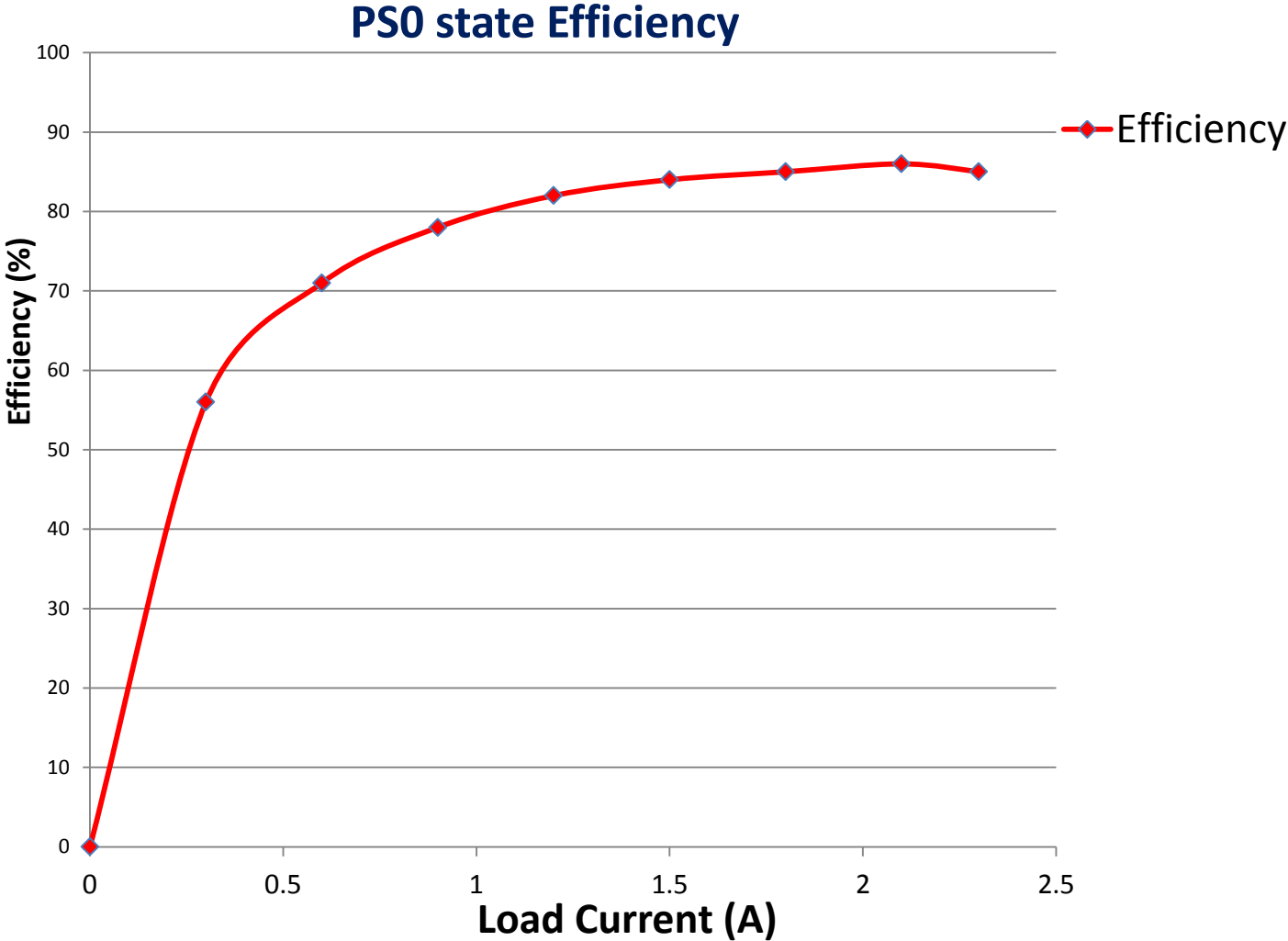

Loadline

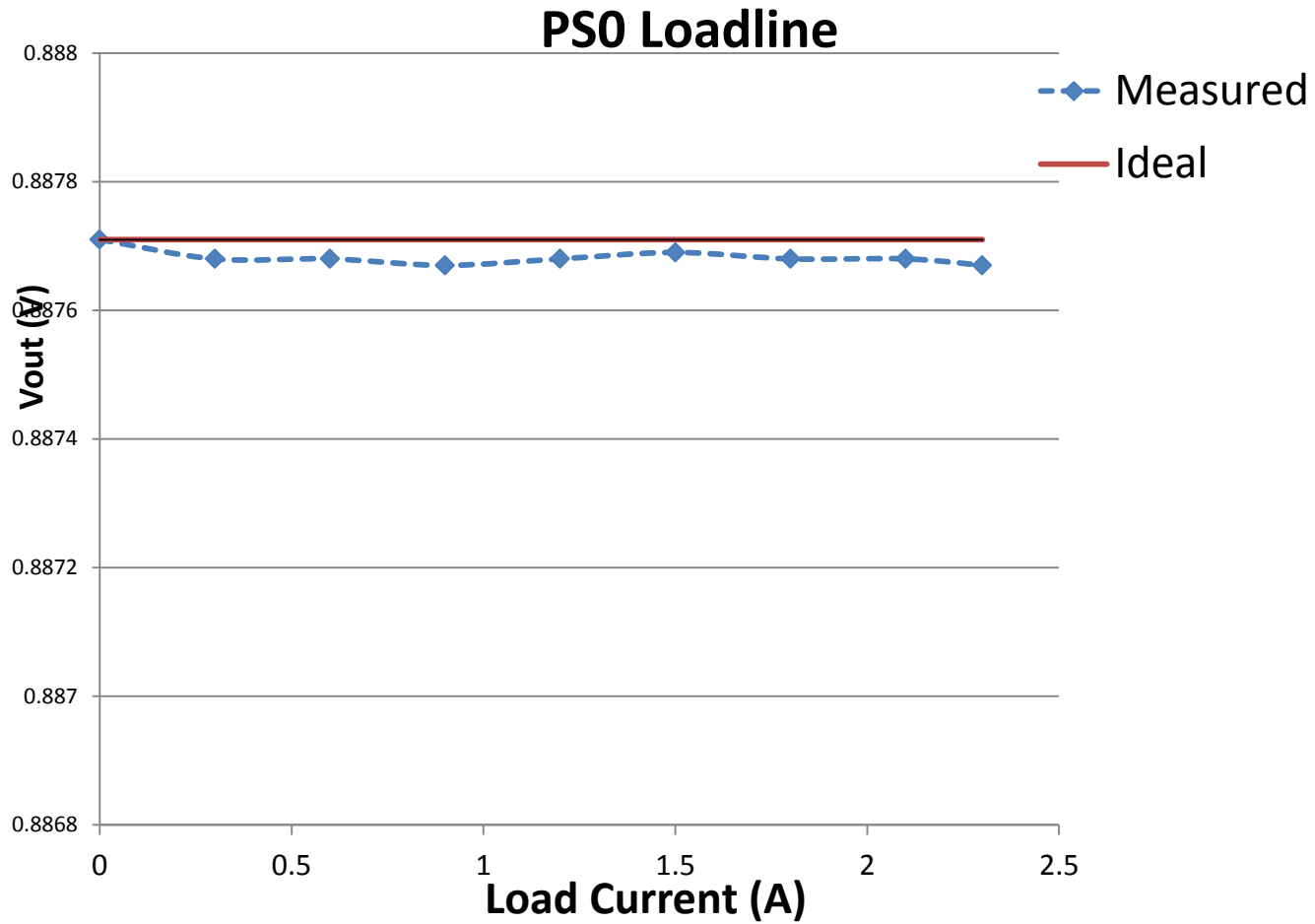

Analog Current Monitor Output (IMON)

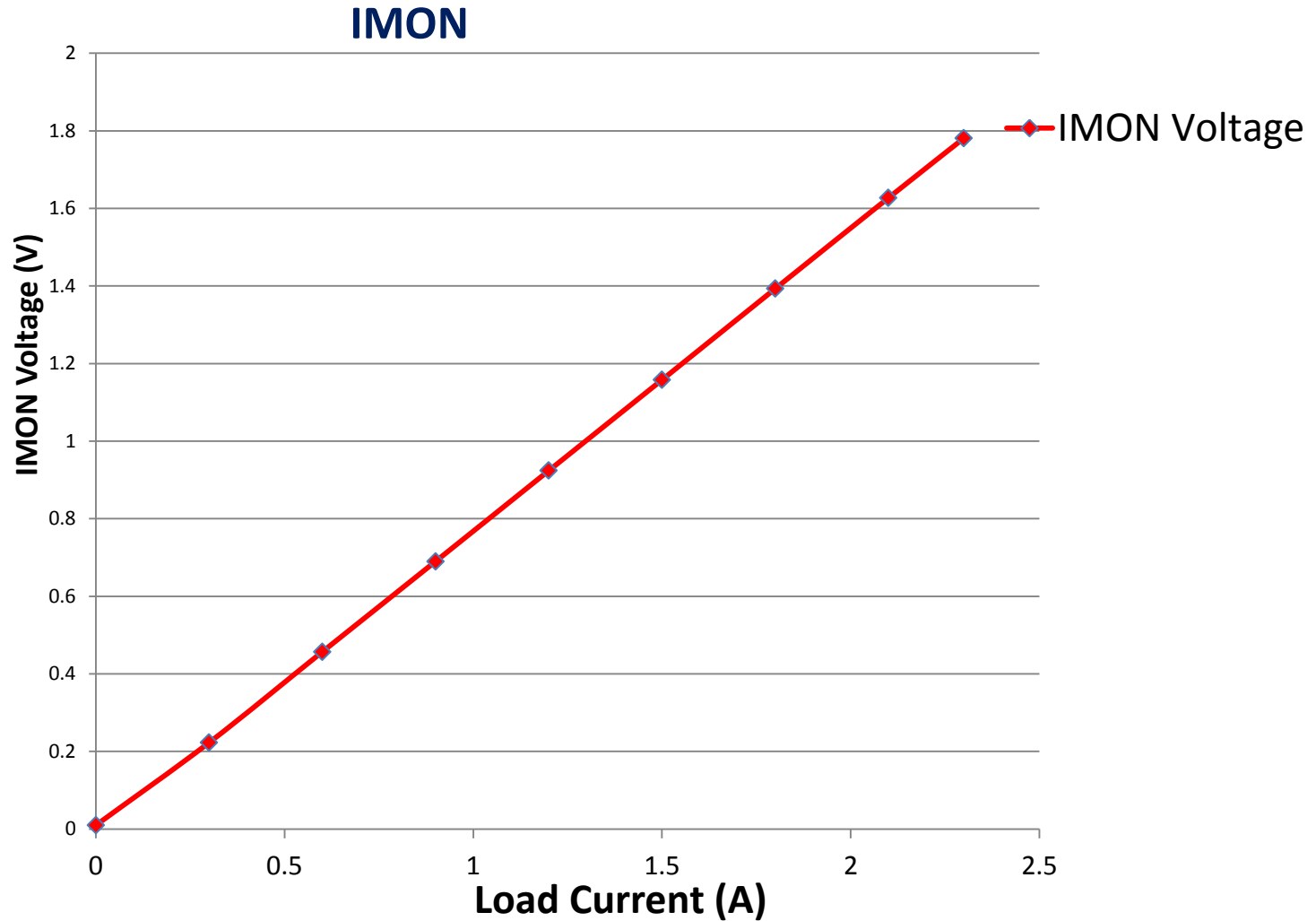

Ripple and jitter

Vin 9V



Load 0A
Ripple: 7.8mV




Load 2.3A
Ripple: 8.1mV

Ripple and jitter Vin 12V



Load 0A
Ripple: 8.4mV

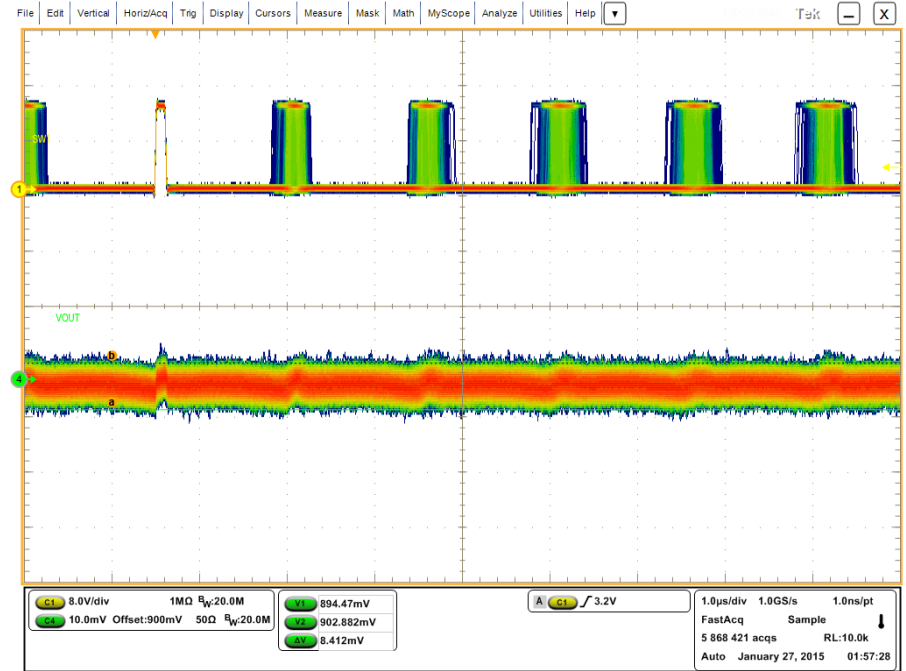


Load 2.3A
Ripple: 8.4mV

Ripple and jitter Vin 15V




Load 0A
Ripple: 8.4mV



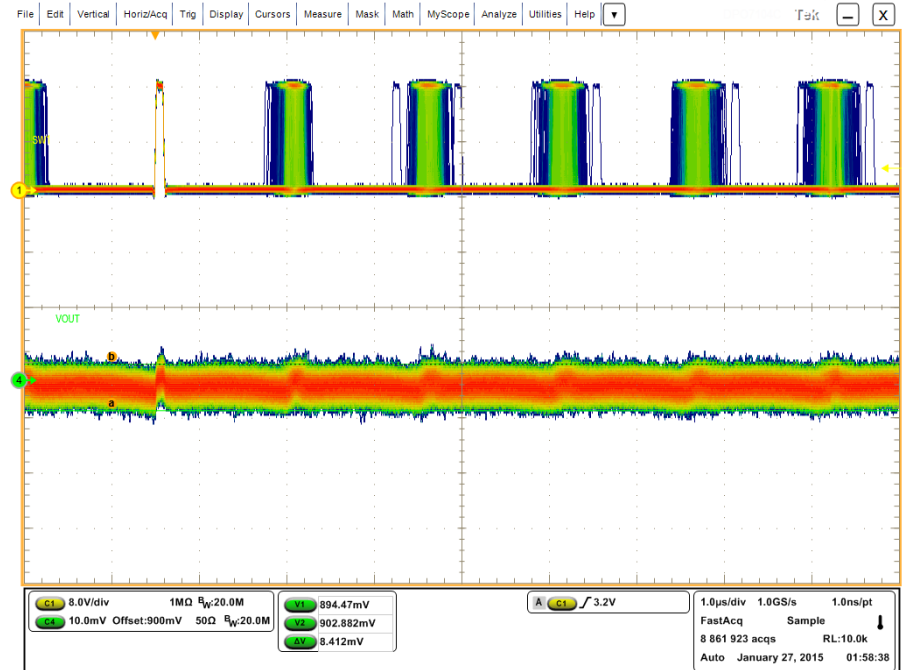


Load 2.3A
Ripple: 8.5mV


Load Transient Performance 1A to 2A (PS0 state)- 50% duty cycle

DC and AC ripple guideline: +/-64mV

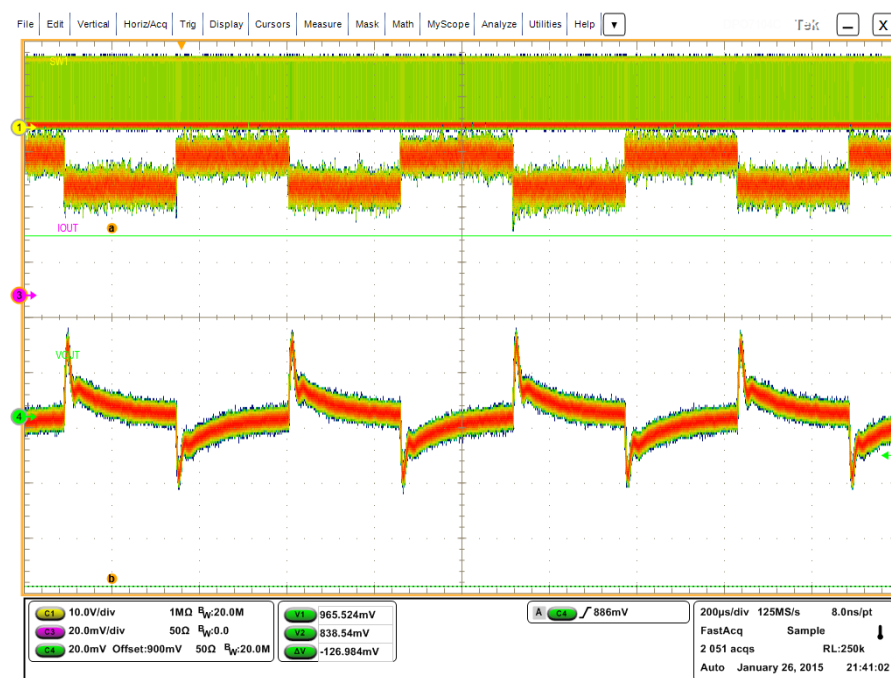


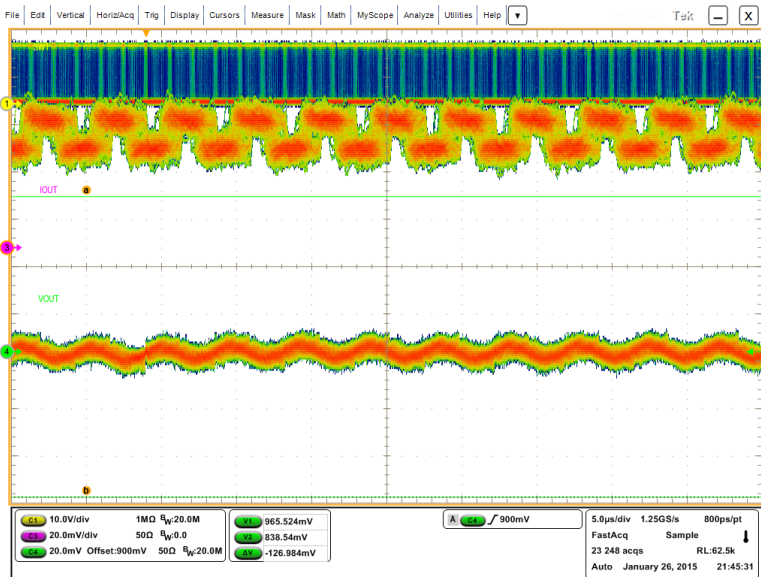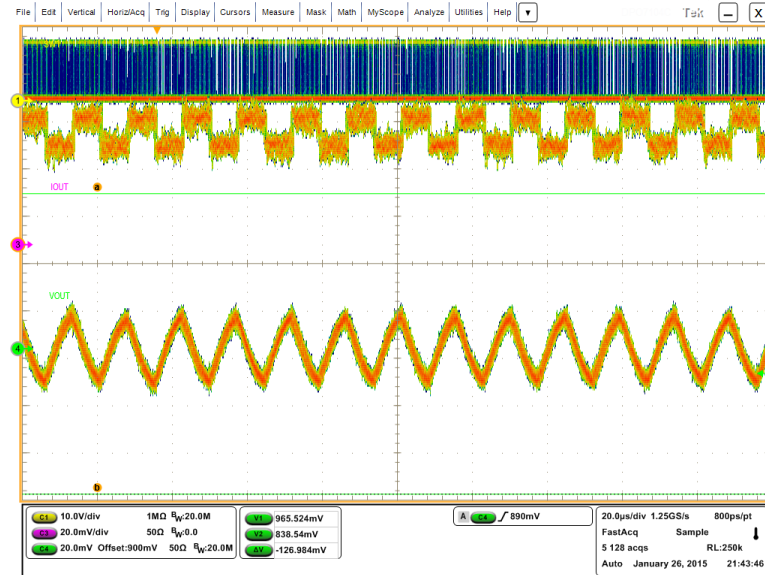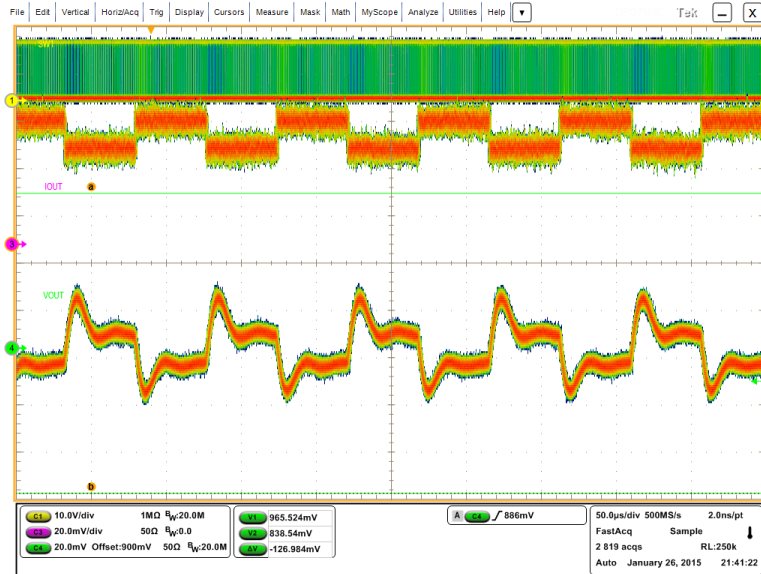

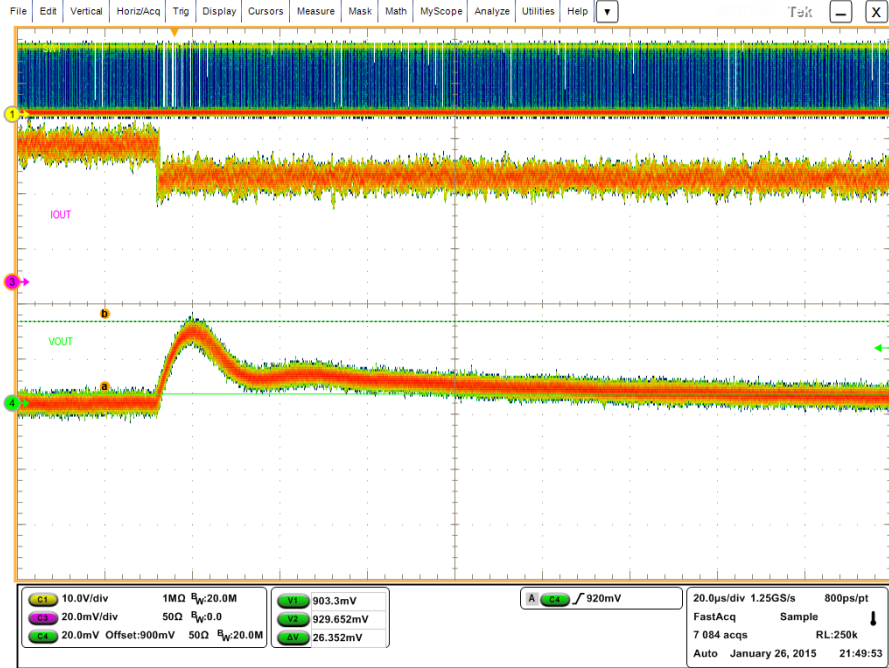Output Voltage waveform well within the +/-64 mV lines



Load fall
 Overshoot: 26mV

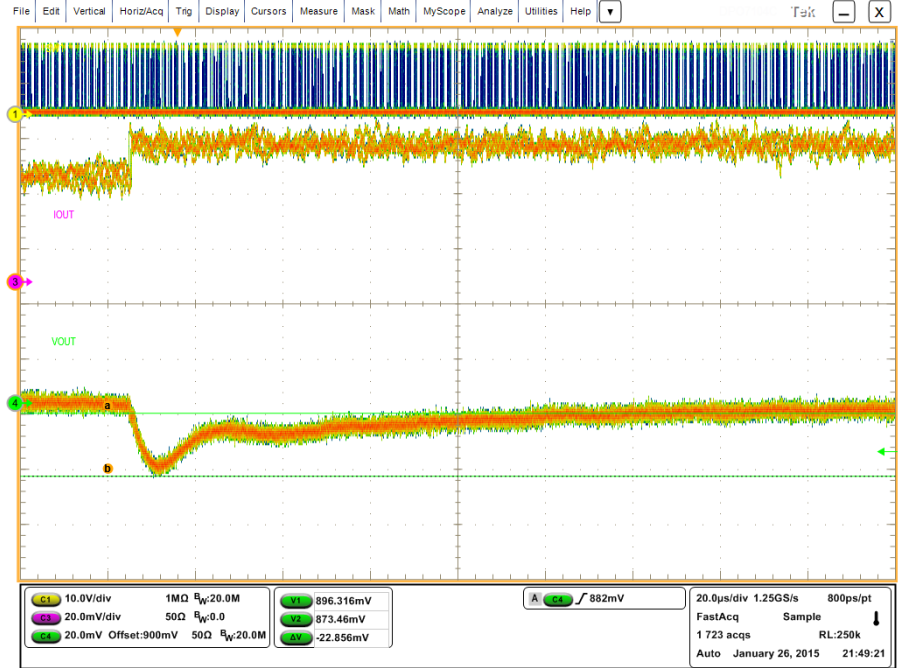


Load rise
 Droop: 23mV

Dynamic VID

0.65V-1.24V Fast up 1A load




Rise Slew rate: 12.05 mV/us

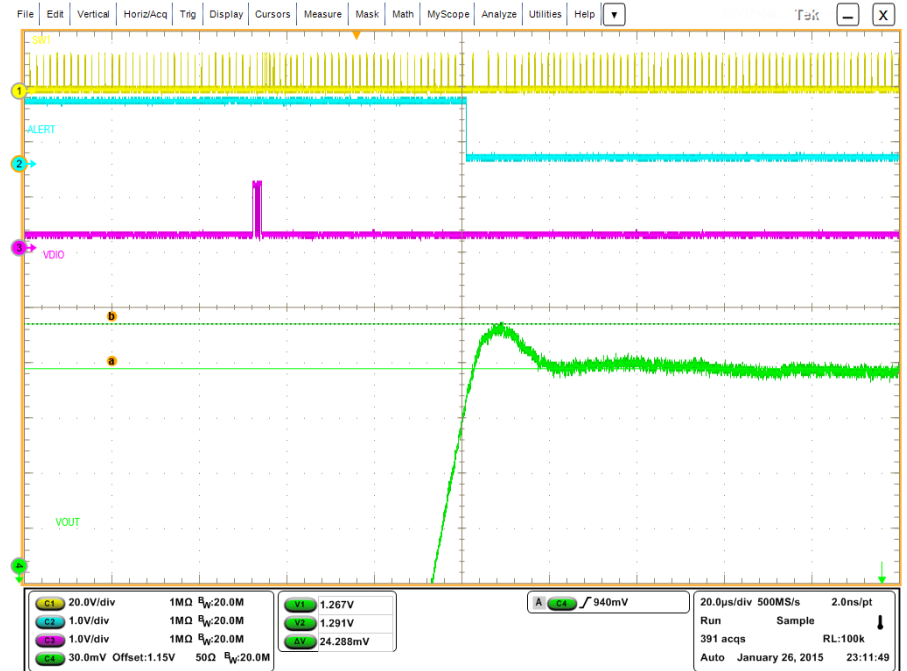


Overshoot: 24.3 mV

Dynamic VID

0.65V-1.24V Fast Down 1A load

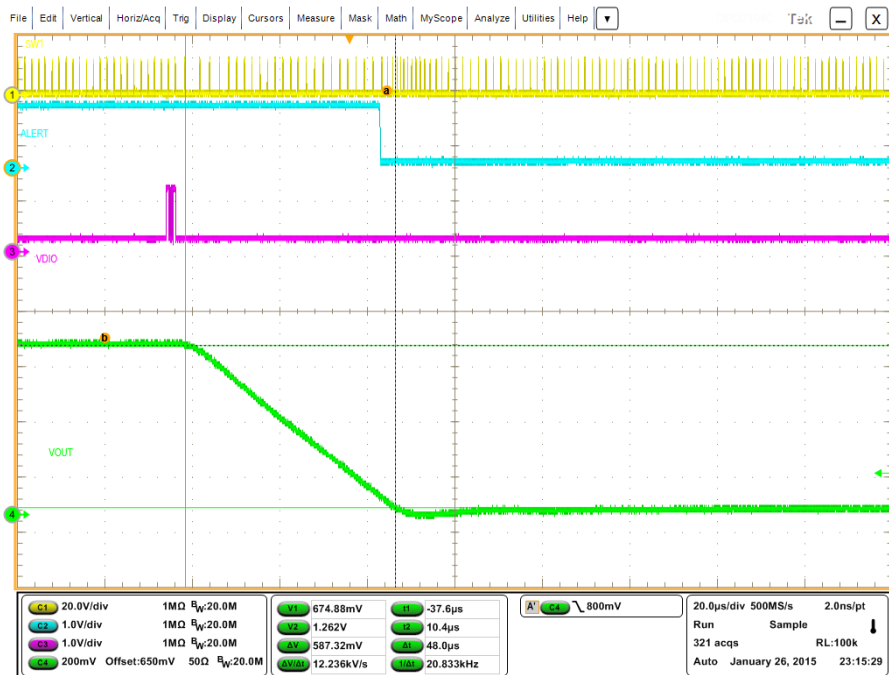

Fall Slew rate: 12.23 mV/us

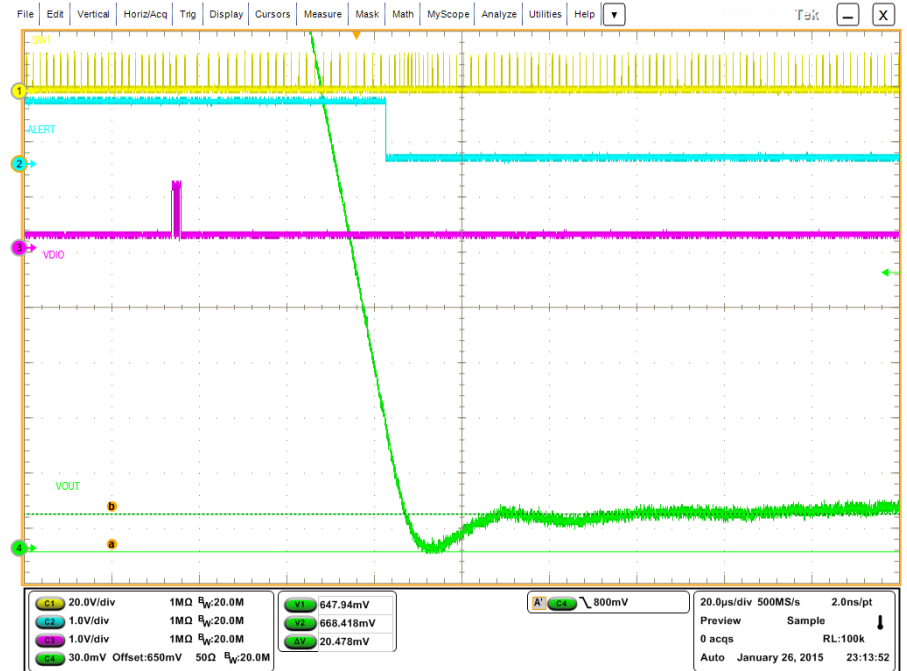


Droop: 20.5mV

Dynamic VID

0.65V-1.24V Slow Up 1A load




Rise Slew rate: 3.21mV/us

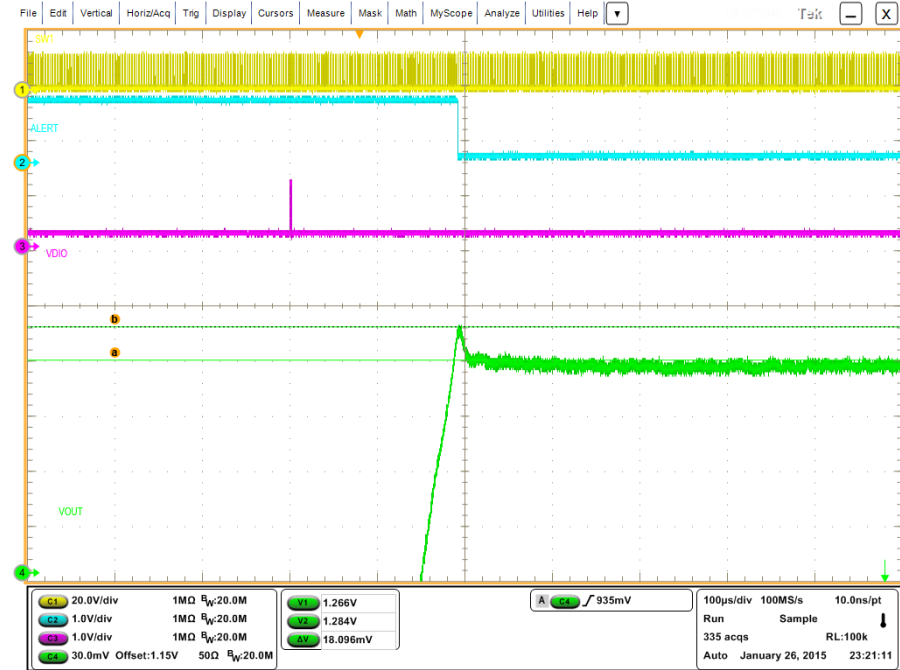


Overshoot: 18.1mV

Dynamic VID

0.65V-1.24V Slow Down 1A load

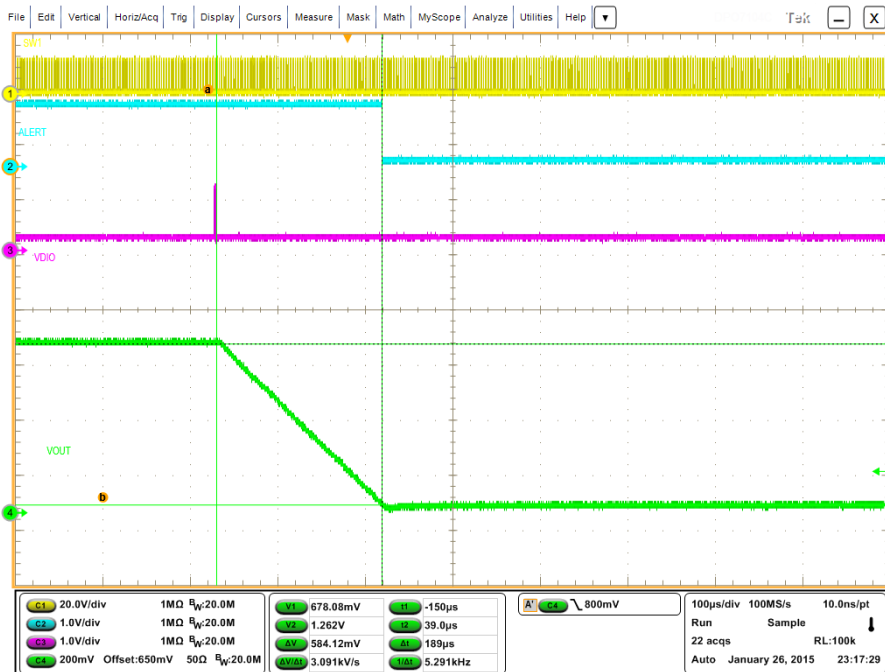

Fall Slew-rate: 3.1mV/us

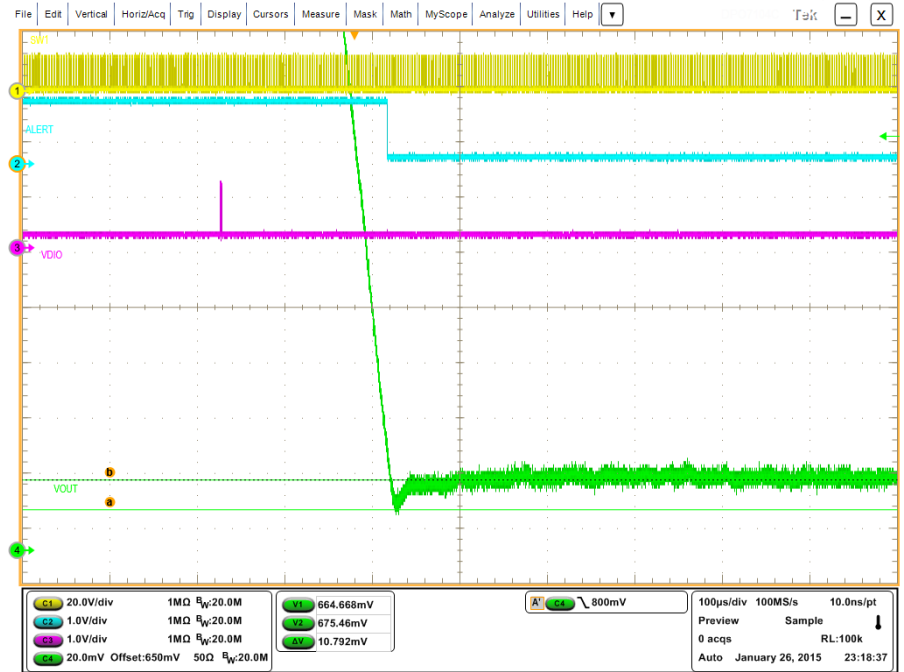


Droop: 10.8mV

Dynamic VID

0.65V-1.24V Decay 1A load




Decay Slew-rate: 6.1mV/us

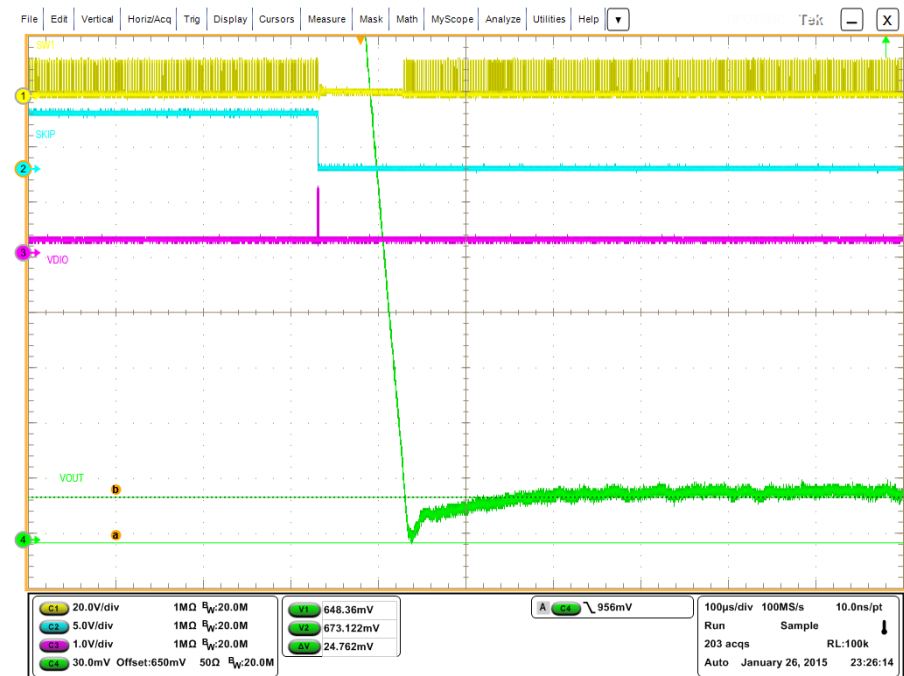

Droop: 24.8 mV


PS transition

PS0-PS2 0A load

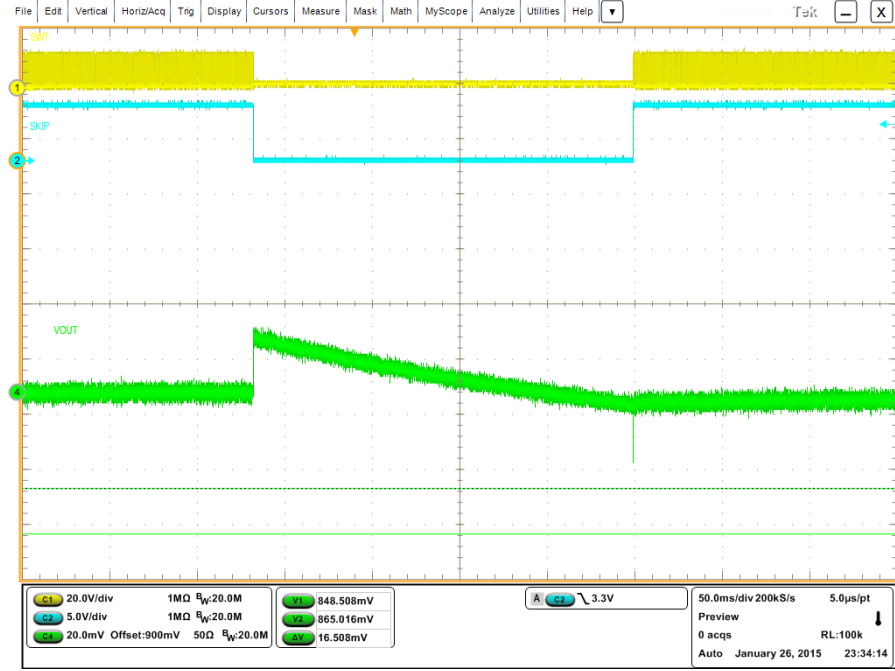

PS transition

PS0-PS2 0.1A load

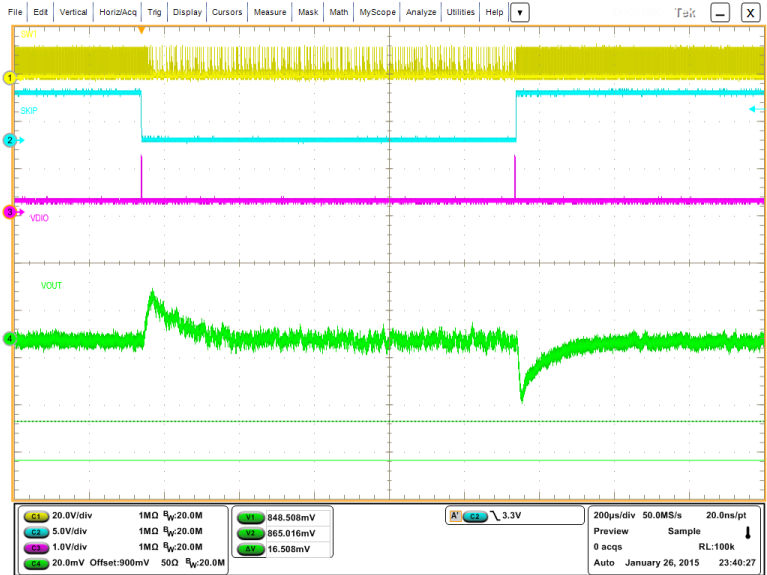


PS0 to PS2 voltage change: 17mV

PS2 to PS0 voltage change: 19mV




PS transition PS0-PS2 0.2A load

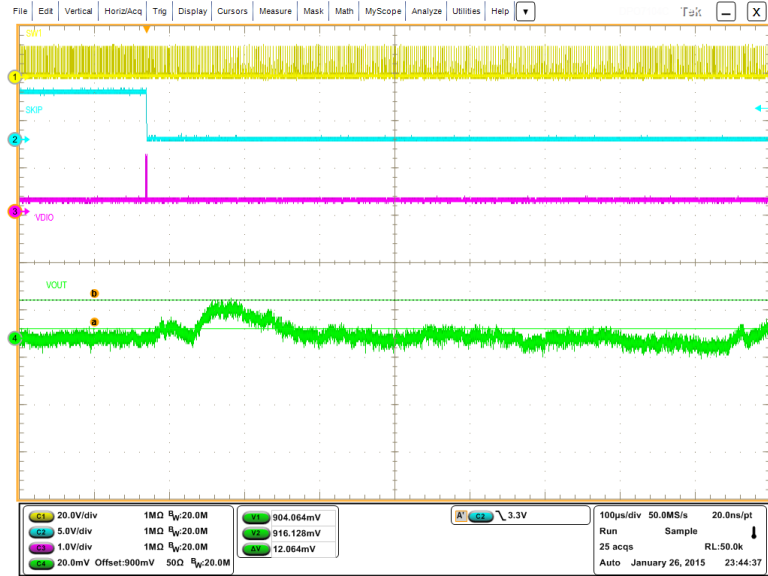


PS0 to PS2 voltage change: 12mV


PS0 to PS2 voltage change: 20mV

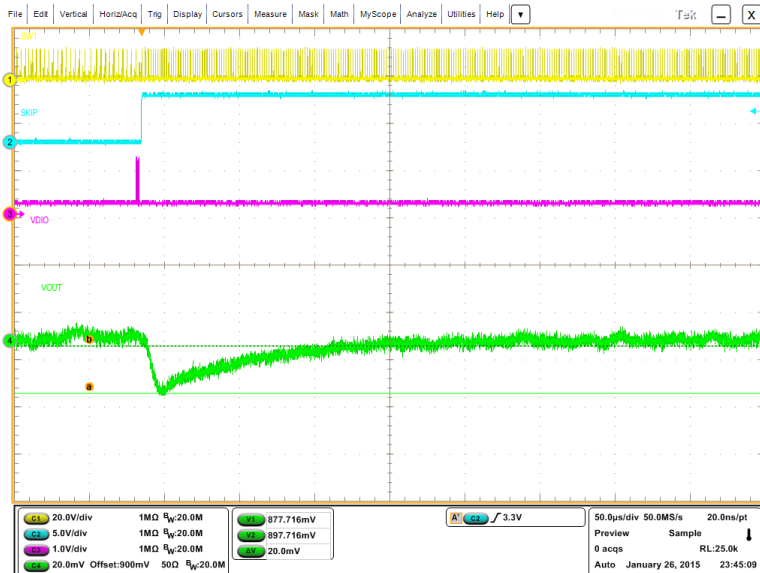

PS transition PS0-PS3 0A load

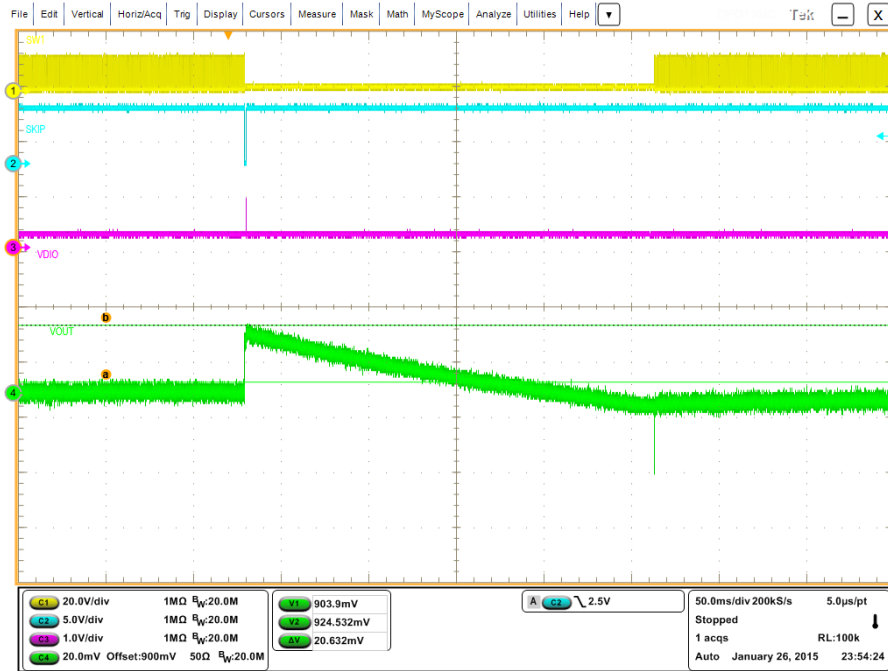


PS transition PS0-PS3 0.1A load

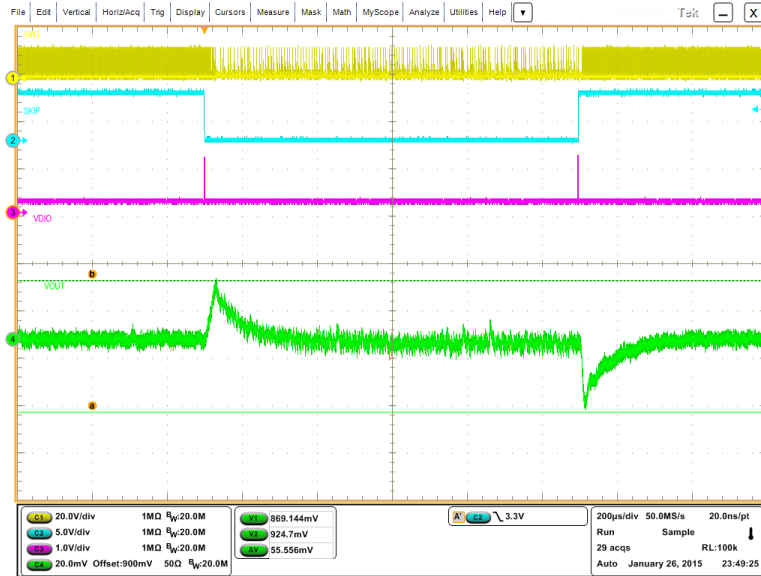


PS0 to PS3 voltage change: 22.2mV

PS3 to PS0 voltage change: 22.8mV

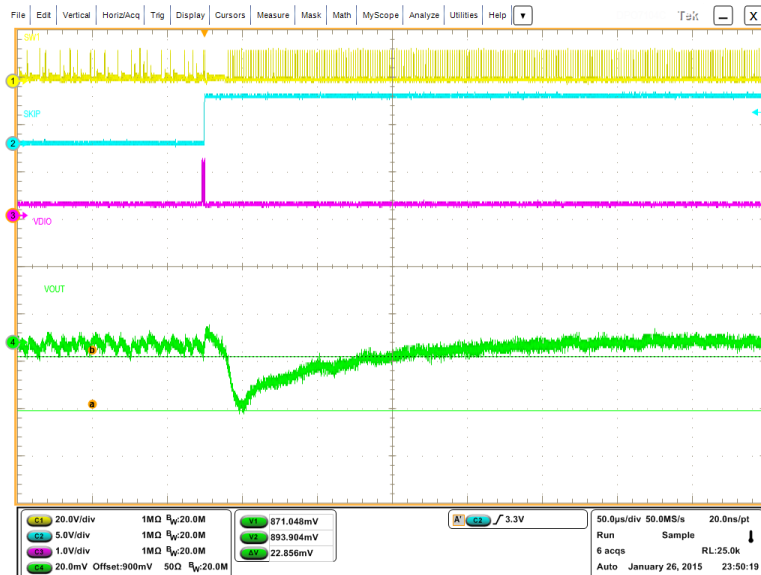

PS transition PS0-PS3 0.5A load

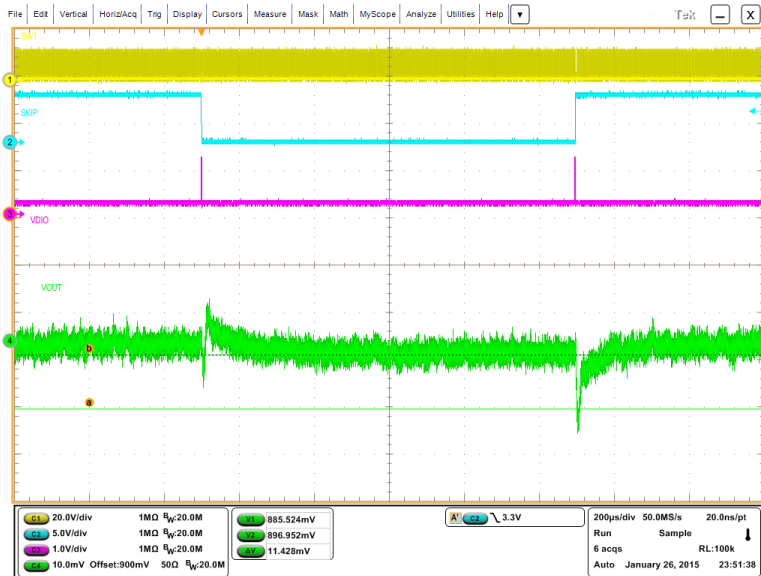

PS0 to PS3 voltage change: 6.7mV

PS3 to PS0 voltage change: 14mV







PS0-PS3 droop: 4.4mV



PS3-PS0 droop: 4.6mV

PS transition PS2-PS3 0.5A load

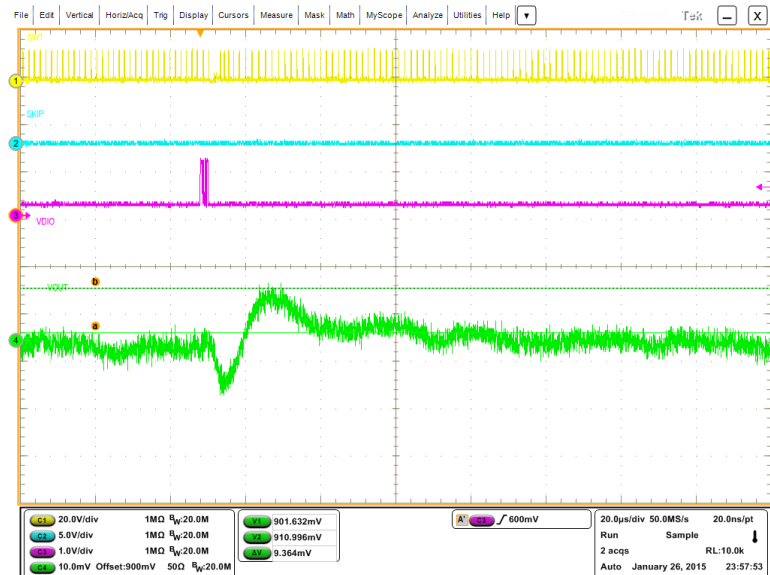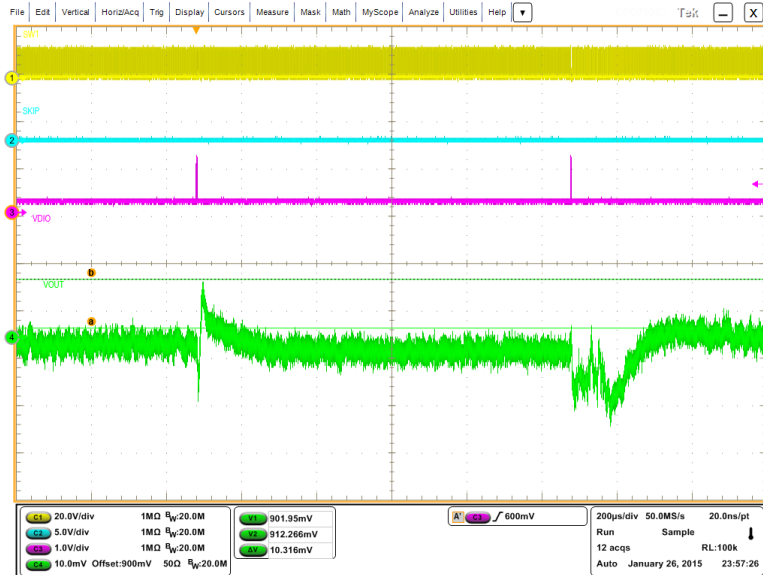


PS2 to PS3 voltage change: 9.3mV

PS3 to PS2 voltage change: 12.5mV





PS2-PS3 droop: 4.5mV

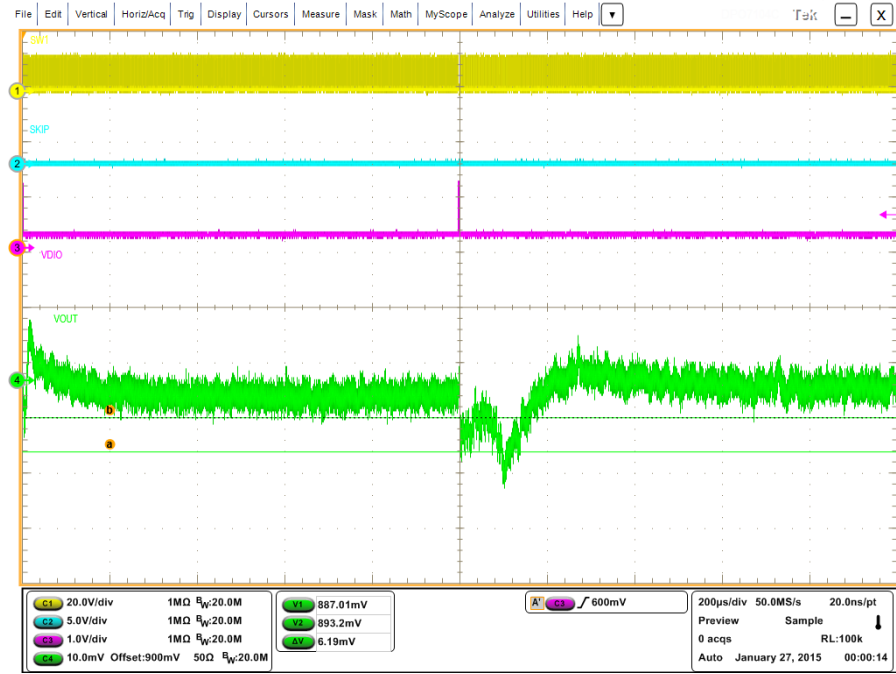

PS3-PS2 droop: 6.2mV

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated